
CMPE-630 Digital IC Design
Laboratory Exercise 7
Autolayout Design Techniques (HDL-Layout)

Brandon Key
Performed: 6 Nov 2019
Submitted: 13 Nov 2019

Instructor: Dr. Amlan Ganguly
TAs: Abhishek Vashist
Andrew Fountain
Piers Kwan

By submitting this report, you attest that you neither have given nor have received any assistance (including writing, collecting data, plotting figures, tables or graphs, or using previous student reports as a reference), and you further acknowledge that giving or receiving such assistance will result in a failing grade for this course.

Your Signature: _____

Contents

1	Abstract	3
2	Design Methodology and Theory	3
2.1	Functional Simulation	3
2.1.1	1 Bit ALU	3
2.1.2	16 Bit ALU	4
2.2	Schematic	5
2.2.1	1-Bit ALU	5
2.2.2	n-Bit ALU	5
3	Results and Analysis	8
3.1	Layout	8
3.1.1	1 Bit ALU	9
3.1.2	16 Bit ALU	10
3.2	Timing	10
3.2.1	1 Bit ALU	11
3.2.2	16 Bit ALU	12
3.3	Power	15
4	Conclusion	15
5	Question	15
6	Appendix	16
6.1	VHDL	16
6.2	SPICE	42
7	References	46

1 Abstract

Integrated Circuit Design is a costly and complex endeavor. Fortunately, automatic tools speed up the process and allow designs that are not possible to create manually. This exercise implemented a 1-Bit ALU and a 16-Bit ALU using autolayout. The autolayout tools generated very reasonable circuits. The 1-Bit ALU has an input frequency of 380.92MHz and a throughput frequency of 553.4MHz, while the 16-bit ALU has an input frequency of 461.02MHz and a throughput frequency of 110.2MHz. The area used by the ALUs was also reasonable with the 1-bit ALU taking up $647.89\mu m^2$ and the 16-bit ALU occupying $9792.5\mu m^2$.

2 Design Methodology and Theory

The world of IC design is a very large and complex one. Engineering time is a critical factor when trying to create designs. An engineer tries to minimize power and cost, while maximizing performance. Modern ICs are very complex and manual engineer effort is not feasible. Fortunately, auto layout tools exists so that non-critical parts can be generated quickly. In this exercise, a single bit ALU and a 16-bit ALU were designed, automatically laid out and then power and timing results were extracted.

For all components designed in this exercise (a 1-bit ALU and a 16-bit ALU), VHDL was written to describe the functionality of the component. Leonardo Spectrum was used to turn the VHDL into synthesizable logic. The VHDL was then functionally tested with a test bench using Questa Sim. Next, a schematic for each ALU was generated with Pyxis.

2.1 Functional Simulation

The ALUs in this exercise had a simple 2 bit op-code which can be seen in Table 1.

Table 1: ALU Operations

OpCode	Operation	Operands
00	AND	A AND B
01	OR	A OR B
10	ADD	A + B
11	SUB	A - B

2.1.1 1 Bit ALU

The 1 Bit ALU designed in this exercise was created from behavioral VHDL (see Listing 10). A Questa Sim simulation was performed to test the functionality of the 1 bit ALU. The test bench can be seen in Listing 9. The test bench went through every op-code and every input. The resulting waveforms can be seen in Figure 1.

 


Figure 1: Functional Simulation of 1-bit ALU

 


Figure 6: Functional Simulation of 16-bit ALU: Subtraction

Figure 7 show subtraction with a negative result.

 


Figure 7: Functional Simulation of 16-bit ALU: Subtraction with negative result

Subtraction with the 16-bit ALU was correct, thus rounding out the functional testing of the design. Next, a schematic could be created.

2.2 Schematic

Schematics were generated by Pyxis Schematic Editor. The tool generated a nearly complete schematic(s), but the component layout needed adjustment as some inverters were overlapping.

2.2.1 1-Bit ALU

The 1-bit ALU schematic spanned one page and can be seen in Figure 8.

 


Figure 8: 1 Bit ALU Schematic

The 1-bit ALU is rather simple.

2.2.2 n-Bit ALU

Pyxis created 3 schematic sheets to satisfy the 16-bit ALU. This likely due to the structural nature of the ALU. The schematic can be seen in Figure 9 through Figure 11.

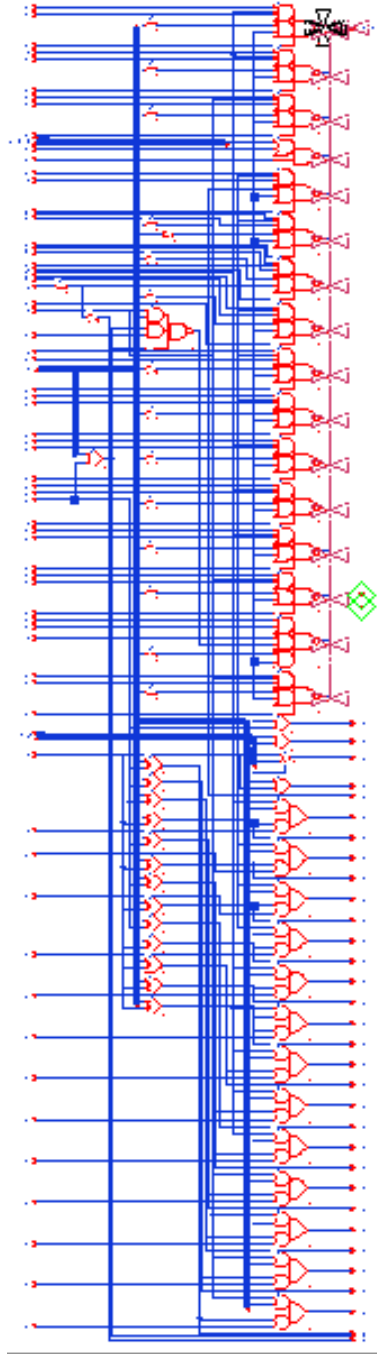


Figure 9: 16 Bit ALU Schematic Page 1

 


Figure 10: 16 Bit ALU Schematic Page 2

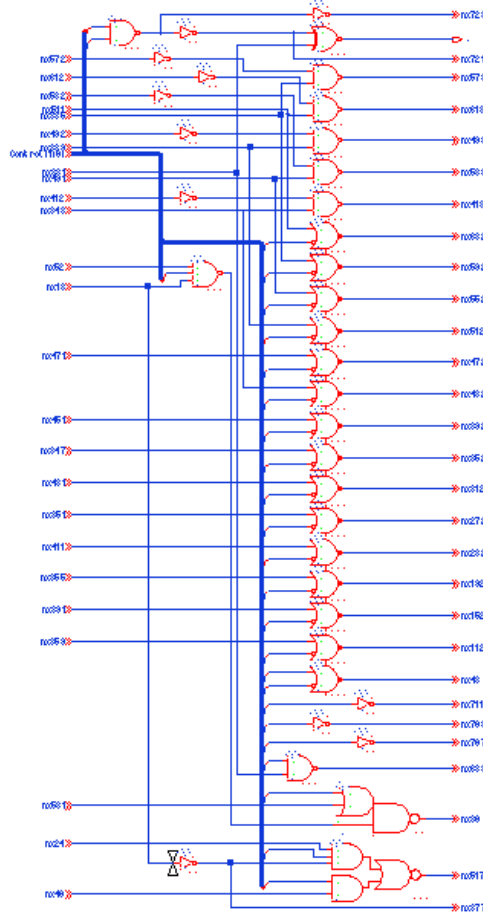


Figure 11: 16 Bit ALU Schematic Page 3

The 16-bit ALU is dramatically more complex than the single bit ALU.

3 Results and Analysis

The ALUs in this exercise had a layout created for them. Then the layout was compared to the schematic via a LVS check. Then timing data was extracted with a PEX extraction. A simulation was run off of the PEX results. Finally, static and dynamic power was measured from the circuit.

3.1 Layout

Pyxis was used to instantiate components from the schematic. Ports were added to the design before a floor plan was generated. To aid in the routing procedure, the area ratio was decreased from 1 to 0.7. Decreasing this area gives room between the cells to route wires. Standard cells were created with default settings. Power routing was run to ease the burden on auto routing and also to clean up the layout. Auto routing settings were adjusted to not route with poly silicon as this tends to cause stray gates. Additionally, the following settings were applied to aid in auto routing:

- Varying levels of routing completion time
- Slight preference for jogs over via to fill the area.

- Rip
- Under rip options:
 - Rips Most Aggressive
 - Automatic Rip Passes
 - Reroute
- Under Advanced:
 - Allow all directions for stubs
 - Via Options > Use via generator

3.1.1 1 Bit ALU

The one bit ALU can be seen in Figure 12.

 


Figure 12: 1 Bit ALU Layout

The 1-bit ALU was $24.045\mu\text{m}$ wide and $26.945\mu\text{m}$ tall, for a total area of $647.893\mu\text{m}^2$.

3.1.2 16 Bit ALU

The one bit ALU can be seen in Figure 13.

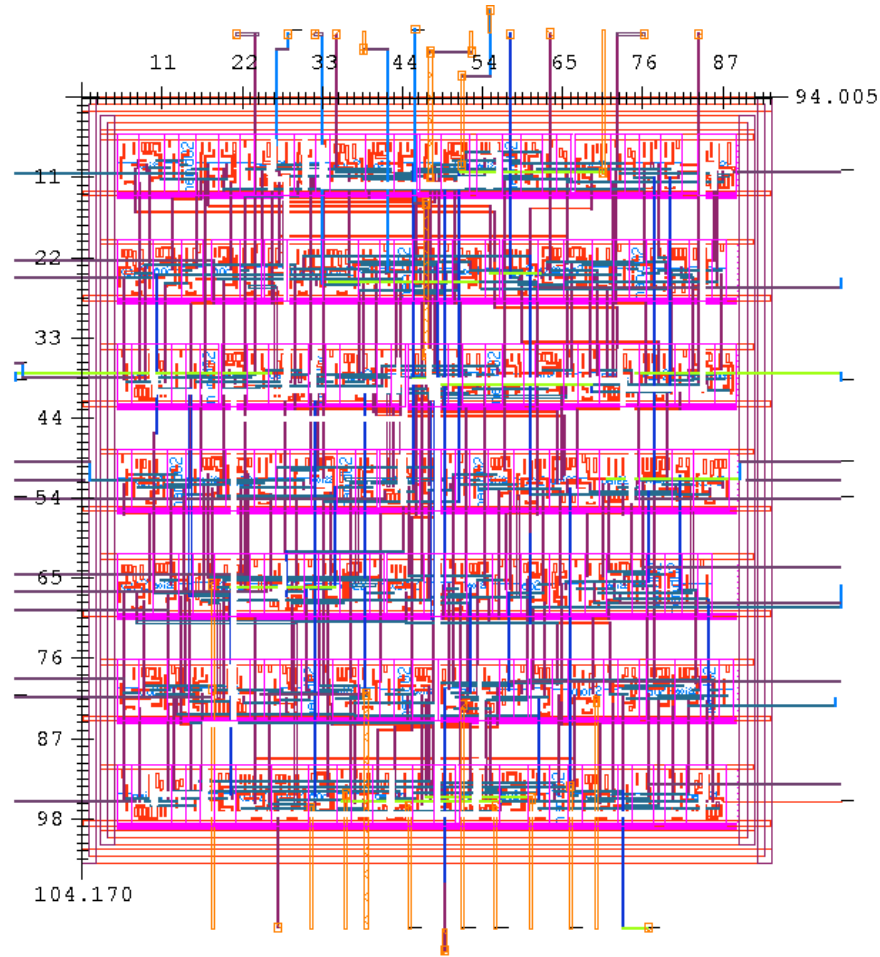


Figure 13: 16 Bit ALU Layout

The 1-bit ALU was $94.005\mu\text{m}$ wide and $104.170\mu\text{m}$ tall, for a total area of $9792.5\mu\text{m}^2$.

3.2 Timing

A SPICE file was written for each ALU, which was based off of the PEX extraction netlist. Eldo was used to run the simulation and ezwave was used to view the waveform and measure rise time, fall time, and propagation delay.

The simulation was run for worst case conditions which are laid out in Figure 14.

Simulation Parameters	
Vdd (V)	1.08
Temp (°C)	125
Load (fF)	120

Figure 14: Simulation Parameters

The maximum input and throughput frequencies were calculated from the measured timing values according to Equation 1 and Equation 2 respectively.

$$F_{input,max} = \frac{1}{t_{rise} + t_{fall}} \quad (1)$$

Equation 1: Max Input Frequency

$$F_{throughput,max} = \frac{1}{T_{P,HL} + T_{P,LH}} \quad (2)$$

Equation 2: Max Throughput Frequency

3.2.1 1 Bit ALU

It was found that subtraction was by far the slowest operation, with the timing difference visible in the waveforms. The SPICE file used to extract timing can be found in Listing 16. The waveform and measurements can be seen in Figure 15.

 


Figure 15: 1 Bit ALU Worst Case Timing Simulation

The rise time was recorded in Table 2.

Table 2: 1-Bit ALU Worst Case Rise Time

Output	Rise Time (ps)	A	B	Operation
Y	1167.5	1	0	SUB
Carry	1557.1	0	1	SUB

The fall time was recorded in Table 3.

Table 3: 1-Bit ALU Worst Case Fall Time

Output	Fall Time (ps)	A	B	Operation
Y	1001.3	1	1	SUB
Carry	1068.1	1	1	SUB

The propagation delay from high output to low output was recorded in Table 4.

Table 4: 1-Bit ALU Worst Case Propagation Time High to Low

Output	Tp,HL (ps)	A	B	Operation
Y	701.8	1	1	SUB
Carry	810.3	1	1	SUB

The propagation delay from low output to high output was recorded in Table 5.

Table 5: 1-Bit ALU Worst Case Propagation Time Low to High

Output	Tp,LH (ps)	A	B	Operation
Y	686.1	1	0	SUB
Carry	996.7	0	1	SUB

The frequency response was calculated and recorded in Table 6.

Table 6: 1-Bit ALU Calculated Max Frequency

Output	Finput,max (MHz)	Fthroughput,max (MHz)
Y	461.08	720.51
Carry	380.92	553.40

3.2.2 16 Bit ALU

The first SPICE file for the 16-bit ALU did not properly force the inputs, resulting in the waveform shown in Figure 16.

 


Figure 16: Simulation with Incorrect Forces

Listing 17 shows final the SPICE file used to simulate the 16-Bit ALU. The waveform with timing measurement can be seen in Figure 17.

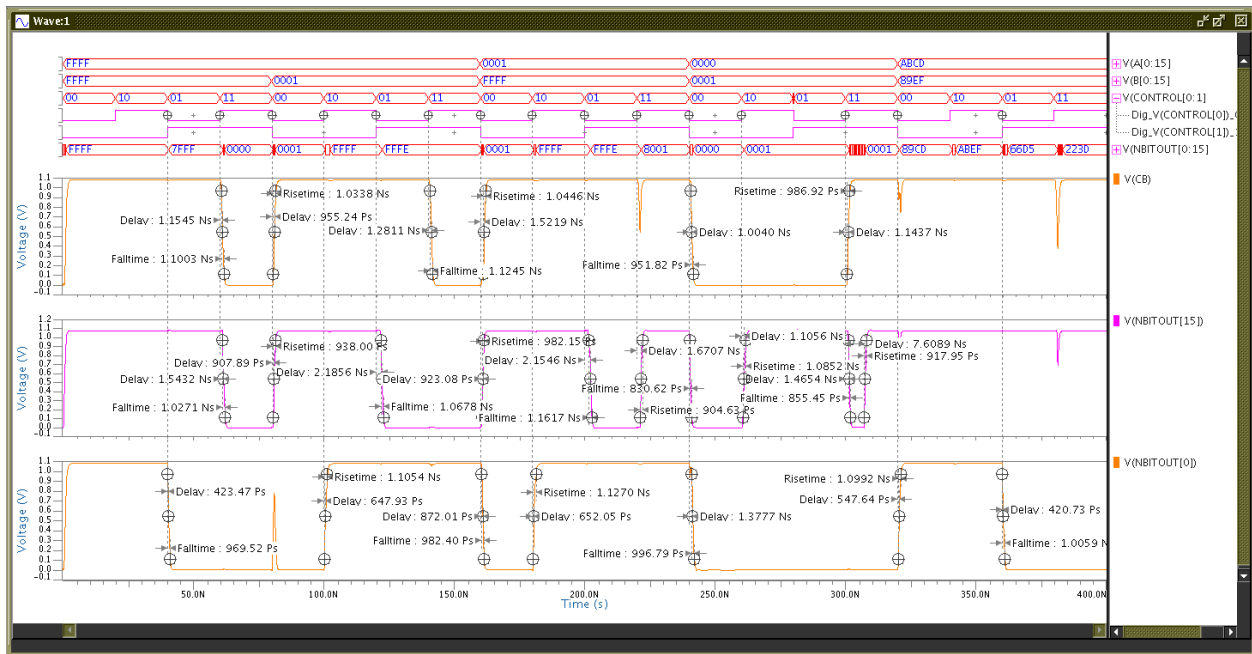


Figure 17: 16-Bit ALU Timing Waveforms

The timing measurements were recorded in Table 7 through Table 10.

Table 7: 16-Bit ALU Worst Case Rise Time

Input		Output	Rise Time (ps)			
A	B	Y	Op	Y	Op	CB
0x0000	0x0000	Y[15]	11	938.0	11	1033.8
0xFFFF	0xFFFF	Y[15]	11	938.0	01	1124.5
0xFFFF	0x0001	Y[15]	11	982.2	11	1044.6
0x0001	0xFFFF	Y[15]	01	904.63	00	1044.6
0x0000	0x0001	Y[0]	00	1085.2	01	986.9
0xABCD	0x89EF	Y[15]	01	917.9	11	951.8

Table 8: 16-Bit ALU Worst Case Fall Time

Input		Output	Fall Time (ps)			
A	B	Y	Op	Y	Op	CB
0x0000	0x0000	Y[15]	01	1100.3	01	1027.1
0xFFFF	0xFFFF	Y[15]	10	1067.0	10	1033.8
0xFFFF	0x0001	Y[15]	11	830.6	01	1124.5
0x0001	0xFFFF	Y[15]	10	1161.7	11	951.8
0x0000	0x0001	Y[0]	00	996.8	10	1005.9
0xABCD	0x89EF	Y[15]	01	855.5	01	969.5

Table 9: 16-Bit ALU Worst Case Propagation Time High to Low

Input		Output	Tp,HL (ps)			
A	B	Y	Op	Y	Op	CB
0x0000	0x0000	Y[15]	01	907.9	01	1154.5
0xFFFF	0xFFFF	Y[15]	10	2185.6	10	1281.1
0xFFFF	0x0001	Y[15]	11	2154.6	01	1004.0
0x0001	0xFFFF	Y[15]	10	1670.7	11	1143.7
0x0000	0x0001	Y[0]	00	1377.7	10	920.7
0xABCD	0x89EF	Y[15]	01	1465.4	01	872.0

Table 10: 16-Bit ALU Worst Case Propagation Time Low to High

Input		Output	Tp,LH (ps)			
A	B	Y	Op	Y	Op	CB
0x0000	0x0000	Y[15]	11	2185.6	11	955.2
0xFFFF	0xFFFF	Y[15]	11	2154.6	01	1521.9
0xFFFF	0x0001	Y[15]	11	1670.7	11	1143.7
0x0001	0xFFFF	Y[15]	01	1085.2	00	947.6
0x0000	0x0001	Y[0]	00	1099.2	01	1047.9
0xABCD	0x89EF	Y[15]	01	7608.9	11	1127.0

The frequency response for the 16-bit ALU was recorded in Table 11.

Table 11: 16-Bit ALU Calculated Max Frequency

A	B	F _{input,max} (MHz)		F _{throughput,max} (MHz)	
		Y	CB	Y	CB
0x0000	0x0000	490.60	485.22	323.26	474.00
0xFFFF	0xFFFF	498.75	463.33	230.40	356.76
0xFFFF	0x0001	551.63	461.02	261.42	465.61
0x0001	0xFFFF	483.95	500.90	362.86	478.17
0x0000	0x0001	480.31	501.81	403.73	507.98
0xABCD	0x89EF	563.89	520.48	110.20	500.25

Considering the increase in complexity between the 1-bit and 16-bit ALU, the performance difference is rather small. The slowest frequency for the 1-bit ALU was 381MHz while the slowest frequency for the 16-bit ALU was 110MHz.

3.3 Power

The power drawn by each ALU was measured using Eldo. This was done by modifying the timing SPICE file to include static and dynamic power usage. The maximum power is drawn when the most amount of transistors are turned on. To capture this, power was measured when all output bits were high. For the 1-Bit ALU this occurred from 70ns to 130ns, for the 16-Bit ALU this occurred from 90ns to 150ns. The power draw was recorded in Table 12.

Table 12: ALU Power Draw

ALU	Static Power (nW)	Dynamic Power (uW)
1-Bit	6303.8	317.8
16-Bit	90463	2922.6

The 16-bit ALU consumed about 10 times the power as single bit ALU. This shows how more computation power drastically increases power draw.

4 Conclusion

While this exercise was successful, routing the ALUs took much trial and error. With default settings, none of the designs were routable. With proper configuration, the automatic tools generate a fast circuit. The 1-Bit ALU has an input frequency of 380.92MHz and a throughput frequency of 553.4MHz, while the 16-bit ALU has an input frequency of 461.02MHz and a throughput frequency of 110.2MHz. The area used by the ALUs was also reasonable with the 1-bit ALU taking up $647.89\mu m^2$ and the 16-bit ALU occupying $9792.5\mu m^2$. The area could have been reduced by increasing the area ratio when configuring the auto-floorplan, that decreased area would have cost more engineer time when routing. Overall, this exercise was successful.

5 Question

The 16-Bit ALU was created with generic VHDL, so creating a 4-bit ALU was simple. The routing actually proved more challenging than the 16-bit ALU. The 4-bit ALU's performance slotted in between the 1 and 16-bit ALU. The timing was recorded in Table 13.

Table 13: Frequency Response of Manual Layout 4-Bit Ripple Adder and Auto Layout 4-Bit ALU

4-Bit Ripple Adder		4-Bit ALU		Difference	
Finput(Hz)	Ftput(Hz)	Finput(Hz)	Ftput(Hz)	Finput	Ftput
302.92	232.32	424.48	531.51	40.13%	128.78%
290.69	244.16	360.85	523.40	24.14%	114.37%

It would be expected that the ALU would be slower than just the adder, however this was not the case. This is likely because the automatic tools were more competent than inexperienced manual layout.

6 Appendix

6.1 VHDL

Listing 1: Controller-16Bit VHDL

```

0  ---Company      : RIT
   ---Author       : Brandon Key
   ---Created      : 02/18/2018
   ---
5  ---Project Name : Lab 3
   ---File         : Controller_16Bit.vhd
   ---
   ---Entity       : Controller_16Bit
   ---Architecture : behav
10  ---
   ---Tool Version : VHDL '93
   ---Description  : *SPECIAL controller , DO NOT USE OUTSIDE THIS PROJECT*
   ---              : Takes 4 bit control signal bit
   ---              : Figures out the proper output
15  ---

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.numeric_std.all;
20  ---use work.controlcodes.all;

entity Controller_16Bit is
    generic (n : integer := 16);
    port(
25      Control : in  std_logic_vector(1 downto 0);

      ADD.SUB_In : in std_logic_vector(N-1 downto 0);
      OR_In      : in std_logic_vector(N-1 downto 0);
      AND_In     : in std_logic_vector(N-1 downto 0);
30      ADD.SUB_SEL : out std_logic;

      nBitOut : out std_logic_vector(N-1 downto 0)
    );
35 end Controller_16Bit;

architecture behav of Controller_16Bit is

```



```

40  constant AND_Code : std_logic_vector(1 downto 0) := "00";
    constant OR_Code  : std_logic_vector(1 downto 0) := "01";
    constant ADD_Code : std_logic_vector(1 downto 0) := "10";
    constant SUB_Code : std_logic_vector(1 downto 0) := "11";

begin
45  --Proces to set the select signal when subtraction should occur
    ADD_SUB_SEL_proc: with Control select
        ADD_SUB_SEL <= '1' when SUB_Code,
                       '0' when others;

50  nBitOut_proc: with Control select
        nBitOut <= ADD_SUB_In when ADD_Code,
                  ADD_SUB_In when SUB_Code,
                  OR_In when OR_Code,
55  AND_In when AND_Code,
                  (others => '0') when others;

end  behav;

```

Listing 2: nBitAdderSubtractor-4Bit VHDL

```

0  --Company      : RIT
   --Author       : Brandon Key
   --Created      : 02/18/2018
   --
5  --Project Name : Lab 3
   --File         : nBitAdderSubtractor_4Bit.vhd
   --
   --Entity       : nBitAdderSubtractor_4Bit
   --Architecture : struct
10  --
   --Tool Version : VHDL '93
   --Description  : Entity and structural description of an adder subtractor
   --              : SEL = 0 : A+B = Y
   --              : SEL = 1 : A-B = Y
15  --

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.numeric_std.all;

20  entity nBitAdderSubtractor_4Bit is
    generic (n : integer := 16);
    port(
25      A,B : in  std_logic_vector(n-1 downto 0);
        SEL : in  std_logic;
        Y   : out std_logic_vector(n-1 downto 0);
        CB  : out std_logic
    );
end  nBitAdderSubtractor_4Bit;

30  architecture struct of nBitAdderSubtractor_4Bit is

    component full_adder is
        port(A,B,Cin : in  std_logic;
35          Sum,Cout : out std_logic

```

```

    );
    end component full_adder;

    --Create an array to hold all of the carries
40  type carry_array is array (n-1 downto 0) of std_logic;
    signal c_array : carry_array;

    signal B_XOR_SEL : std_logic_vector( (n-1) downto 0);

45 begin

    --Generate the xor statements to be mapped to the full adders
    XORator : for i in 0 to n-1 generate
        B_XOR_SEL(i) <= B(i) xor SEL;
50  end generate XORator;

    generate_adders : for i in 0 to n-1 generate
        i_first : if i = 0 generate
            --The first adder gets SEL as the Cin
55         adder : full_adder port map(
                A => A(i),
                B => B_XOR_SEL(i),
                Cin => SEL,
                Sum => Y(i),
60             Cout => c_array(i)
            );
        end generate i_first;

        i_last : if i = (n-1) generate
65         --The last adder doesn't have a carry out
        adder : full_adder port map(
                A => A(i),
                B => B_XOR_SEL(i),
                Cin => c_array(i-1),
70             Sum => Y(i),
                Cout => c_array(i)
            );
        end generate i_last;

75         --Middle adders
        i_mid : if (i /= 0) and (i /= (n-1)) generate
            adder : full_adder port map(
                A => A(i),
                B => B_XOR_SEL(i),
80             Cin => c_array(i-1),
                Sum => Y(i),
                Cout => c_array(i)
            );
        end generate i_mid;

85     end generate generate_adders;

    CB <= c_array(n-1) xor SEL;

90 end struct;

```

Listing 3: FullAdder VHDL

```

--Company      : RIT
--Author       : Brandon Key
--Created      : 02/18/2018
--
5 --Project Name : Lab 3
--File         : Full_Adder.vhd
--
--Entity       : Full_Adder
--Architecture : behav
10 --
--Tool Version : VHDL '93
--Description  : Entity and behavioral description of a full adder

-----

15 library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Full_Adder is
20     port (A,B,Cin : in  std_logic;
           Sum,Cout : out std_logic
           );
end Full_Adder;

25 architecture behav of Full_Adder is
begin
    --uses select assignment to implement the truth table of a full adder

30     sum_proc: with std_logic_vector'(Cin&A&B) select
        Sum <= '0' when "000",
                '1' when "001",
                '1' when "010",
                '0' when "011",
35                '1' when "100",
                '0' when "101",
                '0' when "110",
                '1' when "111",
                '0' when others;

40     Cout_proc: with std_logic_vector'(Cin&A&B) select
        Cout <= '0' when "000",
                 '0' when "001",
                 '0' when "010",
                 '1' when "011",
45                 '0' when "100",
                 '1' when "101",
                 '1' when "110",
                 '1' when "111",
                 '0' when others;

50 end behav;

```

Listing 4: ALU-16Bit-tb VHDL

```

0 -----
-- Company: RIT
-- Engineer: Brandon Key
--

```

```

-- Create Date:    17:51:58 02/28/2018
5 -- Design Name:
-- Module Name:    /home/ise/DSDII/Lab/Lab3/SourceCode/ALU_16Bit_tb.vhd
-- Project Name:   Lab3
-- Target Device:
-- Tool versions:
10 -- Description:
--
-- VHDL Test Bench Created by ISE for module: ALU_16Bit
--
-- Dependencies:
15 --
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--
20 -- Notes:
-- This testbench has been automatically generated using types std_logic and
-- std_logic_vector for the ports of the unit under test.  Xilinx recommends
-- that these types always be used for the top-level I/O of a design in order
-- to guarantee that the testbench will bind correctly to the post-implementation
25 -- simulation model.

```

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;
30 --use work.globals.all;
--use work.controlcodes.all;

ENTITY ALU_16Bit_tb IS
END ALU_16Bit_tb;
35

ARCHITECTURE behavior OF ALU_16Bit_tb IS

    constant AND_Code : std_logic_vector(1 downto 0) := "00";
    constant OR_Code  : std_logic_vector(1 downto 0) := "01";
40    constant ADD_Code : std_logic_vector(1 downto 0) := "10";
    constant SUB_Code : std_logic_vector(1 downto 0) := "11";

    type testRecordArray is array (natural range <>) of std_logic_vector(2 downto 0)
    ;

45    constant n:integer := 16;
    -- "Time" that will elapse between test vectors we submit to the component.
    constant TIMEDELTA : time := 50 ns;

50    -- Component Declaration for the Unit Under Test (UUT)
    COMPONENT ALU_16Bit
    PORT(
        Control : IN  std_logic_vector(1 downto 0);
        A : IN  std_logic_vector(N-1 downto 0);
55        B : IN  std_logic_vector(N-1 downto 0);
        nBitOut : OUT std_logic_vector(N-1 downto 0);
        CB : OUT std_logic
    );
    END COMPONENT;
60

```

```

--Inputs
signal Control : std_logic_vector(1 downto 0) := (others => '0');
signal A : std_logic_vector(N-1 downto 0) := (others => '0');
signal B : std_logic_vector(N-1 downto 0) := (others => '0');

--Outputs
signal nBitOut : std_logic_vector(N-1 downto 0);
signal CB : std_logic;
-- No clocks detected in port list. Replace <clock> below with
-- appropriate port name

BEGIN

-- Instantiate the Unit Under Test (UUT)
ut: ALU_16Bit
PORT MAP (
    Control => Control,
    A => A,
    B => B,
    nBitOut => nBitOut,
    CB => CB
);

-- Stimulus process
stim_proc: process
--create a function to make a vector a string
function vec2str(vec : std_logic_vector) return string is
    variable stmp:string(vec'left+1 downto 1);
begin
    for i in vec'reverse_range loop
        if vec(i) = '1' then
            stmp(i+1) := '1';
        elsif vec(i) = 'U' then
            stmp(i+1) := 'U';
        else
            stmp(i+1) := '0';
        end if;
    end loop;
    return stmp;
end vec2str;

procedure check_add(
    constant in1 : in natural;
    constant in2 : in natural;
    constant res_expected : in natural;
    constant CB_expected : in std_logic) is
    variable res : natural;
begin
    -- Assign values to circuit inputs.
    A <= std_logic_vector(to_unsigned(in1, A'length));
    B <= std_logic_vector(to_unsigned(in2, B'length));
    Control <= ADD.Code;

    wait for TIME_DELTA;
    -- Check output against expected result.
    res := to_integer(unsigned(nBitOut));

```

```

125     assert ((res = res_expected) and ( CB = CB_expected ))
126     report "" & integer'image(in1) & "+" &
127         integer'image(in2) & "=" &
128         integer'image(res_expected) & "!=" &
129         integer'image(res) &
130         "CB exp: " & std_logic'image(CB_expected) &
131         "Got: " & std_logic'image(CB)
132     severity error;
133 end procedure check_add;

134
135 procedure check_sub(
136     constant in1 : in natural;
137     constant in2 : in natural;
138     constant res_expected : in natural;
139     constant CB_expected : in std_logic) is
140     variable res : natural;
141     begin
142         -- Assign values to circuit inputs.
143         A <= std_logic_vector(to_unsigned(in1, A'length));
144         B <= std_logic_vector(to_unsigned(in2, B'length));
145         Control <= SUB_Code;

146
147         wait for TIME_DELTA;
148         -- Check output against expected result.
149         res := to_integer(unsigned(nBitOut));
150         assert ((res = res_expected) and ( CB = CB_expected ))
151         report "" & integer'image(in1) & "-" &
152             integer'image(in2) & "=" &
153             integer'image(res_expected) & "!=" &
154             integer'image(res) &
155             "CB exp: " & std_logic'image(CB_expected) &
156             "Got: " & std_logic'image(CB)
157         severity error;
158     end procedure check_sub;

159
160 procedure check_or(
161     constant in1 : in natural;
162     constant in2 : in natural;
163     constant res_expected : in natural) is
164     variable res : natural;
165     begin
166         -- Assign values to circuit inputs.
167         A <= std_logic_vector(to_unsigned(in1, A'length));
168         B <= std_logic_vector(to_unsigned(in2, B'length));
169         Control <= OR_Code;

170
171         wait for TIME_DELTA;
172         -- Check output against expected result.
173         res := to_integer(unsigned(nBitOut));
174         assert ((res = res_expected) and ( CB = '0' ))
175         report "" & integer'image(in1) & "+" &
176             integer'image(in2) & "=" &
177             integer'image(res_expected) & "!=" &
178             integer'image(res) &

```

```

180         " " &
        "CB: " & std_logic'image(CB)
        severity error;
end procedure check_or;

185

procedure check_and(
    constant in1 : in natural;
    constant in2 : in natural;
    constant res_expected : in natural) is
190     variable res : natural;
    begin
        -- Assign values to circuit inputs.
        A <= std_logic_vector(to_unsigned(in1, A'length));
        B <= std_logic_vector(to_unsigned(in2, B'length));
195     Control <= AND_Code;

        wait for TIME_DELTA;
        -- Check output against expected result.
        res := to_integer(unsigned(nBitOut));
        report " " & integer'image(in1) & "+" &
                integer'image(in2) & "=" &
                integer'image(res_expected);

        assert ((res = res_expected) and (CB = '0' ))
        report "!=" &
                integer'image(res) &
                " " &
                "CB: " & std_logic'image(CB)
210     severity error;
end procedure check_and;

begin

215

    --wait for the outputs to stabilize
    wait for 100 ns;

    --check_add(4,5,9,0);
    --check_add(65535, 2, 1, 1);
220    --check_sub(1234, 234, 1000, 0);
    --check_sub(1, 2, 1, 1);

    control <= OR_Code;
    A <= "0111010101110101";
    B <= "1001110100101101";
    wait for 50 ns;

    control <= AND_Code;
230    wait for 50 ns;

    -- Test adder
    for x in (0) to (5) loop
235        for y in 5432 to 5438 loop
            control <= ADD_Code;
            A <= std_logic_vector(to_unsigned(x, A'length));
            B <= std_logic_vector(to_unsigned(y, B'length));

```

```

240         wait for 50 ns;

        assert(nBitOut = std_logic_vector(to_unsigned(x+y, A'length)) )
        report("Bad Add = " & vec2str(nBitOut)
                & " expected = " & vec2str( std_logic_vector(to_unsigned(x+y, A'
length)) )
                & " A = " & vec2str(A)
                & " B = " & vec2str(B)
        );
    end loop;
end loop;

250 for x in ((2*N)-3) to ((2*N)-1) loop
    for y in 0 to 3 loop
        control <= ADD_Code;
        A <= std_logic_vector(to_unsigned(x, A'length));
        B <= std_logic_vector(to_unsigned(y, B'length));
255         wait for 50 ns;

        assert(nBitOut = std_logic_vector(to_unsigned(x+y, A'length)) )
        report("Bad Add = " & vec2str(nBitOut)
                & " expected = " & vec2str( std_logic_vector(to_unsigned(x+y, A'
length)) )
                & " A = " & vec2str(A)
                & " B = " & vec2str(B)
        );
    end loop;
end loop;

265 -- Test suber
for x in 0 to 5 loop
    for y in 0 to 5 loop
        control <= SUB_Code;
270         A <= std_logic_vector(to_unsigned(x, A'length));
        B <= std_logic_vector(to_unsigned(y, B'length));
        wait for 50 ns;

        assert(nBitOut = std_logic_vector(to_signed(x-y, A'length)) )
275         report("Bad Sub = " & vec2str(nBitOut)
                & " expected = " & vec2str( std_logic_vector(to_signed(x-y, A'length)) )
                & " A = " & vec2str(A)
                & " B = " & vec2str(B)
        );
280     end loop;
end loop;

285 for x in 12345 to 12350 loop
    for y in 5 to 7 loop
        control <= SUB_Code;
        A <= std_logic_vector(to_unsigned(x, A'length));
        B <= std_logic_vector(to_unsigned(y, B'length));
        wait for 50 ns;

290         assert(nBitOut = std_logic_vector(to_signed(x-y, A'length)) )
        report("Bad Sub = " & vec2str(nBitOut)
                & " expected = " & vec2str( std_logic_vector(to_signed(x-y, A'length)) )
                & " A = " & vec2str(A)
                & " B = " & vec2str(B)
        );
295

```



```

        );
        end loop;
    end loop;

    wait;
end process;

END;

```

Listing 5: Controller-4Bit VHDL

```

0  -----
   --Company      : RIT
   --Author       : Brandon Key
   --Created      : 02/18/2018
   --
5  --Project Name : Lab 3
   --File         : Controller_4Bit.vhd
   --
   --Entity       : Controller_4Bit
   --Architecture : behav
10  --
   --Tool Version : VHDL '93
   --Description  : *SPECIAL controller , DO NOT USE OUTSIDE THIS PROJECT*
   --              : Takes 4 bit control signal bit
   --              : Figures out the proper output
15  -----

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.numeric_std.all;
20 --use work.controlcodes.all;

entity Controller_4Bit is
    generic (n : integer := 16);
    port(
25     Control : in std_logic_vector(1 downto 0);

        ADD_SUB_In : in std_logic_vector(N-1 downto 0);
        OR_In      : in std_logic_vector(N-1 downto 0);
        AND_In     : in std_logic_vector(N-1 downto 0);
30     ADD_SUB_SEL : out std_logic;

        nBitOut : out std_logic_vector(N-1 downto 0)
    );
35 end Controller_4Bit;

architecture behav of Controller_4Bit is

    constant AND_Code : std_logic_vector(1 downto 0) := "00";
    constant OR_Code  : std_logic_vector(1 downto 0) := "01";
    constant ADD_Code : std_logic_vector(1 downto 0) := "10";
    constant SUB_Code : std_logic_vector(1 downto 0) := "11";
40

```

```

begin
45  --Proces to set the select signal when subtraction should occur
    ADD_SUB_SEL_proc: with Control select
        ADD_SUB_SEL <= '1' when SUB_Code,
                       '0' when others;

50  nBitOut_proc: with Control select
        nBitOut <= ADD_SUB_In when ADD_Code,
                  ADD_SUB_In when SUB_Code,
                  OR_In when OR_Code,
55  AND_In when AND_Code,
                  (others => '0') when others;

end  behav;

```

Listing 6: nBitOR-4Bit VHDL

```

0  --Company      : RIT
   --Author       : Brandon Key
   --Created      : 1/22/2018
   --
5  --Project Name : Lab 1
   --File         : nBitOR_4Bit.vhd
   --
   --Entity       : nBitOR_4Bit
   --Architecture : Dataflow
10  --
   --Tool Version : VHDL '93
   --Description  : Entity and structural description of an OR gate
   --
15  library IEEE;
   use IEEE.STD_LOGIC_1164.ALL;

   entity nBitOR_4Bit is
       generic (n : integer := 16);
20   port(A,B : in  std_logic_vector(n-1 downto 0);
        Y : out std_logic_vector(n-1 downto 0)
        );
   end nBitOR_4Bit;

25  architecture Dataflow of nBitOR_4Bit is
       begin
           Y <= A or B; -- bitwise or
   end Dataflow;

```

Listing 7: ALU-4Bit VHDL

```

0  --Company      : RIT
   --Author       : Brandon Key
   --Created      : 02/18/2018
   --
5  --Project Name : Lab 3
   --File         : ALU_4Bit.vhd
   --
   --Entity       : ALU_4Bit

```

```

--Architecture : struct
10 --
--Tool Version : VHDL '93
--Description  : ALU_4Bit
-----

15 library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

package globals is
    constant N : integer := 16;
20 end globals;

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

25 package controlcodes is
    constant AND_Code : std_logic_vector(1 downto 0) := "00";
    constant OR_Code  : std_logic_vector(1 downto 0) := "01";
    constant ADD_Code : std_logic_vector(1 downto 0) := "10";
30    constant SUB_Code : std_logic_vector(1 downto 0) := "11";
end controlcodes;

library IEEE;
35 use IEEE.STD_LOGIC_1164.ALL;
use IEEE.numeric_std.all;
use work.controlcodes.all;
use work.globals.all;

40 entity ALU_4Bit is
    port(
        Control : in std_logic_vector(1 downto 0);
        A,B      : in std_logic_vector(N-1 downto 0);
        nBitOut  : out std_logic_vector(N-1 downto 0);
45        CB      : out std_logic
    );
end ALU_4Bit;

architecture struct of ALU_4Bit is
50
    --constant N : integer := 4;

    signal ADD_SUB_Out : std_logic_vector(N-1 downto 0);
    signal OR_Out      : std_logic_vector(N-1 downto 0);
55    signal AND_Out    : std_logic_vector(N-1 downto 0);

    signal ADD_SUB_SEL : std_logic;

60 begin

    nBitAdderSubtractor_4Bit : entity work.nBitAdderSubtractor_4Bit
        generic map (N => N)
        port map ( A => A, B => B, SEL => ADD_SUB_SEL, Y => ADD_SUB_Out, CB => CB);
65

    nBitOR_4Bit : entity work.nBitOR_4Bit

```

```

    generic map (N => N)
    port map ( A => A, B => B, Y => OR_Out);

nBitAND_4Bit : entity work.nBitAND_4Bit
    generic map (N => N)
    port map ( A => A, B => B, Y => AND_Out);

Controller_4Bit : entity work.Controller_4Bit
    generic map (N => N)
    port map(
        Control      => Control,
        ADD_SUB_In   => ADD_SUB_Out,
        OR_In        => OR_Out,
        AND_In       => AND_Out,
        ADD_SUB_SEL  => ADD_SUB_SEL,
        nBitOut      => nBitOut
    );

end struct;

```

Listing 8: nBitAND-4Bit VHDL

```

--Company      : RIT
--Author       : Brandon Key
--Created      : 1/22/2018
--
--Project Name : Lab 1
--File         : nBitAND_4Bit.vhd
--
--Entity       : nBitAND_4Bit
--Architecture : Dataflow
--
--Tool Version : VHDL '93
--Description  : Entity and structural description of an AND gate

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity nBitAND_4Bit is
    generic (n : integer := 16);
    port (A,B : in  std_logic_vector(n-1 downto 0);
          Y : out std_logic_vector(n-1 downto 0)
    );
end nBitAND_4Bit;

architecture Dataflow of nBitAND_4Bit is
    begin
        Y <= A AND B;-- bitwise or
    end Dataflow;

```

Listing 9: ALU-1Bit-tb VHDL

```

-- Company: RIT
-- Engineer: Brandon Key
--

```

```

-- Create Date: 17:51:58 02/28/2018
5 -- Design Name:
-- Module Name: /home/ise/DSDII/Lab/Lab3/SourceCode/ALU_1Bit_tb.vhd
-- Project Name: Lab3
-- Target Device:
-- Tool versions:
10 -- Description:
--
-- VHDL Test Bench Created by ISE for module: ALU_1Bit
--
-- Dependencies:
15 --
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--
20 -- Notes:
-- This testbench has been automatically generated using types std_logic and
-- std_logic_vector for the ports of the unit under test. Xilinx recommends
-- that these types always be used for the top-level I/O of a design in order
-- to guarantee that the testbench will bind correctly to the post-implementation
25 -- simulation model.

```

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;
30 --use work.globals.all;
--use work.controlcodes.all;

ENTITY ALU_1Bit_tb IS
END ALU_1Bit_tb;
35

ARCHITECTURE behavior OF ALU_1Bit_tb IS

    CONSTANT AND_Code : std_logic_vector(1 DOWNTO 0) := "00";
    CONSTANT OR_Code : std_logic_vector(1 DOWNTO 0) := "01";
40    CONSTANT ADD_Code : std_logic_vector(1 DOWNTO 0) := "10";
    CONSTANT SUB_Code : std_logic_vector(1 DOWNTO 0) := "11";

    TYPE testRecordArray IS ARRAY (NATURAL RANGE <>) OF std_logic_vector(2 DOWNTO 0)
    ;
    CONSTANT TIMEDELTA : TIME := 50 ns;
45    -- Component Declaration for the Unit Under Test (UUT)
    COMPONENT ALU_1Bit
        PORT (
            Control : IN std_logic_vector(1 DOWNTO 0);
            A : IN std_logic;
50            B : IN std_logic;
            Y : OUT std_logic;
            CB : OUT std_logic
        );
    END COMPONENT;
55    --Inputs
    SIGNAL Control : std_logic_vector(1 DOWNTO 0) := (OTHERS => '0');
    SIGNAL A : std_logic := '0';
    SIGNAL B : std_logic := '0';

60    --Outputs
    SIGNAL Y : std_logic;

```

```

    SIGNAL CB : std_logic;
BEGIN
    -- Instantiate the Unit Under Test (UUT)
65    uut : ALU_1Bit
    PORT MAP(
        Control => Control,
        A => A,
        B => B,
70        Y => Y,
        CB => CB
    );
    -- Stimulus process
    stim_proc : PROCESS
75        --create a function to make a vector a string
        FUNCTION vec2str(vec : std_logic_vector) RETURN STRING IS
            VARIABLE stmp : STRING(vec'LEFT + 1 DOWNTO 1);
        BEGIN
            FOR i IN vec'reverse_range LOOP
80                IF vec(i) = '1' THEN
                    stmp(i + 1) := '1';
                ELSIF vec(i) = 'U' THEN
                    stmp(i + 1) := 'U';
                ELSE
85                    stmp(i + 1) := '0';
                END IF;
            END LOOP; RETURN stmp;
        END vec2str;

90    BEGIN
        --wait for the outputs to stabilize
        WAIT FOR 100 ns;

        control <= OR_Code;
95        A <= '0';
        B <= '0';
        WAIT FOR 50 ns;
        A <= '0';
        B <= '1';
100        WAIT FOR 50 ns;
        A <= '1';
        B <= '0';
        WAIT FOR 50 ns;
        A <= '1';
        B <= '1';
105        WAIT FOR 50 ns;

        control <= AND_Code;
110        A <= '0';
        B <= '0';
        WAIT FOR 50 ns;
        A <= '0';
        B <= '1';
        WAIT FOR 50 ns;
115        A <= '1';
        B <= '0';
        WAIT FOR 50 ns;
        A <= '1';
        B <= '1';
120        WAIT FOR 50 ns;

```

```

        control <= ADD_Code;
        A <= '0';
        B <= '0';
125 WAIT FOR 50 ns;
        A <= '0';
        B <= '1';
        WAIT FOR 50 ns;
        A <= '1';
130 B <= '0';
        WAIT FOR 50 ns;
        A <= '1';
        B <= '1';
        WAIT FOR 50 ns;
135
        control <= SUB_Code;
        A <= '0';
        B <= '0';
        WAIT FOR 50 ns;
140 A <= '0';
        B <= '1';
        WAIT FOR 50 ns;
        A <= '1';
        B <= '0';
145 WAIT FOR 50 ns;
        A <= '1';
        B <= '1';
        WAIT FOR 50 ns;
150
        WAIT;
        END PROCESS;

END;

```

Listing 10: ALU-1Bit VHDL

```

0  -----
--Company      : RIT
--Author       : Brandon Key
--Created      : 02/18/2018
--
5  --Project Name : Lab 3
--File         : ALU.vhd
--
--Entity       : ALU
--Architecture : struct
10 --
--Tool Version : VHDL '93
--Description  : ALU
-----

15 library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

package controlcodes is
    constant AND_Code : std_logic_vector(1 downto 0) := "00";
    constant OR_Code  : std_logic_vector(1 downto 0) := "01";
20    constant ADD_Code : std_logic_vector(1 downto 0) := "10";
    constant SUB_Code  : std_logic_vector(1 downto 0) := "11";
end controlcodes;

```

```

25 library IEEE;
   use IEEE.STD_LOGIC_1164.ALL;
   use IEEE.numeric_std.all;
   use work.controlcodes.all;

30 entity ALU_1Bit is
    port(
        Control : in std_logic_vector(1 downto 0);
        A,B      : in std_logic;
        Y        : out std_logic;
35        CB      : out std_logic
    );
end ALU_1Bit;

architecture behav of ALU_1Bit is
40 begin

    Y_proc: with Control select
        Y <= A xor B when ADD_Code,
45         A xor B when SUB_Code,
        A or B when OR_Code,
        A and B when AND_Code,
        '0' when others;

50    CB_proc: with Control select
        CB <= A and B when ADD_Code,
        (not A) and B when SUB_Code,
        '0' when OR_Code,
55        '0' when AND_Code,
        '0' when others;

end behav;

```

Listing 11: ALU-4Bit-tb VHDL

```

0  ---
--- Company: RIT
--- Engineer: Brandon Key
---
--- Create Date: 17:51:58 02/28/2018
5 --- Design Name:
--- Module Name: /home/ise/DSDII/Lab/Lab3/SourceCode/ALU_4Bit_tb.vhd
--- Project Name: Lab3
--- Target Device:
--- Tool versions:
10 --- Description:
---
--- VHDL Test Bench Created by ISE for module: ALU_4Bit
---
--- Dependencies:
15 ---
--- Revision:
--- Revision 0.01 - File Created
--- Additional Comments:
---
20 --- Notes:

```

```

-- This testbench has been automatically generated using types std_logic and
-- std_logic_vector for the ports of the unit under test.  Xilinx recommends
-- that these types always be used for the top-level I/O of a design in order
-- to guarantee that the testbench will bind correctly to the post-implementation
25 -- simulation model.

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;
30 --use work.globals.all;
--use work.controlcodes.all;

ENTITY ALU_4Bit_tb IS
END ALU_4Bit_tb;
35

ARCHITECTURE behavior OF ALU_4Bit_tb IS

    constant AND_Code : std_logic_vector(1 downto 0) := "00";
    constant OR_Code  : std_logic_vector(1 downto 0) := "01";
40    constant ADD_Code : std_logic_vector(1 downto 0) := "10";
    constant SUB_Code : std_logic_vector(1 downto 0) := "11";

    type testRecordArray is array (natural range <>) of std_logic_vector(2 downto 0)
    ;

45    constant n:integer := 16;
    -- "Time" that will elapse between test vectors we submit to the component.
    constant TIME_DELTA : time := 50 ns;

50    -- Component Declaration for the Unit Under Test (UUT)
    COMPONENT ALU_4Bit
    PORT(
        Control : IN  std_logic_vector(1 downto 0);
        A : IN  std_logic_vector(N-1 downto 0);
55        B : IN  std_logic_vector(N-1 downto 0);
        nBitOut : OUT std_logic_vector(N-1 downto 0);
        CB : OUT std_logic
    );
    END COMPONENT;
60

    --Inputs
    signal Control : std_logic_vector(1 downto 0) := (others => '0');
    signal A : std_logic_vector(N-1 downto 0) := (others => '0');
65    signal B : std_logic_vector(N-1 downto 0) := (others => '0');

    --Outputs
    signal nBitOut : std_logic_vector(N-1 downto 0);
    signal CB : std_logic;
70    -- No clocks detected in port list. Replace <clock> below with
    -- appropriate port name

BEGIN

75    -- Instantiate the Unit Under Test (UUT)
    uut: ALU_4Bit
    PORT MAP (

```

```

Control => Control ,
80  A => A,
    B => B,
    nBitOut => nBitOut ,
    CB => CB
    );
85

-- Stimulus process
stim_proc: process
--create a function to make a vector a string
90  function vec2str(vec : std_logic_vector) return string is
    variable stmp:string(vec'left+1 downto 1);
    begin
        for i in vec'reverse_range loop
            if vec(i) = '1' then
95              stmp(i+1) := '1';
            elsif vec(i) = 'U' then
                stmp(i+1) := 'U';
            else
                stmp(i+1) := '0';
100            end if;
        end loop;
        return stmp;
    end vec2str;

105  procedure check_add(
    constant in1 : in natural;
    constant in2 : in natural;
    constant res_expected : in natural;
    constant CB_expected : in std_logic) is
110  variable res : natural;
    begin
        -- Assign values to circuit inputs.
        A <= std_logic_vector(to_unsigned(in1, A'length));
        B <= std_logic_vector(to_unsigned(in2, B'length));
115        Control <= ADD_Code;

        wait for TIME_DELTA;
        -- Check output against expected result.
120        res := to_integer(unsigned(nBitOut));
        assert ((res = res_expected) and ( CB = CB_expected ))
        report " " & integer'image(in1) & "+" &
            integer'image(in2) & "=" &
            integer'image(res_expected) & "!=" &
125            integer'image(res) &
            " " &
            "CB exp: " & std_logic'image(CB_expected) &
            "Got: " & std_logic'image(CB)
            severity error;
130    end procedure check_add;

    procedure check_sub(
        constant in1 : in natural;
        constant in2 : in natural;
        constant res_expected : in natural;
        constant CB_expected : in std_logic) is
135        variable res : natural;

```

```

begin
-- Assign values to circuit inputs.
140 A <= std_logic_vector(to_unsigned(in1, A'length));
    B <= std_logic_vector(to_unsigned(in2, B'length));
    Control <= SUB_Code;

145 wait for TIME_DELTA;
-- Check output against expected result.
    res := to_integer(unsigned(nBitOut));
    assert ((res = res_expected) and (CB = CB_expected))
150 report "" & integer'image(in1) & "-" &
        integer'image(in2) & "=" &
        integer'image(res_expected) & "!=" &
        integer'image(res) &
        "" &
        "CB exp: " & std_logic'image(CB_expected) &
155 "Got: " & std_logic'image(CB)
        severity error;
end procedure check_sub;

160 procedure check_or(
    constant in1 : in natural;
    constant in2 : in natural;
    constant res_expected : in natural) is
    variable res : natural;
165 begin
-- Assign values to circuit inputs.
    A <= std_logic_vector(to_unsigned(in1, A'length));
    B <= std_logic_vector(to_unsigned(in2, B'length));
    Control <= OR_Code;

170 wait for TIME_DELTA;
-- Check output against expected result.
    res := to_integer(unsigned(nBitOut));
    assert ((res = res_expected) and (CB = '0'))
175 report "" & integer'image(in1) & "+" &
        integer'image(in2) & "=" &
        integer'image(res_expected) & "!=" &
        integer'image(res) &
        "" &
        "CB: " & std_logic'image(CB)
        severity error;
180 end procedure check_or;

185 procedure check_and(
    constant in1 : in natural;
    constant in2 : in natural;
    constant res_expected : in natural) is
    variable res : natural;
190 begin
-- Assign values to circuit inputs.
    A <= std_logic_vector(to_unsigned(in1, A'length));
    B <= std_logic_vector(to_unsigned(in2, B'length));
195 Control <= AND_Code;

```

```

wait for TIME_DELTA;
-- Check output against expected result.
res := to_integer(unsigned(nBitOut));
report "" & integer'image(in1) & "+" &
integer'image(in2) & "=" &
integer'image(res-expected);

assert ((res = res-expected) and ( CB = '0' ))
report "!=" &
integer'image(res) &
" " &
"CB: " & std_logic'image(CB)
severity error;
end procedure check_and;

begin

--wait for the outputs to stabilize
wait for 100 ns;

--check_add(4,5,9,0);
--check_add(65535, 2, 1, 1);
--check_sub(1234, 234, 1000, 0);
--check_sub(1, 2, 1, 1);

control <= OR_Code;
A <= "0111010101110101";
B <= "1001110100101101";
wait for 50 ns;

control <= AND_Code;
wait for 50 ns;

-- Test adder
for x in (0) to (5) loop
for y in 5432 to 5438 loop
control <= ADD_Code;
A <= std_logic_vector(to_unsigned(x, A'length));
B <= std_logic_vector(to_unsigned(y, B'length));
wait for 50 ns;

assert(nBitOut = std_logic_vector(to_unsigned(x+y, A'length) ) )
report("Bad Add = " & vec2str(nBitOut)
& " expected = " & vec2str( std_logic_vector(to_unsigned(x+y, A'
length)) ) )
& " A = " & vec2str(A)
& " B = " & vec2str(B)
);
end loop;
end loop;

for x in ((2**N)-3) to ((2**N)-1) loop
for y in 0 to 3 loop
control <= ADD_Code;
A <= std_logic_vector(to_unsigned(x, A'length));
B <= std_logic_vector(to_unsigned(y, B'length));

```

```

255     wait for 50 ns;

        assert(nBitOut = std_logic_vector(to_unsigned(x+y, A'length) ) )
        report("Bad Add = " & vec2str(nBitOut)
                & " expected = " & vec2str( std_logic_vector(to_unsigned(x+y, A'
length)) )
                & " A = " & vec2str(A)
                & " B = " & vec2str(B)
        );
    end loop;
end loop;

265
-- Test suber
for x in 0 to 5 loop
    for y in 0 to 5 loop
        control <= SUB.Code;
270     A <= std_logic_vector(to_unsigned(x, A'length));
        B <= std_logic_vector(to_unsigned(y, B'length));
        wait for 50 ns;

        assert(nBitOut = std_logic_vector(to_signed(x-y, A'length)) )
275     report("Bad Sub = " & vec2str(nBitOut)
            & " expected = " & vec2str( std_logic_vector(to_signed(x-y, A'length)) )
            & " A = " & vec2str(A)
            & " B = " & vec2str(B)
        );
280
    end loop;
end loop;

    for x in 12345 to 12350 loop
285     for y in 5 to 7 loop
        control <= SUB.Code;
        A <= std_logic_vector(to_unsigned(x, A'length));
        B <= std_logic_vector(to_unsigned(y, B'length));
        wait for 50 ns;

290     assert(nBitOut = std_logic_vector(to_signed(x-y, A'length)) )
        report("Bad Sub = " & vec2str(nBitOut)
            & " expected = " & vec2str( std_logic_vector(to_signed(x-y, A'length)) )
            & " A = " & vec2str(A)
            & " B = " & vec2str(B)
295
        );
    end loop;
end loop;

300

    wait;
305 end process;

END;

```

Listing 12: ALU-16Bit VHDL

```

--Author      : Brandon Key
--Created     : 02/18/2018
--
5  --Project Name : Lab 3
--File       : ALU_16Bit.vhd
--
--Entity      : ALU_16Bit
--Architecture : struct
10 --
--Tool Version : VHDL '93
--Description  : ALU_16Bit
--
-----

15 library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

package globals is
    constant N : integer := 16;
20 end globals;

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
25 package controlcodes is
    constant AND_Code : std_logic_vector(1 downto 0) := "00";
    constant OR_Code  : std_logic_vector(1 downto 0) := "01";
    constant ADD_Code  : std_logic_vector(1 downto 0) := "10";
30    constant SUB_Code : std_logic_vector(1 downto 0) := "11";
end controlcodes;

library IEEE;
35 use IEEE.STD_LOGIC_1164.ALL;
use IEEE.numeric_std.all;
use work.controlcodes.all;
use work.globals.all;

40 entity ALU_16Bit is
    port(
        Control : in std_logic_vector(1 downto 0);
        A,B      : in std_logic_vector(N-1 downto 0);
        nBitOut  : out std_logic_vector(N-1 downto 0);
45        CB      : out std_logic
    );
end ALU_16Bit;

architecture struct of ALU_16Bit is
50
    --constant N : integer := 4;

    signal ADD_SUB_Out : std_logic_vector(N-1 downto 0);
    signal OR_Out      : std_logic_vector(N-1 downto 0);
55    signal AND_Out    : std_logic_vector(N-1 downto 0);

    signal ADD_SUB_SEL : std_logic;

60 begin

```

```

nBitAdderSubtractor_16Bit : entity work.nBitAdderSubtractor_16Bit
    generic map (N => N)
    port map ( A => A, B => B, SEL => ADD.SUB_SEL, Y => ADD.SUB_Out, CB => CB);

nBitOR_16Bit : entity work.nBitOR_16Bit
    generic map (N => N)
    port map ( A => A, B => B, Y => OR_Out);

nBitAND_16Bit : entity work.nBitAND_16Bit
    generic map (N => N)
    port map ( A => A, B => B, Y => AND_Out);

Controller_16Bit : entity work.Controller_16Bit
    generic map (N => N)
    port map(
        Control      => Control ,
        ADD.SUB_In   => ADD.SUB_Out,
        OR_In        => OR_Out ,
        AND_In        => AND_Out ,
        ADD.SUB_SEL  => ADD.SUB_SEL,
        nBitOut       => nBitOut
    );
end struct;

```

Listing 13: nBitOR-16Bit VHDL

```

--Company      : RIT
--Author       : Brandon Key
--Created      : 1/22/2018
--
--Project Name : Lab 1
--File         : nBitOR_16Bit.vhd
--
--Entity       : nBitOR_16Bit
--Architecture : Dataflow
--
--Tool Version : VHDL '93
--Description  : Entity and structural description of an OR gate

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity nBitOR_16Bit is
    generic (n : integer := 16);
    port(A,B : in std_logic_vector(n-1 downto 0);
         Y : out std_logic_vector(n-1 downto 0)
    );
end nBitOR_16Bit;

architecture Dataflow of nBitOR_16Bit is
begin
    Y <= A or B;-- bitwise or
end Dataflow;

```

Listing 14: nBitAdderSubtractor-16Bit VHDL

```

0  --Company      : RIT
   --Author      : Brandon Key
   --Created     : 02/18/2018
   --
5  --Project Name : Lab 3
   --File        : nBitAdderSubtractor_16Bit.vhd
   --
   --Entity      : nBitAdderSubtractor_16Bit
   --Architecture : struct
10 --
   --Tool Version : VHDL '93
   --Description  : Entity and structural description of an adder subtractor
   --              : SEL = 0 : A+B = Y
   --              : SEL = 1 : A-B = Y
15 --

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.numeric_std.all;

20 entity nBitAdderSubtractor_16Bit is
    generic (n : integer := 16);
    port(
25     A,B : in  std_logic_vector(n-1 downto 0);
        SEL : in  std_logic;
        Y  : out std_logic_vector(n-1 downto 0);
        CB : out std_logic
    );
end nBitAdderSubtractor_16Bit;

30 architecture struct of nBitAdderSubtractor_16Bit is

    component full_adder is
        port(A,B,Cin : in  std_logic;
35         Sum,Cout : out std_logic
        );
    end component full_adder;

    --Create an array to hold all of the carries
40    type carry_array is array (n-1 downto 0) of std_logic;
    signal c_array : carry_array;

    signal B_XOR_SEL : std_logic_vector( (n-1) downto 0);

45 begin

    --Generate the xor statements to be mapped to the full adders
    XORator : for i in 0 to n-1 generate
        B_XOR_SEL(i) <= B(i) xor SEL;
50    end generate XORator;

    generate_adders : for i in 0 to n-1 generate
        i_first: if i = 0 generate
            --The first adder gets SEL as the Cin

```



```

55      adder : full_adder port map(
          A => A(i),
          B => B_XOR_SEL(i),
          Cin => SEL,
          Sum => Y(i),
60      Cout => c_array(i)
        );
    end generate i_first;

    i_last : if i = (n-1) generate
65      --The last adder doesn't have a carry out
      adder : full_adder port map(
          A => A(i),
          B => B_XOR_SEL(i),
          Cin => c_array(i-1),
70      Sum => Y(i),
          Cout => c_array(i)
        );
    end generate i_last;

75    --Middle adders
    i_mid : if (i /= 0) and (i /= (n-1)) generate
      adder : full_adder port map(
          A => A(i),
          B => B_XOR_SEL(i),
80      Cin => c_array(i-1),
          Sum => Y(i),
          Cout => c_array(i)
        );
    end generate i_mid;

85    end generate generate_adders;

    CB <= c_array(n-1) xor SEL;

90 end struct;

```

Listing 15: nBitAND-16Bit VHDL

```

0  -----
--Company      : RIT
--Author       : Brandon Key
--Created      : 1/22/2018
--
5  --Project Name : Lab 1
--File         : nBitAND_16Bit.vhd
--
--Entity       : nBitAND_16Bit
--Architecture : Dataflow
10 --
--Tool Version : VHDL '93
--Description  : Entity and structural description of an AND gate
-----

15 library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity nBitAND_16Bit is
    generic (n : integer := 16);

```

```

20     port(A,B : in  std_logic_vector(n-1 downto 0);
        Y : out  std_logic_vector(n-1 downto 0)
        );
end  nBitAND_16Bit;

25 architecture Dataflow of nBitAND_16Bit is
    begin
        Y <= A AND B; -- bitwise or
end  Dataflow;

```

6.2 SPICE

Listing 16: 1Bit ALU SPICE

```

0 * Example circuit file for simulating PEX

.OPTION DOINODE
.HIER /

5 .INCLUDE "/home/bxk5113/Pyxis_SPT_HEP/ic_projects/Pyxis_SPT/digicdesign/ALU_1Bit/
    ALU_1Bit.cal/ALU_1Bit.pex.netlist"

.LIB /home/bxk5113/Pyxis_SPT_HEP/ic_reflibs/tech_libs/generic13/models/lib.eldo TT

* - Instantiate your parasitic netlist and add the load capacitor
10 ** FORMAT :
* XLAYOUT [all inputs as listed by the ".subckt" line in the included netlist, in
    the order that they appear there] [name of the subcircuit as listed in the
    included netlist]
XLAYOUT CB Y A B CONTROL[1] CONTROL[0] ALU_1Bit
C1 Y 0 120f
C2 CB 0 120f

15

* - Analysis Setup - DC sweep
* FORMAT : .DC [name] [low] [high] [step]
*.DC VFORCE_A 0 1.2 0.01

20

* - Analysis Setup - Trans
* FORMAT : .TRAN [start time] [end time] [time step]
.TRAN 0 160n 0.001n

25

* --- Forces
* FORMAT --- PULSE : [name] [port] [reference (0 means ground)] PULSE [low] [high] [
    delay] [fall time] [rise time] [pulse width] [period]
*
* FORMAT --- DC : [name] [port] [reference (0 means ground)] DC [voltage]
*

30
VFORCE_A A 0 PULSE (0 1.08 40n 0.1n 0.1n 40n 80n)
VFORCE_B B 0 PULSE (0 1.08 80n 0.1n 0.1n 80n 160n)
VFORCE_C1 CONTROL[1] 0 DC 1.08
VFORCE_C0 CONTROL[0] 0 DC 1.08

35
VFORCE_VDD VDD 0 DC 1.08
VFORCE_VSS VSS 0 DC 0

```

```

* — Waveform Outputs
40 .PLOT TRAN V(A)
.PLOT TRAN V(B)
.PLOT TRAN V(CONTROL[1])
.PLOT TRAN V(CONTROL[0])
.PLOT TRAN V(Y)
45 .PLOT TRAN V(CB)

* — Params
.TEMP 125

50 * — Power Measurement
.measure tran static_pwr AVG power from=90ns to=150ns
.measure tran inst_pwr MAX power from=90ns to=150ns

```

Listing 17: 6Bit ALU SPICE

```

0 * Example circuit file for simulating PEX

.OPTION DOINODE
.HIER /

5 .INCLUDE "/home/bxk5113/Pyxis_SPT-HEP/ic_projects/Pyxis_SPT/digicdesign/ALU_16Bit/
  ALU_16Bit.cal/ALU_16Bit.pex.netlist"

.LIB /home/bxk5113/Pyxis_SPT-HEP/ic_reflibs/tech_libs/generic13/models/lib.eldo TT

* - Instantiate your parasitic netlist and add the load capacitor
10 ** FORMAT :
* XLAYOUT [all inputs as listed by the ".subckt" line in the included netlist, in
  the order that they appear there] [name of the subcircuit as listed in the
  included netlist]
XLAYOUT CB NBITOUT[15] NBITOUT[14] NBITOUT[13] NBITOUT[12] NBITOUT[11] NBITOUT[10]
  NBITOUT[9] NBITOUT[8] NBITOUT[7] NBITOUT[6] NBITOUT[5] NBITOUT[4] NBITOUT[3]
  NBITOUT[2] NBITOUT[1] NBITOUT[0] A[15] A[14] A[13] A[12] A[11] A[10] A[9] A[8] A
  [7] A[6] A[5] A[4] A[3] A[2] A[1] A[0] B[15] B[14] B[13] B[12] B[11] B[10] B[9] B
  [8] B[7] B[6] B[5] B[4] B[3] B[2] B[1] B[0] CONTROL[1] CONTROL[0] ALU_16Bit

* Output Capacitance
15 C_CB CB 0 120f
C_NBITOUT[15] NBITOUT[15] 0 120f
C_NBITOUT[14] NBITOUT[14] 0 120f
C_NBITOUT[13] NBITOUT[13] 0 120f
C_NBITOUT[12] NBITOUT[12] 0 120f
20 C_NBITOUT[11] NBITOUT[11] 0 120f
C_NBITOUT[10] NBITOUT[10] 0 120f
C_NBITOUT[9] NBITOUT[9] 0 120f
C_NBITOUT[8] NBITOUT[8] 0 120f
C_NBITOUT[7] NBITOUT[7] 0 120f
25 C_NBITOUT[6] NBITOUT[6] 0 120f
C_NBITOUT[5] NBITOUT[5] 0 120f
C_NBITOUT[4] NBITOUT[4] 0 120f
C_NBITOUT[3] NBITOUT[3] 0 120f
C_NBITOUT[2] NBITOUT[2] 0 120f
30 C_NBITOUT[1] NBITOUT[1] 0 120f
C_NBITOUT[0] NBITOUT[0] 0 120f

* - Analysis Setup - DC sweep

```

```

35 * FORMAT : .DC [name] [low] [high] [step]
*.DC VFORCE_A 0 1.2 0.01

* — Analysis Setup — Trans
* FORMAT : .TRAN [start time] [end time] [time step]
40 .TRAN 0 400n 0.001n

* — Forces
* FORMAT — PULSE : [name] [port] [reference (0 means ground)] PULSE [low] [high] [
    delay] [fall time] [rise time] [pulse width] [period]
*
45 * FORMAT — DC      : [name] [port] [reference (0 means ground)] DC [voltage]
*

VFORCE_C1 CONTROL[1] 0 PULSE (0 1.08 40n 0.1n 0.1n 40n 80n)
VFORCE_C0 CONTROL[0] 0 PULSE (0 1.08 20n 0.1n 0.1n 20n 40n)

50 VFORCE_VDD VDD 0 DC 1.08
VFORCE_VSS VSS 0 DC 0

VFORCE_A[0] A[0] 0 PBIT 0 1.08 0 0 0.01n 0 0.01n 80n 011001 R
55 VFORCE_A[1] A[1] 0 PBIT 0 1.08 0 0 0.01n 0 0.01n 80n 011000 R
VFORCE_A[2] A[2] 0 PBIT 0 1.08 0 0 0.01n 0 0.01n 80n 011001 R
VFORCE_A[3] A[3] 0 PBIT 0 1.08 0 0 0.01n 0 0.01n 80n 011000 R
VFORCE_A[4] A[4] 0 PBIT 0 1.08 0 0 0.01n 0 0.01n 80n 011001 R
VFORCE_A[5] A[5] 0 PBIT 0 1.08 0 0 0.01n 0 0.01n 80n 011000 R
60 VFORCE_A[6] A[6] 0 PBIT 0 1.08 0 0 0.01n 0 0.01n 80n 011001 R
VFORCE_A[7] A[7] 0 PBIT 0 1.08 0 0 0.01n 0 0.01n 80n 011001 R
VFORCE_A[8] A[8] 0 PBIT 0 1.08 0 0 0.01n 0 0.01n 80n 011001 R
VFORCE_A[9] A[9] 0 PBIT 0 1.08 0 0 0.01n 0 0.01n 80n 011001 R
VFORCE_A[10] A[10] 0 PBIT 0 1.08 0 0 0.01n 0 0.01n 80n 011000 R
65 VFORCE_A[11] A[11] 0 PBIT 0 1.08 0 0 0.01n 0 0.01n 80n 011000 R
VFORCE_A[12] A[12] 0 PBIT 0 1.08 0 0 0.01n 0 0.01n 80n 011001 R
VFORCE_A[13] A[13] 0 PBIT 0 1.08 0 0 0.01n 0 0.01n 80n 011001 R
VFORCE_A[14] A[14] 0 PBIT 0 1.08 0 0 0.01n 0 0.01n 80n 011000 R
VFORCE_A[15] A[15] 0 PBIT 0 1.08 0 0 0.01n 0 0.01n 80n 011101 R
70 VFORCE_B[0] B[0] 0 PBIT 0 1.08 0 0 0.01n 0 0.01n 80n 010101 R
VFORCE_B[1] B[1] 0 PBIT 0 1.08 0 0 0.01n 0 0.01n 80n 010100 R
VFORCE_B[2] B[2] 0 PBIT 0 1.08 0 0 0.01n 0 0.01n 80n 010100 R
VFORCE_B[3] B[3] 0 PBIT 0 1.08 0 0 0.01n 0 0.01n 80n 010100 R
VFORCE_B[4] B[4] 0 PBIT 0 1.08 0 0 0.01n 0 0.01n 80n 010101 R
75 VFORCE_B[5] B[5] 0 PBIT 0 1.08 0 0 0.01n 0 0.01n 80n 010100 R
VFORCE_B[6] B[6] 0 PBIT 0 1.08 0 0 0.01n 0 0.01n 80n 010100 R
VFORCE_B[7] B[7] 0 PBIT 0 1.08 0 0 0.01n 0 0.01n 80n 010101 R
VFORCE_B[8] B[8] 0 PBIT 0 1.08 0 0 0.01n 0 0.01n 80n 010101 R
VFORCE_B[9] B[9] 0 PBIT 0 1.08 0 0 0.01n 0 0.01n 80n 010101 R
80 VFORCE_B[10] B[10] 0 PBIT 0 1.08 0 0 0.01n 0 0.01n 80n 010101 R
VFORCE_B[11] B[11] 0 PBIT 0 1.08 0 0 0.01n 0 0.01n 80n 010100 R
VFORCE_B[12] B[12] 0 PBIT 0 1.08 0 0 0.01n 0 0.01n 80n 010101 R
VFORCE_B[13] B[13] 0 PBIT 0 1.08 0 0 0.01n 0 0.01n 80n 010101 R
VFORCE_B[14] B[14] 0 PBIT 0 1.08 0 0 0.01n 0 0.01n 80n 010101 R
85 VFORCE_B[15] B[15] 0 PBIT 0 1.08 0 0 0.01n 0 0.01n 80n 011111 R

90
* — Waveform Outputs
.PLOT TRAN V(CB)

```

```

. PLOT TRAN V(NBITOUT[15])
. PLOT TRAN V(NBITOUT[14])
95 . PLOT TRAN V(NBITOUT[13])
. PLOT TRAN V(NBITOUT[12])
. PLOT TRAN V(NBITOUT[11])
. PLOT TRAN V(NBITOUT[10])
. PLOT TRAN V(NBITOUT[9])
100 . PLOT TRAN V(NBITOUT[8])
. PLOT TRAN V(NBITOUT[7])
. PLOT TRAN V(NBITOUT[6])
. PLOT TRAN V(NBITOUT[5])
. PLOT TRAN V(NBITOUT[4])
105 . PLOT TRAN V(NBITOUT[3])
. PLOT TRAN V(NBITOUT[2])
. PLOT TRAN V(NBITOUT[1])
. PLOT TRAN V(NBITOUT[0])
. PLOT TRAN V(A[15])
110 . PLOT TRAN V(A[14])
. PLOT TRAN V(A[13])
. PLOT TRAN V(A[12])
. PLOT TRAN V(A[11])
. PLOT TRAN V(A[10])
115 . PLOT TRAN V(A[9])
. PLOT TRAN V(A[8])
. PLOT TRAN V(A[7])
. PLOT TRAN V(A[6])
. PLOT TRAN V(A[5])
120 . PLOT TRAN V(A[4])
. PLOT TRAN V(A[3])
. PLOT TRAN V(A[2])
. PLOT TRAN V(A[1])
. PLOT TRAN V(A[0])
125 . PLOT TRAN V(B[15])
. PLOT TRAN V(B[14])
. PLOT TRAN V(B[13])
. PLOT TRAN V(B[12])
. PLOT TRAN V(B[11])
130 . PLOT TRAN V(B[10])
. PLOT TRAN V(B[9])
. PLOT TRAN V(B[8])
. PLOT TRAN V(B[7])
. PLOT TRAN V(B[6])
135 . PLOT TRAN V(B[5])
. PLOT TRAN V(B[4])
. PLOT TRAN V(B[3])
. PLOT TRAN V(B[2])
. PLOT TRAN V(B[1])
140 . PLOT TRAN V(B[0])
. PLOT TRAN V(CONTROL[1])
. PLOT TRAN V(CONTROL[0])

145 * — Params
. TEMP 125

* — Power Measurement
. measure tran static_pwr AVG power from=90ns to=150ns
150 . measure tran inst_pwr MAX power from=90ns to=150ns

```

7 References

Key, Brandon A. *CMPE 260 Laboratory Exercise 3 Arithmetic Logic Unit*. CMPE 260 Laboratory Exercise 3 Arithmetic Logic Unit.