
CMPE-630 Digital IC Design
Laboratory Exercise 7
Autolayout Design Techniques (HDL-Layout)

Brandon Key
Performed: 6 Nov 2019
Submitted: 13 Nov 2019

Instructor: Dr. Amlan Ganguly
TAs: Abhishek Vashist
Andrew Fountain
Piers Kwan

By submitting this report, you attest that you neither have given nor have received any assistance (including writing, collecting data, plotting figures, tables or graphs, or using previous student reports as a reference), and you further acknowledge that giving or receiving such assistance will result in a failing grade for this course.

Your Signature: _____

1 Abstract

2 Design Methodology and Theory

The world of IC design is a very large and complex one. Engineering time is a critical factor when trying to create designs. An engineer tries to minimize power and cost, while maximizing performance. Modern ICs are very complex and manual engineer effort is not feasible. Fortunately, auto layout tools exists so that non-critical parts can be generated quickly. In this exercise, a single bit ALU and a 16-bit ALU were designed, automatically laid out and then power and timing results were extracted.

For all components designed in this exercise, VHDL was written to describe the functionality of the component. Leonardo Spectrum was used to turn the VHDL into synthesizable logic. The VHDL was then functionally tested with a test bench using Questa Sim.

2.1 Functional Simulation

The ALUs in this exercise had a simple 2 bit op-code which can be seen in Table 1.

Table 1: ALU Operations

OpCode	Operation	Operands
00	AND	A AND B
01	OR	A OR B
10	ADD	A + B
11	SUB	A - B

2.1.1 1 Bit ALU

The 1 Bit ALU designed in this exercise was created from behavioral VHDL (see Listing 10). A Questa Sim simulation was performed to test the functionality of the 1 bit ALU. The test bench can be seen in Listing 9. The test bench went through every op-code and every input. The resulting waveforms can be seen in Figure 1.

 


Figure 1: Functional Simulation of 1-bit ALU

The 1 Bit ALU functioned properly.

2.1.2 16 Bit ALU

The 16-bit ALU was created structurally with generically large structures. The VHDL that describes the ALU can be seen in Listing 12. While the 1-bit ALU could have a full test bench that tested every input, the 16-bit ALU was far too large to do the same. Instead, a few test cases were selected to test each function of the ALU. Each component in the ALU was previously tested, so

the main goal was to test the setup of the ALU itself. The testbench code can be seen in Listing 4. The AND functionality was tested first and captured in Figure 2.

 


Figure 2: Functional Simulation of 16-bit ALU: AND

Once the and functionality was verified, the OR functionality was tested and recorded in Figure 3.

 


Figure 3: Functional Simulation of 16-bit ALU: OR

X

 


Figure 4: Functional Simulation of 16-bit ALU: Addition

 


Figure 5: Functional Simulation of 16-bit ALU: Addition with carry

 


Figure 6: Functional Simulation of 16-bit ALU: Subtraction

 


Figure 7: Functional Simulation of 16-bit ALU: Subtraction with negative result

2.2 Schematic

2.2.1 1-Bit ALU

Behavioral

 


Figure 8: 1 Bit ALU Schematic

2.2.2 n-Bit ALU

Structural

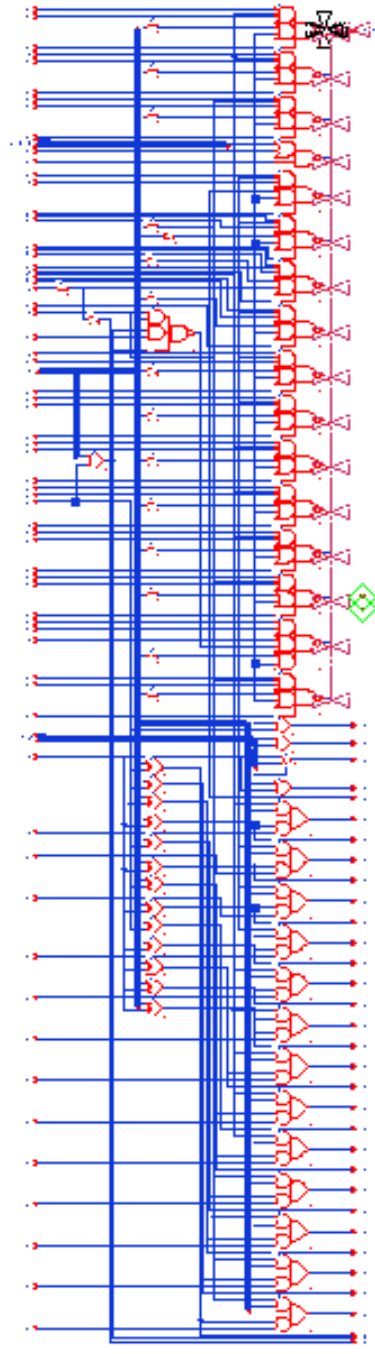


Figure 9: 16 Bit ALU Schematic Page 1

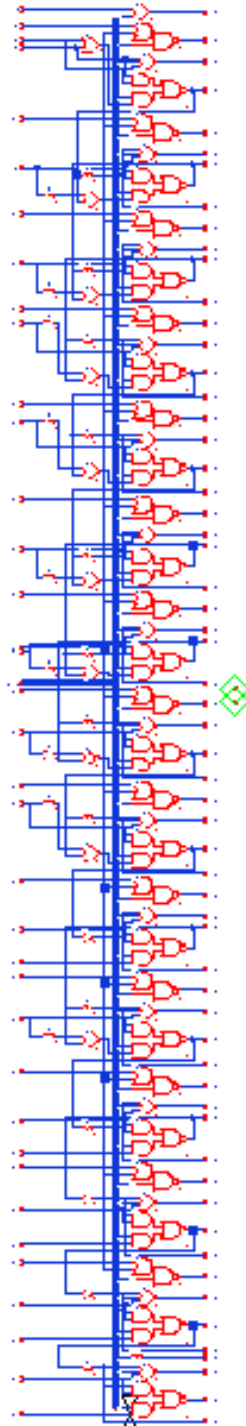


Figure 10: 16 Bit ALU Schematic Page 2

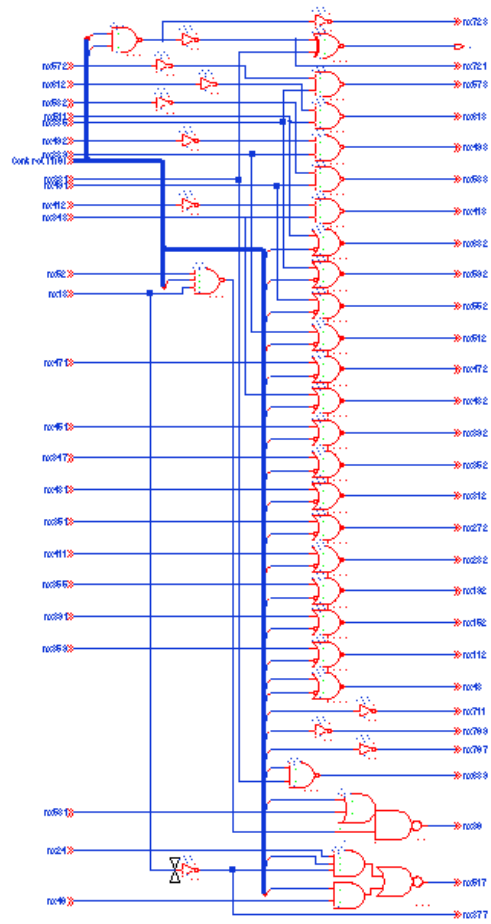


Figure 11: 16 Bit ALU Schematic Page 3

3 Results and Analysis

3.1 Layout

3.1.1 1 Bit ALU

 


Figure 12: 1 Bit ALU Layout

3.1.2 16 Bit ALU

Area 0.7

Power Routing

- Varying levels of routing completion time
- Slight preference for jogs over via to fill the area.
- Rip
- Under rip options:
 - Rips Most Aggressive
 - Automatic Rip Passes
 - Reroute

- Under Advanced:
Allow all directions for stubs
Via Options \checkmark Use via generator

 


Figure 13: 16 Bit ALU Layout

3.2 Timing

3.2.1 1 Bit ALU

It was found that subtraction was by far the slowest operation, with the timing difference visible in the waveforms.

 


Figure 14: 1 Bit ALU Worst Case Timing Simulation

Table 2: 1-Bit ALU Worst Case Rise Time

Output	Rise Time (ps)	A	B	Operation
Y	1167.5	1	0	SUB
Carry	1557.1	0	1	SUB

Table 3: 1-Bit ALU Worst Case Fall Time

Output	Fall Time (ps)	A	B	Operation
Y	1001.3	1	1	SUB
Carry	1068.1	1	1	SUB

Table 4: 1-Bit ALU Worst Case Propagation Time High to Low

Output	Tp,HL (ps)	A	B	Operation
Y	701.8	1	1	SUB
Carry	810.3	1	1	SUB

Table 5: 1-Bit ALU Worst Case Propagation Time Low to High

Output	Tp,LH (ps)	A	B	Operation
Y	686.1	1	0	SUB
Carry	996.7	0	1	SUB

3.2.2 16 Bit ALU

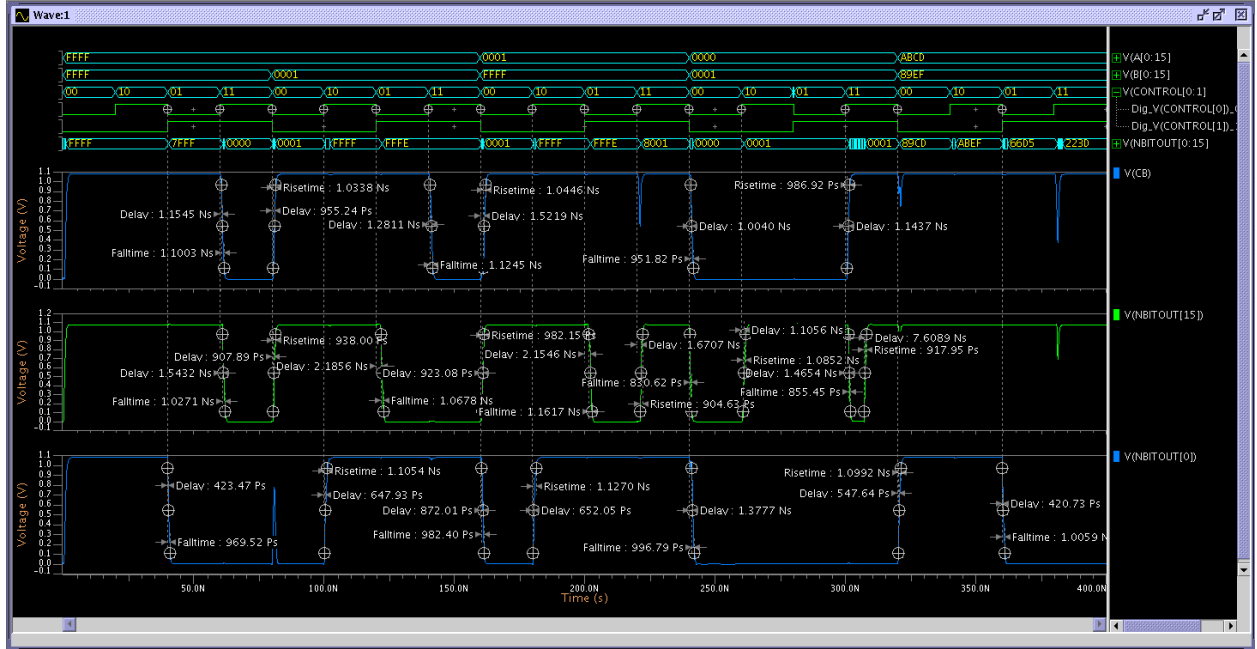


Figure 15: 16-Bit ALU Timing Waveforms

Table 6: 16-Bit ALU Worst Case Rise Time

Input		Output		Rise Time (ps)		
A	B	Y	Op	Y	Op	CB
0x0000	0x0000	Y[15]	11	938.0	11	1033.8
0xFFFF	0xFFFF	Y[15]	11	938.0	01	1124.5
0xFFFF	0x0001	Y[15]	11	982.2	11	1044.6
0x0001	0xFFFF	Y[15]	01	904.63	00	1044.6
0x0000	0x0001	Y[0]	00	1085.2	01	986.9
0xABCD	0x89EF	Y[15]	01	917.9	11	951.8

Table 7: 16-Bit ALU Worst Case Fall Time

Input		Output		Fall Time (ps)		
A	B	Y	Op	Y	Op	CB
0x0000	0x0000	Y[15]	01	1100.3	01	1027.1
0xFFFF	0xFFFF	Y[15]	10	1067.0	10	1033.8
0xFFFF	0x0001	Y[15]	11	830.6	01	1124.5
0x0001	0xFFFF	Y[15]	10	1161.7	11	951.8
0x0000	0x0001	Y[0]	00	996.8	10	1005.9
0xABCD	0x89EF	Y[15]	01	855.5	01	969.5

Table 8: 16-Bit ALU Worst Case Propagation Time High to Low

Input		Output	Op	Tp,HL (ps)		
A	B	Y		Y	Op	CB
0x0000	0x0000	Y[15]	01	907.9	01	1154.5
0xFFFF	0xFFFF	Y[15]	10	2185.6	10	1281.1
0xFFFF	0x0001	Y[15]	11	2154.6	01	1004.0
0x0001	0xFFFF	Y[15]	10	1670.7	11	1143.7
0x0000	0x0001	Y[0]	00	1377.7	10	920.7
0xABCD	0x89EF	Y[15]	01	1465.4	01	872.0

Table 9: 16-Bit ALU Worst Case Propagation Time Low to High

Input		Output	Op	Tp,LH (ps)		
A	B	Y		Y	Op	CB
0x0000	0x0000	Y[15]	11	2185.6	11	955.2
0xFFFF	0xFFFF	Y[15]	11	2154.6	01	1521.9
0xFFFF	0x0001	Y[15]	11	1670.7	11	1143.7
0x0001	0xFFFF	Y[15]	01	1085.2	00	947.6
0x0000	0x0001	Y[0]	00	1099.2	01	1047.9
0xABCD	0x89EF	Y[15]	01	7608.9	11	1127.0

3.3 Power

3.3.1 1 Bit ALU

3.3.2 16 Bit ALU

4 Conclusion

5 Appendix

5.1 VHDL

Listing 1: Controller-16Bit VHDL

```

0  ---Company      : RIT
   ---Author       : Brandon Key
   ---Created      : 02/18/2018
   ---
5  ---Project Name : Lab 3
   ---File         : Controller_16Bit.vhd
   ---
   ---Entity       : Controller_16Bit
   ---Architecture : behav
10 ---
   ---Tool Version : VHDL '93
   ---Description  : *SPECIAL controller, DO NOT USE OUTSIDE THIS PROJECT*
   ---              : Takes 4 bit control signal bit
   ---              : Figures out the proper output
15 ---

```

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.numeric_std.all;
20 --use work.controlcodes.all;

entity Controller_16Bit is
    generic (n : integer := 16);
    port(
25         Control : in std_logic_vector(1 downto 0);

        ADD_SUB_In : in std_logic_vector(N-1 downto 0);
        OR_In      : in std_logic_vector(N-1 downto 0);
        AND_In     : in std_logic_vector(N-1 downto 0);
30
        ADD_SUB_SEL : out std_logic;

        nBitOut : out std_logic_vector(N-1 downto 0)
    );
35 end Controller_16Bit;

architecture behav of Controller_16Bit is

    constant AND_Code : std_logic_vector(1 downto 0) := "00";
    constant OR_Code  : std_logic_vector(1 downto 0) := "01";
    constant ADD_Code : std_logic_vector(1 downto 0) := "10";
    constant SUB_Code : std_logic_vector(1 downto 0) := "11";
40

begin
45
    --Proces to set the select signal when subtraction should occur
    ADD_SUB_SEL_proc: with Control select
        ADD_SUB_SEL <= '1' when SUB_Code,
                       '0' when others;
50

    nBitOut_proc: with Control select
        nBitOut <= ADD_SUB_In when ADD_Code,
                  ADD_SUB_In when SUB_Code,
                  OR_In when OR_Code,
                  AND_In when AND_Code,
55                  (others => '0') when others;

end behav;

```

Listing 2: nBitAdderSubtractor-4Bit VHDL

```

0  --Company      : RIT
   --Author       : Brandon Key
   --Created      : 02/18/2018
   --
5  --Project Name : Lab 3
   --File        : nBitAdderSubtractor_4Bit.vhd
   --
   --Entity       : nBitAdderSubtractor_4Bit
   --Architecture : struct
10 --
   --Tool Version : VHDL '93
   --Description  : Entity and structural description of an adder subtractor

```

```

--          : SEL = 0 : A+B = Y
--          : SEL = 1 : A-B = Y
15
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.numeric_std.all;
20
entity nBitAdderSubtractor_4Bit is
    generic (n : integer := 16);
    port(
        A,B : in  std_logic_vector(n-1 downto 0);
        SEL : in  std_logic;
        Y   : out std_logic_vector(n-1 downto 0);
        CB  : out std_logic
    );
end nBitAdderSubtractor_4Bit;
30
architecture struct of nBitAdderSubtractor_4Bit is

    component full_adder is
        port(A,B,Cin : in  std_logic;
              Sum,Cout : out std_logic
        );
    end component full_adder;

    --Create an array to hold all of the carries
    type carry_array is array (n-1 downto 0) of std_logic;
    signal c_array : carry_array;

    signal B_XOR_SEL : std_logic_vector( (n-1) downto 0);
45
begin

    --Generate the xor statements to be mapped to the full adders
    XORator : for i in 0 to n-1 generate
        B_XOR_SEL(i) <= B(i) xor SEL;
    end generate XORator;
50

    generate_adders : for i in 0 to n-1 generate
        i_first : if i = 0 generate
            --The first adder gets SEL as the Cin
            adder : full_adder port map(
                A => A(i),
                B => B_XOR_SEL(i),
                Cin => SEL,
                Sum => Y(i),
                Cout => c_array(i)
            );
        end generate i_first;

        i_last : if i = (n-1) generate
            --The last adder doesn't have a carry out
            adder : full_adder port map(
                A => A(i),
                B => B_XOR_SEL(i),
                Cin => c_array(i-1),
                Sum => Y(i),
                Cout => c_array(i)
            );
        end generate i_last;
65
    end generate generate_adders;
70
end struct;

```

```

    );
    end generate i_last;

75    --Middle adders
    i_mid : if (i /= 0) and (i /= (n-1)) generate
        adder : full_adder port map(
            A => A(i),
            B => B_XOR_SEL(i),
80            Cin => c_array(i-1),
            Sum => Y(i),
            Cout => c_array(i)
        );
    end generate i_mid;

85    end generate generate_adders;

    CB <= c_array(n-1) xor SEL;

90 end struct;

```

Listing 3: FullAdder VHDL

```

0  --Company      : RIT
   --Author       : Brandon Key
   --Created      : 02/18/2018
   --
5  --Project Name : Lab 3
   --File         : Full_Adder.vhd
   --
   --Entity       : Full_Adder
   --Architecture : behav
10 --
   --Tool Version : VHDL '93
   --Description  : Entity and behavioral description of a full adder
   --
15
   library IEEE;
   use IEEE.STD_LOGIC_1164.ALL;

   entity Full_Adder is
20       port (A,B,Cin : in std_logic;
              Sum,Cout : out std_logic
              );
   end Full_Adder;

25 architecture behav of Full_Adder is
   begin
       --uses select assignment to implement the truth table of a full adder

30       sum_proc: with std_logic_vector'(Cin&A&B) select
           Sum <= '0' when "000",
                   '1' when "001",
                   '1' when "010",
                   '0' when "011",
35                   '1' when "100",
                   '0' when "101",

```

```

        '0' when "110",
        '1' when "111",
        '0' when others;

40 Cout_proc: with std_logic_vector'(Cin&A&B) select
        Cout <= '0' when "000",
        '0' when "001",
        '0' when "010",
45        '1' when "011",
        '0' when "100",
        '1' when "101",
        '1' when "110",
        '1' when "111",
50        '0' when others;

end behav;

```

Listing 4: ALU-16Bit-tb VHDL

```

0  -- Company: RIT
   -- Engineer: Brandon Key
   --
   -- Create Date: 17:51:58 02/28/2018
5  -- Design Name:
   -- Module Name: /home/ise/DSDII/Lab/Lab3/SourceCode/ALU_16Bit_tb.vhd
   -- Project Name: Lab3
   -- Target Device:
   -- Tool versions:
10  -- Description:
   --
   -- VHDL Test Bench Created by ISE for module: ALU_16Bit
   --
   -- Dependencies:
15  --
   -- Revision:
   -- Revision 0.01 - File Created
   -- Additional Comments:
   --
20  -- Notes:
   -- This testbench has been automatically generated using types std_logic and
   -- std_logic_vector for the ports of the unit under test. Xilinx recommends
   -- that these types always be used for the top-level I/O of a design in order
   -- to guarantee that the testbench will bind correctly to the post-implementation
25  -- simulation model.

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;
30 --use work.globals.all;
--use work.controlcodes.all;

ENTITY ALU_16Bit_tb IS
END ALU_16Bit_tb;

35 ARCHITECTURE behavior OF ALU_16Bit_tb IS

    constant AND_Code : std_logic_vector(1 downto 0) := "00";
    constant OR_Code : std_logic_vector(1 downto 0) := "01";

```



```

40  constant ADD_Code : std_logic_vector(1 downto 0) := "10";
    constant SUB_Code : std_logic_vector(1 downto 0) := "11";

    type testRecordArray is array (natural range <>) of std_logic_vector(2 downto 0)
    ;

45  constant n:integer := 16;
    -- "Time" that will elapse between test vectors we submit to the component.
    constant TIMEDELTA : time := 50 ns;

50  -- Component Declaration for the Unit Under Test (UUT)
    COMPONENT ALU_16Bit
    PORT(
        Control : IN  std_logic_vector(1 downto 0);
        A : IN  std_logic_vector(N-1 downto 0);
55        B : IN  std_logic_vector(N-1 downto 0);
        nBitOut : OUT std_logic_vector(N-1 downto 0);
        CB : OUT std_logic
    );
    END COMPONENT;

60

    --Inputs
    signal Control : std_logic_vector(1 downto 0) := (others => '0');
    signal A : std_logic_vector(N-1 downto 0) := (others => '0');
65    signal B : std_logic_vector(N-1 downto 0) := (others => '0');

    --Outputs
    signal nBitOut : std_logic_vector(N-1 downto 0);
    signal CB : std_logic;
70    -- No clocks detected in port list. Replace <clock> below with
    -- appropriate port name

BEGIN

75    -- Instantiate the Unit Under Test (UUT)
    uut: ALU_16Bit
    PORT MAP (
        Control => Control,
80        A => A,
        B => B,
        nBitOut => nBitOut,
        CB => CB
    );

85

    -- Stimulus process
    stim_proc: process
        --create a function to make a vector a string
90        function vec2str(vec : std_logic_vector) return string is
            variable stmp:string(vec'left+1 downto 1);
            begin
                for i in vec'reverse_range loop
                    if vec(i) = '1' then
95                        stmp(i+1) := '1';
                    elsif vec(i) = 'U' then
                        stmp(i+1) := 'U';

```

```

else
    stmp(i+1) := '0';
100 end if;
end loop;
return stmp;
end vec2str;

105 procedure check_add(
    constant in1 : in natural;
    constant in2 : in natural;
    constant res_expected : in natural;
    constant CB_expected : in std_logic) is
110 variable res : natural;
begin
    -- Assign values to circuit inputs.
    A <= std_logic_vector(to_unsigned(in1, A'length));
    B <= std_logic_vector(to_unsigned(in2, B'length));
115 Control <= ADD_Code;

    wait for TIME_DELTA;
    -- Check output against expected result.
120 res := to_integer(unsigned(nBitOut));
    assert ((res = res_expected) and (CB = CB_expected))
    report "" & integer'image(in1) & "+" &
        integer'image(in2) & "=" &
        integer'image(res_expected) & "!=" &
125 integer'image(res) &
        " " &
        "CB exp: " & std_logic'image(CB_expected) &
        "Got: " & std_logic'image(CB)
        severity error;
130 end procedure check_add;

procedure check_sub(
    constant in1 : in natural;
    constant in2 : in natural;
135 constant res_expected : in natural;
    constant CB_expected : in std_logic) is
    variable res : natural;
begin
    -- Assign values to circuit inputs.
    A <= std_logic_vector(to_unsigned(in1, A'length));
    B <= std_logic_vector(to_unsigned(in2, B'length));
140 Control <= SUB_Code;

    wait for TIME_DELTA;
    -- Check output against expected result.
    res := to_integer(unsigned(nBitOut));
    assert ((res = res_expected) and (CB = CB_expected))
    report "" & integer'image(in1) & "-" &
145 integer'image(in2) & "=" &
        integer'image(res_expected) & "!=" &
        integer'image(res) &
        " " &
        "CB exp: " & std_logic'image(CB_expected) &
        "Got: " & std_logic'image(CB)
        severity error;
150
155

```

```

end procedure check_sub;

160 procedure check_or(
    constant in1 : in natural;
    constant in2 : in natural;
    constant res_expected : in natural) is
165 variable res : natural;
begin
    -- Assign values to circuit inputs.
    A <= std_logic_vector(to_unsigned(in1, A'length));
    B <= std_logic_vector(to_unsigned(in2, B'length));
    Control <= OR_Code;

170

    wait for TIME_DELTA;
    -- Check output against expected result.
    res := to_integer(unsigned(nBitOut));
175 assert ((res = res_expected) and ( CB = '0' ))
    report " " & integer'image(in1) & "+" &
        integer'image(in2) & "=" &
        integer'image(res_expected) & "!=" &
        integer'image(res) &
180 " " &
        "CB: " & std_logic'image(CB)
    severity error;
end procedure check_or;

185

190 procedure check_and(
    constant in1 : in natural;
    constant in2 : in natural;
    constant res_expected : in natural) is
    variable res : natural;
begin
    -- Assign values to circuit inputs.
    A <= std_logic_vector(to_unsigned(in1, A'length));
    B <= std_logic_vector(to_unsigned(in2, B'length));
195 Control <= AND_Code;

    wait for TIME_DELTA;
    -- Check output against expected result.
    res := to_integer(unsigned(nBitOut));
200 report " " & integer'image(in1) & "+" &
        integer'image(in2) & "=" &
        integer'image(res_expected);

    assert ((res = res_expected) and ( CB = '0' ))
205 report "!=" &
        integer'image(res) &
        " " &
        "CB: " & std_logic'image(CB)
    severity error;
210 end procedure check_and;

begin
215

```

```

--wait for the outputs to stabilize
wait for 100 ns;

--check_add(4,5,9,0);
220 --check_add(65535, 2, 1, 1);
--check_sub(1234, 234, 1000, 0);
--check_sub(1, 2, 1, 1);

control <= OR_Code;
225 A <= "0111010101110101";
B <= "1001110100101101";
wait for 50 ns;

control <= AND_Code;
230 wait for 50 ns;

-- Test adder
for x in (0) to (5) loop
235   for y in 5432 to 5438 loop
     control <= ADD_Code;
     A <= std_logic_vector(to_unsigned(x, A'length));
     B <= std_logic_vector(to_unsigned(y, B'length));
     wait for 50 ns;

240     assert(nBitOut = std_logic_vector(to_unsigned(x+y, A'length) ) )
     report("Bad Add = " & vec2str(nBitOut)
           & " expected = " & vec2str( std_logic_vector(to_unsigned(x+y, A'
length)) )
           & " A = " & vec2str(A)
           & " B = " & vec2str(B)
245     );
   end loop;
end loop;

250 for x in ((2**N)-3) to ((2**N)-1) loop
   for y in 0 to 3 loop
     control <= ADD_Code;
     A <= std_logic_vector(to_unsigned(x, A'length));
     B <= std_logic_vector(to_unsigned(y, B'length));
255     wait for 50 ns;

     assert(nBitOut = std_logic_vector(to_unsigned(x+y, A'length) ) )
     report("Bad Add = " & vec2str(nBitOut)
           & " expected = " & vec2str( std_logic_vector(to_unsigned(x+y, A'
length)) )
           & " A = " & vec2str(A)
           & " B = " & vec2str(B)
260     );
   end loop;
end loop;

265 -- Test suber
for x in 0 to 5 loop
   for y in 0 to 5 loop
     control <= SUB_Code;
270     A <= std_logic_vector(to_unsigned(x, A'length));
     B <= std_logic_vector(to_unsigned(y, B'length));
     wait for 50 ns;

```

```

275     assert(nBitOut = std_logic_vector(to_signed(x-y, A'length)) )
    report("Bad Sub = " & vec2str(nBitOut)
        & " expected = " & vec2str( std_logic_vector(to_signed(x-y, A'length)) )
        & " A = " & vec2str(A)
        & " B = " & vec2str(B)
    );

280     end loop;
end loop;

285     for x in 12345 to 12350 loop
        for y in 5 to 7 loop
            control <= SUB.Code;
            A <= std_logic_vector(to_unsigned(x, A'length));
            B <= std_logic_vector(to_unsigned(y, B'length));
            wait for 50 ns;

290             assert(nBitOut = std_logic_vector(to_signed(x-y, A'length)) )
            report("Bad Sub = " & vec2str(nBitOut)
                & " expected = " & vec2str( std_logic_vector(to_signed(x-y, A'length)) )
                & " A = " & vec2str(A)
                & " B = " & vec2str(B)
            );

295             end loop;
        end loop;

300

        wait;
    end process;

305
END;

```

Listing 5: Controller-4Bit VHDL

```

0  -----
--Company      : RIT
--Author       : Brandon Key
--Created      : 02/18/2018
--
5  --Project Name : Lab 3
--File         : Controller_4Bit.vhd
--
--Entity       : Controller_4Bit
--Architecture : behav
10 --
--Tool Version : VHDL '93
--Description  : *SPECIAL controller , DO NOT USE OUTSIDE THIS PROJECT*
--              : Takes 4 bit control signal bit
--              : Figures out the proper output
15 -----

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.numeric_std.all;
20 --use work.controlcodes.all;

```

```

entity Controller_4Bit is
    generic (n : integer := 16);
    port(
25      Control : in  std_logic_vector(1 downto 0);

        ADD_SUB_In : in std_logic_vector(N-1 downto 0);
        OR_In      : in std_logic_vector(N-1 downto 0);
        AND_In     : in std_logic_vector(N-1 downto 0);
30
        ADD_SUB_SEL : out std_logic;

        nBitOut : out std_logic_vector(N-1 downto 0)
        );
35 end Controller_4Bit;

architecture behav of Controller_4Bit is

    constant AND_Code : std_logic_vector(1 downto 0) := "00";
    constant OR_Code  : std_logic_vector(1 downto 0) := "01";
    constant ADD_Code : std_logic_vector(1 downto 0) := "10";
    constant SUB_Code : std_logic_vector(1 downto 0) := "11";

begin
45
    --Proces to set the select signal when subtraction should occur
    ADD_SUB_SEL_proc: with Control select
        ADD_SUB_SEL <= '1' when SUB_Code,
                       '0' when others;

50
    nBitOut_proc: with Control select
        nBitOut <= ADD_SUB_In when ADD_Code,
                  ADD_SUB_In when SUB_Code,
                  OR_In when OR_Code,
                  AND_In when AND_Code,
55
                  (others => '0') when others;

end behav;

```

Listing 6: nBitOR-4Bit VHDL

```

0  -----
--Company      : RIT
--Author       : Brandon Key
--Created      : 1/22/2018
--
5  --Project Name : Lab 1
--File         : nBitOR_4Bit.vhd
--
--Entity       : nBitOR_4Bit
--Architecture : Dataflow
10 -----
--Tool Version : VHDL '93
--Description  : Entity and structural description of an OR gate
-----

15 library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

```

```

entity nBitOR_4Bit is
    generic (n : integer := 16);
20    port(A,B : in std_logic_vector(n-1 downto 0);
        Y : out std_logic_vector(n-1 downto 0)
        );
end nBitOR_4Bit;

25 architecture Dataflow of nBitOR_4Bit is
    begin
        Y <= A or B;-- bitwise or
    end Dataflow;

```

Listing 7: ALU-4Bit VHDL

```

0  --Company      : RIT
   --Author       : Brandon Key
   --Created      : 02/18/2018
   --
5  --Project Name : Lab 3
   --File         : ALU_4Bit.vhd
   --
   --Entity       : ALU_4Bit
   --Architecture : struct
10  --
   --Tool Version : VHDL '93
   --Description  : ALU_4Bit
   --
15 library IEEE;
   use IEEE.STD_LOGIC_1164.ALL;

   package globals is
       constant N : integer := 16;
20 end globals;

   library IEEE;
   use IEEE.STD_LOGIC_1164.ALL;

25 package controlcodes is
       constant AND_Code : std_logic_vector(1 downto 0) := "00";
       constant OR_Code  : std_logic_vector(1 downto 0) := "01";
       constant ADD_Code : std_logic_vector(1 downto 0) := "10";
       constant SUB_Code : std_logic_vector(1 downto 0) := "11";
30 end controlcodes;

   library IEEE;
35 use IEEE.STD_LOGIC_1164.ALL;
   use IEEE.numeric_std.all;
   use work.controlcodes.all;
   use work.globals.all;

40 entity ALU_4Bit is
    port(
        Control : in std_logic_vector(1 downto 0);
        A,B     : in std_logic_vector(N-1 downto 0);
        nBitOut : out std_logic_vector(N-1 downto 0);

```

```

45      CB      : out std_logic
        );
end   ALU_4Bit;

architecture struct of ALU_4Bit is
50
    --constant N : integer := 4;

    signal ADD_SUB_Out : std_logic_vector(N-1 downto 0);
    signal OR_Out      : std_logic_vector(N-1 downto 0);
55    signal AND_Out    : std_logic_vector(N-1 downto 0);

    signal ADD_SUB_SEL : std_logic;

60 begin

    nBitAdderSubtractor_4Bit : entity work.nBitAdderSubtractor_4Bit
        generic map (N => N)
        port map ( A => A, B => B, SEL => ADD_SUB_SEL, Y => ADD_SUB_Out, CB => CB);
65

    nBitOR_4Bit : entity work.nBitOR_4Bit
        generic map (N => N)
        port map ( A => A, B => B, Y => OR_Out);
70

    nBitAND_4Bit : entity work.nBitAND_4Bit
        generic map (N => N)
        port map ( A => A, B => B, Y => AND_Out);
75

    Controller_4Bit : entity work.Controller_4Bit
        generic map (N => N)
        port map(
80      Control      => Control,
      ADD_SUB_In    => ADD_SUB_Out,
      OR_In         => OR_Out,
      AND_In        => AND_Out,
      ADD_SUB_SEL   => ADD_SUB_SEL,
      nBitOut       => nBitOut
85      );

end   struct;

```

Listing 8: nBitAND-4Bit VHDL

```

0  ---Company      : RIT
   ---Author       : Brandon Key
   ---Created      : 1/22/2018
   ---
5  ---Project Name : Lab 1
   ---File         : nBitAND_4Bit.vhd
   ---
   ---Entity       : nBitAND_4Bit
   ---Architecture : Dataflow
10 ---
   ---Tool Version : VHDL '93
   ---Description  : Entity and structural description of an AND gate

```



```

15 library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity nBitAND_4Bit is
    generic (n : integer := 16);
20 port (A,B : in std_logic_vector(n-1 downto 0);
        Y : out std_logic_vector(n-1 downto 0)
        );
end nBitAND_4Bit;

25 architecture Dataflow of nBitAND_4Bit is
begin
    Y <= A AND B; -- bitwise or
end Dataflow;

```

Listing 9: ALU-1Bit-tb VHDL

```

0  -- Company: RIT
   -- Engineer: Brandon Key
   --
   -- Create Date: 17:51:58 02/28/2018
5  -- Design Name:
   -- Module Name: /home/ise/DSDII/Lab/Lab3/SourceCode/ALU_1Bit_tb.vhd
   -- Project Name: Lab3
   -- Target Device:
   -- Tool versions:
10 -- Description:
   --
   -- VHDL Test Bench Created by ISE for module: ALU_1Bit
   --
   -- Dependencies:
15 --
   -- Revision:
   -- Revision 0.01 - File Created
   -- Additional Comments:
   --
20 -- Notes:
   -- This testbench has been automatically generated using types std_logic and
   -- std_logic_vector for the ports of the unit under test. Xilinx recommends
   -- that these types always be used for the top-level I/O of a design in order
   -- to guarantee that the testbench will bind correctly to the post-implementation
25 -- simulation model.

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;
30 --use work.globals.all;
--use work.controlcodes.all;

ENTITY ALU_1Bit_tb IS
END ALU_1Bit_tb;

35 ARCHITECTURE behavior OF ALU_1Bit_tb IS

    CONSTANT AND_Code : std_logic_vector(1 DOWNTO 0) := "00";
    CONSTANT OR_Code  : std_logic_vector(1 DOWNTO 0) := "01";

```

```

40  CONSTANT ADD_Code : std_logic_vector(1 DOWNTO 0) := "10";
    CONSTANT SUB_Code : std_logic_vector(1 DOWNTO 0) := "11";

    TYPE testRecordArray IS ARRAY (NATURAL RANGE <>) OF std_logic_vector(2 DOWNTO 0)
    ;
    CONSTANT TIMEDELTA : TIME := 50 ns;
45  -- Component Declaration for the Unit Under Test (UUT)
    COMPONENT ALU_1Bit
        PORT (
            Control : IN std_logic_vector(1 DOWNTO 0);
            A : IN std_logic;
            B : IN std_logic;
50            Y : OUT std_logic;
            CB : OUT std_logic
        );
    END COMPONENT;
55  --Inputs
    SIGNAL Control : std_logic_vector(1 DOWNTO 0) := (OTHERS => '0');
    SIGNAL A : std_logic := '0';
    SIGNAL B : std_logic := '0';

60  --Outputs
    SIGNAL Y : std_logic;
    SIGNAL CB : std_logic;
BEGIN
    -- Instantiate the Unit Under Test (UUT)
65    uut : ALU_1Bit
    PORT MAP(
        Control => Control,
        A => A,
        B => B,
70        Y => Y,
        CB => CB
    );
    -- Stimulus process
    stim_proc : PROCESS
75        --create a function to make a vector a string
        FUNCTION vec2str(vec : std_logic_vector) RETURN STRING IS
            VARIABLE stmp : STRING(vec'LEFT + 1 DOWNTO 1);
        BEGIN
            FOR i IN vec'reverse_range LOOP
80                IF vec(i) = '1' THEN
                    stmp(i + 1) := '1';
                ELSIF vec(i) = 'U' THEN
                    stmp(i + 1) := 'U';
                ELSE
85                    stmp(i + 1) := '0';
                END IF;
            END LOOP; RETURN stmp;
        END vec2str;

90    BEGIN
        --wait for the outputs to stabilize
        WAIT FOR 100 ns;

        control <= OR_Code;
95        A <= '0';
        B <= '0';
        WAIT FOR 50 ns;

```

```

100      A <= '0';
      B <= '1';
      WAIT FOR 50 ns;
      A <= '1';
      B <= '0';
      WAIT FOR 50 ns;
105      A <= '1';
      B <= '1';
      WAIT FOR 50 ns;

      control <= AND_Code;
110      A <= '0';
      B <= '0';
      WAIT FOR 50 ns;
      A <= '0';
      B <= '1';
      WAIT FOR 50 ns;
115      A <= '1';
      B <= '0';
      WAIT FOR 50 ns;
      A <= '1';
      B <= '1';
120      WAIT FOR 50 ns;

      control <= ADD_Code;
      A <= '0';
      B <= '0';
125      WAIT FOR 50 ns;
      A <= '0';
      B <= '1';
      WAIT FOR 50 ns;
      A <= '1';
      B <= '0';
130      WAIT FOR 50 ns;
      A <= '1';
      B <= '1';
      WAIT FOR 50 ns;
135

      control <= SUB_Code;
      A <= '0';
      B <= '0';
140      WAIT FOR 50 ns;
      A <= '0';
      B <= '1';
      WAIT FOR 50 ns;
      A <= '1';
      B <= '0';
145      WAIT FOR 50 ns;
      A <= '1';
      B <= '1';
      WAIT FOR 50 ns;
150      WAIT;
      END PROCESS;

END;
```

Listing 10: ALU-1Bit VHDL

```

0  --Company      : RIT
   --Author       : Brandon Key
   --Created      : 02/18/2018
   --
5  --Project Name : Lab 3
   --File        : ALU.vhd
   --
   --Entity       : ALU
   --Architecture : struct
10 --
   --Tool Version : VHDL '93
   --Description  : ALU
   --
library IEEE;
15 use IEEE.STD_LOGIC_1164.ALL;

package controlcodes is
    constant AND_Code : std_logic_vector(1 downto 0) := "00";
    constant OR_Code  : std_logic_vector(1 downto 0) := "01";
20    constant ADD_Code : std_logic_vector(1 downto 0) := "10";
    constant SUB_Code  : std_logic_vector(1 downto 0) := "11";
end controlcodes;

25 library IEEE;
   use IEEE.STD_LOGIC_1164.ALL;
   use IEEE.numeric_std.all;
   use work.controlcodes.all;

30 entity ALU_1Bit is
    port(
        Control : in std_logic_vector(1 downto 0);
        A,B     : in std_logic;
        Y       : out std_logic;
35        CB     : out std_logic
    );
end ALU_1Bit;

architecture behav of ALU_1Bit is
40 begin

    Y_proc: with Control select
        Y <= A xor B when ADD_Code,
45        A xor B when SUB_Code,
        A or B when OR_Code,
        A and B when AND_Code,
        '0' when others;

    CB_proc: with Control select
50        CB <= A and B when ADD_Code,
        (not A) and B when SUB_Code,
        '0' when OR_Code,
        '0' when AND_Code,
55        '0' when others;

end behav;

```

Listing 11: ALU-4Bit-tb VHDL

```

0  --- Company: RIT
   --- Engineer: Brandon Key
   ---
   --- Create Date:    17:51:58 02/28/2018
5  --- Design Name:
   --- Module Name:    /home/ise/DSDII/Lab/Lab3/SourceCode/ALU_4Bit_tb.vhd
   --- Project Name:   Lab3
   --- Target Device:
   --- Tool versions:
10  --- Description:
   ---
   --- VHDL Test Bench Created by ISE for module: ALU_4Bit
   ---
   --- Dependencies:
15  ---
   --- Revision:
   --- Revision 0.01 - File Created
   --- Additional Comments:
   ---
20  --- Notes:
   --- This testbench has been automatically generated using types std_logic and
   --- std_logic_vector for the ports of the unit under test.  Xilinx recommends
   --- that these types always be used for the top-level I/O of a design in order
   --- to guarantee that the testbench will bind correctly to the post-implementation
25  --- simulation model.
   ---
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;
30  ---use work.globals.all;
   ---use work.controlcodes.all;

ENTITY ALU_4Bit_tb IS
END ALU_4Bit_tb;
35

ARCHITECTURE behavior OF ALU_4Bit_tb IS

    constant AND_Code : std_logic_vector(1 downto 0) := "00";
    constant OR_Code  : std_logic_vector(1 downto 0) := "01";
40  constant ADD_Code  : std_logic_vector(1 downto 0) := "10";
    constant SUB_Code  : std_logic_vector(1 downto 0) := "11";

    type testRecordArray is array (natural range <>) of std_logic_vector(2 downto 0)
    ;

45  constant n:integer := 16;
   --- "Time" that will elapse between test vectors we submit to the component.
    constant TIMEDELTA : time := 50 ns;

50  --- Component Declaration for the Unit Under Test (UUT)
    COMPONENT ALU_4Bit
    PORT(
        Control : IN  std_logic_vector(1 downto 0);
        A : IN  std_logic_vector(N-1 downto 0);
55  B : IN  std_logic_vector(N-1 downto 0);

```

```

        nBitOut : OUT std_logic_vector(N-1 downto 0);
        CB : OUT std_logic
    );
END COMPONENT;

--Inputs
signal Control : std_logic_vector(1 downto 0) := (others => '0');
signal A : std_logic_vector(N-1 downto 0) := (others => '0');
signal B : std_logic_vector(N-1 downto 0) := (others => '0');

--Outputs
signal nBitOut : std_logic_vector(N-1 downto 0);
signal CB : std_logic;
-- No clocks detected in port list. Replace <clock> below with
-- appropriate port name

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: ALU_4Bit
    PORT MAP (
        Control => Control,
        A => A,
        B => B,
        nBitOut => nBitOut,
        CB => CB
    );

    -- Stimulus process
    stim_proc: process
        --create a function to make a vector a string
        function vec2str(vec : std_logic_vector) return string is
            variable stmp:string(vec'left+1 downto 1);
        begin
            for i in vec'reverse_range loop
                if vec(i) = '1' then
                    stmp(i+1) := '1';
                elsif vec(i) = 'U' then
                    stmp(i+1) := 'U';
                else
                    stmp(i+1) := '0';
                end if;
            end loop;
            return stmp;
        end vec2str;

        procedure check_add(
            constant in1 : in natural;
            constant in2 : in natural;
            constant res_expected : in natural;
            constant CB_expected : in std_logic) is
            variable res : natural;
        begin
            -- Assign values to circuit inputs.
            A <= std_logic_vector(to_unsigned(in1, A'length));
            B <= std_logic_vector(to_unsigned(in2, B'length));

```

```

115      Control <= ADD_Code;

      wait for TIME_DELTA;
      — Check output against expected result.
120      res := to_integer(unsigned(nBitOut));
      assert ((res = res_expected) and ( CB = CB_expected ))
      report "" & integer'image(in1) & "+" &
              integer'image(in2) & "=" &
              integer'image(res_expected) & "!=" &
125      integer'image(res) &
              " " &
              "CB exp: " & std_logic'image(CB_expected) &
              "Got: " & std_logic'image(CB)
              severity error;
130 end procedure check_add;

procedure check_sub(
      constant in1 : in natural;
      constant in2 : in natural;
135      constant res_expected : in natural;
      constant CB_expected : in std_logic) is
      variable res : natural;
      begin
      — Assign values to circuit inputs.
140      A <= std_logic_vector(to_unsigned(in1, A'length));
      B <= std_logic_vector(to_unsigned(in2, B'length));
      Control <= SUB_Code;

      wait for TIME_DELTA;
      — Check output against expected result.
      res := to_integer(unsigned(nBitOut));
      assert ((res = res_expected) and ( CB = CB_expected ))
145      report "" & integer'image(in1) & "-" &
              integer'image(in2) & "=" &
              integer'image(res_expected) & "!=" &
              integer'image(res) &
150      " " &
              "CB exp: " & std_logic'image(CB_expected) &
              "Got: " & std_logic'image(CB)
              severity error;
155 end procedure check_sub;

procedure check_or(
      constant in1 : in natural;
      constant in2 : in natural;
160      constant res_expected : in natural) is
      variable res : natural;
      begin
      — Assign values to circuit inputs.
165      A <= std_logic_vector(to_unsigned(in1, A'length));
      B <= std_logic_vector(to_unsigned(in2, B'length));
      Control <= OR_Code;

      wait for TIME_DELTA;
      — Check output against expected result.
170

```

```

175     res := to_integer(unsigned(nBitOut));
    assert ((res = res_expected) and ( CB = '0' ))
180     report "" & integer'image(in1) & "+" &
        integer'image(in2) & "=" &
        integer'image(res_expected) & "!=" &
        integer'image(res) &
        "" &
        "CB: " & std_logic'image(CB)
        severity error;
    end procedure check_or;

185
    procedure check_and(
        constant in1 : in natural;
        constant in2 : in natural;
        constant res_expected : in natural) is
190     variable res : natural;
    begin
        -- Assign values to circuit inputs.
        A <= std_logic_vector(to_unsigned(in1, A'length));
        B <= std_logic_vector(to_unsigned(in2, B'length));
195     Control <= AND_Code;

        wait for TIME_DELTA;
        -- Check output against expected result.
200     res := to_integer(unsigned(nBitOut));
    report "" & integer'image(in1) & "+" &
        integer'image(in2) & "=" &
        integer'image(res_expected);

205     assert ((res = res_expected) and ( CB = '0' ))
    report "!=" &
        integer'image(res) &
        "" &
        "CB: " & std_logic'image(CB)
        severity error;
210     end procedure check_and;

    begin

215
        --wait for the outputs to stabilize
        wait for 100 ns;

        --check_add(4,5,9,0);
        --check_add(65535, 2, 1, 1);
220     --check_sub(1234, 234, 1000, 0);
        --check_sub(1, 2, 1, 1);

        control <= OR_Code;
225     A <= "0111010101110101";
        B <= "1001110100101101";
        wait for 50 ns;

        control <= AND_Code;
230     wait for 50 ns;

```



```

-- Test adder
for x in (0) to (5) loop
235   for y in 5432 to 5438 loop
       control <= ADD.Code;
       A <= std_logic_vector(to_unsigned(x, A'length));
       B <= std_logic_vector(to_unsigned(y, B'length));
       wait for 50 ns;

240       assert(nBitOut = std_logic_vector(to_unsigned(x+y, A'length)) )
       report("Bad Add = " & vec2str(nBitOut)
              & " expected = " & vec2str( std_logic_vector(to_unsigned(x+y, A'
length)) ) )
              & " A = " & vec2str(A)
              & " B = " & vec2str(B)
           );
       end loop;
   end loop;

250 for x in ((2**N)-3) to ((2**N)-1) loop
       for y in 0 to 3 loop
           control <= ADD.Code;
           A <= std_logic_vector(to_unsigned(x, A'length));
           B <= std_logic_vector(to_unsigned(y, B'length));
255           wait for 50 ns;

           assert(nBitOut = std_logic_vector(to_unsigned(x+y, A'length)) )
           report("Bad Add = " & vec2str(nBitOut)
                  & " expected = " & vec2str( std_logic_vector(to_unsigned(x+y, A'
length)) ) )
                  & " A = " & vec2str(A)
                  & " B = " & vec2str(B)
               );
           end loop;
       end loop;

265 -- Test suber
for x in 0 to 5 loop
       for y in 0 to 5 loop
           control <= SUB.Code;
270           A <= std_logic_vector(to_unsigned(x, A'length));
           B <= std_logic_vector(to_unsigned(y, B'length));
           wait for 50 ns;

           assert(nBitOut = std_logic_vector(to_signed(x-y, A'length)) )
275           report("Bad Sub = " & vec2str(nBitOut)
                  & " expected = " & vec2str( std_logic_vector(to_signed(x-y, A'length)) )
                  & " A = " & vec2str(A)
                  & " B = " & vec2str(B)
               );
           end loop;
       end loop;

280 for x in 12345 to 12350 loop
       for y in 5 to 7 loop
           control <= SUB.Code;
285           A <= std_logic_vector(to_unsigned(x, A'length));
           B <= std_logic_vector(to_unsigned(y, B'length));
           wait for 50 ns;

```

```

290      assert(nBitOut = std_logic_vector(to_signed(x-y, A'length)) )
      report("Bad Sub = " & vec2str(nBitOut)
        & " expected = " & vec2str( std_logic_vector(to_signed(x-y, A'length)) )
        & " A = " & vec2str(A)
        & " B = " & vec2str(B)
295      );

      end loop;
      end loop;
300

      wait;
      end process;
305

END;

```

Listing 12: ALU-16Bit VHDL

```

0  -----
  --Company       : RIT
  --Author        : Brandon Key
  --Created       : 02/18/2018
  --
5  --Project Name : Lab 3
  --File         : ALU_16Bit.vhd
  --
  --Entity        : ALU_16Bit
  --Architecture : struct
10 --
  --Tool Version  : VHDL '93
  --Description   : ALU_16Bit
  -----

15 library IEEE;
   use IEEE.STD_LOGIC_1164.ALL;

   package globals is
       constant N : integer := 16;
20 end globals;

   library IEEE;
   use IEEE.STD_LOGIC_1164.ALL;

25 package controlcodes is
       constant AND_Code : std_logic_vector(1 downto 0) := "00";
       constant OR_Code  : std_logic_vector(1 downto 0) := "01";
       constant ADD_Code : std_logic_vector(1 downto 0) := "10";
       constant SUB_Code : std_logic_vector(1 downto 0) := "11";
30 end controlcodes;

   library IEEE;
35 use IEEE.STD_LOGIC_1164.ALL;
   use IEEE.numeric_std.all;
   use work.controlcodes.all;

```

```

use work.globals.all;

40 entity ALU_16Bit is
    port(
        Control : in std_logic_vector(1 downto 0);
        A,B      : in std_logic_vector(N-1 downto 0);
        nBitOut  : out std_logic_vector(N-1 downto 0);
45         CB     : out std_logic
    );
end ALU_16Bit;

architecture struct of ALU_16Bit is
50
    --constant N : integer := 4;

    signal ADD_SUB_Out : std_logic_vector(N-1 downto 0);
    signal OR_Out      : std_logic_vector(N-1 downto 0);
55    signal AND_Out    : std_logic_vector(N-1 downto 0);

    signal ADD_SUB_SEL : std_logic;

60 begin

    nBitAdderSubtractor_16Bit : entity work.nBitAdderSubtractor_16Bit
        generic map (N => N)
        port map ( A => A, B => B, SEL => ADD_SUB_SEL, Y => ADD_SUB_Out, CB => CB);
65

    nBitOR_16Bit : entity work.nBitOR_16Bit
        generic map (N => N)
        port map ( A => A, B => B, Y => OR_Out);
70

    nBitAND_16Bit : entity work.nBitAND_16Bit
        generic map (N => N)
        port map ( A => A, B => B, Y => AND_Out);
75

    Controller_16Bit : entity work.Controller_16Bit
        generic map (N => N)
        port map(
80         Control      => Control,
        ADD_SUB_In    => ADD_SUB_Out,
        OR_In         => OR_Out,
        AND_In        => AND_Out,
        ADD_SUB_SEL    => ADD_SUB_SEL,
        nBitOut        => nBitOut
85         );
end struct;

```

Listing 13: nBitOR-16Bit VHDL

```

0
---Company      : RIT
---Author       : Brandon Key
---Created      : 1/22/2018
---
5 ---Project Name : Lab 1

```

```

--File           : nBitOR_16Bit.vhd
--
--Entity         : nBitOR_16Bit
--Architecture   : Dataflow
10 --
--Tool Version   : VHDL '93
--Description    : Entity and structural description of an OR gate
--
--
15 library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity nBitOR_16Bit is
    generic (n : integer := 16);
20     port(A,B : in  std_logic_vector(n-1 downto 0);
          Y : out std_logic_vector(n-1 downto 0)
          );
end nBitOR_16Bit;

25 architecture Dataflow of nBitOR_16Bit is
begin
    Y <= A or B;-- bitwise or
end Dataflow;

```

Listing 14: nBitAdderSubtractor-16Bit VHDL

```

0 --
--Company       : RIT
--Author        : Brandon Key
--Created       : 02/18/2018
--
5 --Project Name : Lab 3
--File          : nBitAdderSubtractor_16Bit.vhd
--
--Entity        : nBitAdderSubtractor_16Bit
--Architecture  : struct
10 --
--Tool Version  : VHDL '93
--Description   : Entity and structural description of an adder subtractor
--              : SEL = 0 : A+B = Y
--              : SEL = 1 : A-B = Y
15 --
--
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.numeric_std.all;
20
entity nBitAdderSubtractor_16Bit is
    generic (n : integer := 16);
    port(
25         A,B : in  std_logic_vector(n-1 downto 0);
         SEL : in  std_logic;
         Y   : out std_logic_vector(n-1 downto 0);
         CB  : out std_logic
        );
end nBitAdderSubtractor_16Bit;
30
architecture struct of nBitAdderSubtractor_16Bit is

```

```

component full_adder is
    port(A,B,Cin : in  std_logic;
35         Sum,Cout : out  std_logic
    );
    end component full_adder;

--Create an array to hold all of the carries
40 type carry_array is array (n-1 downto 0) of std_logic;
    signal c_array : carry_array;

    signal B_XOR_SEL : std_logic_vector( (n-1) downto 0);

45 begin

    --Generate the xor statements to be mapped to the full adders
    XORator : for i in 0 to n-1 generate
        B_XOR_SEL(i) <= B(i) xor SEL;
50    end generate XORator;

    generate_adders : for i in 0 to n-1 generate
        i_first: if i = 0 generate
            --The first adder gets SEL as the Cin
55            adder : full_adder port map(
                A => A(i),
                B => B_XOR_SEL(i),
                Cin => SEL,
                Sum => Y(i),
60                Cout => c_array(i)
            );
        end generate i_first;

        i_last : if i = (n-1) generate
65            --The last adder doesn't have a carry out
            adder : full_adder port map(
                A => A(i),
                B => B_XOR_SEL(i),
                Cin => c_array(i-1),
70                Sum => Y(i),
                Cout => c_array(i)
            );
        end generate i_last;

75        --Middle adders
        i_mid : if (i /= 0) and (i /= (n-1)) generate
            adder : full_adder port map(
                A => A(i),
                B => B_XOR_SEL(i),
80                Cin => c_array(i-1),
                Sum => Y(i),
                Cout => c_array(i)
            );
        end generate i_mid;

85    end generate generate_adders;

    CB <= c_array(n-1) xor SEL;

90 end struct;

```

Listing 15: nBitAND-16Bit VHDL

```

0  -----
   --Company       : RIT
   --Author        : Brandon Key
   --Created       : 1/22/2018
   --
5  --Project Name  : Lab 1
   --File          : nBitAND_16Bit.vhd
   --
   --Entity        : nBitAND_16Bit
   --Architecture  : Dataflow
10  --
   --Tool Version  : VHDL '93
   --Description   : Entity and structural description of an AND gate
   -----

15 library IEEE;
   use IEEE.STD_LOGIC_1164.ALL;

   entity nBitAND_16Bit is
       generic (n : integer := 16);
20   port (A,B : in  std_logic_vector(n-1 downto 0);
         Y : out std_logic_vector(n-1 downto 0)
       );
   end nBitAND_16Bit;

25 architecture Dataflow of nBitAND_16Bit is
   begin
       Y <= A AND B; -- bitwise or
   end Dataflow;

```

5.2 SPICE

Listing 16: 1Bit ALU SPICE

```

0  * Example circuit file for simulating PEX

   .OPTION DOTNODE
   .HIER /

5  .INCLUDE "/home/bxk5113/Pyxis_SPT_HEP/ic_projects/Pyxis_SPT/digicdesign/ALU_1Bit/
   ALU_1Bit.cal/ALU_1Bit.pex.netlist"

   .LIB /home/bxk5113/Pyxis_SPT_HEP/ic_reflibs/tech_libs/generic13/models/lib.eldo TT

   * - Instantiate your parasitic netlist and add the load capacitor
10  ** FORMAT :
   * XLAYOUT [all inputs as listed by the ".subckt" line in the included netlist, in
       the order that they appear there] [name of the subcircuit as listed in the
       included netlist]
   XLAYOUT CB Y A B CONTROL[1] CONTROL[0] ALU_1Bit
   C1 Y 0 120f
   C2 CB 0 120f

15

   * - Analysis Setup - DC sweep
   * FORMAT : .DC [name] [low] [high] [step]

```

```

20 *.DC VFORCE_A 0 1.2 0.01
* - Analysis Setup - Trans
* FORMAT : .TRAN [start time] [end time] [time step]
.TRAN 0 160n 0.001n
25 * --- Forces
* FORMAT --- PULSE : [name] [port] [reference (0 means ground)] PULSE [low] [high] [
    delay] [fall time] [rise time] [pulse width] [period]
*
* FORMAT --- DC : [name] [port] [reference (0 means ground)] DC [voltage]
*
30 VFORCE_A A 0 PULSE (0 1.08 40n 0.1n 0.1n 40n 80n)
VFORCE_B B 0 PULSE (0 1.08 80n 0.1n 0.1n 80n 160n)
VFORCE_C1 CONTROL[1] 0 DC 1.08
VFORCE_C0 CONTROL[0] 0 DC 1.08
35 VFORCE_VDD VDD 0 DC 1.08
VFORCE_VSS VSS 0 DC 0
* --- Waveform Outputs
40 .PLOT TRAN V(A)
.PLOT TRAN V(B)
.PLOT TRAN V(CONTROL[1])
.PLOT TRAN V(CONTROL[0])
.PLOT TRAN V(Y)
45 .PLOT TRAN V(CB)
* --- Params
.TEMP 125

```

Listing 16: 1Bit ALU SPICE