
CMPE-630 Digital IC Design
Laboratory Exercise 7
Autolayout Design Techniques (HDL-Layout)

Brandon Key and Chris Guarini
Performed: 9 Dec 2019
Submitted: 9 Dec 2019

Instructor: Dr. Amlan Ganguly
TAs: Abhishek Vashist
Andrew Fountain
Piers Kwan

By submitting this report, you attest that you neither have given nor have received any assistance (including writing, collecting data, plotting figures, tables or graphs, or using previous student reports as a reference), and you further acknowledge that giving or receiving such assistance will result in a failing grade for this course.

Your Signature: _____

Contents

1	Abstract	3
2	Design Methodology and Theory	3
3	Results and Analysis	4
3.1	Layout	31
3.2	Timing	31
3.3	Power	31
4	Conclusion	31
5	Appendix	31
5.1	VHDL	31
5.2	Leonardo Scripts	31
5.3	SPICE	31
6	References	31

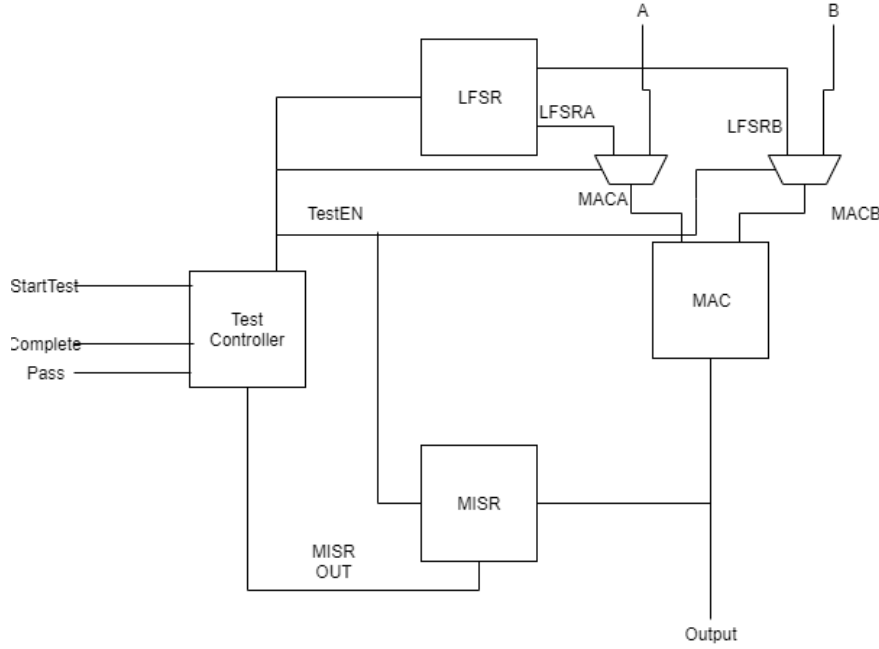


Figure 1: **Figure 1:** High Level Block Diagram of the MAC with BIST.

1 Abstract

Integrated Circuit Design is a costly and complex endeavor. Fortunately, automatic tools speed up the process and allow designs that are not possible to create manually. This exercise implemented a 1-Bit ALU and a 16-Bit ALU using autolayout. The autolayout tools generated very reasonable circuits. The 1-Bit ALU has an input frequency of 380.92MHz and a throughput frequency of 553.4MHz, while the 16-bit ALU has an input frequency of 461.02MHz and a throughput frequency of 110.2MHz. The area used by the ALUs was also reasonable with the 1-bit ALU taking up $647.89\mu m^2$ and the 16-bit ALU occupying $9792.5\mu m^2$.

2 Design Methodology and Theory

A cornerstone of IC design is the ability to create large, complex designs from smaller more manageable parts. The project outlined in this exercise calls for the design, testing and layout of a multiply and accumulate (MAC) unit, which takes two 16-bit inputs, multiplies them together, adds them to the value stored in a register, and then stores that output back into the register. The final component should contain a built in self test (BIST) that verifies the functionality of the MAC.

The MAC is composed of a carry-save multiplier, ripple carry full-adder, and parallel register. The BIST is implemented through the use of an LFSR for the inputs, an MISR for the output, and a test controller which controls the timing and sets the test passed and test complete outputs. A full diagram of the MAC with BIST can be seen below in *Figure 1*.

3 Results and Analysis

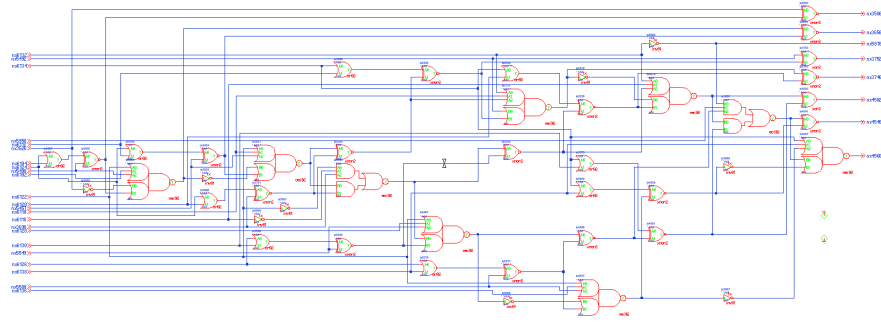


Figure 2: Full Schematic Page 7

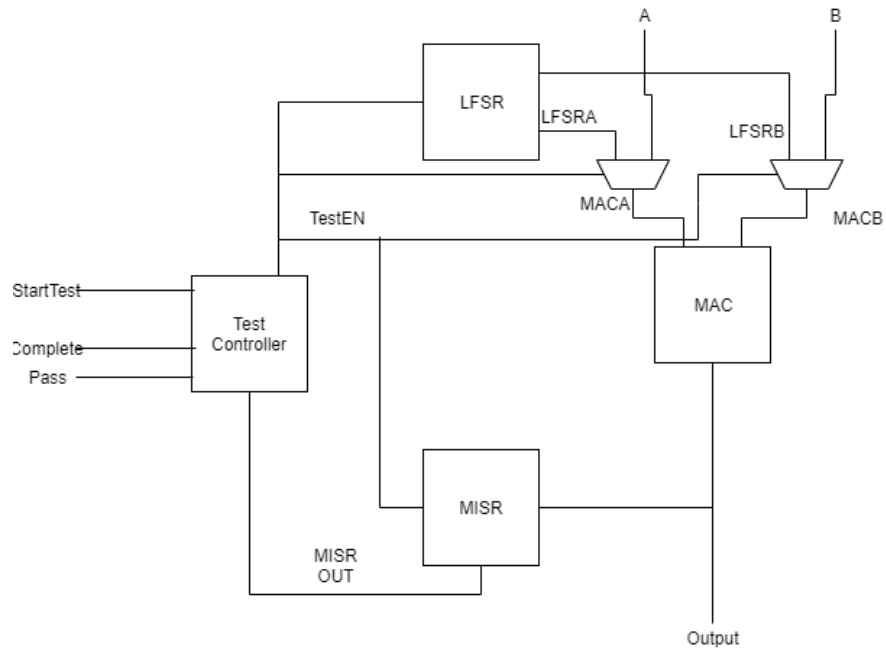


Figure 3: Full Project Block


 


Figure 4: Full Layout

 

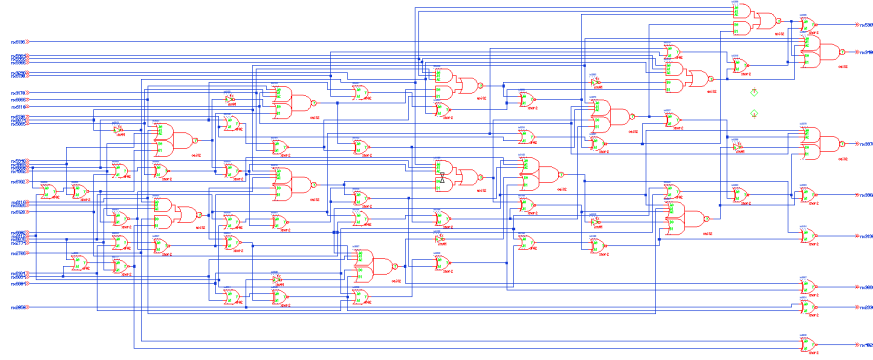


Figure 6: Full Schematic Page 2

 


Figure 7: Multiplier Schematic Page 2

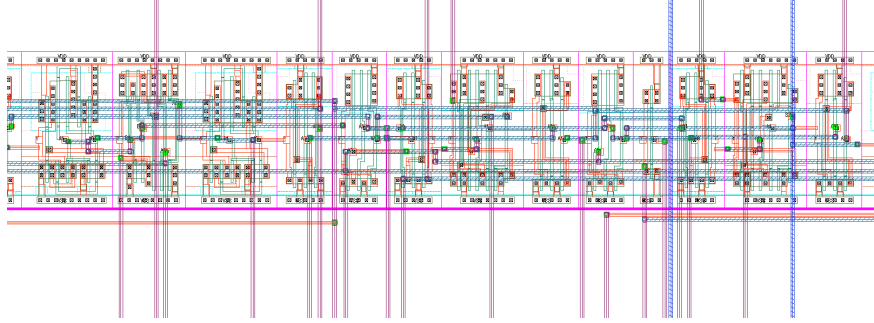


Figure 8: Full Layout Close Up View

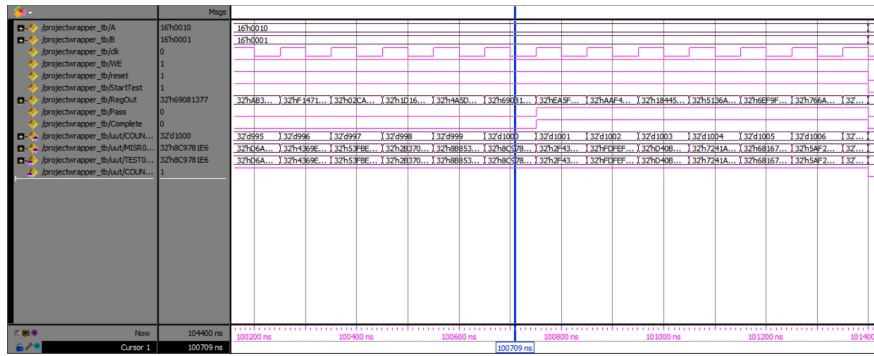


Figure 9: BIST Test Bench

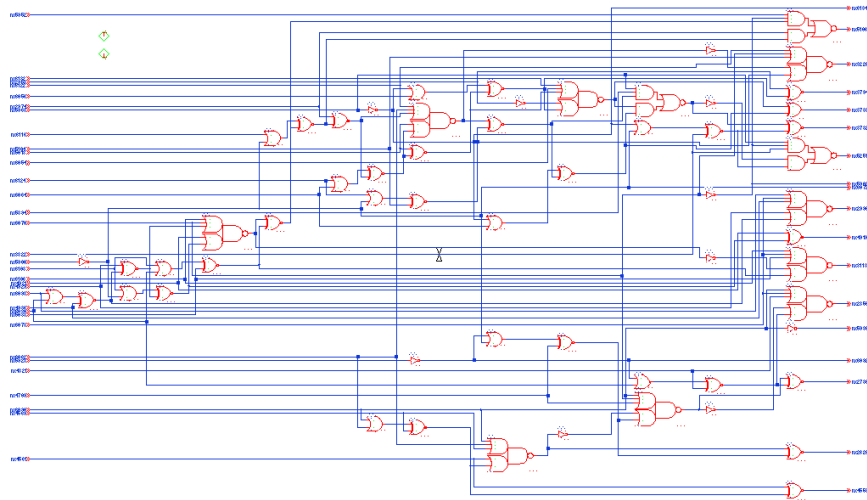


Figure 10: Full Schematic Page 17

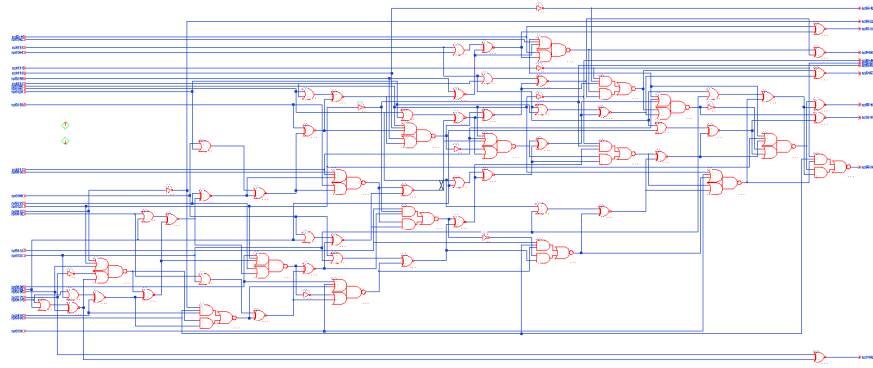


Figure 11: Full Schematic Page 6

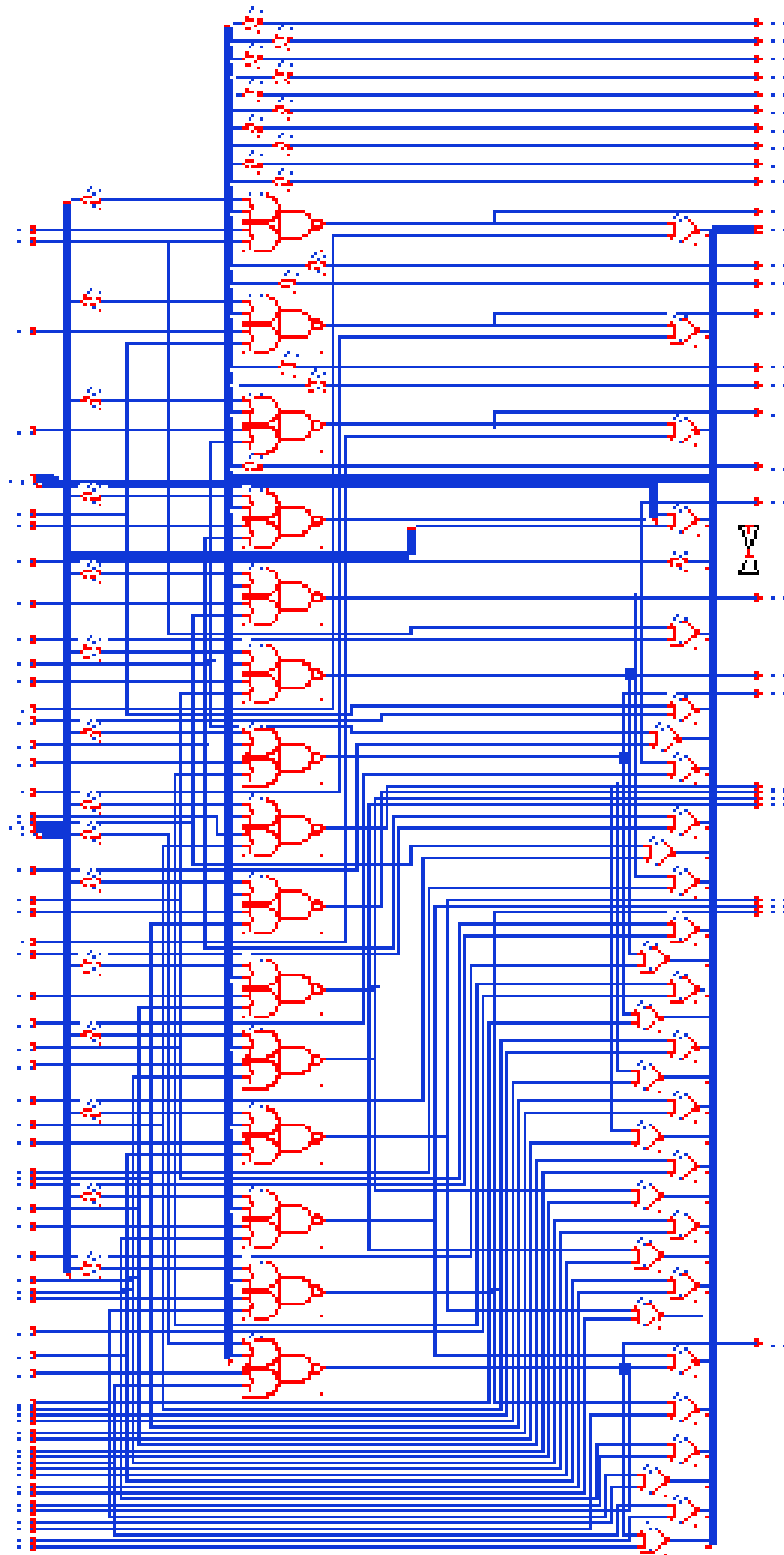


Figure 12: nBitAdder Schematic Page 1

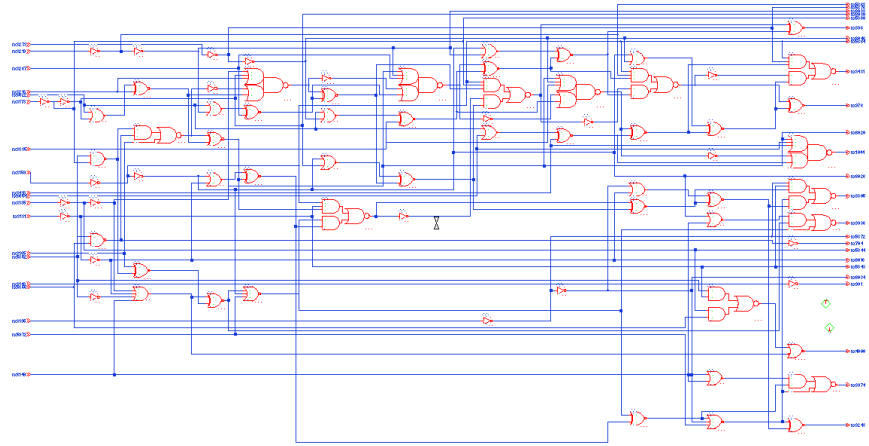


Figure 13: Full Schematic Page 27

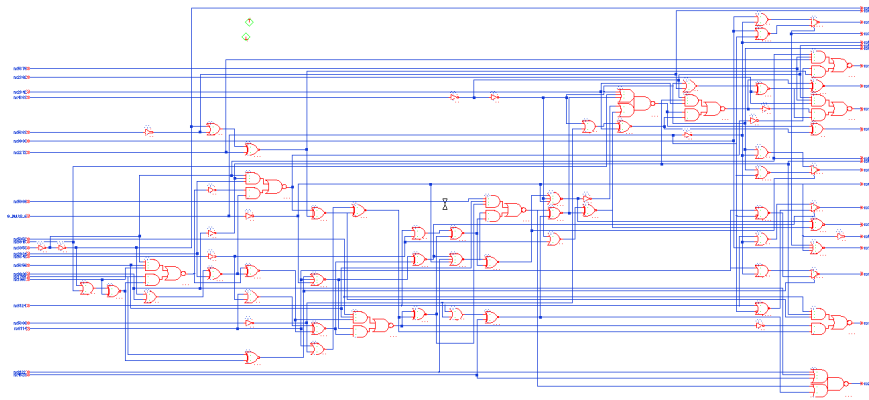


Figure 14: Full Schematic Page 15




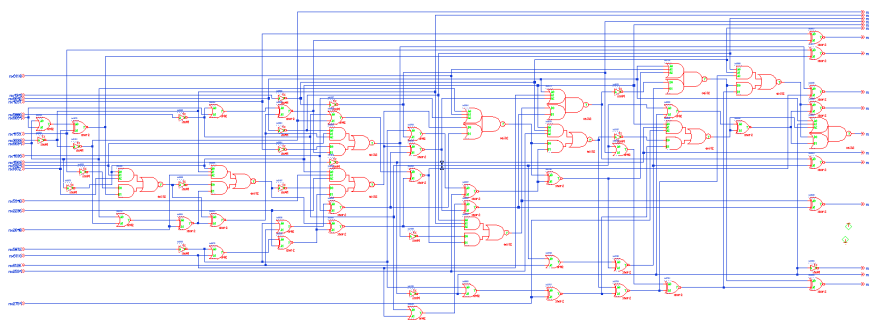


Figure 15: Full Schematic Page 19

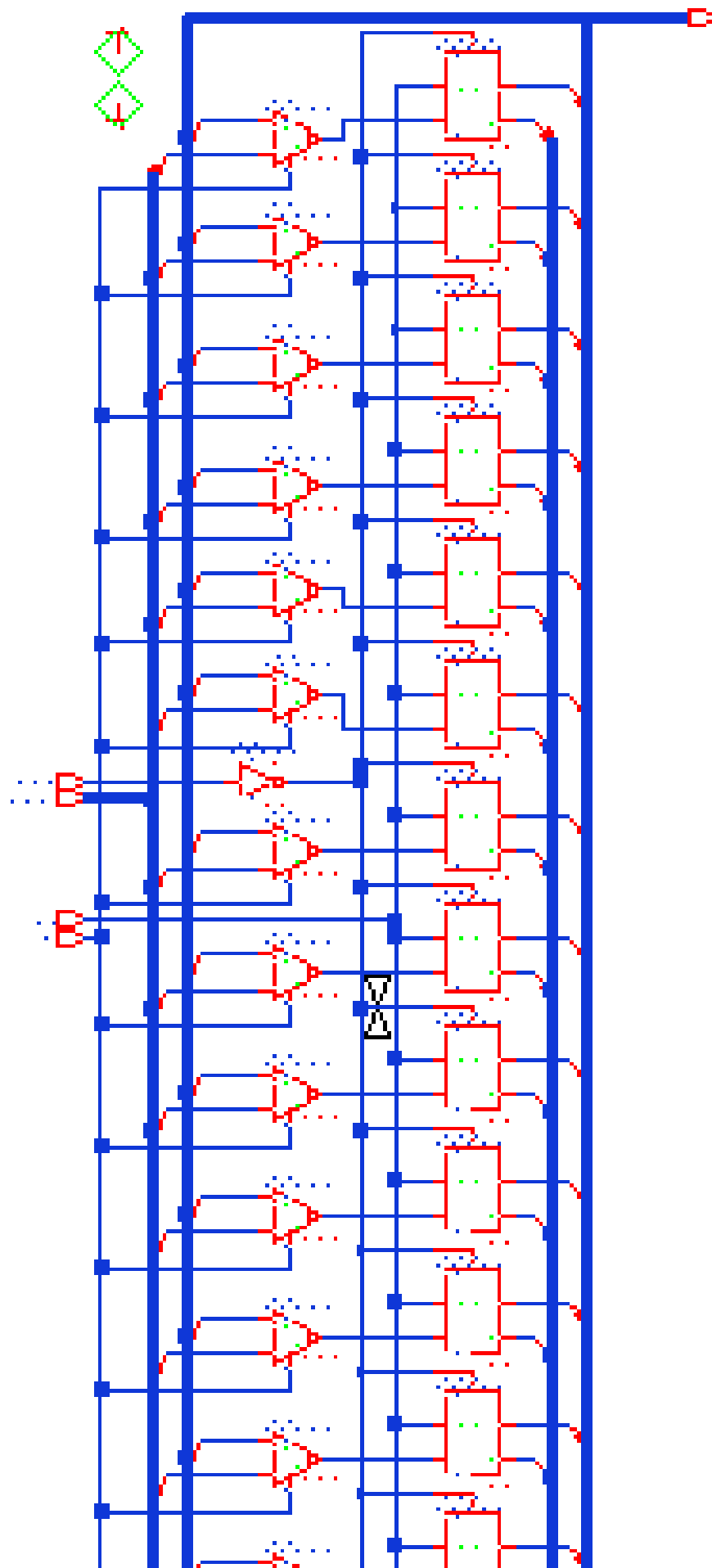

 

 

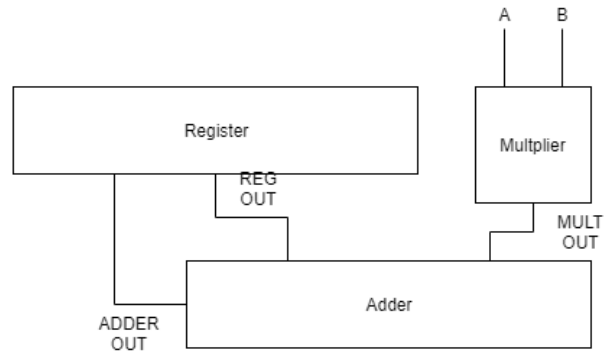


Figure 19: MAC block

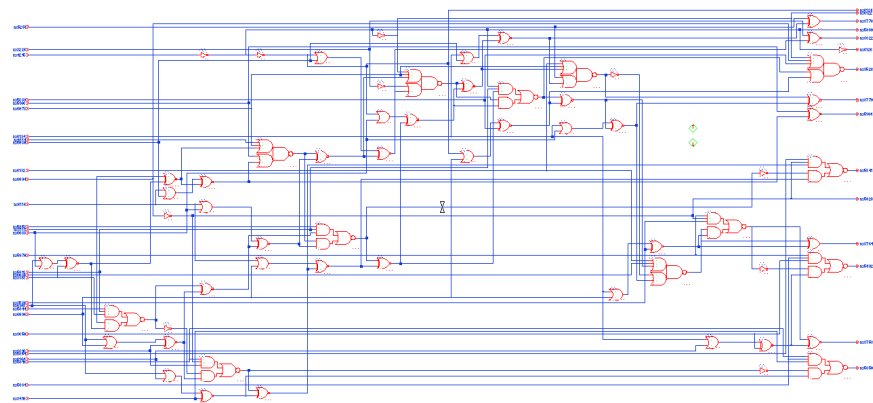


Figure 20: Full Schematic Page 5


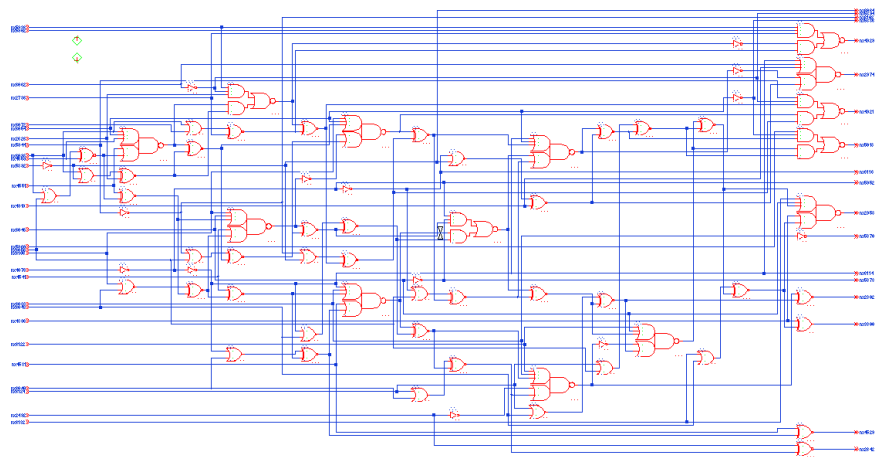


Figure 21: Full Schematic Page 16

 


 


Figure 23: Full Schematic Page 26

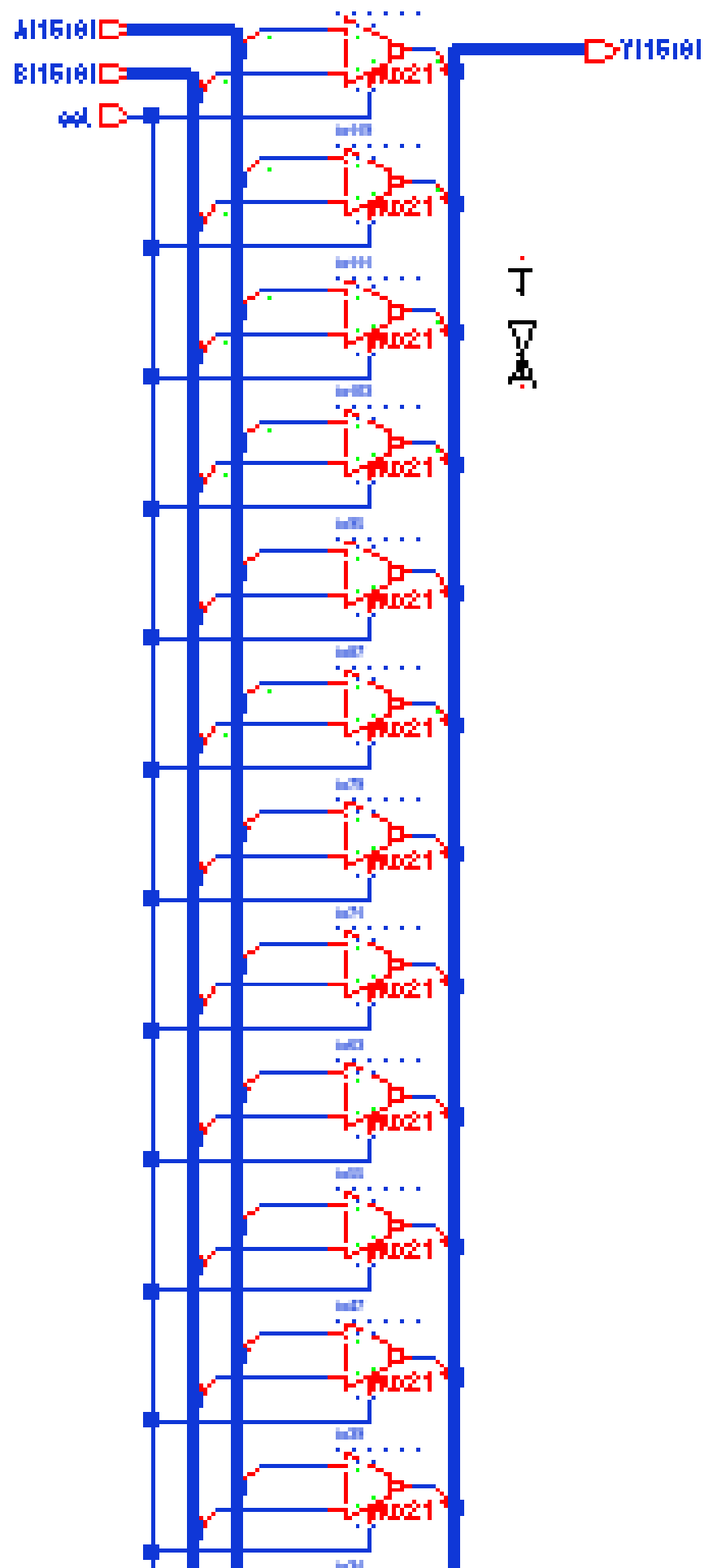

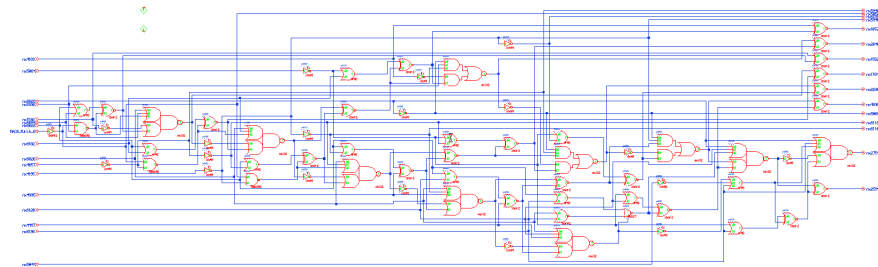


Figure 25: Full Schematic Page 1

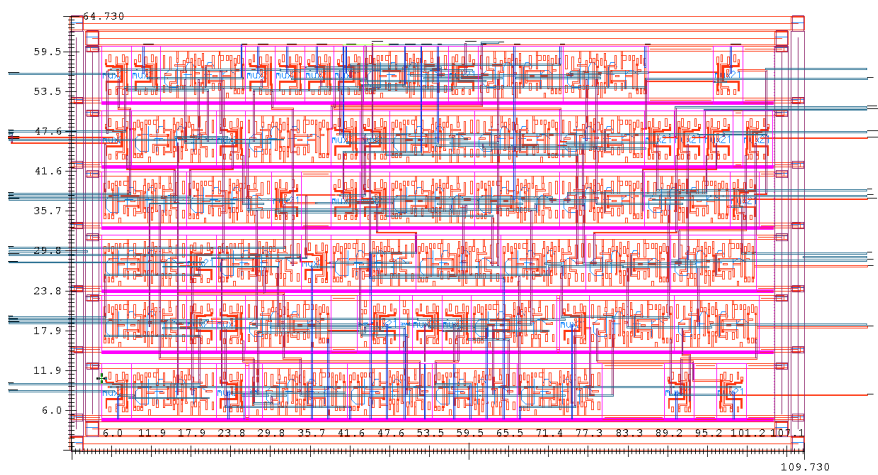


Figure 26: nBitRegister 32 Bit Layout

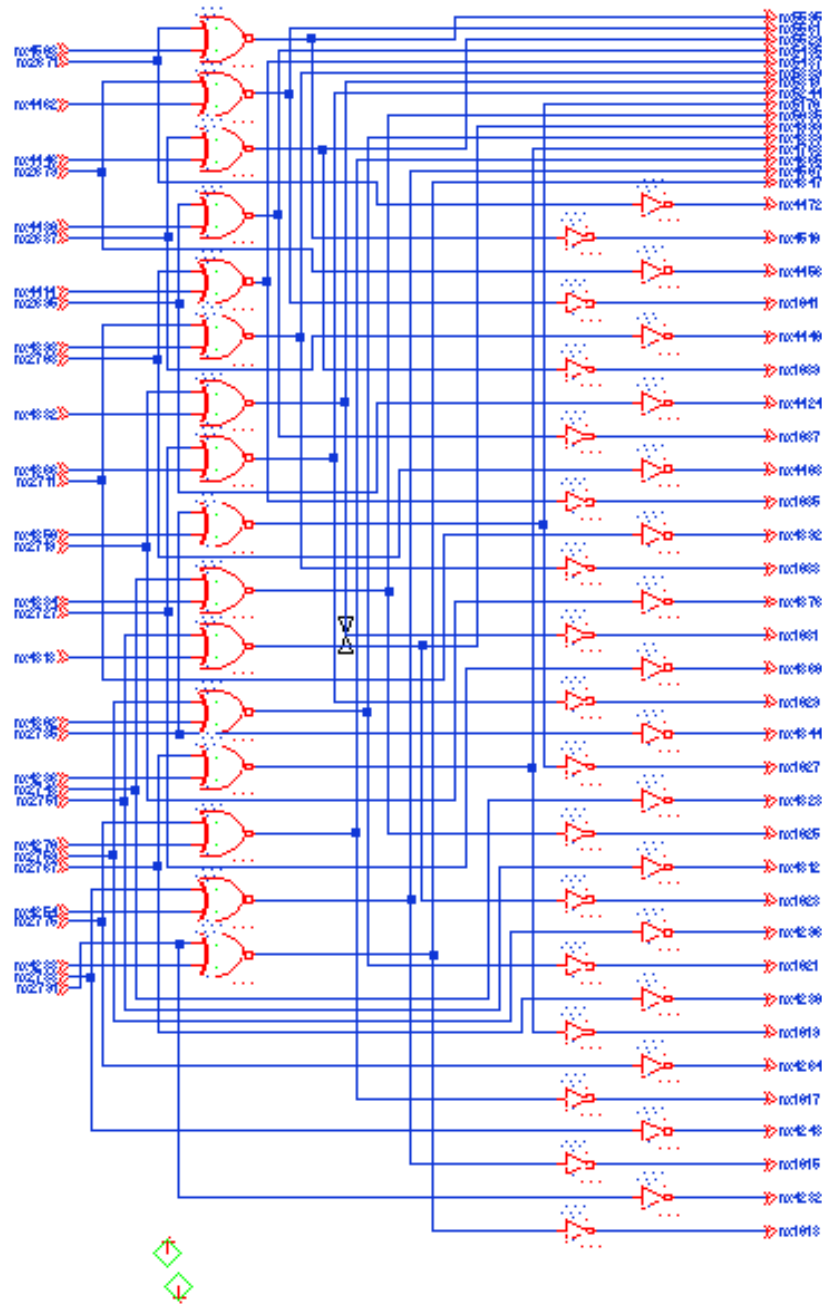


Figure 27: Full Schematic Page 9

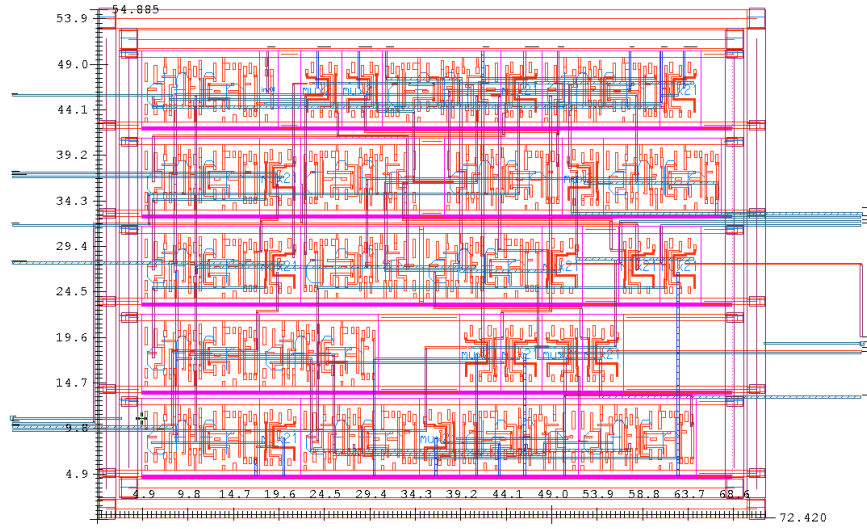


Figure 28: nBitRegister 16 Bit Layout

 


Figure 29: Full Schematic Page 23

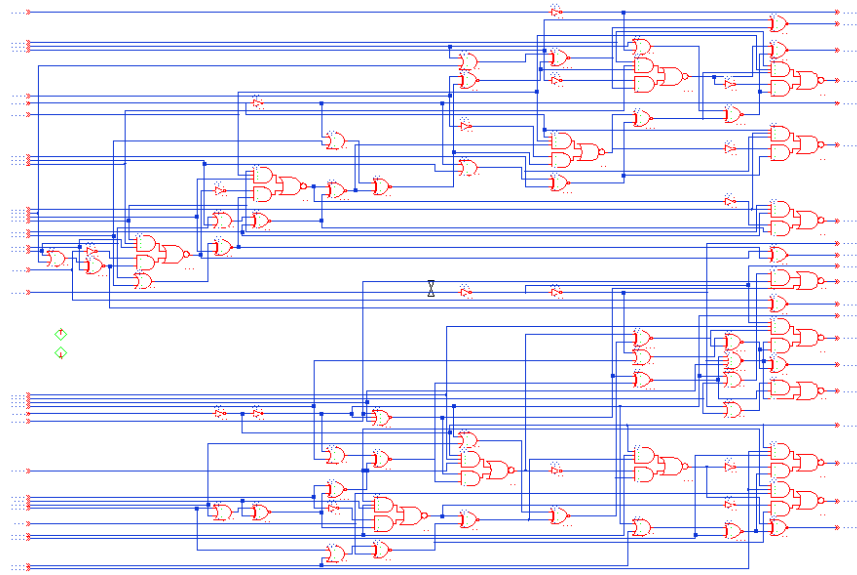


Figure 30: Full Schematic Page 28

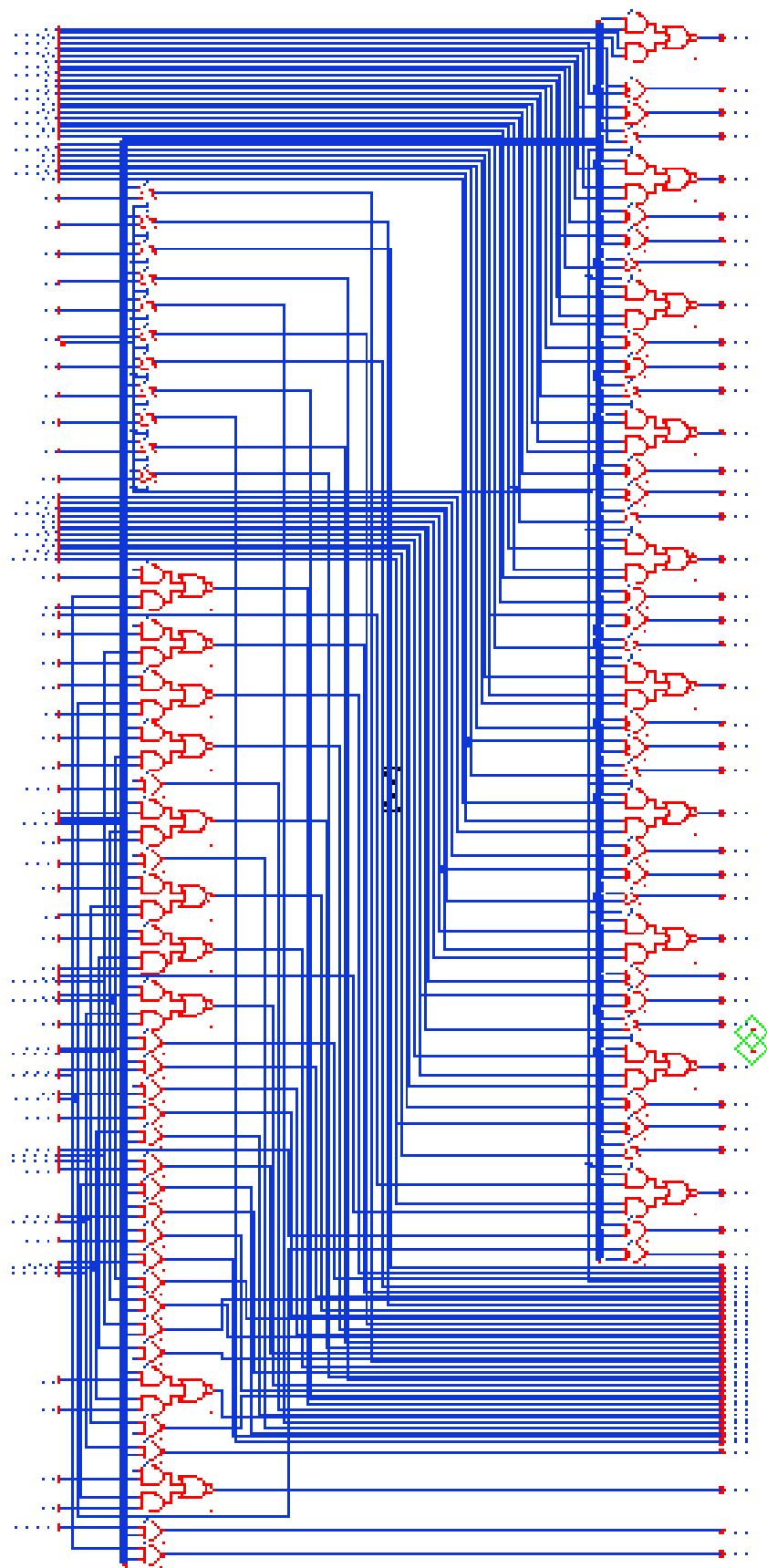


Figure 31: Full Schematic Page 22

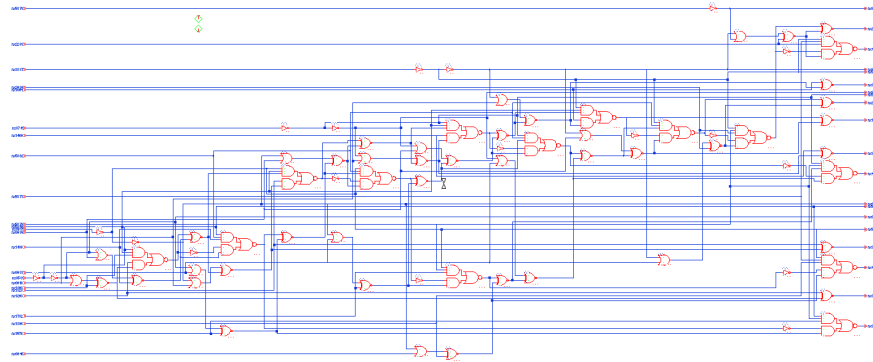


Figure 32: Full Schematic Page 14

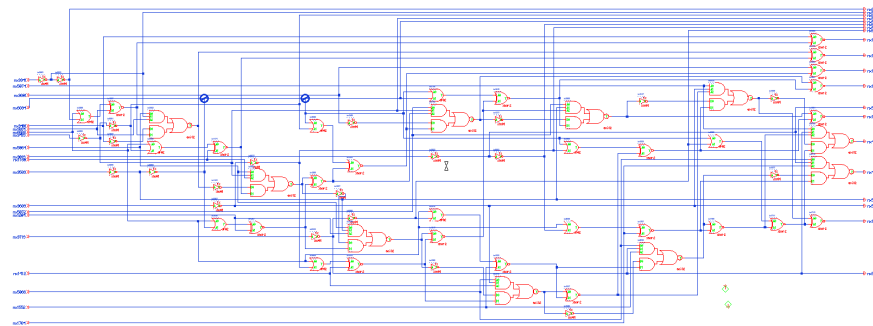


Figure 33: Full Schematic Page 13


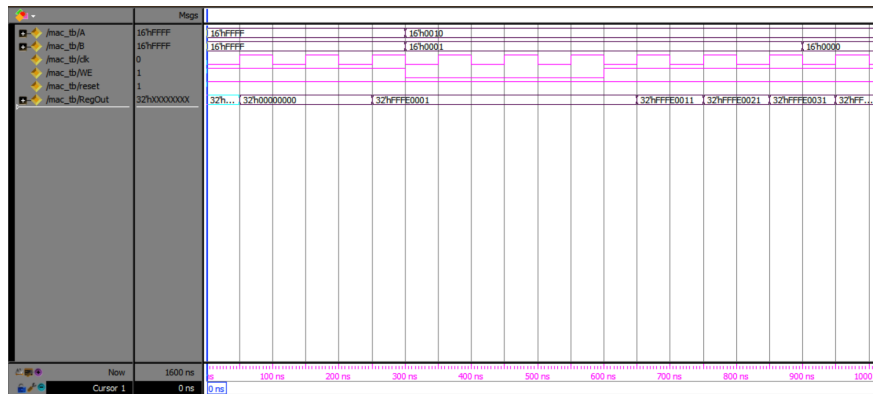


Figure 34: MAC 16bit Test Bench

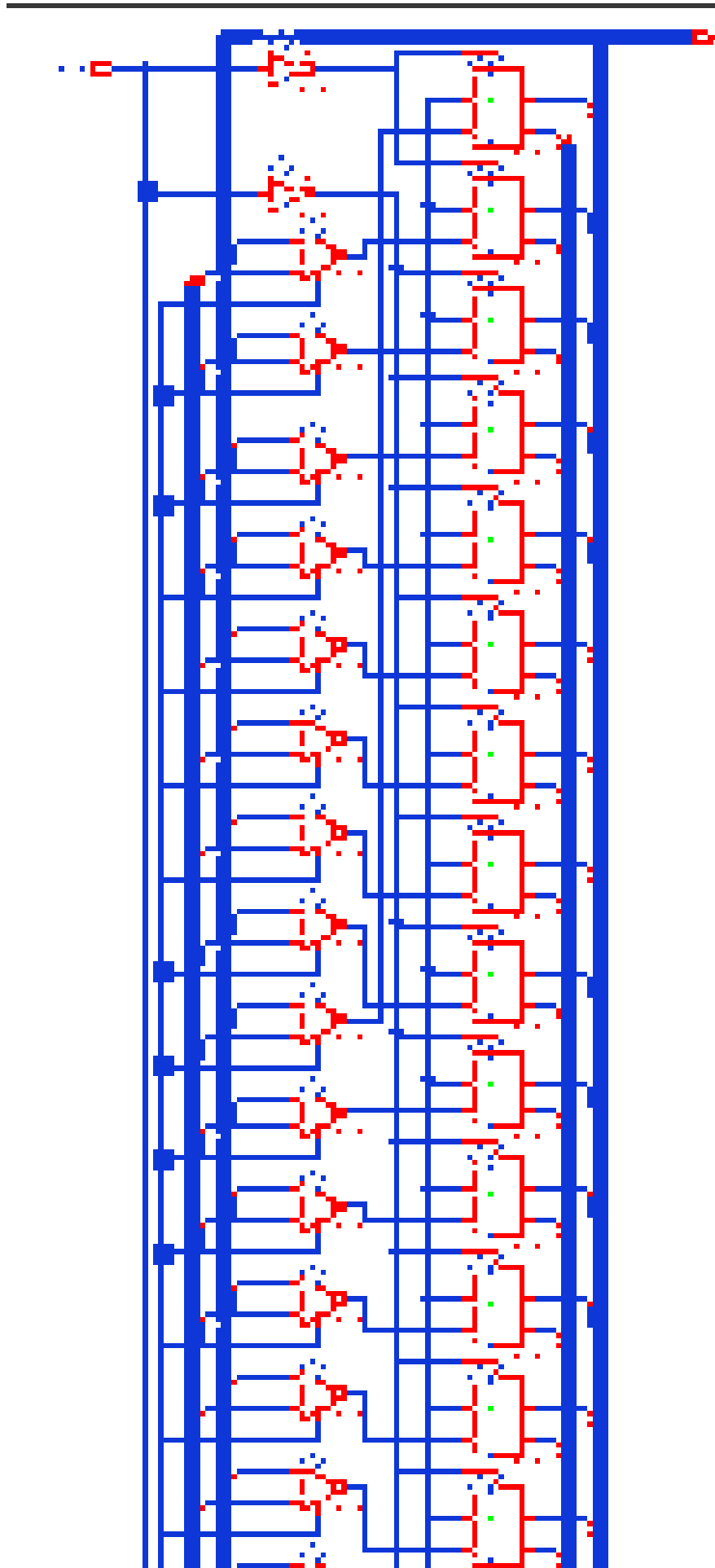

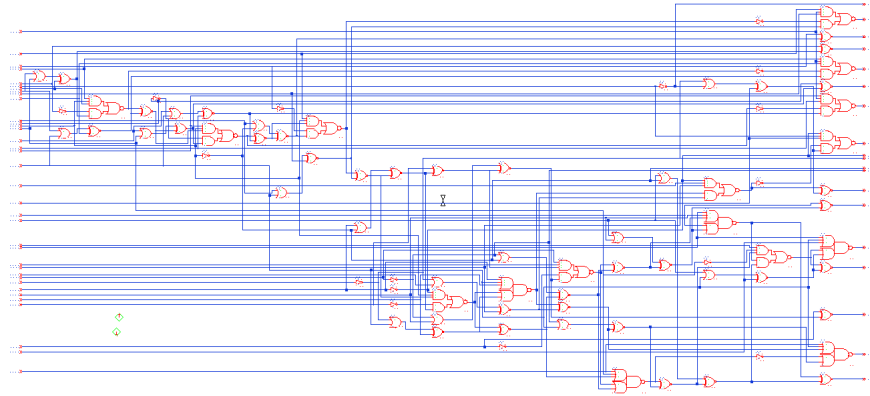


Figure 36: Full Schematic Page 18

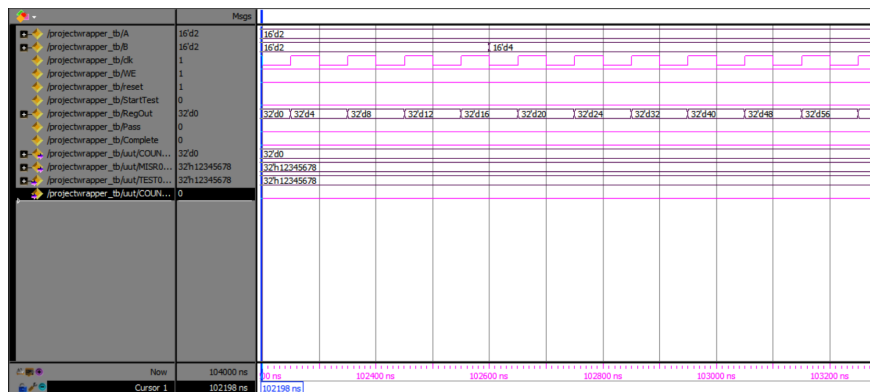


Figure 37: MAC Test Bench

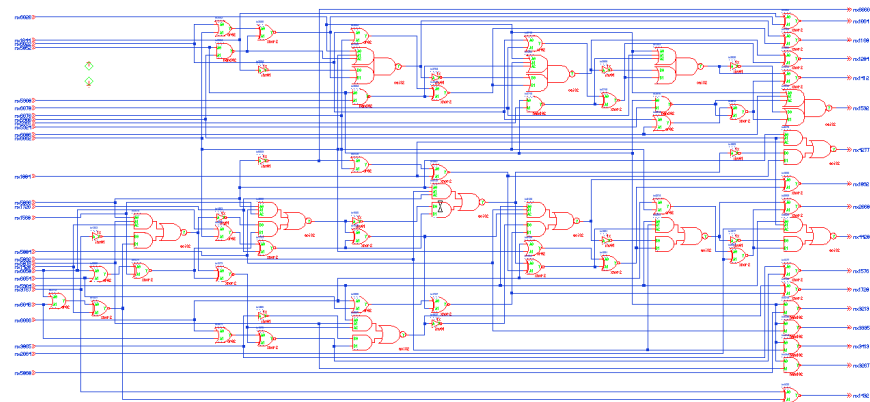


Figure 38: Full Schematic Page 12

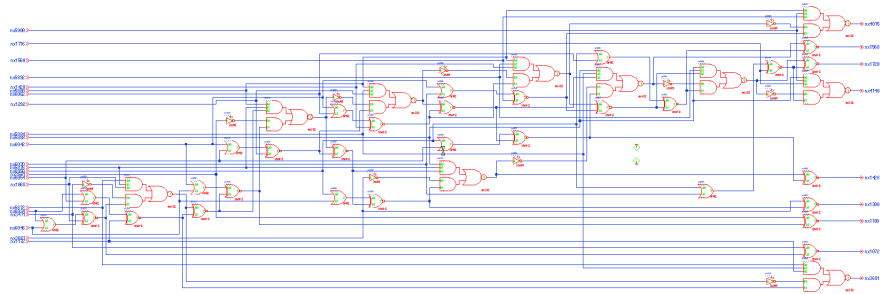


Figure 39: Full Schematic Page 11


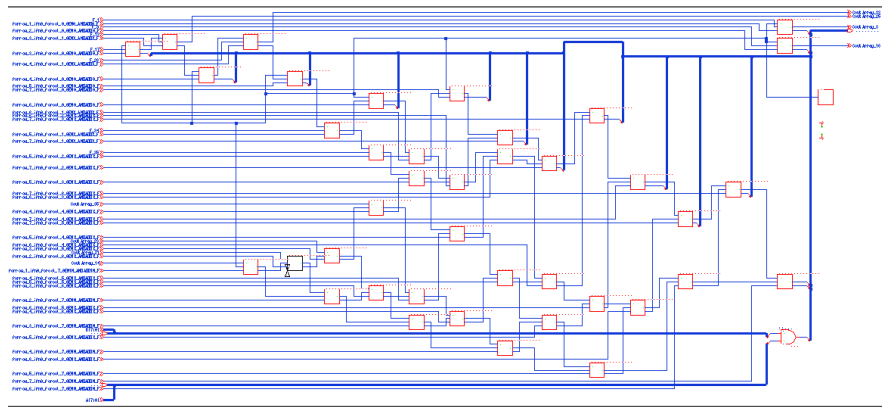


Figure 40: Multiplier Schematic Page 1

 

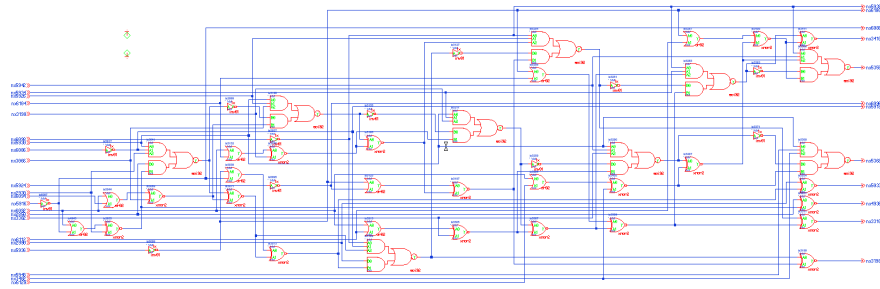


Figure 42: Full Schematic Page 4

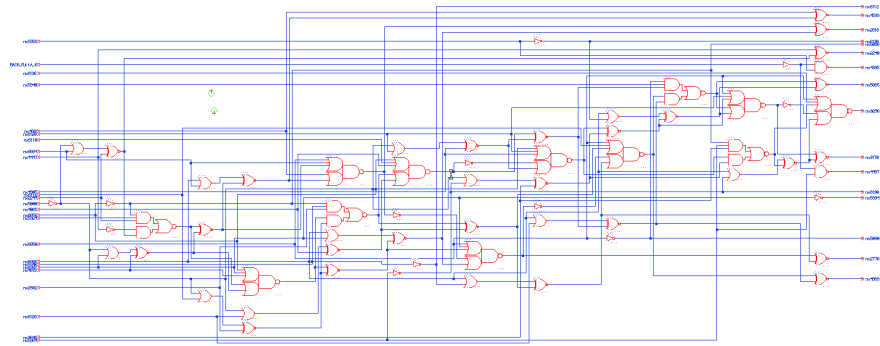


Figure 43: Full Schematic Page 3

 


Figure 44: Full Schematic Page 25

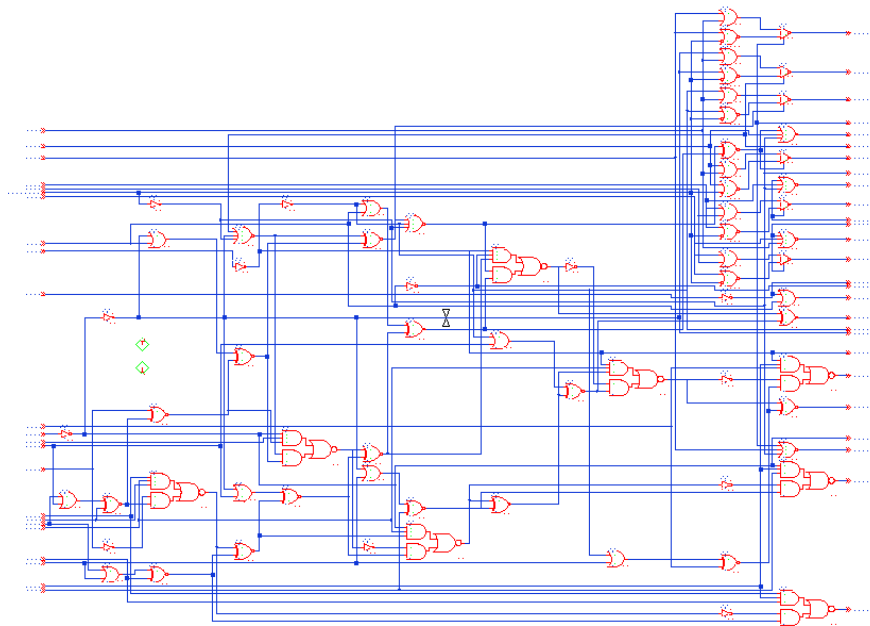


Figure 45: Full Schematic Page 10

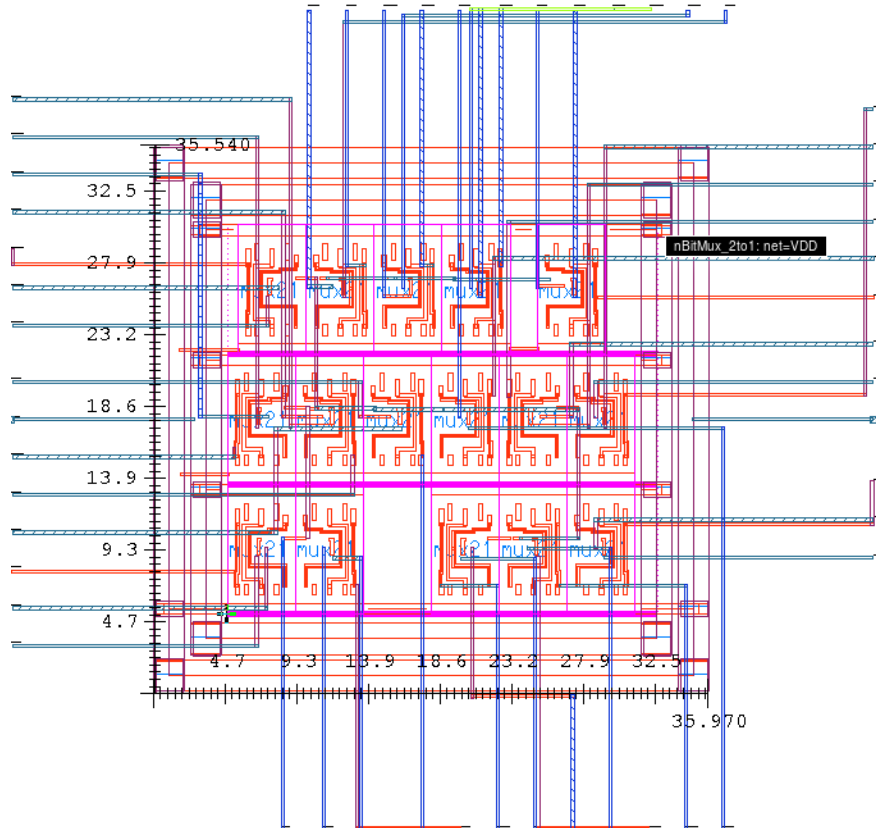


Figure 46: nBitMux 2to1 Layout

3.1 Layout

3.2 Timing

3.3 Power

4 Conclusion

5 Appendix

5.1 VHDL

5.2 Leonardo Scripts

5.3 SPICE

6 References

Key, Brandon A. *CMPE 260 Laboratory Exercise 3 Arithmetic Logic Unit*. CMPE 260 Laboratory Exercise 3 Arithmetic Logic Unit.

// TODO add BIST from DSD II