

---

**CMPE-630 Digital IC Design**  
**Laboratory Exercise 7**  
**Autolayout Design Techniques (HDL-Layout)**

Brandon Key  
Performed: 6 Nov 2019  
Submitted: 13 Nov 2019

Instructor: Dr. Amlan Ganguly  
TAs: Abhishek Vashist  
Andrew Fountain  
Piers Kwan

By submitting this report, you attest that you neither have given nor have received any assistance (including writing, collecting data, plotting figures, tables or graphs, or using previous student reports as a reference), and you further acknowledge that giving or receiving such assistance will result in a failing grade for this course.

Your Signature: \_\_\_\_\_

---

# 1 Abstract

## 2 Design Methodology and Theory

### 2.1 1-Bit ALU

The 1 Bit ALU designed in this exercise was created from behavioral VHDL (see Listing



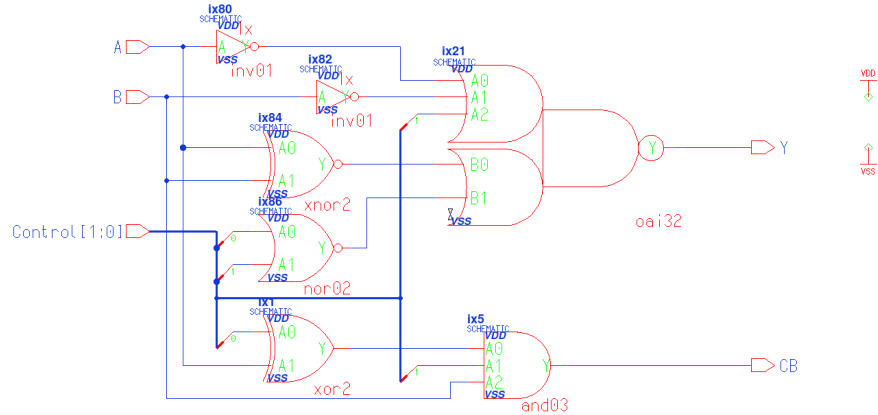


Figure 1: 1 Bit ALU Schematic

### 2.2 n-Bit ALU

Structural

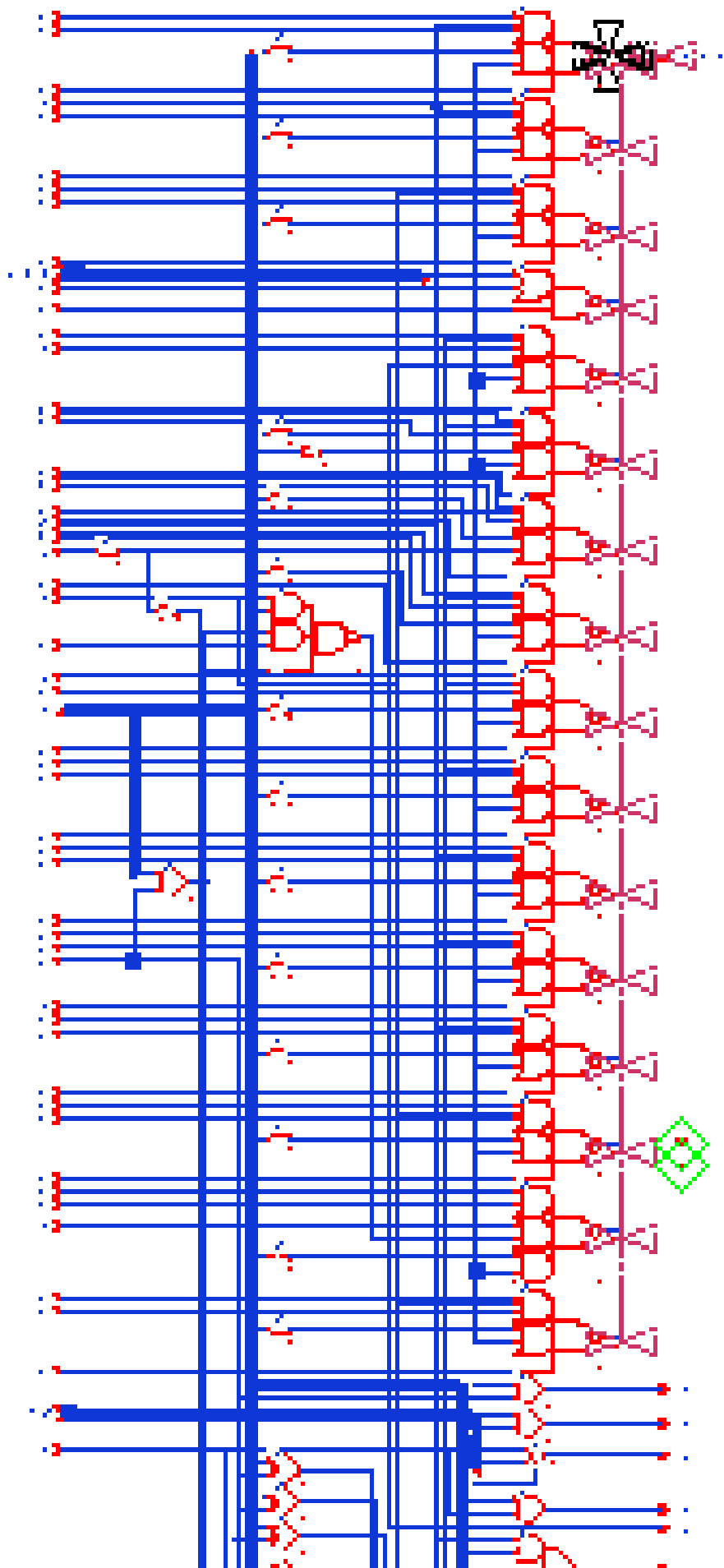

 

 


Figure 4: 16 Bit ALU Schematic Page 3

## 3 Results and Analysis

### 3.1 Functional Simulation

#### 3.1.1 1 Bit ALU

 


Figure 5: Functional Simulation of 1-bit ALU

#### 3.1.2 16 Bit ALU

 


Figure 6: Functional Simulation of 16-bit ALU: OR

 


Figure 7: Functional Simulation of 16-bit ALU: AND

 


Figure 8: Functional Simulation of 16-bit ALU: Addition

 


Figure 9: Functional Simulation of 16-bit ALU: Addition with carry

 


Figure 10: Functional Simulation of 16-bit ALU: Subtraction

 


Figure 11: Functional Simulation of 16-bit ALU: Subtraction with negative result

## 3.2 Layout

### 3.2.1 1 Bit ALU

 


Figure 12: 1 Bit ALU Layout

### 3.2.2 16 Bit ALU

Area 0.7

Power Routing

- 
- Varying levels of routing completion time
  - Slight preference for jogs over via to fill the area.
  - Rip
  - Under rip options:
    - Rips Most Aggressive
    - Automatic Rip Passes
    - Reroute
  - Under Advanced:
    - Allow all directions for stubs
    - Via Options  $\checkmark$  Use via generator

 


Figure 13: 16 Bit ALU Layout



### 3.3 Timing

#### 3.3.1 1 Bit ALU

It was found that subtraction was by far the slowest operation, with the timing difference visible in the waveforms.

 


Figure 14: 1 Bit ALU Worst Case Timing Simulation

#### 3.3.2 16 Bit ALU

Table 1: 16-Bit ALU Worst Case Rise Time

Input A	Output B	Rise Time (ps) Y	Op	Y	Op	CB
0x0000	0x0000	Y[15]	11	938	11	1033.8
0xFFFF	0xFFFF	Y[15]	11	938	01	1124.5
0xFFFF	0x0001	Y[15]	11	982.2	11	1044.6
0x0001	0xFFFF	Y[15]	01	904.63	00	1044.6
0x0000	0x0001	Y[0]	00	1085.2	01	986.9
0xABCD	0x89EF	Y[15]	01	917.9	11	951.8

### 3.4 Power

#### 3.4.1 1 Bit ALU

#### 3.4.2 16 Bit ALU

## 4 Conclusion

## 5 Appendix

### 5.1 VHDL

---

Listing 1: Controller\_16Bit VHDL

---

```
--Company      : RIT
--Author       : Brandon Key
--Created      : 02/18/2018
--
--Project Name : Lab 3
--File         : Controller_16Bit.vhd
--
--Entity       : Controller_16Bit
--Architecture : behav
--
--Tool Version : VHDL '93
--Description  : *SPECIAL controller, DO NOT USE OUTSIDE THIS PROJECT*
--              : Takes 4 bit control signal bit
--              : Figures out the proper output
```

---

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.numeric_std.all;
--use work.controlcodes.all;

entity Controller_16Bit is
  generic (n : integer := 16);
  port(
    Control : in std_logic_vector(1 downto 0);

    ADD_SUB_In : in std_logic_vector(N-1 downto 0);
    OR_In      : in std_logic_vector(N-1 downto 0);
    AND_In     : in std_logic_vector(N-1 downto 0);

    ADD_SUB_SEL : out std_logic;

    nBitOut : out std_logic_vector(N-1 downto 0)
  );
end Controller_16Bit;

architecture behav of Controller_16Bit is

  constant AND_Code : std_logic_vector(1 downto 0) := "00";
  constant OR_Code  : std_logic_vector(1 downto 0) := "01";
  constant ADD_Code : std_logic_vector(1 downto 0) := "10";
  constant SUB_Code : std_logic_vector(1 downto 0) := "11";

begin
```

---

```

--Proces to set the select signal when subtraction should occur
ADD_SUB_SEL_proc: with Control select
    ADD_SUB_SEL <= '1' when SUB_Code,
                '0' when others;

nBitOut_proc: with Control select
    nBitOut <= ADD_SUB_In when ADD_Code,
              ADD_SUB_In when SUB_Code,
              OR_In when OR_Code,
              AND_In when AND_Code,
              (others => '0') when others;

end   behav;

```

Listing 1: Controller\_16Bit VHDL

Listing 2: nBitAdderSubtractor\_4Bit VHDL

---

```

--Company       : RIT
--Author        : Brandon Key
--Created       : 02/18/2018
--
--Project Name  : Lab 3
--File          : nBitAdderSubtractor_4Bit.vhd
--
--Entity        : nBitAdderSubtractor_4Bit
--Architecture  : struct
--
--Tool Version  : VHDL '93
--Description   : Entity and structural description of an adder subtractor
--              : SEL = 0 : A+B = Y
--              : SEL = 1 : A-B = Y

```

---

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.numeric_std.all;

entity   nBitAdderSubtractor_4Bit is
    generic (n : integer := 16);
    port(
        A,B : in   std_logic_vector(n-1 downto 0);
        SEL : in   std_logic;
        Y   : out  std_logic_vector(n-1 downto 0);
        CB  : out  std_logic
    );
end   nBitAdderSubtractor_4Bit;

```

---

```

architecture   struct of   nBitAdderSubtractor_4Bit   is

    component full_adder is
        port(A,B,Cin : in   std_logic;
            Sum,Cout : out   std_logic
        );
    end component full_adder;

    —Create an array to hold all of the carries
    type carry_array is array (n-1 downto 0) of std_logic;
    signal c_array : carry_array;

    signal B_XOR_SEL : std_logic_vector( (n-1) downto 0);

begin

    —Generate the xor statements to be mapped to the full adders
    XORator : for i in 0 to n-1 generate
        B_XOR_SEL(i) <= B(i) xor SEL;
    end generate XORator;

    generate_adders : for i in 0 to n-1 generate
        i_first: if i = 0 generate
            —The first adder gets SEL as the Cin
            adder : full_adder port map(
                A => A(i),
                B => B_XOR_SEL(i),
                Cin => SEL,
                Sum => Y(i),
                Cout => c_array(i)
            );
        end generate i_first;

        i_last : if i = (n-1) generate
            —The last adder doesn't have a carry out
            adder : full_adder port map(
                A => A(i),
                B => B_XOR_SEL(i),
                Cin => c_array(i-1),
                Sum => Y(i),
                Cout => c_array(i)
            );
        end generate i_last;

        —Middle adders
        i_mid : if (i /= 0) and (i /= (n-1)) generate
            adder : full_adder port map(
                A => A(i),

```

---

```

        B => B_XOR_SEL(i),
        Cin => c_array(i-1),
        Sum => Y(i),
        Cout => c_array(i)
    );
end generate i_mid;

end generate generate_adders;

CB <= c_array(n-1) xor SEL;

end struct;

```

Listing 2: nBitAdderSubtractor\_4Bit VHDL

Listing 3: FullAdder VHDL

---

```

--Company      : RIT
--Author       : Brandon Key
--Created      : 02/18/2018
--
--Project Name : Lab 3
--File         : Full_Adder.vhd
--
--Entity       : Full_Adder
--Architecture : behav
--
--Tool Version : VHDL '93
--Description  : Entity and behavioral description of a full adder

```

---

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Full_Adder is
    port(A,B,Cin : in std_logic;
         Sum,Cout : out std_logic);
end Full_Adder;

architecture behav of Full_Adder is
begin
    --uses select assignment to implement the truth table of a full adder

    sum_proc: with std_logic_vector'(Cin&A&B) select
        Sum <= '0' when "000",

```

---

```

        '1' when "001",
        '1' when "010",
        '0' when "011",
        '1' when "100",
        '0' when "101",
        '0' when "110",
        '1' when "111",
        '0' when others;

    Cout_proc: with std_logic_vector '( Cin&A&B) select
        Cout <= '0' when "000",
                '0' when "001",
                '0' when "010",
                '1' when "011",
                '0' when "100",
                '1' when "101",
                '1' when "110",
                '1' when "111",
                '0' when others;

end    behav;

```

Listing 3: FullAdder VHDL

Listing 4: ALU\_16Bit.tb VHDL

---

```

-- Company: RIT
-- Engineer: Brandon Key
--
-- Create Date:    17:51:58 02/28/2018
-- Design Name:
-- Module Name:    /home/ise/DSDII/Lab/Lab3/SourceCode/ALU_16Bit.tb.vhd
-- Project Name:   Lab3
-- Target Device:
-- Tool versions:
-- Description:
--
-- VHDL Test Bench Created by ISE for module: ALU_16Bit
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--
-- Notes:
-- This testbench has been automatically generated using types std_logic and
-- std_logic_vector for the ports of the unit under test.  Xilinx recommends

```

---

— *that these types always be used for the top-level I/O of a design in order*  
— *to guarantee that the testbench will bind correctly to the post-implementation*  
— *simulation model.*

---

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;
—use work.globals.all;
—use work.controlcodes.all;
```

```
ENTITY ALU_16Bit_tb IS
END ALU_16Bit_tb;
```

```
ARCHITECTURE behavior OF ALU_16Bit_tb IS
```

```
    constant AND_Code : std_logic_vector(1 downto 0) := "00";
    constant OR_Code  : std_logic_vector(1 downto 0) := "01";
    constant ADD_Code : std_logic_vector(1 downto 0) := "10";
    constant SUB_Code : std_logic_vector(1 downto 0) := "11";
```

```
    type testRecordArray is array (natural range <>) of std_logic_vector(2 downto 0);
```

```
    constant n:integer := 16;
    — "Time" that will elapse between test vectors we submit to the component.
    constant TIME_DELTA : time := 50 ns;
```

— *Component Declaration for the Unit Under Test (UUT)*

```
COMPONENT ALU_16Bit
PORT(
    Control : IN  std_logic_vector(1 downto 0);
    A : IN  std_logic_vector(N-1 downto 0);
    B : IN  std_logic_vector(N-1 downto 0);
    nBitOut : OUT std_logic_vector(N-1 downto 0);
    CB : OUT std_logic
);
END COMPONENT;
```

— *Inputs*

```
signal Control : std_logic_vector(1 downto 0) := (others => '0');
signal A : std_logic_vector(N-1 downto 0) := (others => '0');
signal B : std_logic_vector(N-1 downto 0) := (others => '0');
```

— *Outputs*

```
signal nBitOut : std_logic_vector(N-1 downto 0);
signal CB : std_logic;
— No clocks detected in port list. Replace <clock> below with
```

---

*-- appropriate port name*

**BEGIN**

*-- Instantiate the Unit Under Test (UUT)*

uut: ALU\_16Bit

**PORT MAP** (

Control => Control,

A => A,

B => B,

nBitOut => nBitOut,

CB => CB

);

*-- Stimulus process*

stim\_proc: **process**

*--create a function to make a vector a string*

**function** vec2str(vec : std\_logic\_vector) **return** string **is**

**variable** stmp:string(vec'left+1 **downto** 1);

**begin**

**for** i **in** vec'reverse\_range **loop**

**if** vec(i) = '1' **then**

stmp(i+1) := '1';

**elsif** vec(i) = 'U' **then**

stmp(i+1) := 'U';

**else**

stmp(i+1) := '0';

**end if;**

**end loop;**

**return** stmp;

**end** vec2str;

**procedure** check\_add(

**constant** in1 : **in** natural;

**constant** in2 : **in** natural;

**constant** res\_expected : **in** natural;

**constant** CB\_expected : **in** std\_logic) **is**

**variable** res : natural;

**begin**

*-- Assign values to circuit inputs.*

A <= std\_logic\_vector(to\_unsigned(in1, A'length));

B <= std\_logic\_vector(to\_unsigned(in2, B'length));

Control <= ADD\_Code;

**wait for** TIME\_DELTA;



---

```

    — Check output against expected result.
    res := to_integer(unsigned(nBitOut));
    assert ((res = res_expected) and ( CB = CB_expected ))
    report "" & integer'image(in1) & "+" &
           integer'image(in2) & "=" &
           integer'image(res_expected) & "!=" &
           integer'image(res) &
           "____" &
           "CB_exp:_" & std_logic'image(CB_expected) &
           "Got:_" & std_logic'image(CB)
    severity error;
end procedure check_add;

procedure check_sub(
    constant in1 : in natural;
    constant in2 : in natural;
    constant res_expected : in natural;
    constant CB_expected : in std_logic) is
    variable res : natural;
    begin
    — Assign values to circuit inputs.
    A <= std_logic_vector(to_unsigned(in1, A'length));
    B <= std_logic_vector(to_unsigned(in2, B'length));
    Control <= SUB_Code;

    wait for TIME_DELTA;
    — Check output against expected result.
    res := to_integer(unsigned(nBitOut));
    assert ((res = res_expected) and ( CB = CB_expected ))
    report "" & integer'image(in1) & "-" &
           integer'image(in2) & "=" &
           integer'image(res_expected) & "!=" &
           integer'image(res) &
           "____" &
           "CB_exp:_" & std_logic'image(CB_expected) &
           "Got:_" & std_logic'image(CB)
    severity error;
end procedure check_sub;

procedure check_or(
    constant in1 : in natural;
    constant in2 : in natural;
    constant res_expected : in natural) is
    variable res : natural;
    begin
    — Assign values to circuit inputs.

```

---

```

A <= std_logic_vector(to_unsigned(in1, A'length));
B <= std_logic_vector(to_unsigned(in2, B'length));
Control <= OR_Code;

wait for TIME_DELTA;
-- Check output against expected result.
res := to_integer(unsigned(nBitOut));
assert ((res = res_expected) and (CB = '0' ))
report "" & integer'image(in1) & "+" &
integer'image(in2) & "=" &
integer'image(res_expected) & "!=" &
integer'image(res) &
"____" &
"CB:_" & std_logic'image(CB)
severity error;
end procedure check_or;

```

```

procedure check_and(
    constant in1 : in natural;
    constant in2 : in natural;
    constant res_expected : in natural) is
    variable res : natural;
begin
    -- Assign values to circuit inputs.
    A <= std_logic_vector(to_unsigned(in1, A'length));
    B <= std_logic_vector(to_unsigned(in2, B'length));
    Control <= AND_Code;

```

```

wait for TIME_DELTA;
-- Check output against expected result.
res := to_integer(unsigned(nBitOut));
report "" & integer'image(in1) & "+" &
integer'image(in2) & "=" &
integer'image(res_expected);

assert ((res = res_expected) and (CB = '0' ))
report "!=" &
integer'image(res) &
"____" &
"CB:_" & std_logic'image(CB)
severity error;
end procedure check_and;

```

```

begin

```

---

```

--wait for the outputs to stabilize
wait for 100 ns;

--check_add(4,5,9,0);
--check_add(65535, 2, 1, 1);
--check_sub(1234, 234, 1000, 0);
--check_sub(1, 2, 1, 1);

control <= OR_Code;
A <= "0111010101110101";
B <= "1001110100101101";
wait for 50 ns;

control <= AND_Code;
wait for 50 ns;

-- Test adder
for x in (0) to (5) loop
    for y in 5432 to 5438 loop
        control <= ADD_Code;
        A <= std_logic_vector(to_unsigned(x, A'length));
        B <= std_logic_vector(to_unsigned(y, B'length));
        wait for 50 ns;

        assert(nBitOut = std_logic_vector(to_unsigned(x+y, A'length) ) )
        report("Bad_Add=_ " & vec2str(nBitOut)
            & "_expected=_ " & vec2str( std_logic_vector(to_unsigned(x+y, A'length) ) )
            & "_A=_ " & vec2str(A)
            & "_B=_ " & vec2str(B)
        );
    end loop;
end loop;

for x in ((2**N)-3) to ((2**N)-1) loop
    for y in 0 to 3 loop
        control <= ADD_Code;
        A <= std_logic_vector(to_unsigned(x, A'length));
        B <= std_logic_vector(to_unsigned(y, B'length));
        wait for 50 ns;

        assert(nBitOut = std_logic_vector(to_unsigned(x+y, A'length) ) )
        report("Bad_Add=_ " & vec2str(nBitOut)
            & "_expected=_ " & vec2str( std_logic_vector(to_unsigned(x+y, A'length) ) )
            & "_A=_ " & vec2str(A)
            & "_B=_ " & vec2str(B)
        );
    end loop;
end loop;

```

---

```

        end loop;
    end loop;

    -- Test suber
    for x in 0 to 5 loop
        for y in 0 to 5 loop
            control <= SUB_Code;
            A <= std_logic_vector(to_unsigned(x, A'length));
            B <= std_logic_vector(to_unsigned(y, B'length));
            wait for 50 ns;

            assert(nBitOut = std_logic_vector(to_signed(x-y, A'length)) )
            report("Bad_Sub_=" & vec2str(nBitOut)
                & "_expected_=" & vec2str( std_logic_vector(to_signed(x-y, A'length))
                & "_A_=" & vec2str(A)
                & "_B_=" & vec2str(B)
            );

        end loop;
    end loop;

    for x in 12345 to 12350 loop
        for y in 5 to 7 loop
            control <= SUB_Code;
            A <= std_logic_vector(to_unsigned(x, A'length));
            B <= std_logic_vector(to_unsigned(y, B'length));
            wait for 50 ns;

            assert(nBitOut = std_logic_vector(to_signed(x-y, A'length)) )
            report("Bad_Sub_=" & vec2str(nBitOut)
                & "_expected_=" & vec2str( std_logic_vector(to_signed(x-y, A'length))
                & "_A_=" & vec2str(A)
                & "_B_=" & vec2str(B)
            );

        end loop;
    end loop;

    wait;
end process;

END;
```

Listing 4: ALU\_16Bit\_tb VHDL

---

Listing 5: Controller\_4Bit VHDL

---

```
--Company      : RIT
--Author       : Brandon Key
--Created      : 02/18/2018
--
--Project Name : Lab 3
--File         : Controller_4Bit.vhd
--
--Entity       : Controller_4Bit
--Architecture : behav
--
--Tool Version : VHDL '93
--Description  : *SPECIAL controller, DO NOT USE OUTSIDE THIS PROJECT*
--              : Takes 4 bit control signal bit
--              : Figures out the proper output
```

---

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.numeric_std.all;
--use work.controlcodes.all;

entity Controller_4Bit is
    generic (n : integer := 16);
    port(
        Control : in std_logic_vector(1 downto 0);

        ADD_SUB_In : in std_logic_vector(N-1 downto 0);
        OR_In      : in std_logic_vector(N-1 downto 0);
        AND_In     : in std_logic_vector(N-1 downto 0);

        ADD_SUB_SEL : out std_logic;

        nBitOut : out std_logic_vector(N-1 downto 0)
    );
end Controller_4Bit;

architecture behav of Controller_4Bit is

    constant AND_Code : std_logic_vector(1 downto 0) := "00";
    constant OR_Code  : std_logic_vector(1 downto 0) := "01";
    constant ADD_Code : std_logic_vector(1 downto 0) := "10";
    constant SUB_Code : std_logic_vector(1 downto 0) := "11";

begin
```

---

```

--Proces to set the select signal when subtraction should occur
ADD_SUB_SEL_proc: with Control select
    ADD_SUB_SEL <= '1' when SUB_Code,
                '0' when others;

nBitOut_proc: with Control select
    nBitOut <= ADD_SUB_In when ADD_Code,
              ADD_SUB_In when SUB_Code,
              OR_In when OR_Code,
              AND_In when AND_Code,
              (others => '0') when others;

end   behav;

```

Listing 5: Controller\_4Bit VHDL

Listing 6: nBitOR\_4Bit VHDL

---

```

--Company       : RIT
--Author        : Brandon Key
--Created       : 1/22/2018
--
--Project Name  : Lab 1
--File          : nBitOR_4Bit.vhd
--
--Entity        : nBitOR_4Bit
--Architecture  : Dataflow
--
--Tool Version  : VHDL '93
--Description   : Entity and structural description of an OR gate

```

---

```

library IEEE;
use IEEE.STD.LOGIC_1164.ALL;

entity nBitOR_4Bit is
    generic (n : integer := 16);
    port (A,B : in std_logic_vector(n-1 downto 0);
         Y : out std_logic_vector(n-1 downto 0)
         );
end nBitOR_4Bit;

architecture Dataflow of nBitOR_4Bit is
    begin
        Y <= A or B; -- bitwise or
    end Dataflow;

```

Listing 6: nBitOR\_4Bit VHDL

---

Listing 7: ALU\_4Bit VHDL

---

```
--Company      : RIT
--Author       : Brandon Key
--Created      : 02/18/2018
--
--Project Name : Lab 3
--File         : ALU_4Bit.vhd
--
--Entity       : ALU_4Bit
--Architecture : struct
--
--Tool Version : VHDL '93
--Description  : ALU_4Bit
```

---

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

package globals is
    constant N : integer := 16;
end globals;
```

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

package controlcodes is
    constant AND_Code : std_logic_vector(1 downto 0) := "00";
    constant OR_Code  : std_logic_vector(1 downto 0) := "01";
    constant ADD_Code : std_logic_vector(1 downto 0) := "10";
    constant SUB_Code : std_logic_vector(1 downto 0) := "11";
end controlcodes;
```

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.numeric_std.all;
use work.controlcodes.all;
use work.globals.all;
```

```
entity ALU_4Bit is
    port(
        Control : in std_logic_vector(1 downto 0);
        A,B      : in std_logic_vector(N-1 downto 0);
        nBitOut  : out std_logic_vector(N-1 downto 0);
        CB       : out std_logic
```

---

```

    );
end   ALU_4Bit;

architecture   struct   of   ALU_4Bit   is

    —constant N : integer := 4;

    signal ADD_SUB_Out : std_logic_vector(N-1 downto 0);
    signal OR_Out       : std_logic_vector(N-1 downto 0);
    signal AND_Out      : std_logic_vector(N-1 downto 0);

    signal ADD_SUB_SEL : std_logic;

begin

    nBitAdderSubtractor_4Bit : entity work.nBitAdderSubtractor_4Bit
        generic map (N => N)
        port map ( A => A, B => B, SEL => ADD_SUB_SEL, Y => ADD_SUB_Out, CB => CB);

    nBitOR_4Bit : entity work.nBitOR_4Bit
        generic map (N => N)
        port map ( A => A, B => B, Y => OR_Out);

    nBitAND_4Bit : entity work.nBitAND_4Bit
        generic map (N => N)
        port map ( A => A, B => B, Y => AND_Out);

    Controller_4Bit : entity work.Controller_4Bit
        generic map (N => N)
        port map(
            Control      => Control ,
            ADD_SUB_In   => ADD_SUB_Out,
            OR_In        => OR_Out ,
            AND_In       => AND_Out ,
            ADD_SUB_SEL  => ADD_SUB_SEL,
            nBitOut      => nBitOut
        );

end   struct;

```

Listing 7: ALU\_4Bit VHDL

Listing 8: nBitAND\_4Bit VHDL



---

```

--Author      : Brandon Key
--Created     : 1/22/2018
--
--Project Name : Lab 1
--File        : nBitAND_4Bit.vhd
--
--Entity      : nBitAND_4Bit
--Architecture : Dataflow
--
--Tool Version : VHDL '93
--Description  : Entity and structural description of an AND gate

```

---

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity nBitAND_4Bit is
    generic (n : integer := 16);
    port(A,B : in std_logic_vector(n-1 downto 0);
         Y : out std_logic_vector(n-1 downto 0)
        );
end nBitAND_4Bit;

architecture Dataflow of nBitAND_4Bit is
    begin
        Y <= A AND B;-- bitwise or
end Dataflow;

```

Listing 8: nBitAND\_4Bit VHDL

Listing 9: ALU\_1Bit\_tb VHDL

---

```

-- Company: RIT
-- Engineer: Brandon Key
--
-- Create Date: 17:51:58 02/28/2018
-- Design Name:
-- Module Name: /home/ise/DSDII/Lab/Lab3/SourceCode/ALU_1Bit_tb.vhd
-- Project Name: Lab3
-- Target Device:
-- Tool versions:
-- Description:
--
-- VHDL Test Bench Created by ISE for module: ALU_1Bit
--
-- Dependencies:
--
-- Revision:

```

---

```

-- Revision 0.01 -- File Created
-- Additional Comments:
--
-- Notes:
-- This testbench has been automatically generated using types std_logic and
-- std_logic_vector for the ports of the unit under test. Xilinx recommends
-- that these types always be used for the top-level I/O of a design in order
-- to guarantee that the testbench will bind correctly to the post-implementation
-- simulation model.

```

---

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;
--use work.globals.all;
--use work.controlcodes.all;

```

```

ENTITY ALU_1Bit_tb IS
END ALU_1Bit_tb;

```

```

ARCHITECTURE behavior OF ALU_1Bit_tb IS

```

```

    CONSTANT AND_Code : std_logic_vector(1 DOWNTO 0) := "00";
    CONSTANT OR_Code  : std_logic_vector(1 DOWNTO 0) := "01";
    CONSTANT ADD_Code : std_logic_vector(1 DOWNTO 0) := "10";
    CONSTANT SUB_Code : std_logic_vector(1 DOWNTO 0) := "11";

```

```

    TYPE testRecordArray IS ARRAY (NATURAL RANGE <>) OF std_logic_vector(2 DOWNTO 0);

```

```

    CONSTANT TIME_DELTA : TIME := 50 ns;

```

```

    -- Component Declaration for the Unit Under Test (UUT)

```

```

    COMPONENT ALU_1Bit

```

```

        PORT (

```

```

            Control : IN std_logic_vector(1 DOWNTO 0);

```

```

            A : IN std_logic;

```

```

            B : IN std_logic;

```

```

            Y : OUT std_logic;

```

```

            CB : OUT std_logic

```

```

        );

```

```

    END COMPONENT;

```

```

    --Inputs

```

```

    SIGNAL Control : std_logic_vector(1 DOWNTO 0) := (OTHERS => '0');

```

```

    SIGNAL A : std_logic := '0';

```

```

    SIGNAL B : std_logic := '0';

```

```

    --Outputs

```

```

    SIGNAL Y : std_logic;

```

```

    SIGNAL CB : std_logic;

```

```

BEGIN

```

```

    -- Instantiate the Unit Under Test (UUT)

```

---

```

    uut : ALU_1Bit
PORT MAP(
    Control => Control,
    A => A,
    B => B,
    Y => Y,
    CB => CB
);
-- Stimulus process
stim_proc : PROCESS
    -- create a function to make a vector a string
    FUNCTION vec2str(vec : std_logic_vector) RETURN STRING IS
        VARIABLE stmp : STRING(vec'LEFT + 1 DOWNTO 1);
    BEGIN
        FOR i IN vec'reverse_range LOOP
            IF vec(i) = '1' THEN
                stmp(i + 1) := '1';
            ELSIF vec(i) = 'U' THEN
                stmp(i + 1) := 'U';
            ELSE
                stmp(i + 1) := '0';
            END IF;
        END LOOP; RETURN stmp;
    END vec2str;

BEGIN
    -- wait for the outputs to stabilize
    WAIT FOR 100 ns;

    control <= OR_Code;
    A <= '0';
    B <= '0';
    WAIT FOR 50 ns;
    A <= '0';
    B <= '1';
    WAIT FOR 50 ns;
    A <= '1';
    B <= '0';
    WAIT FOR 50 ns;
    A <= '1';
    B <= '1';
    WAIT FOR 50 ns;

    control <= AND_Code;
    A <= '0';
    B <= '0';
    WAIT FOR 50 ns;
    A <= '0';

```

---

```

    B <= '1';
    WAIT FOR 50 ns;
    A <= '1';
    B <= '0';
    WAIT FOR 50 ns;
    A <= '1';
    B <= '1';
    WAIT FOR 50 ns;

    control <= ADD.Code;
    A <= '0';
    B <= '0';
    WAIT FOR 50 ns;
    A <= '0';
    B <= '1';
    WAIT FOR 50 ns;
    A <= '1';
    B <= '0';
    WAIT FOR 50 ns;
    A <= '1';
    B <= '1';
    WAIT FOR 50 ns;

    control <= SUB.Code;
    A <= '0';
    B <= '0';
    WAIT FOR 50 ns;
    A <= '0';
    B <= '1';
    WAIT FOR 50 ns;
    A <= '1';
    B <= '0';
    WAIT FOR 50 ns;
    A <= '1';
    B <= '1';
    WAIT FOR 50 ns;

    WAIT;
END PROCESS;

END;
```

Listing 9: ALU\_1Bit.tb VHDL

Listing 10: ALU\_1Bit VHDL

---

—Company : RIT  
—Author : Brandon Key

---

```

--Created      : 02/18/2018
--
--Project Name : Lab 3
--File        : ALU.vhd
--
--Entity       : ALU
--Architecture : struct
--
--Tool Version : VHDL '93
--Description  : ALU

```

---

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

```

```

package controlcodes is
    constant AND_Code : std_logic_vector(1 downto 0) := "00";
    constant OR_Code  : std_logic_vector(1 downto 0) := "01";
    constant ADD_Code : std_logic_vector(1 downto 0) := "10";
    constant SUB_Code : std_logic_vector(1 downto 0) := "11";
end controlcodes;

```

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.numeric_std.all;
use work.controlcodes.all;

```

```

entity ALU_1Bit is
    port(
        Control : in std_logic_vector(1 downto 0);
        A,B      : in std_logic;
        Y        : out std_logic;
        CB       : out std_logic;
    );
end ALU_1Bit;

```

```

architecture behav of ALU_1Bit is

```

```

begin

```

```

    Y_proc: with Control select
        Y <= A xor B when ADD_Code,
            A xor B when SUB_Code,
            A or B when OR_Code,
            A and B when AND_Code,
            '0' when others;

```

```

    CB_proc: with Control select

```

---

```

        CB <= A and B          when ADD_Code,
            (not A) and B when SUB_Code,
            '0'              when OR_Code,
            '0'              when AND_Code,
            '0'              when others;

end   behav;

```

Listing 10: ALU\_1Bit VHDL

Listing 11: ALU\_4Bit\_tb VHDL

---

```

-- Company: RIT
-- Engineer: Brandon Key
--
-- Create Date:    17:51:58 02/28/2018
-- Design Name:
-- Module Name:    /home/ise/DSDII/Lab/Lab3/SourceCode/ALU_4Bit_tb.vhd
-- Project Name:   Lab3
-- Target Device:
-- Tool versions:
-- Description:
--
-- VHDL Test Bench Created by ISE for module: ALU_4Bit
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--
-- Notes:
-- This testbench has been automatically generated using types std_logic and
-- std_logic_vector for the ports of the unit under test.  Xilinx recommends
-- that these types always be used for the top-level I/O of a design in order
-- to guarantee that the testbench will bind correctly to the post-implementation
-- simulation model.

```

---

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;
--use work.globals.all;
--use work.controlcodes.all;

ENTITY ALU_4Bit_tb IS
END ALU_4Bit_tb;

ARCHITECTURE behavior OF ALU_4Bit_tb IS

```

---

```

constant AND_Code : std_logic_vector(1 downto 0) := "00";
constant OR_Code  : std_logic_vector(1 downto 0) := "01";
constant ADD_Code : std_logic_vector(1 downto 0) := "10";
constant SUB_Code : std_logic_vector(1 downto 0) := "11";

type testRecordArray is array (natural range <>) of std_logic_vector(2 downto 0)

constant n:integer := 16;
-- "Time" that will elapse between test vectors we submit to the component.
constant TIMEDELTA : time := 50 ns;

-- Component Declaration for the Unit Under Test (UUT)
COMPONENT ALU_4Bit
PORT(
    Control : IN  std_logic_vector(1 downto 0);
    A : IN  std_logic_vector(N-1 downto 0);
    B : IN  std_logic_vector(N-1 downto 0);
    nBitOut : OUT std_logic_vector(N-1 downto 0);
    CB : OUT std_logic
);
END COMPONENT;

--Inputs
signal Control : std_logic_vector(1 downto 0) := (others => '0');
signal A : std_logic_vector(N-1 downto 0) := (others => '0');
signal B : std_logic_vector(N-1 downto 0) := (others => '0');

--Outputs
signal nBitOut : std_logic_vector(N-1 downto 0);
signal CB : std_logic;
-- No clocks detected in port list. Replace <clock> below with
-- appropriate port name

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: ALU_4Bit
PORT MAP (
        Control => Control,
        A => A,
        B => B,
        nBitOut => nBitOut,
        CB => CB
    );

```

---

```

-- Stimulus process
stim_proc: process
    --create a function to make a vector a string
    function vec2str(vec : std_logic_vector) return string is
        variable stmp:string(vec'left+1 downto 1);
    begin
        for i in vec'reverse_range loop
            if vec(i) = '1' then
                stmp(i+1) := '1';
            elsif vec(i) = 'U' then
                stmp(i+1) := 'U';
            else
                stmp(i+1) := '0';
            end if;
        end loop;
        return stmp;
    end vec2str;

    procedure check_add(
        constant in1 : in natural;
        constant in2 : in natural;
        constant res_expected : in natural;
        constant CB_expected : in std_logic) is
        variable res : natural;
    begin
        -- Assign values to circuit inputs.
        A <= std_logic_vector(to_unsigned(in1, A'length));
        B <= std_logic_vector(to_unsigned(in2, B'length));
        Control <= ADD_Code;

        wait for TIME_DELTA;
        -- Check output against expected result.
        res := to_integer(unsigned(nBitOut));
        assert ((res = res_expected) and ( CB = CB_expected ))
        report "" & integer'image(in1) & "+" &
            integer'image(in2) & "=" &
            integer'image(res_expected) & "!=" &
            integer'image(res) &
            "____" &
            "CB_exp:_" & std_logic'image(CB_expected) &
            "Got:_" & std_logic'image(CB)
            severity error;
    end procedure check_add;

    procedure check_sub(

```



---

```

constant in1 : in natural;
constant in2 : in natural;
constant res_expected : in natural;
constant CB_expected : in std_logic) is
variable res : natural;
begin
— Assign values to circuit inputs.
A <= std_logic_vector(to_unsigned(in1, A'length));
B <= std_logic_vector(to_unsigned(in2, B'length));
Control <= SUB_Code;

wait for TIMEDELTA;
— Check output against expected result.
res := to_integer(unsigned(nBitOut));
assert ((res = res_expected) and ( CB = CB_expected ))
report "" & integer'image(in1) & "-" &
integer'image(in2) & "=" &
integer'image(res_expected) & "!=" &
integer'image(res) &
"____" &
"CB_exp:_" & std_logic'image(CB_expected) &
"Got:_" & std_logic'image(CB)
severity error;
end procedure check_sub;

procedure check_or(
constant in1 : in natural;
constant in2 : in natural;
constant res_expected : in natural) is
variable res : natural;
begin
— Assign values to circuit inputs.
A <= std_logic_vector(to_unsigned(in1, A'length));
B <= std_logic_vector(to_unsigned(in2, B'length));
Control <= OR_Code;

wait for TIMEDELTA;
— Check output against expected result.
res := to_integer(unsigned(nBitOut));
assert ((res = res_expected) and ( CB = '0' ))
report "" & integer'image(in1) & "+" &
integer'image(in2) & "=" &
integer'image(res_expected) & "!=" &
integer'image(res) &
"____" &

```

---

```

        "CB:_" & std_logic'image(CB)
    severity error;
end procedure check_or;

procedure check_and(
    constant in1 : in natural;
    constant in2 : in natural;
    constant res_expected : in natural) is
    variable res : natural;
begin
    -- Assign values to circuit inputs.
    A <= std_logic_vector(to_unsigned(in1, A'length));
    B <= std_logic_vector(to_unsigned(in2, B'length));
    Control <= AND_Code;

    wait for TIME_DELTA;
    -- Check output against expected result.
    res := to_integer(unsigned(nBitOut));
    report "" & integer'image(in1) & "+" &
        integer'image(in2) & "=" &
        integer'image(res_expected);

    assert ((res = res_expected) and (CB = '0' ))
    report "!=" &
        integer'image(res) &
        "____" &
        "CB:_" & std_logic'image(CB)
    severity error;
end procedure check_and;

begin

    --wait for the outputs to stabilize
    wait for 100 ns;

    --check_add(4,5,9,0);
    --check_add(65535, 2, 1, 1);
    --check_sub(1234, 234, 1000, 0);
    --check_sub(1, 2, 1, 1);

    control <= OR_Code;
    A <= "0111010101110101";
    B <= "1001110100101101";
    wait for 50 ns;

```

---

```

    control <= AND_Code;
    wait for 50 ns;

    -- Test adder
    for x in (0) to (5) loop
        for y in 5432 to 5438 loop
            control <= ADD_Code;
            A <= std_logic_vector(to_unsigned(x, A'length));
            B <= std_logic_vector(to_unsigned(y, B'length));
            wait for 50 ns;

            assert(nBitOut = std_logic_vector(to_unsigned(x+y, A'length) ) )
            report("Bad_Add=" & vec2str(nBitOut)
                & "expected=" & vec2str( std_logic_vector(to_unsigned(x+y, A'length) ) )
                & "A=" & vec2str(A)
                & "B=" & vec2str(B)
            );
        end loop;
    end loop;

    for x in ((2**N)-3) to ((2**N)-1) loop
        for y in 0 to 3 loop
            control <= ADD_Code;
            A <= std_logic_vector(to_unsigned(x, A'length));
            B <= std_logic_vector(to_unsigned(y, B'length));
            wait for 50 ns;

            assert(nBitOut = std_logic_vector(to_unsigned(x+y, A'length) ) )
            report("Bad_Add=" & vec2str(nBitOut)
                & "expected=" & vec2str( std_logic_vector(to_unsigned(x+y, A'length) ) )
                & "A=" & vec2str(A)
                & "B=" & vec2str(B)
            );
        end loop;
    end loop;

    -- Test suber
    for x in 0 to 5 loop
        for y in 0 to 5 loop
            control <= SUB_Code;
            A <= std_logic_vector(to_unsigned(x, A'length));
            B <= std_logic_vector(to_unsigned(y, B'length));
            wait for 50 ns;

            assert(nBitOut = std_logic_vector(to_signed(x-y, A'length)) )
            report("Bad_Sub=" & vec2str(nBitOut)
                & "expected=" & vec2str( std_logic_vector(to_signed(x-y, A'length)) )
            );
        end loop;
    end loop;

```

---

```

        & "A=" & vec2str(A)
        & "B=" & vec2str(B)
    );

    end loop;
end loop;

for x in 12345 to 12350 loop
    for y in 5 to 7 loop
        control <= SUB_Code;
        A <= std_logic_vector(to_unsigned(x, A'length));
        B <= std_logic_vector(to_unsigned(y, B'length));
        wait for 50 ns;

        assert(nBitOut = std_logic_vector(to_signed(x-y, A'length)) )
        report("Bad_Sub=" & vec2str(nBitOut)
            & "expected=" & vec2str( std_logic_vector(to_signed(x-y, A'length))
            & "A=" & vec2str(A)
            & "B=" & vec2str(B)
        );

    end loop;
end loop;

wait;
end process;

END;
```

Listing 11: ALU\_4Bit\_tb VHDL

Listing 12: ALU\_16Bit VHDL

---

```

--Company      : RIT
--Author       : Brandon Key
--Created      : 02/18/2018
--
--Project Name : Lab 3
--File         : ALU_16Bit.vhd
--
--Entity       : ALU_16Bit
--Architecture : struct
--
--Tool Version : VHDL '93
--Description  : ALU_16Bit
```

---

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

package globals is
    constant N : integer := 16;
end globals;

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

package controlcodes is
    constant AND_Code : std_logic_vector(1 downto 0) := "00";
    constant OR_Code  : std_logic_vector(1 downto 0) := "01";
    constant ADD_Code : std_logic_vector(1 downto 0) := "10";
    constant SUB_Code : std_logic_vector(1 downto 0) := "11";
end controlcodes;

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.numeric_std.all;
use work.controlcodes.all;
use work.globals.all;

entity ALU_16Bit is
    port(
        Control : in std_logic_vector(1 downto 0);
        A,B      : in std_logic_vector(N-1 downto 0);
        nBitOut  : out std_logic_vector(N-1 downto 0);
        CB       : out std_logic
    );
end ALU_16Bit;

architecture struct of ALU_16Bit is

    --constant N : integer := 4;

    signal ADD_SUB_Out : std_logic_vector(N-1 downto 0);
    signal OR_Out      : std_logic_vector(N-1 downto 0);
    signal AND_Out     : std_logic_vector(N-1 downto 0);

    signal ADD_SUB_SEL : std_logic;

begin

```

---

```

nBitAdderSubtractor_16Bit : entity work.nBitAdderSubtractor_16Bit
    generic map (N => N)
    port map ( A => A, B => B, SEL => ADD.SUB_SEL, Y => ADD.SUB_Out, CB => CB);

nBitOR_16Bit : entity work.nBitOR_16Bit
    generic map (N => N)
    port map ( A => A, B => B, Y => OR_Out);

nBitAND_16Bit : entity work.nBitAND_16Bit
    generic map (N => N)
    port map ( A => A, B => B, Y => AND_Out);

Controller_16Bit : entity work.Controller_16Bit
    generic map (N => N)
    port map(
        Control      => Control ,
        ADD.SUB_In   => ADD.SUB_Out,
        OR_In        => OR_Out,
        AND_In       => AND_Out,
        ADD.SUB_SEL  => ADD.SUB_SEL,
        nBitOut      => nBitOut
    );

end    struct;

```

Listing 12: ALU\_16Bit VHDL

Listing 13: nBitOR\_16Bit VHDL

---

```

--Company      : RIT
--Author       : Brandon Key
--Created      : 1/22/2018
--
--Project Name : Lab 1
--File         : nBitOR_16Bit.vhd
--
--Entity       : nBitOR_16Bit
--Architecture : Dataflow
--
--Tool Version : VHDL '93
--Description  : Entity and structural description of an OR gate

```

---

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

```

---

```

entity  nBitOR_16Bit  is
    generic (n : integer := 16);
    port(A,B : in  std_logic_vector(n-1 downto 0);
        Y : out  std_logic_vector(n-1 downto 0)
        );
end  nBitOR_16Bit;

architecture  Dataflow  of  nBitOR_16Bit  is
    begin
        Y <= A or B;-- bitwise or
    end  Dataflow;

```

Listing 13: nBitOR\_16Bit VHDL

Listing 14: nBitAdderSubtractor\_16Bit VHDL

---

```

--Company      : RIT
--Author       : Brandon Key
--Created      : 02/18/2018
--
--Project Name : Lab 3
--File         : nBitAdderSubtractor_16Bit.vhd
--
--Entity       : nBitAdderSubtractor_16Bit
--Architecture : struct
--
--Tool Version : VHDL '93
--Description  : Entity and structural description of an adder subtractor
--              : SEL = 0 : A+B = Y
--              : SEL = 1 : A-B = Y

```

---

```

library  IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.numeric_std.all;

entity  nBitAdderSubtractor_16Bit  is
    generic (n : integer := 16);
    port(
        A,B : in  std_logic_vector(n-1 downto 0);
        SEL : in  std_logic;
        Y   : out std_logic_vector(n-1 downto 0);
        CB  : out std_logic
    );
end  nBitAdderSubtractor_16Bit;

architecture  struct  of  nBitAdderSubtractor_16Bit  is

```

---

```

component full_adder is
    port(A,B,Cin : in  std_logic;
        Sum,Cout : out  std_logic
    );
end component full_adder;

--Create an array to hold all of the carries
type carry_array is array (n-1 downto 0) of std_logic;
signal c_array : carry_array;

signal B_XOR_SEL : std_logic_vector( (n-1) downto 0);

begin

--Generate the xor statements to be mapped to the full adders
XORator : for i in 0 to n-1 generate
    B_XOR_SEL(i) <= B(i) xor SEL;
end generate XORator;

generate_adders : for i in 0 to n-1 generate
    i_first: if i = 0 generate
        --The first adder gets SEL as the Cin
        adder : full_adder port map(
            A => A(i),
            B => B_XOR_SEL(i),
            Cin => SEL,
            Sum => Y(i),
            Cout => c_array(i)
        );
    end generate i_first;

    i_last : if i = (n-1) generate
        --The last adder doesn't have a carry out
        adder : full_adder port map(
            A => A(i),
            B => B_XOR_SEL(i),
            Cin => c_array(i-1),
            Sum => Y(i),
            Cout => c_array(i)
        );
    end generate i_last;

--Middle adders
i_mid : if (i /= 0) and (i /= (n-1)) generate
    adder : full_adder port map(
        A => A(i),
        B => B_XOR_SEL(i),

```



---

```

        Cin => c_array(i-1),
        Sum => Y(i),
        Cout => c_array(i)
    );
end generate i_mid;

end generate generate_adders;

CB <= c_array(n-1) xor SEL;

end struct;

```

Listing 14: nBitAdderSubtractor\_16Bit VHDL

Listing 15: nBitAND\_16Bit VHDL

---

```

--Company      : RIT
--Author       : Brandon Key
--Created      : 1/22/2018
--
--Project Name : Lab 1
--File         : nBitAND_16Bit.vhd
--
--Entity       : nBitAND_16Bit
--Architecture : Dataflow
--
--Tool Version : VHDL '93
--Description  : Entity and structural description of an AND gate

```

---

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity nBitAND_16Bit is
    generic (n : integer := 16);
    port(A,B : in std_logic_vector(n-1 downto 0);
         Y : out std_logic_vector(n-1 downto 0)
    );
end nBitAND_16Bit;

architecture Dataflow of nBitAND_16Bit is
    begin
        Y <= A AND B;-- bitwise or
    end Dataflow;

```

Listing 15: nBitAND\_16Bit VHDL

## 5.2 SPICE

---

Listing 16: 1-Bit ALU SPICE

\* Example circuit file for simulating PEX

.OPTION DONTNODE

.HIER /

.INCLUDE "/home/bxk5113/Pyxis\_SPT\_HEP/ic\_projects/Pyxis\_SPT/digicdesign/ALU\_1Bit/ALU\_1Bit.cir

.LIB /home/bxk5113/Pyxis\_SPT\_HEP/ic\_reflibs/tech\_libs/generic13/models/lib.eldo TT

\* — Instantiate your parasitic netlist and add the load capacitor

\*\* FORMAT :

\* XLAYOUT [all inputs as listed by the ".subckt" line in the included netlist, in t

XLAYOUT CB Y A B CONTROL[1] CONTROL[0] ALU\_1Bit

C1 Y 0 120f

C2 CB 0 120f

\* — Analysis Setup — DC sweep

\* FORMAT : .DC [name] [low] [high] [step]

\*.DC VFORCE\_A 0 1.2 0.01

\* — Analysis Setup — Trans

\* FORMAT : .TRAN [start time] [end time] [time step]

.TRAN 0 160n 0.001n

\* — Forces

\* FORMAT — PULSE : [name] [port] [reference (0 means ground)] PULSE [low] [high] [

\*

\* FORMAT — DC : [name] [port] [reference (0 means ground)] DC [voltage]

\*

VFORCE\_A A 0 PULSE (0 1.08 40n 0.1n 0.1n 40n 80n)

VFORCE\_B B 0 PULSE (0 1.08 80n 0.1n 0.1n 80n 160n)

VFORCE\_C1 CONTROL[1] 0 DC 1.08

VFORCE\_C0 CONTROL[0] 0 DC 1.08

VFORCE\_VDD VDD 0 DC 1.08

VFORCE\_VSS VSS 0 DC 0

\* — Waveform Outputs

.PLOT TRAN V(A)

.PLOT TRAN V(B)

.PLOT TRAN V(CONTROL[1])

.PLOT TRAN V(CONTROL[0])

.PLOT TRAN V(Y)

.PLOT TRAN V(CB)

---

\* — Params  
.TEMP 125

Listing 16: 1-Bit ALU SPICE