
CMPE-630 Digital IC Design
Laboratory Exercise 7
Autolayout Design Techniques (HDL-Layout)

Brandon Key and Chris Guarini
Performed: 9 Dec 2019
Submitted: 9 Dec 2019

Instructor: Dr. Amlan Ganguly
TAs: Abhishek Vashist
Andrew Fountain
Piers Kwan

By submitting this report, you attest that you neither have given nor have received any assistance (including writing, collecting data, plotting figures, tables or graphs, or using previous student reports as a reference), and you further acknowledge that giving or receiving such assistance will result in a failing grade for this course.

Your Signature: _____

Contents

1	Abstract	3
2	Design Methodology and Theory	3
3	Results and Analysis	4
3.1	Layout	31
3.2	Timing	31
3.3	Power	31
4	Conclusion	31
5	Appendix	31
5.1	VHDL	31
5.2	Leonardo Scripts	81
5.3	SPICE	83
6	References	89

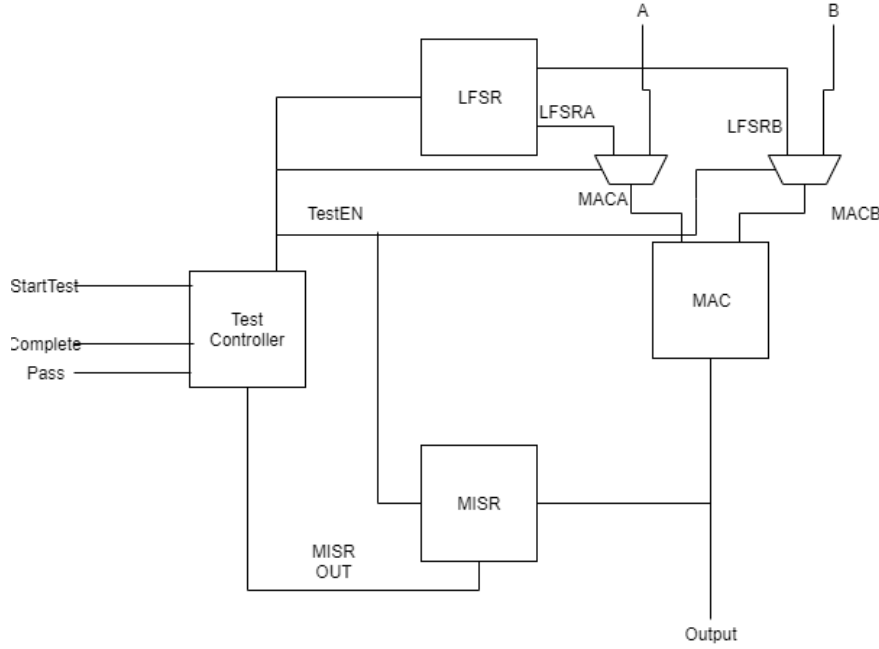


Figure 1: **Figure 1:** High Level Block Diagram of the MAC with BIST.

1 Abstract

Integrated Circuit Design is a costly and complex endeavor. Fortunately, automatic tools speed up the process and allow designs that are not possible to create manually. This exercise implemented a 1-Bit ALU and a 16-Bit ALU using autolayout. The autolayout tools generated very reasonable circuits. The 1-Bit ALU has an input frequency of 380.92MHz and a throughput frequency of 553.4MHz, while the 16-bit ALU has an input frequency of 461.02MHz and a throughput frequency of 110.2MHz. The area used by the ALUs was also reasonable with the 1-bit ALU taking up $647.89\mu m^2$ and the 16-bit ALU occupying $9792.5\mu m^2$.

2 Design Methodology and Theory

A cornerstone of IC design is the ability to create large, complex designs from smaller more manageable parts. The project outlined in this exercise calls for the design, testing and layout of a multiply and accumulate (MAC) unit, which takes two 16-bit inputs, multiplies them together, adds them to the value stored in a register, and then stores that output back into the register. The final component should contain a built in self test (BIST) that verifies the functionality of the MAC.

The MAC is composed of a carry-save multiplier, ripple carry full-adder, and parallel register. The BIST is implemented through the use of an LFSR for the inputs, an MISR for the output, and a test controller which controls the timing and sets the test passed and test complete outputs. A full diagram of the MAC with BIST can be seen below in *Figure 1*.

3 Results and Analysis

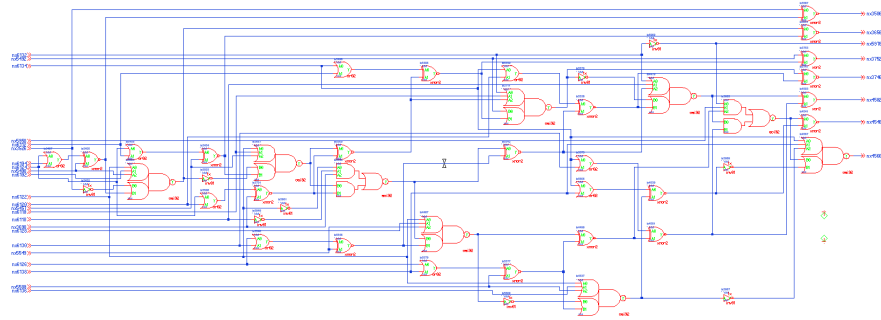


Figure 2: Full Schematic Page 7

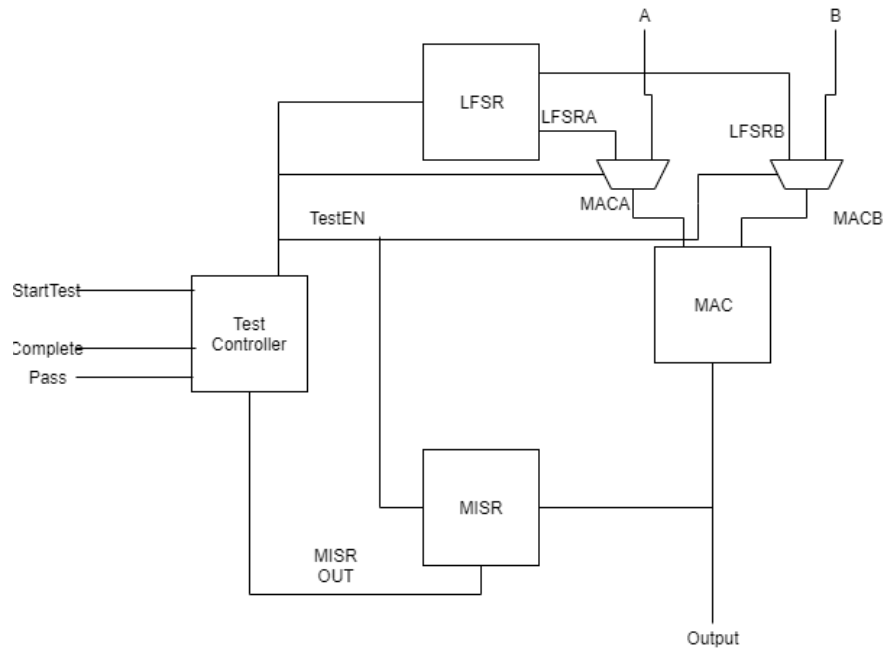


Figure 3: Full Project Block


 


Figure 4: Full Layout

 

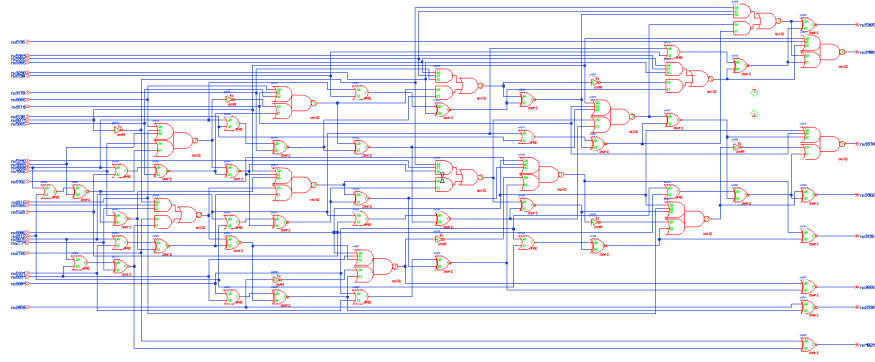


Figure 6: Full Schematic Page 2

 


Figure 7: Multiplier Schematic Page 2

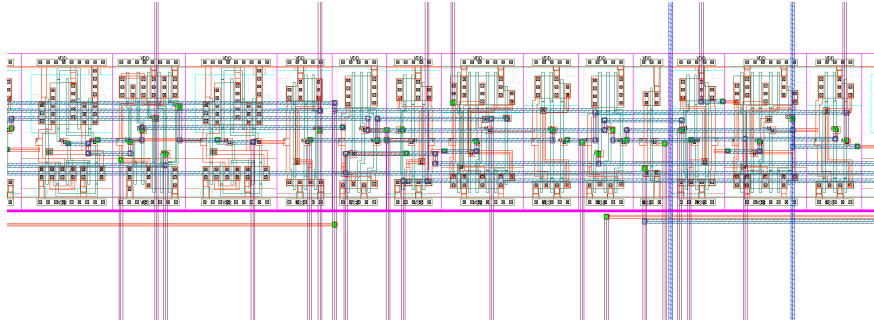


Figure 8: Full Layout Close Up View

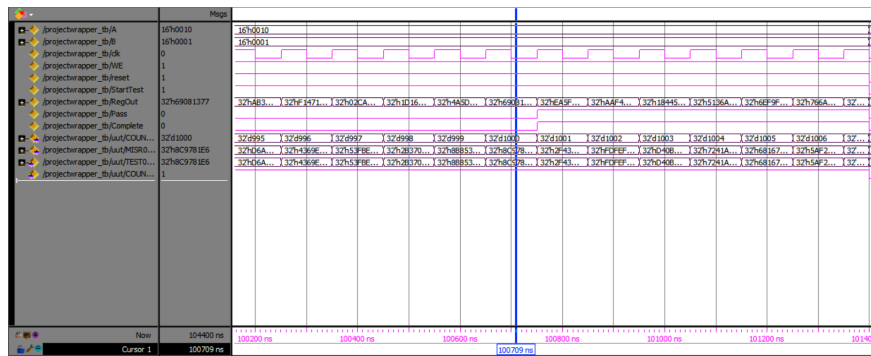


Figure 9: BIST Test Bench

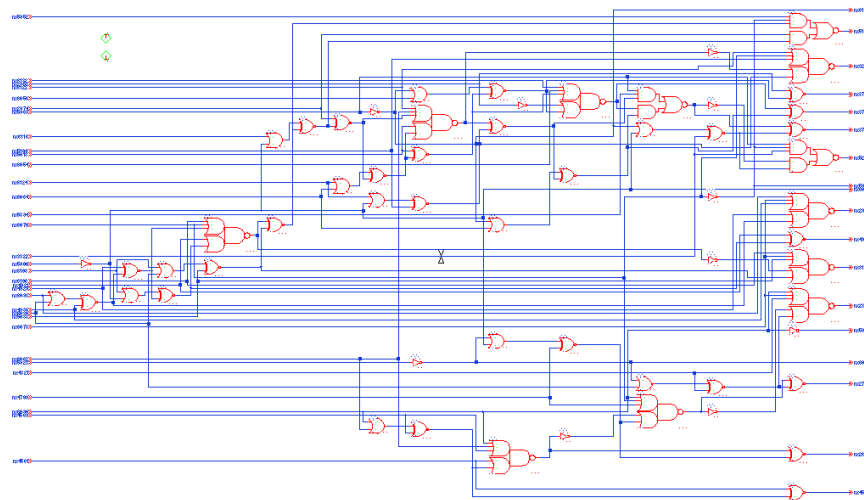


Figure 10: Full Schematic Page 17



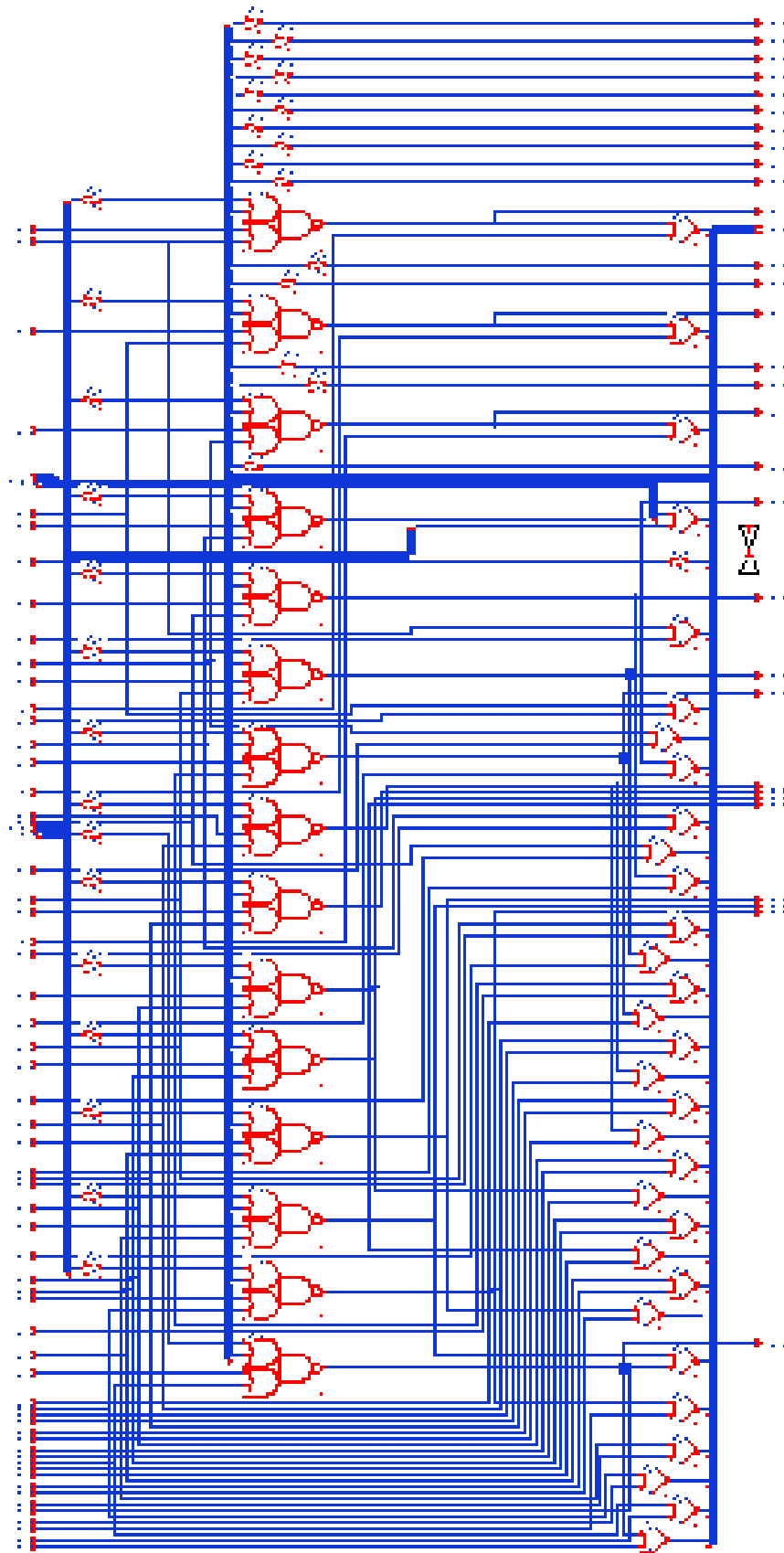


Figure 12: nBitAdder Schematic Page 1

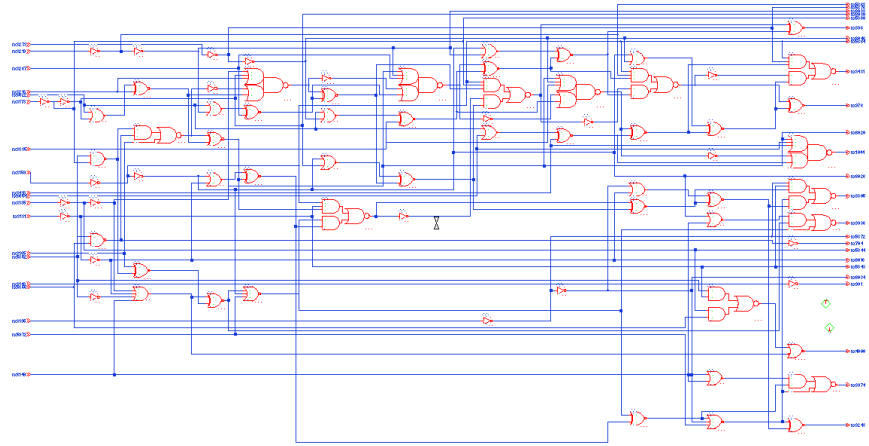


Figure 13: Full Schematic Page 27

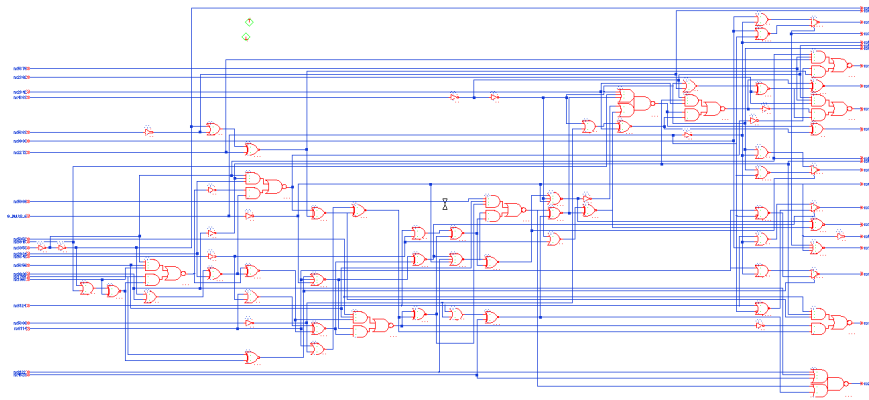


Figure 14: Full Schematic Page 15




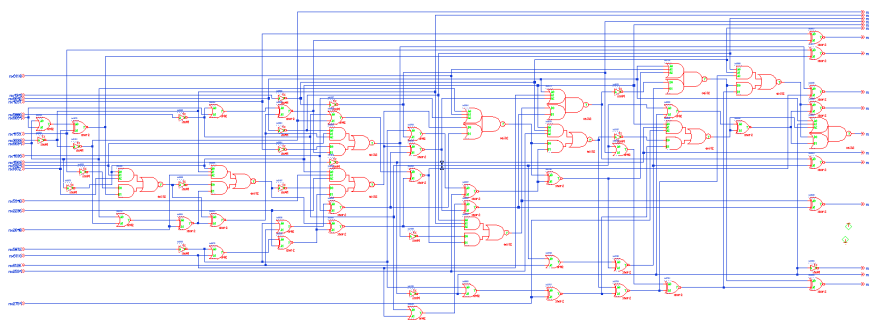


Figure 15: Full Schematic Page 19

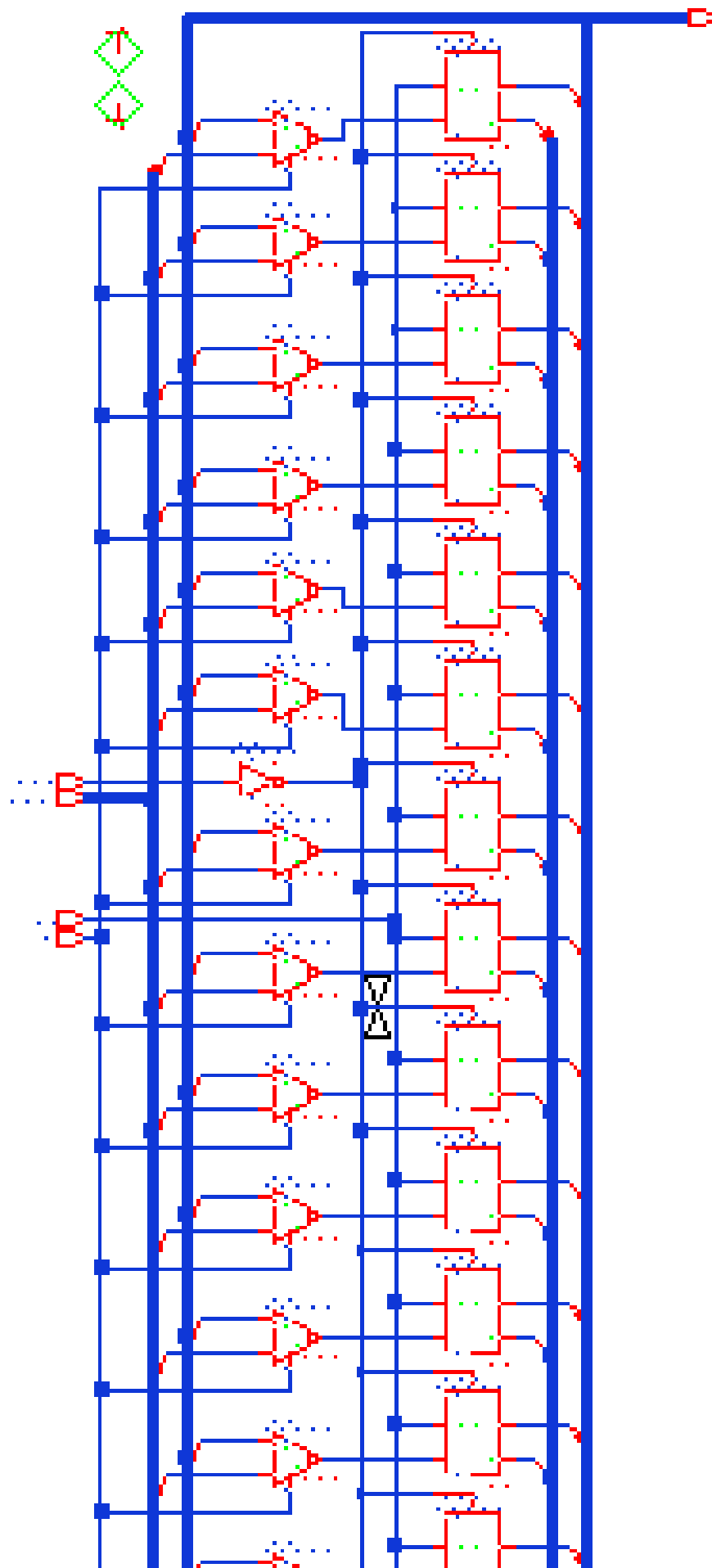

 

 

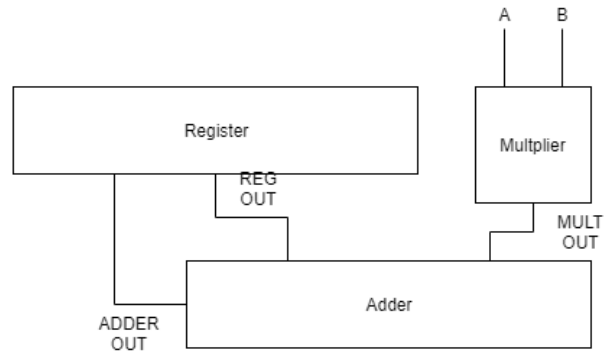


Figure 19: MAC block

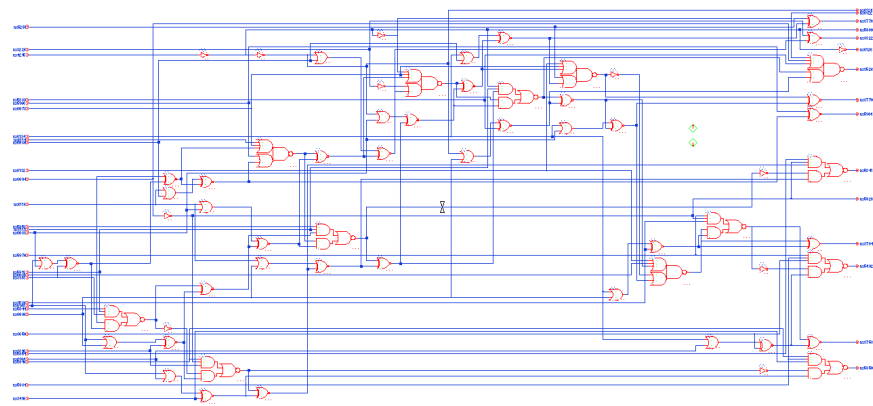


Figure 20: Full Schematic Page 5


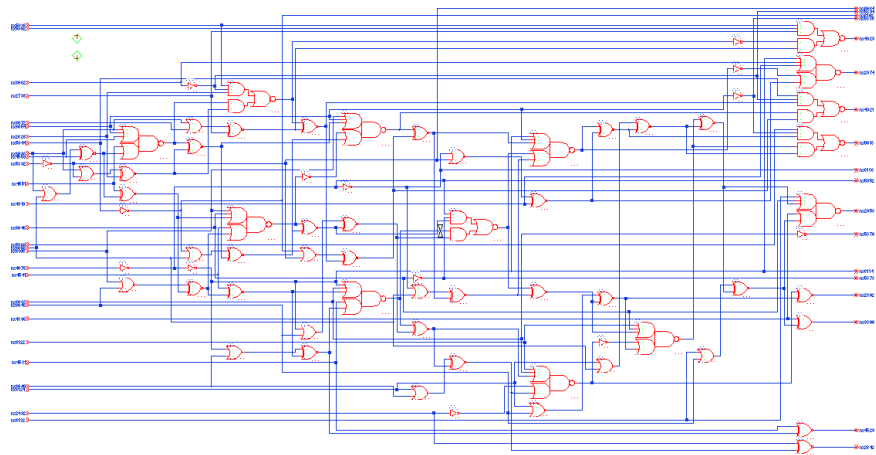


Figure 21: Full Schematic Page 16

 


 


Figure 23: Full Schematic Page 26

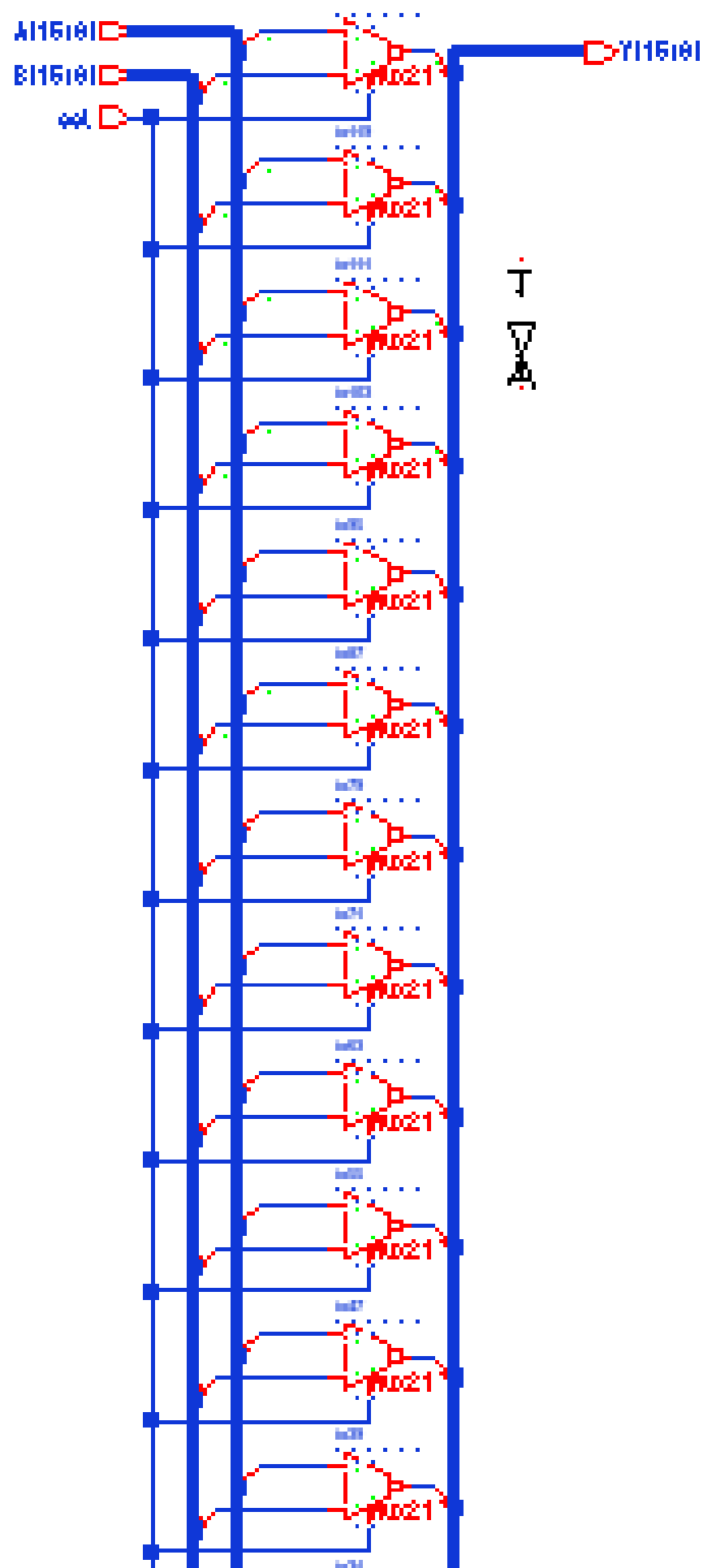

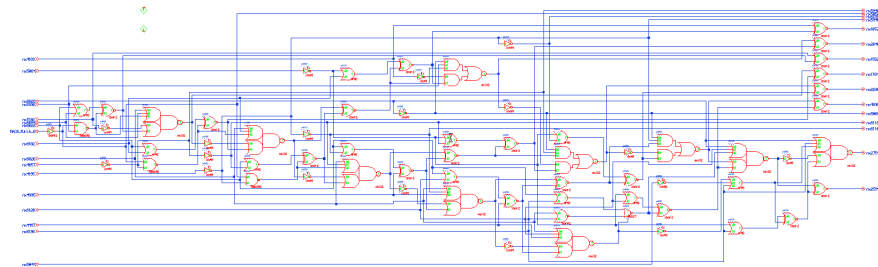


Figure 25: Full Schematic Page 1

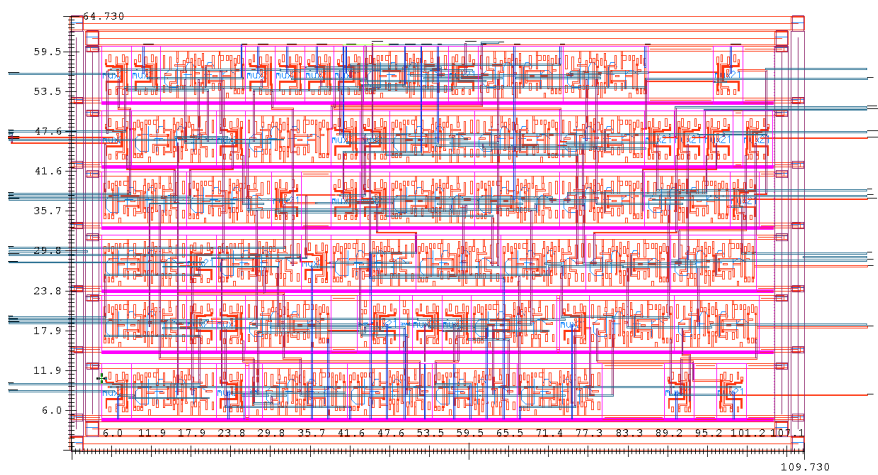


Figure 26: nBitRegister 32 Bit Layout

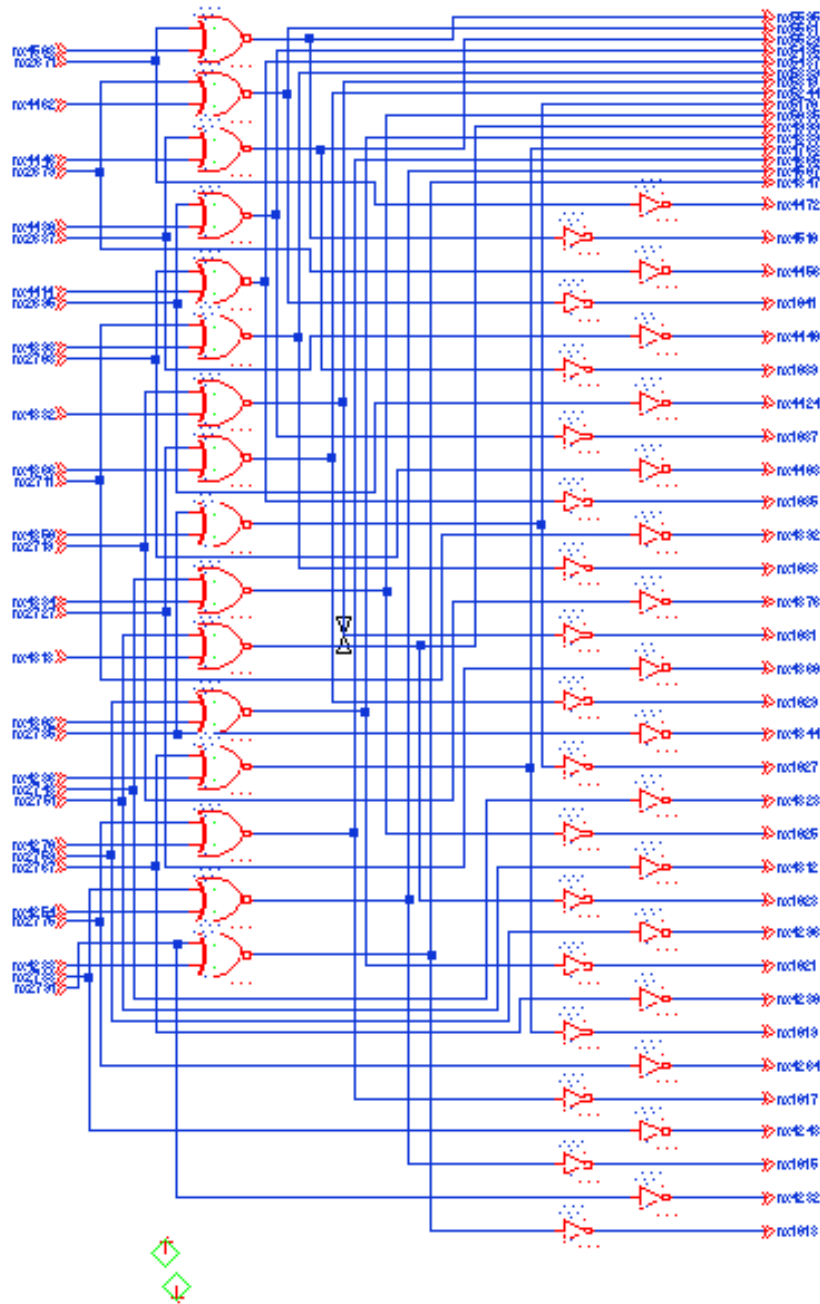


Figure 27: Full Schematic Page 9

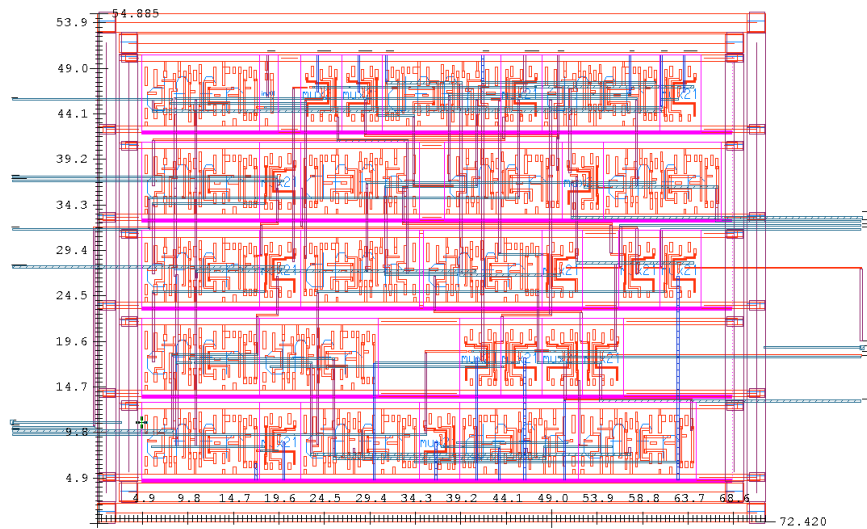


Figure 28: nBitRegister 16 Bit Layout

 


Figure 29: Full Schematic Page 23

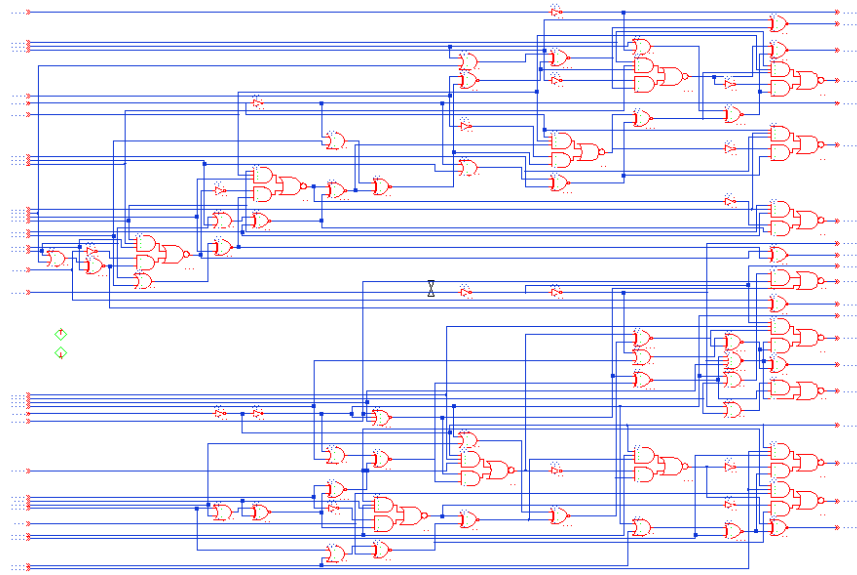


Figure 30: Full Schematic Page 28

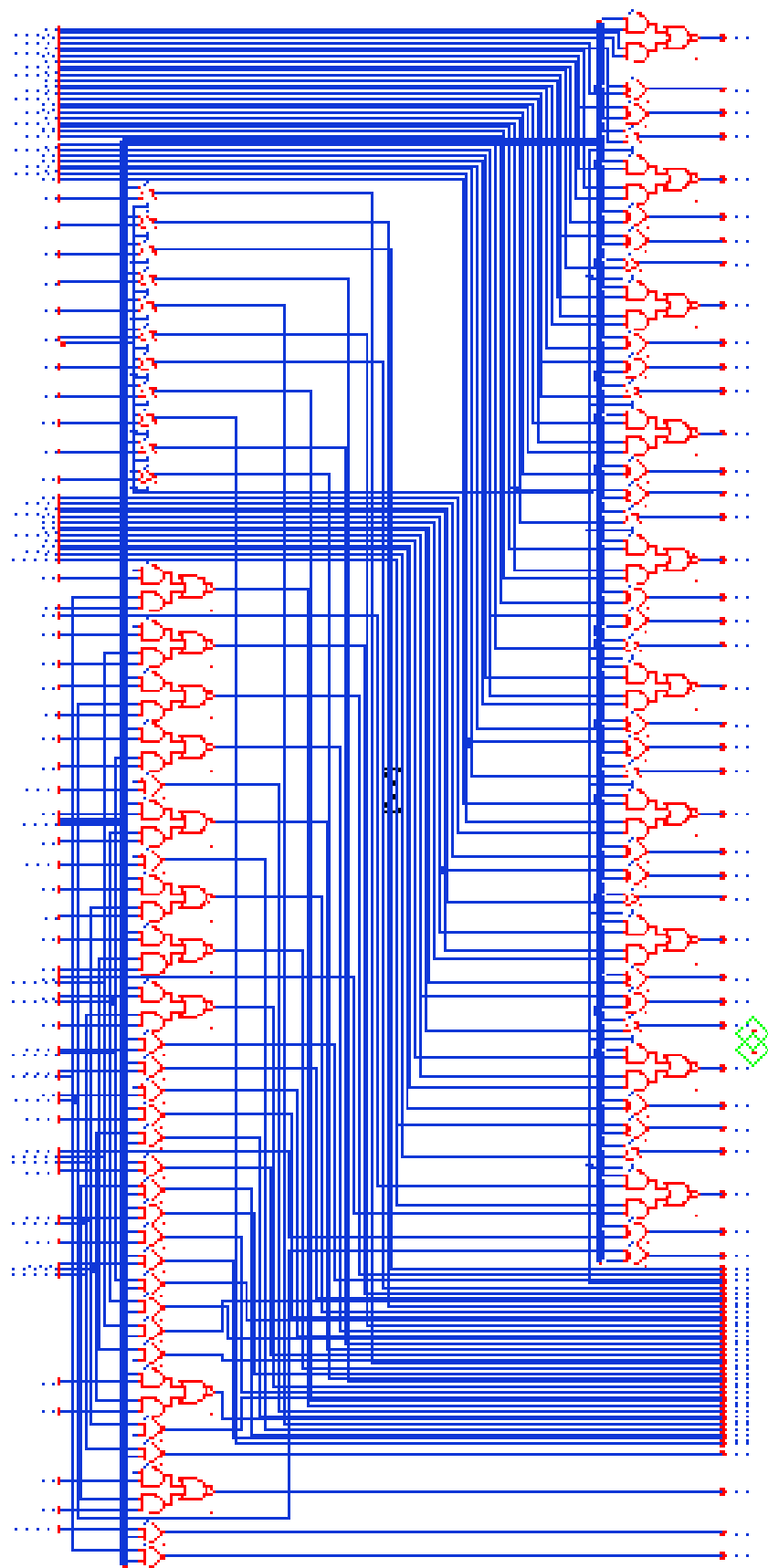


Figure 31: Full Schematic Page 22

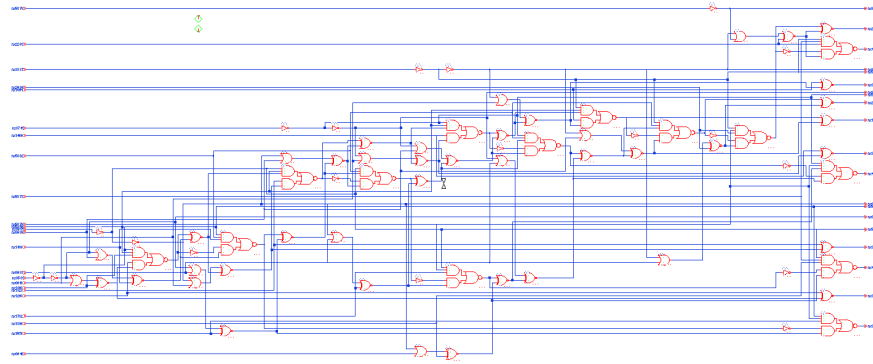


Figure 32: Full Schematic Page 14

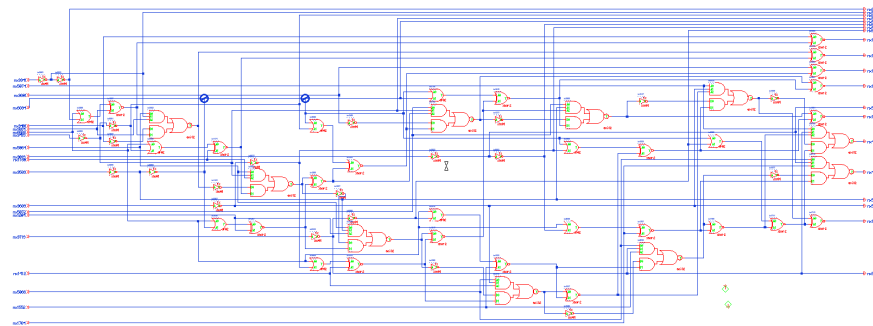


Figure 33: Full Schematic Page 13

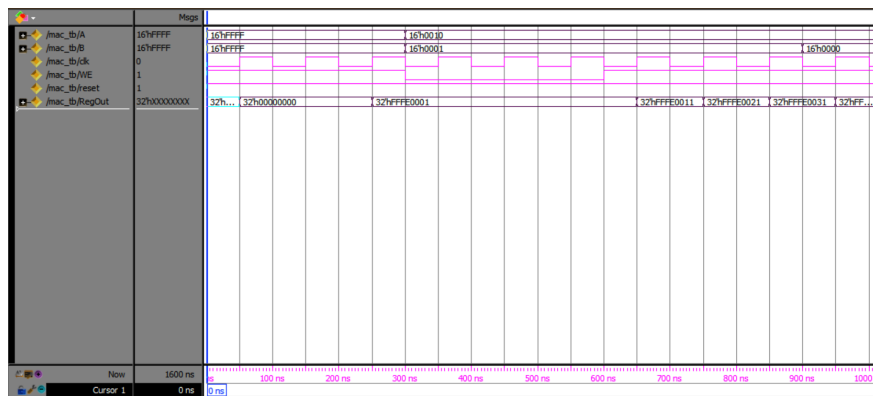


Figure 34: MAC 16bit Test Bench

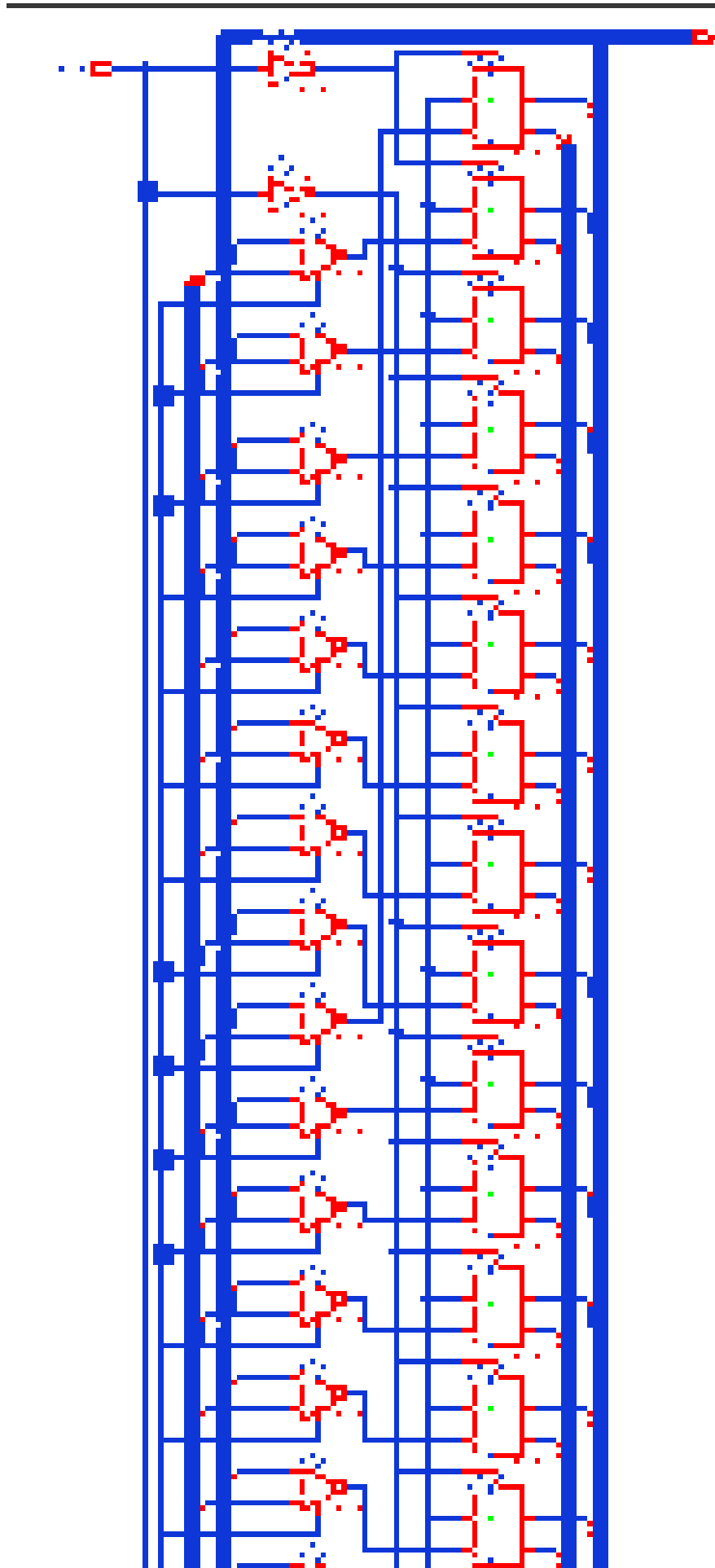


Figure 36: Full Schematic Page 18

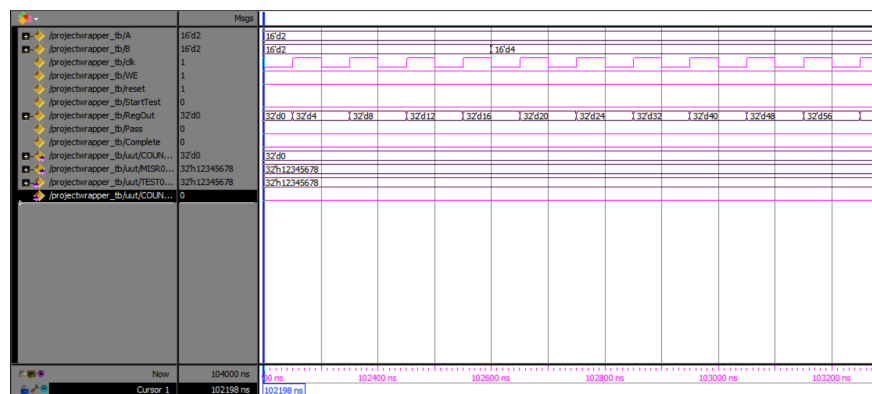


Figure 37: MAC Test Bench

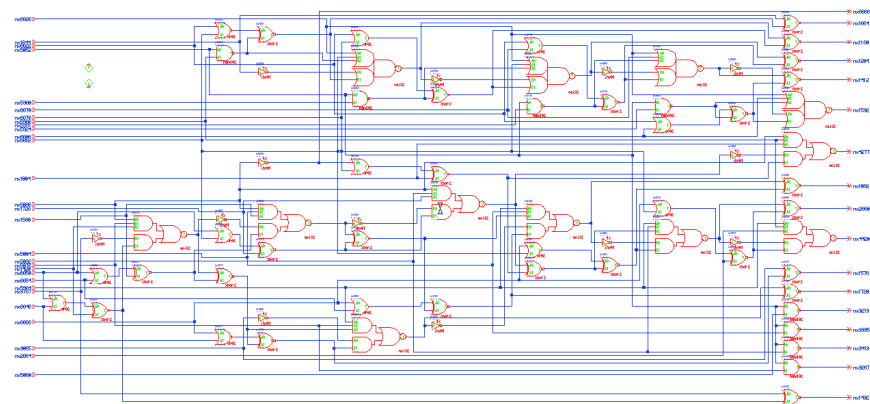


Figure 38: Full Schematic Page 12



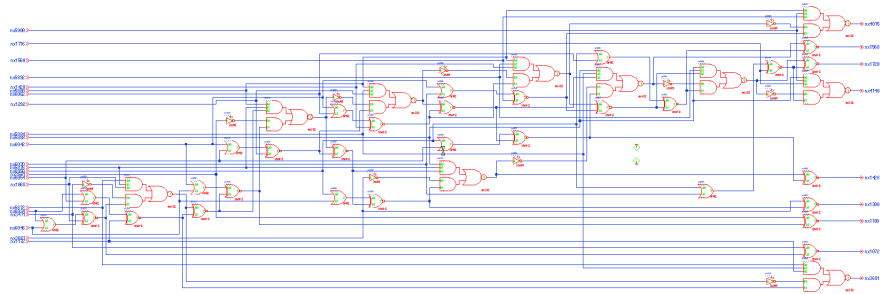


Figure 39: Full Schematic Page 11

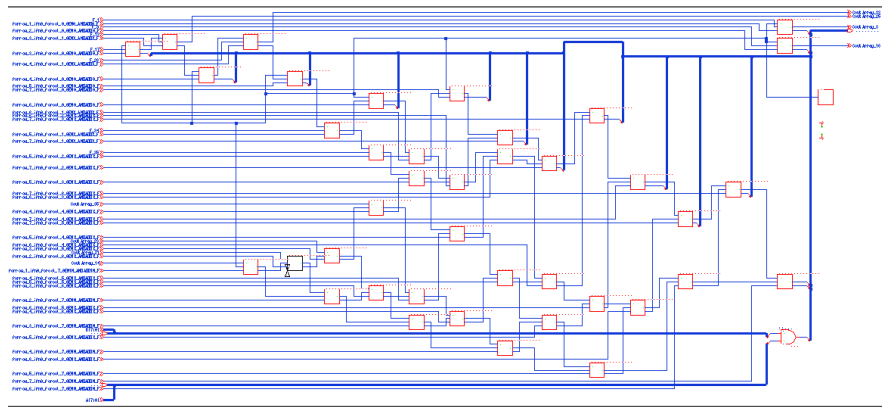

 

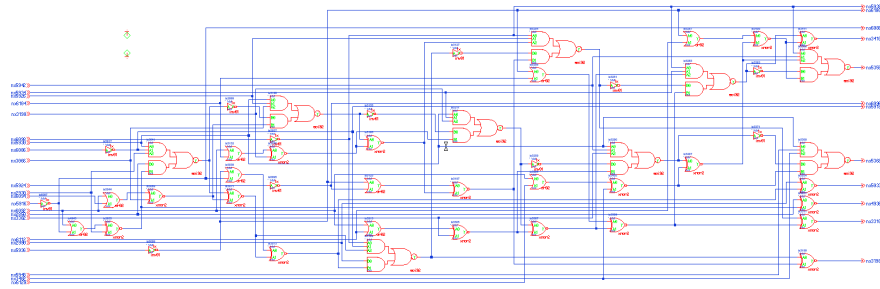


Figure 42: Full Schematic Page 4

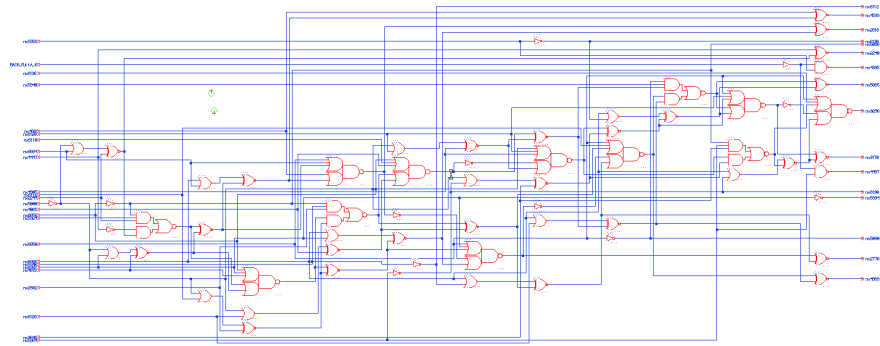


Figure 43: Full Schematic Page 3

 


Figure 44: Full Schematic Page 25

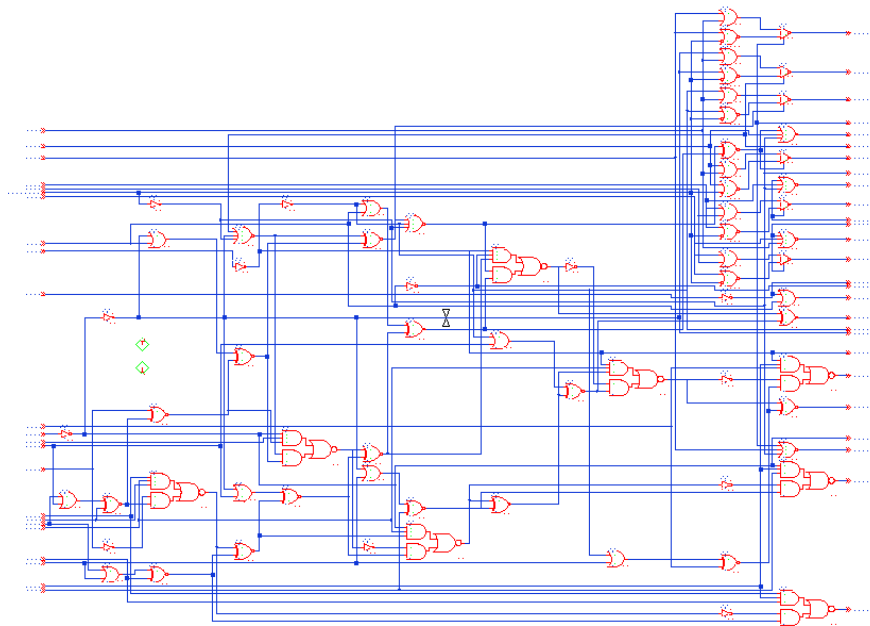


Figure 45: Full Schematic Page 10

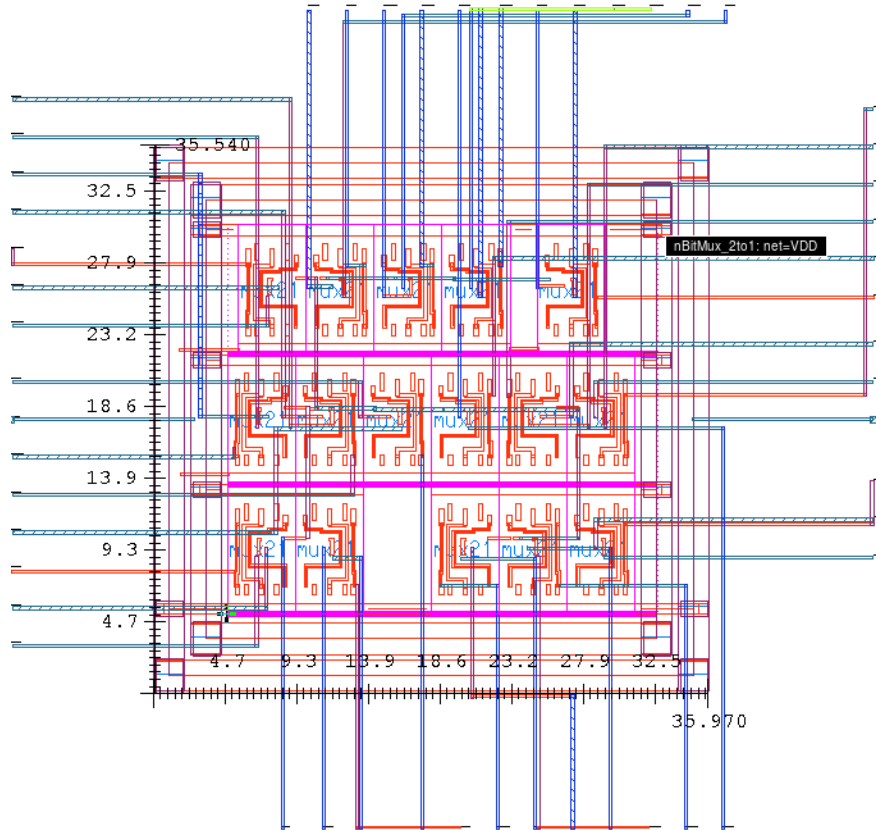


Figure 46: nBitMux 2to1 Layout

3.1 Layout

3.2 Timing

3.3 Power

4 Conclusion

5 Appendix

5.1 VHDL

Listing 1: MAC tb VHDL

```

0  — Testbench created online at:
   — www.doulos.com/knowhow/perl/testbench_creation/
   — Copyright Doulos Ltd
   — SD, 03 November 2002

5  library IEEE;
   use IEEE.Std_logic_1164.all;
   use IEEE.Numeric_Std.all;

   entity MAC_tb is
10 end;
```

```

architecture bench of MAC_tb is

    constant N : integer := 32;

15
    component MAC
        generic( N : integer := 32);
        Port ( A : in  STD_LOGIC_VECTOR ((N/2) - 1  downto 0);
              B : in  STD_LOGIC_VECTOR ((N/2) - 1  downto 0);
20
              clk : in  STD_LOGIC;
              WE : in  STD_LOGIC;
              reset : in  STD_LOGIC;
              RegOut : out  STD_LOGIC_VECTOR (N-1  downto 0));
    end component;

25
    signal A: STD_LOGIC_VECTOR ((N/2) - 1  downto 0);
    signal B: STD_LOGIC_VECTOR ((N/2) - 1  downto 0);
    signal clk: STD_LOGIC;
    signal WE: STD_LOGIC;
30
    signal reset: STD_LOGIC;
    signal RegOut: STD_LOGIC_VECTOR (N-1  downto 0);

begin

35
    -- Insert values for generic parameters !!
    uut: MAC generic map ( N      => 32)
        port map ( A      => A,
                  B      => B,
                  clk     => clk ,
40
                  WE     => WE,
                  reset  => reset ,
                  RegOut => RegOut );

    clk_proc : process
45
    begin
        if clk = '0' then
            clk <= '1';
        else
            clk <= '0';
50
        end if;
        wait for 50 ns;
    end process;

    stimulus: process
55
    begin

        -- Put initialisation code here
        WE <= '1';
        reset <= '1';
60
        A <= "1111111111111111";
        B <= "1111111111111111";

        wait for 300 ns;
        WE <= '0';
65
        A <= "0000000000010000";
        B <= "0000000000000001";
        wait for 300 ns;
        WE <= '1';

70
        wait for 300 ns;

```



```

    B <= "0000000000000000";

    wait for 300 ns;
    reset <= '0';

    -- Put test bench stimulus code here

    wait;
end process;

end;

```

Listing 2: ProjectWrapper tb VHDL

```

0 library IEEE;
  use IEEE.Std_logic_1164.all;
  use IEEE.Numeric_Std.all;

  entity ProjectWrapper_tb is
5  end;

  architecture bench of ProjectWrapper_tb is

    constant N : integer := 32;

10   component ProjectWrapper
      generic( N : integer := 32);
      Port ( A : in  STDLOGIC_VECTOR ((N/2) - 1  downto 0);
        B : in  STDLOGIC_VECTOR ((N/2) - 1  downto 0);
15      clk : in STDLOGIC;
        WE : in STDLOGIC;
        reset : in STDLOGIC;
        StartTest : in STDLOGIC;
        RegOut : out STDLOGIC_VECTOR (N-1  downto 0);
20      Pass : out STDLOGIC;
        Complete : out STDLOGIC
      );
    end component;

25   signal A: STDLOGIC_VECTOR ((N/2) - 1  downto 0);
   signal B: STDLOGIC_VECTOR ((N/2) - 1  downto 0);
   signal clk: STDLOGIC;
   signal WE: STDLOGIC;
   signal reset: STDLOGIC;
30   signal StartTest: STDLOGIC;
   signal RegOut: STDLOGIC_VECTOR (N-1  downto 0);
   signal Pass : STDLOGIC;
   signal Complete : STDLOGIC;

35 begin

    -- Insert values for generic parameters !!
    uut: ProjectWrapper generic map ( N      => 32)
                          port map ( A      => A,
40                                B      => B,
                                clk     => clk ,
                                WE      => WE,

```

```

45         reset    => reset ,
           StartTest => StartTest ,
           RegOut   => RegOut ,
           Pass     => Pass ,
           Complete => Complete );

clk_proc : process
50 begin
    if clk = '0' then
        clk <= '1';
    else
        clk <= '0';
55     end if;
    wait for 50 ns;
end process;

stimulus: process
60 begin

    -- Put initialisation code here

65     -- Put test bench stimulus code here

    -- Put initialisation code here
    WE <= '1';
    reset <= '0';
    StartTest <= '1';
70 A <= "0000000000000010";
    B <= "0000000000000010";
    wait for 300 ns;
    WE <= '0';
    wait for 300 ns;
    reset <= '1';
    A <= "0000000000010000";
    B <= "0000000000000001";
75 WE <= '1';
    wait for 100800 ns;
    reset <= '0';
    StartTest <= '0';
    A <= "0000000000000010";
    B <= "0000000000000010";
80 wait for 600 ns;
    reset <= '1';
    wait for 600 ns;
    B <= "0000000000000100";
85

    wait;
end process;

90

end;
95

```

Listing 3: FullAdder VHDL

```

0  --Company      : RIT
   --Author       : Brandon Key
   --Created      : 02/18/2018
   --
5  --Project Name : Lab 3
   --File         : Full_Adder.vhd
   --
   --Entity        : Full_Adder
   --Architecture  : behav
10  --
   --Tool Version  : VHDL '93
   --Description   : Entity and behavioral description of a full adder
   --
15
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Full_Adder is
20     port (A,B,Cin : in  std_logic;
           Sum,Cout : out std_logic
           );
end Full_Adder;

25 architecture behav of Full_Adder is
begin
    --uses select assignment to implement the truth table of a full adder

30     sum_proc: with std_logic_vector'(Cin&A&B) select
           Sum <= '0' when "000",
                  '1' when "001",
                  '1' when "010",
                  '0' when "011",
35                 '1' when "100",
                  '0' when "101",
                  '0' when "110",
                  '1' when "111",
                  '0' when others;

40     Cout_proc: with std_logic_vector'(Cin&A&B) select
           Cout <= '0' when "000",
                  '0' when "001",
                  '0' when "010",
45                 '1' when "011",
                  '0' when "100",
                  '1' when "101",
                  '1' when "110",
                  '1' when "111",
                  '0' when others;

50 end behav;

```

Listing 4: FA 1bit VHDL

```

0  --
   -- Company:

```

```

-- Engineer:
--
-- Create Date:      08:18:41 03/02/2017
5 -- Design Name:
-- Module Name:      FA_1bit - Behavioral
-- Project Name:
-- Target Devices:
-- Tool versions:
10 -- Description:
--
-- Dependencies:
--
-- Revision:
15 -- Revision 0.01 - File Created
-- Additional Comments:
--

```

```

library IEEE;
20 use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;
25
-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
30
entity FA_1bit is
    Port ( A : in  STD_LOGIC;
          B : in  STD_LOGIC;
          Cin : in  STD_LOGIC;
          S : out STD_LOGIC;
          Cout : out STD_LOGIC);
35 end FA_1bit;

architecture Behavioral of FA_1bit is
40
begin
    S<=((A xor B) xor Cin); --Sum
    Cout<=((A xor B) and Cin) or (A and B); --Cout
45
end Behavioral;

```

Listing 5: AND2 VHDL

```

0 --
-- Company:
-- Engineer:
--
-- Create Date:      15:02:42 03/15/2017
5 -- Design Name:
-- Module Name:      AND2 - Behavioral
-- Project Name:
-- Target Devices:
-- Tool versions:
10 -- Description:

```

```

--
-- Dependencies:
--
-- Revision:
15 -- Revision 0.01 - File Created
-- Additional Comments:
--

```

```

library IEEE;
20 use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;
25
-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
30
entity AND2 is
    Port ( A : in  STD_LOGIC;
           B : in  STD_LOGIC;
           F : out STD_LOGIC);
35 end AND2;

architecture Behavioral of AND2 is

begin
40     F <= A AND B;

end Behavioral;

```

Listing 6: nBitRegister VHDL

```

0 --
--Company      : RIT
--Author       : Brandon Key
--Created      : 2/8/2017
--
5 --Project Name : Lab 2
--File         : nBitRegister.vhd
--
--Entity       : nBitRegister
--Architecture : struct
10 --Revision    :
--Rev 0.01     : 2/8/2017
--
--Tool Version : VHDL '93
--Description  : Entity and behavioral description of an n-bit register
15 --
--Notes       :

```

```

library ieee;
20 use ieee.std_logic_1164.all;

entity nBitRegister is

```

```

generic (n : integer := 32);
Port (
    nBitIn : in std_logic_vector(n-1 downto 0); -- n bits to store in the
    register
    WE      : in std_logic; -- Active high write enable
    Reset   : in std_logic; -- Async reset, disabled when low
    clk     : in std_logic;
    Y : out std_logic_vector(n-1 downto 0) -- 1 output, n bits wide
);
end nBitRegister;

architecture behav of nBitRegister is

begin

    output_proc : process (clk, Reset) begin

        if Reset = '0' then
            Y <= (others => '0');
        elsif clk'event and clk = '1' then
            if WE = '1' then
                Y <= nBitIn;
            end if;
        end if;

    end process output_proc;

end behav;

```

Listing 7: Shifter VHDL

```

-- Company:
-- Engineer:
--
-- Create Date:    09:15:01 03/02/2017
-- Design Name:
-- Module Name:    Shifter - Behavioral
-- Project Name:
-- Target Devices:
-- Tool versions:
-- Description:
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.MATHREAL.ALL;
use IEEE.NUMERIC_STD.ALL;

```

```

25  -- Uncomment the following library declaration if using
    -- arithmetic functions with Signed or Unsigned values
    --use IEEE.NUMERIC.STD.ALL;

    -- Uncomment the following library declaration if instantiating
    -- any Xilinx primitives in this code.
30  --library UNISIM;
    --use UNISIM.VComponents.all;

entity Shifter is
    generic( N : integer:=16; Namnt : integer :=integer(ceil(log2(real(16)))));
35
    Port ( A : in  STD_LOGIC_VECTOR (N-1 downto 0);
          amnt : in  STD_LOGIC_VECTOR (Namnt-1 downto 0);
          Control : in  STD_LOGIC_VECTOR (3 downto 0);
          output : out  STD_LOGIC_VECTOR (N-1 downto 0));
40 end Shifter;

--1100 LSL
--1101 LSR
45 --1110 ASR
architecture Behavioral of Shifter is
    signal temp : integer;
begin
    proc1 : process(Control,amnt,A)
50     begin
        if control ="1101" then--LSR
            for i in integer range 0 to N-1 loop
                temp<=to_integer(unsigned(amnt));--convert amnt to unsigned integer
            for indexing
                if i+temp > N-1 then--bits at leftmost
55                 output(i) <='0';
                else
                    output(i)<=A(i+temp);--right Shift
                end if;
            end loop;

60         elsif control ="1100" then --LSL
            for i in integer range 0 to N-1 loop
                temp<=to_integer(unsigned(amnt));--convert amnt to unsigned integer
            for indexing
                if i-temp < 0 then --rightmost bits
65                 output(i) <='0';
                else
                    output(i)<=A(i-temp);--left shift
                end if;
            end loop;
70         else --ASR
            for i in integer range 0 to N-1 loop
                temp<=to_integer(unsigned(amnt));--convert amnt to unsigned integer
            for indexing
                if A(N-1)='1' then--negative
                    if i+temp > N-1 then--leftmost bits
75                     output(i) <='1';--preserve the negative sign
                    else
                        output(i)<=A(i+temp);-- Right Shift
                    end if;
                else--Positive

```

```

80         if i+temp > N-1 then --leftmost bits
            output(i) <='0';
        else
            output(i) <= A(i+temp); --right shift
        end if;
85     end if;
    end loop;
end if;
end process;
end Behavioral;

```

Listing 8: TestController VHDL

```

0  --
-- Company:
-- Engineer:
--
-- Create Date:      14:56:40 03/15/2017
5  -- Design Name:
-- Module Name:      Multiplier - Behavioral
-- Project Name:
-- Target Devices:
-- Tool versions:
10 -- Description:
--
-- Dependencies:
--
-- Revision:
15 -- Revision 0.01 - File Created
-- Additional Comments:
--
--
library IEEE;
20 use IEEE.STD_LOGIC_1164.ALL;
use IEEE.numeric_std.all;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
25 --use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
30 --library UNISIM;
--use UNISIM.VComponents.all;

entity TestController is
    generic( N : integer := 32);
35    Port ( clk : in STD_LOGIC;
        StartTest : in STD_LOGIC;
        reset_n : in STD_LOGIC;
        Count : in STD_LOGIC_VECTOR (N-1 downto 0);
        MISR_IN : in STD_LOGIC_VECTOR (N-1 downto 0);
40        Complete : out STD_LOGIC;
        Pass : out STD_LOGIC;
        TestEN : out STD_LOGIC
    );
end TestController;
45

```



```

architecture Datapath of TestController is

    signal complete_v, pass_v : STD_LOGIC;

50 begin

    PassProc : process (clk, reset_n) begin

        if reset_n = '0' then
55             Pass_v <= '0';
        elsif rising_edge(clk) then
            if (count = "00000000000000000000111101000" and MISR_IN = "
10001100100101111000000111100110") or Pass_v = '1' then
                Pass_v <= '1';
            else
60                 Pass_v <= '0';
            end if;
        end if;
    end process;

    CompleteProc : process (clk, reset_n) begin
65         if reset_n = '0' then
            Complete_v <= '0';
        elsif rising_edge(clk) then
            if count = "00000000000000000000111101000" or Complete_v = '1' then
70                 Complete_v <= '1';
            else
                Complete_v <= '0';
            end if;
        end if;
75     end process;

    TestProc : process (clk, reset_n) begin
        if reset_n = '0' then
            TestEN <= '0';
80         elsif rising_edge(clk) then
            if StartTest = '1' then
                TestEN <= '1';
            else
                TestEN <= '0';
85         end if;
        end if;
    end process;

    --Assign outputs
90     Complete <= Complete_v;
    Pass <= Pass_v;

95 end Datapath;

```

Listing 9: Subtractor VHDL

```

-- Company:
-- Engineer:
--

```

```

5  -- Create Date:      10:15:15 03/19/2017
-- Design Name:
-- Module Name:      Subtractor - Behavioral
-- Project Name:
-- Target Devices:
-- Tool versions:
10 -- Description:
--
-- Dependencies:
--
-- Revision:
15 -- Revision 0.01 - File Created
-- Additional Comments:
--

```

```

20 library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

25 -- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

30 entity Subtractor is
    generic(N : integer :=16);
    Port ( A : in  STD_LOGIC_VECTOR (15 downto 0);
          B : in  STD_LOGIC_VECTOR (15 downto 0);
35       Output : out STD_LOGIC_VECTOR (15 downto 0));
end Subtractor;

architecture Behavioral of Subtractor is
--Component Declarations
40 --Adder, to add 1
    component Ripple_Carry_FA is
        generic(N : integer :=16);--Number of bits in A and B
        Port ( A : in  STD_LOGIC_VECTOR (N-1 downto 0);
              B : in  STD_LOGIC_VECTOR (N-1 downto 0);
45         Cin : in STD_LOGIC;
              Sum : out STD_LOGIC_VECTOR (N-1 downto 0);
              Cout : out STD_LOGIC);
    end component;

50 --Logic, for bitwise not
    component Logic_Unit is
        generic( N : integer :=16);
        Port ( A : in  STD_LOGIC_VECTOR (N-1 downto 0);
              B : in  STD_LOGIC_VECTOR (N-1 downto 0);
55         Control : in  STD_LOGIC_VECTOR (3 downto 0);
              output : out STD_LOGIC_VECTOR (N-1 downto 0));
    end component;

--Signal declarations
60 signal logicOut, negative : STD_LOGIC_VECTOR(N-1 downto 0);
signal logicControl : STD_LOGIC_VECTOR(3 downto 0):="1001";--Set to bitwise NOT
signal one : STD_LOGIC_VECTOR(N-1 downto 0) := "0000000000000001";

```

```

signal Cout : STD_LOGIC;—Not used

65 begin
—Convert Input 2 to a negative number
—Bitwise not input2
LOGIC : Logic_Unit
    generic map(N=>N)
70     port map(A=>B, B=>A, Control=>logicControl, output=>logicOut);—A=>B because
    it does bitwise NOT only on A

—Add 1
ADD1 : Ripple_Carry_FA
    generic map(N=>N)
75     port map(A=>logicOut, B=>one, Cin=>'0', Sum=>negative, Cout=>Cout);

—Add the positive A with the newly created negative B
ADD2 : Ripple_Carry_FA
    generic map(N=>N)
80     port map(A=>A, B=>negative, Cin=>'0', Sum=>Output, Cout=>Cout);
—output now has the result of A-B

end Behavioral;

```

Listing 10: Controller VHDL

```

0  —————
—Company      : RIT
—Author       : Brandon Key
—Created      : 03/29/2018
—
5  —Project Name : Lab 5
—File         : Controller.vhd
—
—Entity       : Controller
—Architecture : behav
10 —
—Tool Version : VHDL '93
—Description  : Contoller For BIST
—————

15 library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.numeric_std.all;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

20 entity Controller is
    port(
        start_BIST : in std_logic;

        clk : in std_logic;
25     rst_n : in std_logic;

        is_testing : out std_logic;
        mul_input_ctrl : out std_logic;
        EN_LFSR : out std_logic;
30     rst_n_LFSR : out std_logic;
        EN_MISR : out std_logic;
        rst_n_MISR : out std_logic;
    );

```

```

end Controller;
35
architecture struct of Controller is

    type state_type is (multiply, start_test, testing, test_hold);
    signal state, next_state : state_type := multiply;
40

    signal counter : integer;

    begin

        --update the state to the next_state
        state_proc : process (clk, rst_n) begin
            if rst_n = '0' then
                state <= multiply;
            elsif rising_edge(clk) then
50                state <= next_state;
            end if;
        end process state_proc;

        --How to change the state
65
        next_state_proc : process (clk, rst_n) begin
            if rst_n = '0' then
                next_state <= multiply;
            elsif rising_edge(clk) then
                case (next_state) is
60                    when multiply =>
                        if start_BIST = '1' then
                            next_state <= start_test;
                        else
                            next_state <= multiply;
                        end if;

                        when testing =>
70                            counter <= counter + 1;
                            if counter = 255 then
                                next_state <= test_hold;
                            else
                                next_state <= testing;
                            end if;

                        when start_test =>
75                            next_state <= testing;
                            counter <= 0;
                        when test_hold =>
                            if start_BIST = '1' then
80                                next_state <= test_hold;
                            else
                                next_state <= multiply;
                            end if;
                        when others =>
85                            next_state <= multiply;
                        end case;

                    end if;
                end process next_state_proc;
90

        --Outputs for the states
        out_proc : process (clk) begin

```

```

    if rising_edge(clk) then
        case (state) is
95         when multiply =>
            is_testing <= '0';
            mul_input_ctrl <= '1';
            EN_LFSR <= '0';
            rst_n_LFSR <= '0';
            EN_MISR <= '0';
            rst_n_MISR <= '1';

100         when start_test =>
            is_testing <= '1';
            mul_input_ctrl <= '0';
            EN_LFSR <= '1';
            rst_n_LFSR <= '1';
            EN_MISR <= '0';
            rst_n_MISR <= '0';

105         when testing =>
            is_testing <= '1';
            mul_input_ctrl <= '0';
            EN_LFSR <= '1';
            rst_n_LFSR <= '1';
            EN_MISR <= '1';
            rst_n_MISR <= '1';

110         when test_hold =>
            is_testing <= '0';
            mul_input_ctrl <= '0';
            EN_LFSR <= '0';
            rst_n_LFSR <= '1';
            EN_MISR <= '0';
            rst_n_MISR <= '1';

115         when others =>
            is_testing <= '0';
            mul_input_ctrl <= '1';
            EN_LFSR <= '0';
            rst_n_LFSR <= '0';
            EN_MISR <= '0';
            rst_n_MISR <= '0';

120         end case;
    end if;
125 end process out_proc;

end struct;
130
135

```

Listing 11: ProjectWrapper VHDL

```

0 library IEEE;
  use IEEE.STD_LOGIC_1164.ALL;
  use IEEE.NUMERIC_STD.ALL;

  -- Uncomment the following library declaration if using
  -- arithmetic functions with Signed or Unsigned values
  --use IEEE.NUMERIC_STD.ALL;

  -- Uncomment the following library declaration if instantiating
  -- any Xilinx primitives in this code.
5

```

```

10 --library UNISIM;
--use UNISIM.VComponents.all;

entity ProjectWrapper is
    generic( N : integer := 32);
15 Port ( A : in  STD_LOGIC_VECTOR ((N/2) - 1  downto 0);
        B : in  STD_LOGIC_VECTOR ((N/2) - 1  downto 0);
        clk : in  STD_LOGIC;
        WE : in  STD_LOGIC;
        reset : in  STD_LOGIC;
20 StartTest : in  STD_LOGIC;
        RegOut : out  STD_LOGIC_VECTOR (N-1  downto 0);
        Pass : out  STD_LOGIC;
        Complete : out  STD_LOGIC
    );
25 end ProjectWrapper;

architecture Behavioral of ProjectWrapper is
    --COMPONENT DECLARATIONS
    component MAC is
30         generic( N : integer := 32);
        Port ( A : in  STD_LOGIC_VECTOR ((N/2) - 1  downto 0);
            B : in  STD_LOGIC_VECTOR ((N/2) - 1  downto 0);
            clk : in  STD_LOGIC;
            WE : in  STD_LOGIC;
35            reset : in  STD_LOGIC;
            RegOut : out  STD_LOGIC_VECTOR (N-1  downto 0));
    end component;

    component LFSR_32_4 is
40         generic (N : integer := 32);
        port(
            clk : in  std_logic;
            rst_n : in  std_logic;
            en : in  std_logic;
45            bit_pattern : out  std_logic_vector(N-1  downto 0)
        );
    end component;

    component MISR_32_4 is
50         generic (N : integer := 32);
        port(
            MISR_in : in  std_logic_vector(N-1  downto 0);
            clk : in  std_logic;
            rst_n : in  std_logic;
55            en : in  std_logic;
            MISR_out : out  std_logic_vector(N-1  downto 0)
        );
    end component;

    component nBitMux_2to1 is
60         generic (n : integer := 16);
        port(
            A,B : in  std_logic_vector(n-1  downto 0);
            sel : in  std_logic;
65            Y : out  std_logic_vector(n-1  downto 0)
        );
    end component;

```

```

70 component TestController is
    generic( N : integer := 32);
    Port ( clk : in STD_LOGIC;
          StartTest : in STD_LOGIC;
          reset_n : in STD_LOGIC;
          Count : in STD_LOGIC_VECTOR (N-1 downto 0);
75 MISR_IN : in STD_LOGIC_VECTOR (N-1 downto 0);
          Complete : out STD_LOGIC;
          Pass : out STD_LOGIC;
          TestEN: out STD_LOGIC
        );
80 end component;

component Counter is
    generic( N : integer := 32);
    Port ( clk : in STD_LOGIC;
          TestEN : in STD_LOGIC;
          reset : in STD_LOGIC;
          Count : out STD_LOGIC_VECTOR (N-1 downto 0));
85 end component;

--SIGNAL DECLARATIONS
90 signal MACA, MACB : STD_LOGIC_VECTOR ((N/2) - 1 downto 0);
signal MACOUT : STD_LOGIC_VECTOR (N-1 downto 0);
signal LFSROUT : std_logic_vector(N-1 downto 0);
signal MISR_out, CounterOut : std_logic_vector(N-1 downto 0);
95 signal TestEN : STD_LOGIC;
begin
    --Map those ports
    MAC0 : MAC
        generic map(N => 32)
        port map ( A => MACA, B => MACB,
100          clk => clk, WE => WE, reset => reset,
          RegOut => MACOUT);

    LFSR0 : LFSR_32_4
105     generic map (N => 32)
        port map( clk => clk, rst_n => reset, en => TestEN,
          bit_pattern => LFSROUT);

    MUXA : nBitMux_2to1
110     generic map (N => 16)
        port map (A => A, B => LFSROUT(N-1 downto N/2),
          sel => TestEN, Y => MACA);

    MUXB : nBitMux_2to1
115     generic map (N => 16)
        port map (A => B, B => LFSROUT((N/2) - 1 downto 0),
          sel => TestEN, Y => MACB);

    MISR0 : MISR_32_4
120     generic map(N => 32)
        port map( MISR_in => MACOUT, clk => clk,
          rst_n => reset, en => TestEN,
          MISR_out => MISR_out);

    TEST0 : TestController
125     generic map( N => 32)
        port map(clk => clk, StartTest => StartTest,

```

```

130         reset_n => reset , Count => CounterOut ,
        MISR_IN => MISR_out , Complete => Complete ,
        Pass => Pass , TestEN => TestEN);

COUNT0 : Counter
    generic map( N => 32)
    port map( clk => clk , TestEN => TestEN , reset => reset ,
135         Count => CounterOut);

    RegOut <= MACOUT;

end Behavioral;

```

Listing 12: Counter VHDL

```

0  ---
--- Company:
--- Engineer:
---
--- Create Date:      14:56:40 03/15/2017
5  --- Design Name:
--- Module Name:      Multiplier - Behavioral
--- Project Name:
--- Target Devices:
--- Tool versions:
10 --- Description:
---
--- Dependencies:
---
--- Revision:
15 --- Revision 0.01 - File Created
--- Additional Comments:
---
---
library IEEE;
20 use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

--- Uncomment the following library declaration if using
--- arithmetic functions with Signed or Unsigned values
25 ---use IEEE.NUMERIC_STD.ALL;

--- Uncomment the following library declaration if instantiating
--- any Xilinx primitives in this code.
---library UNISIM;
30 ---use UNISIM.VComponents.all;

entity Counter is
    generic( N : integer := 32);
    Port ( clk : in STD_LOGIC;
35         TestEN : in STD_LOGIC;
        reset : in STD_LOGIC;
        Count : out STD_LOGIC_VECTOR (N-1 downto 0));
end Counter;

40 architecture Behavioral of Counter is
    ---COMPONENT DECLARATIONS

```



```

45 component nBitAdder is
    generic (n : integer := 32);
    port(
        A,B : in  std_logic_vector(N-1 downto 0);
        Y   : out std_logic_vector(N-1 downto 0);
        CB  : out std_logic
50    );
end component;

component nBitRegister_32 is
    generic (n : integer := 32);
55    Port (
        nBitIn : in std_logic_vector(n-1 downto 0); -- n bits to store in the
register
        WE      : in std_logic; -- Active high write enable
        Reset   : in std_logic; -- Async reset , disabled when low
        clk     : in std_logic;
60        Y : out std_logic_vector(n-1 downto 0) -- 1 output , n bits wide
    );
end component;

--SIGNAL DECLARATIONS
65 signal RegOut, RegIn : STDLOGIC.VECTOR(N-1 downto 0);
signal cout : STDLOGIC;

begin

70 --16 bit adder, always adds 1 to value in register
ADDER0 : nBitAdder
    generic map(N => 32)
    port map(A => RegOut, B => "00000000000000000000000000000001", Y => RegIn,
CB => cout);

75 --Holds the current counter value
REG0 : nBitRegister_32
    generic map(N => 32)
    port map(nBitIn => RegIn, clk => clk, WE => TestEN, Reset => reset, Y =>
RegOut);

80 --Map output
Count <= RegOut;

end Behavioral;

```

Listing 13: BIST tb VHDL

```

0 --Company      : RIT
--Author       : Brandon Key
--Created      : 03/29/2018
--
5 --Project Name : Lab 5
--File         : BIST_tb.vhd
--
--Entity       : BIST_tb
--Architecture : behav
10 --
--Tool Version : VHDL '93
--Description  : BIST

```

```

LIBRARY ieee;
15 USE ieee.std_logic_1164.ALL;
   use ieee.numeric_std.all;

   -- Uncomment the following library declaration if using
   -- arithmetic functions with Signed or Unsigned values
20 --USE ieee.numeric_std.ALL;

ENTITY BIST_tb IS
END BIST_tb;

25 ARCHITECTURE behavior OF BIST_tb IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT Wrapper
30     PORT(
        mul_input : IN  std_logic_vector(7 downto 0);
        start_BIST : IN  std_logic;
        disp_Sig : IN  std_logic;
        clk : IN  std_logic;
35        rst_n : IN  std_logic;
        unused_anode : OUT std_logic;
        hund_anode : OUT std_logic;
        tens_anode : OUT std_logic;
        ones_anode : OUT std_logic;
40        CAn : OUT std_logic;
        CBn : OUT std_logic;
        CCn : OUT std_logic;
        CDn : OUT std_logic;
        CEn : OUT std_logic;
45        CFn : OUT std_logic;
        CGn : OUT std_logic;
        is_Testing : OUT std_logic;
        mul_disp : OUT std_logic_vector(7 downto 0);
        sig_disp : OUT std_logic_vector(7 downto 0)
50    );
    END COMPONENT;

    --Inputs
55    signal mul_input : std_logic_vector(7 downto 0) := (others => '0');
    signal start_BIST : std_logic := '0';
    signal disp_Sig : std_logic := '0';
    signal clk : std_logic := '0';
    signal rst_n : std_logic := '0';

60    --Outputs
    signal unused_anode : std_logic;
    signal hund_anode : std_logic;
    signal tens_anode : std_logic;
65    signal ones_anode : std_logic;
    signal CAn : std_logic;
    signal CBn : std_logic;
    signal CCn : std_logic;
    signal CDn : std_logic;
70    signal CEn : std_logic;
    signal CFn : std_logic;

```

```

signal CGn : std_logic;
signal is_Testing : std_logic;
signal mul_disp : std_logic_vector(7 downto 0);
75 signal sig_disp : std_logic_vector(7 downto 0);

-- Clock period definitions
constant clk_period : time := 10 ns;

80 BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: Wrapper PORT MAP (
        mul_input => mul_input,
        start_BIST => start_BIST,
85         disp_Sig => disp_Sig,
        clk => clk,
        rst_n => rst_n,
        unused_anode => unused_anode,
        hund_anode => hund_anode,
90         tens_anode => tens_anode,
        ones_anode => ones_anode,
        CAn => CAn,
        CBn => CBn,
95         CCn => CCn,
        CDn => CDn,
        CEn => CEn,
        CFn => CFn,
        CGn => CGn,
100        is_Testing => is_Testing,
        mul_disp => mul_disp,
        sig_disp => sig_disp
    );

105 -- Clock process definitions
    clk_process : process
    begin
        clk <= '0';
        wait for clk_period/2;
110        clk <= '1';
        wait for clk_period/2;
    end process;

115 -- Stimulus process
    stim_proc: process
    begin
        -- hold reset state for 100 ns.
        rst_n <= '0';
120        wait for 100 ns;
        rst_n <= '1';
        wait for clk_period*3;
        -- insert stimulus here

125        start_BIST <= '1';
        wait for clk_period*10;
        start_BIST <= '0';
        wait for clk_period*30;

130        for i in 0 to 5 loop

```

```

    start_BIST <= '1';
    mul_input <= std_logic_vector(to_unsigned(i, mul_input'length));
    wait for clk_period*2;
    start_BIST <= '0';
    wait for clk_period*2;
135 end loop;

    wait for clk_period*270;

140 start_BIST <= '1';
    wait for clk_period*300;
    start_BIST <= '0';
    wait for clk_period*10;

145 wait;
end process;

END;

```

Listing 14: Multiplier VHDL

```

0  --- Company:
    --- Engineer:
    ---
    --- Create Date:      14:56:40 03/15/2017
5  --- Design Name:
    --- Module Name:      Multiplier - Behavioral
    --- Project Name:
    --- Target Devices:
    --- Tool versions:
10  --- Description:
    ---
    --- Dependencies:
    ---
    --- Revision:
15  --- Revision 0.01 - File Created
    --- Additional Comments:
    ---

20 library IEEE;
    use IEEE.STD_LOGIC_1164.ALL;
    use IEEE.NUMERIC_STD.ALL;

    --- Uncomment the following library declaration if using
    --- arithmetic functions with Signed or Unsigned values
25  ---use IEEE.NUMERIC_STD.ALL;

    --- Uncomment the following library declaration if instantiating
    --- any Xilinx primitives in this code.
    ---library UNISIM;
30  ---use UNISIM.VComponents.all;

    entity Multiplier is
        generic( N : integer :=32);
        Port ( A : in  STD_LOGIC_VECTOR ((N/2)-1 downto 0);
35          B : in  STD_LOGIC_VECTOR ((N/2)-1 downto 0);
            Product : out STD_LOGIC_VECTOR (N-1 downto 0));
    end Multiplier;

```

```

architecture Behavioral of Multiplier is
40  --COMPONENT DECLARATIONS
  component ANDADD is
    Port ( A : in  STD_LOGIC;
           B : in  STD_LOGIC;
           D : in  STD_LOGIC;
45           Cin : in  STD_LOGIC;
           Sum : out STD_LOGIC;
           Cout : out STD_LOGIC);
  end component;

  component AND2 is
50    Port ( A : in  STD_LOGIC;
           B : in  STD_LOGIC;
           F : out  STD_LOGIC);
  end component;
55  --SIGNAL DECLARATIONS
  signal Cin : STD_LOGIC := '0';
  signal Cout : STD_LOGIC := '0';
  signal F : STD_LOGIC_VECTOR(N*N downto 0); --interconnections within multiplier
  between adders and AND gates
  signal CoutArray : STD_LOGIC_VECTOR(N*N downto 0); --Signals used by the Cout
  between the 1 bit full adders
60 begin

  forrow : for i in integer range 0 to (N/2)-1 generate --Loop down the levels
    if0 : if i = 0 generate --top level, just AND gates
65      ANDOGEN : for j in integer range 0 to (N/2)-1 generate
        AND0 : AND2
          port map(A=>A(i), B=>B(j), F=>F(j));
        end generate ANDOGEN;
        Product(0)<=F(0); --Assign first product
70      end generate if0;
      ifn0 : if i>0 generate --everything else
        forcol : for j in integer range 0 to (N/2)-1 generate

          --Generate the first full adder / and gate combo of the row
75          GEN0 : if j = 0 generate
            ANDADD0 : ANDADD
              port map(A=>A(i), B=>B(j), D=>F((N/2)*(i-1)+(j+1)), Cin=>
Cin, Cout=>CoutArray((N/2)*i+j), Sum=>F((N/2)*i+j)); --Tons of 2D arrays as 1D
arrays
              --D=>The sum of the full adder in the previous row and
next column (i-1) (j+1).
              --Cout=>Corresponding coordinate in CoutArray for this
full adder [i,j].
80              --Sum=> Corresponding coordinate in F array for this
full adder [i,j].

              --Assign the sum of the first adder of the row to its
respective product bit
              Product(i)<=F((N/2)*i+j);
            end generate GEN0;
85          --Last full adder of the first row, D has to be 0
          GEN1N : if i=1 AND j=((N/2)-1) generate
            ANDADD1N : ANDADD

```

```

port map(A=>A(i), B=>B(j), D=>Cin, Cin=>CoutArray((N/2)*i+(
j-1)), Cout=>CoutArray((N/2)*i+j), Sum=>F((N/2)*i+j));
--D=>Cin, which is equal to 0
--Cin=>Cout of previous full adder in same row (j-1)
--Cout=>Corresponding coordinate in CoutArray for
this full adder [i,j].
--Sum=> Corresponding coordinate in F array for this
full adder [i,j].
end generate GENIN;

--Generate the last full adder / and gate combo of the row
GENN : if i/=1 AND j= ((N/2)-1) generate
ANDADDN : ANDADD
port map(A=>A(i), B=>B(j), D=>CoutArray((N/2)*(i-1)+j), Cin
=>CoutArray((N/2)*i+(j-1)), Cout=>CoutArray((N/2)*i+j), Sum=>F((N/2)*i+j)); --Map
the last full adder in line
--D=>The Cout of the last full adder of the previous
row (i-1)
--Cin=>Cout of previous full adder in same row (j-1)
--Cout=>Corresponding coordinate in CoutArray for
this full adder [i,j].
--Sum=> Corresponding coordinate in F array for this
full adder [i,j].

--Assign Sum and Cout to Product of the last row's last full
adder
GENNI : if i=(N/2)-1 generate
Product(N-1)<=CoutArray((N/2)*i+j); --Product bit from
Cout
Product(i+j)<=F((N/2)*i+j); --Product bit from Sum
end generate GENNI;
end generate GENN;

--Generate all the other full adders / AND gate combos
GENX : if j/=((N/2)-1) AND j>0 generate
ANDADDX : ANDADD
port map(A=>A(i), B=>B(j), D=>F((N/2)*(i-1)+(j+1)), Cin
=>CoutArray((N/2)*i+(j-1)), Cout=>CoutArray((N/2)*i+j), Sum=>F((N/2)*i+j));
--D=>The Cout of the last full adder of the previous
row (i-1)
--Cin=>Cout of previous full adder in same row (j-1)
--Cout=>Corresponding coordinate in CoutArray for
this full adder [i,j].
--Sum=> Corresponding coordinate in F array for this
full adder [i,j].

--Assign Product bits the sum bits of the last row of full
adders
GENXI : if i=((N/2)-1) generate
Product(i+j)<=F((N/2)*i+j); --Assign the sum to the
respective product bit
end generate GENXI;

end generate GENX;

end generate forcol;

```

```

        end generate ifn0;
        end generate forrow;
135 end Behavioral;

```

Listing 15: LFSR 32 4 VHDL

```

0  -----
1  --Company       : RIT
2  --Author        : Brandon Key
3  --Created       : 03/08/2018
4  --
5  --Project Name  : Lab 5
6  --File          : LFSR_32_4.vhd
7  --
8  --Entity        : LFSR_32_4
9  --Architecture  : behav
10 --
11 --Tool Version  : VHDL '93
12 --Description   : LFSR_32_4 8 bit output, 4 tap LFSR.
13 -----
14
15 library IEEE;
16 use IEEE.STD_LOGIC_1164.ALL;
17 use IEEE.numeric_std.all;
18 use IEEE.STD_LOGIC_UNSIGNED.ALL;
19
20 entity LFSR_32_4 is
21     generic (N : integer := 32);
22     port(
23         clk      : in std_logic;
24         rst_n    : in std_logic;
25         en       : in std_logic;
26         bit_pattern : out std_logic_vector(N-1 downto 0)
27     );
28 end LFSR_32_4;
29
30 architecture behav of LFSR_32_4 is
31
32     signal internal_reg : std_logic_vector(N-1 downto 0);
33
34     constant SEED : std_logic_vector(N-1 downto 0) := x"12345678";
35
36     begin
37
38         bit_pattern <= internal_reg;
39
40         --update the state to the next state
41         the_proc : process (clk, rst_n) begin
42             if rst_n = '0' then
43                 internal_reg <= SEED;
44             elsif rising_edge(clk) then
45                 if en = '1' then
46                     --taps at 32,20,26,25
47                     internal_reg(0) <= internal_reg(1);
48                     internal_reg(1) <= internal_reg(2);
49                     internal_reg(2) <= internal_reg(3);
50                     internal_reg(3) <= internal_reg(4);

```

```

55         internal_reg(4) <= internal_reg(5);
           internal_reg(5) <= internal_reg(6);
           internal_reg(6) <= internal_reg(7);
           internal_reg(7) <= internal_reg(8);
           internal_reg(8) <= internal_reg(9);
           internal_reg(9) <= internal_reg(10);
           internal_reg(10) <= internal_reg(11);
           internal_reg(11) <= internal_reg(12);
           internal_reg(12) <= internal_reg(13);
60         internal_reg(13) <= internal_reg(14);
           internal_reg(14) <= internal_reg(15);
           internal_reg(15) <= internal_reg(16);
           internal_reg(16) <= internal_reg(17);
           internal_reg(17) <= internal_reg(18);
65         internal_reg(18) <= internal_reg(19);
           internal_reg(19) <= internal_reg(20) xor internal_reg(0);
           internal_reg(20) <= internal_reg(21);
           internal_reg(21) <= internal_reg(22);
           internal_reg(22) <= internal_reg(23);
70         internal_reg(23) <= internal_reg(24);
           internal_reg(24) <= internal_reg(25) xor internal_reg(0);
           internal_reg(25) <= internal_reg(26) xor internal_reg(0);
           internal_reg(26) <= internal_reg(27);
           internal_reg(27) <= internal_reg(28);
75         internal_reg(28) <= internal_reg(29);
           internal_reg(29) <= internal_reg(30);
           internal_reg(30) <= internal_reg(31);
           internal_reg(31) <= internal_reg(0);

80         end if;
           end if;
           end process the_proc;

85 end   behav;

```

Listing 16: LFSR 8 4 VHDL

```

0  -----
   --Company       : RIT
   --Author        : Brandon Key
   --Created       : 03/08/2018
   --
5  --Project Name  : Lab 5
   --File         : LFSR_8_4.vhd
   --
   --Entity        : LFSR_8_4
   --Architecture  : behav
10  --
   --Tool Version  : VHDL '93
   --Description   : LFSR_8_4 8 bit output , 4 tap LFSR.
   -----

15 library IEEE;
   use IEEE.STD_LOGIC_1164.ALL;
   use IEEE.numeric_std.all;
   use IEEE.STD_LOGIC_UNSIGNED.ALL;

20 entity LFSR_8_4 is

```



```

    port(
        clk      : in  std_logic;
        rst_n    : in  std_logic;
        en       : in  std_logic;
25      bit_pattern : out std_logic_vector(7 downto 0)
    );
end LFSR_8-4;

architecture behav of LFSR_8-4 is
30
    signal internal_reg : std_logic_vector(7 downto 0);

    constant SEED : std_logic_vector(7 downto 0) := x"6A";

35
begin

    bit_pattern <= internal_reg;

    --update the state to the next_state
40    the_proc : process (clk, rst_n) begin
        if rst_n = '0' then
            internal_reg <= SEED;
        elsif rising_edge(clk) then
            if en = '1' then
45                --taps at 7,5,4,3
                internal_reg(0) <= internal_reg(1);
                internal_reg(1) <= internal_reg(2);
                internal_reg(2) <= internal_reg(3);
                internal_reg(3) <= internal_reg(4) xor internal_reg(0);
50                internal_reg(4) <= internal_reg(5) xor internal_reg(0);
                internal_reg(5) <= internal_reg(6) xor internal_reg(0);
                internal_reg(6) <= internal_reg(7);
                internal_reg(7) <= internal_reg(0);

                end if;
55            end if;
        end process the_proc;

end behav;

```

Listing 17: MAC VHDL

```

0  -- Company:
   -- Engineer:
   --
   -- Create Date:      14:56:40 03/15/2017
5  -- Design Name:
   -- Module Name:      Multiplier - Behavioral
   -- Project Name:
   -- Target Devices:
   -- Tool versions:
10 -- Description:
   --
   -- Dependencies:
   --
   -- Revision:
15 -- Revision 0.01 - File Created
   -- Additional Comments:

```

```

--
library IEEE;
20 use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
25 --use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
30 --use UNISIM.VComponents.all;

entity MAC is
    generic( N : integer := 32);
    Port ( A : in  STD_LOGIC_VECTOR ((N/2) - 1  downto 0);
35         B : in  STD_LOGIC_VECTOR ((N/2) - 1  downto 0);
        clk : in  STD_LOGIC;
        WE : in  STD_LOGIC;
        reset : in  STD_LOGIC;
        RegOut : out  STD_LOGIC_VECTOR (N-1  downto 0));
40 end MAC;

architecture Behavioral of MAC is
    --COMPONENT DECLARATIONS
    component Multiplier is
45         generic( N : integer := 32);
        Port ( A : in  STD_LOGIC_VECTOR ((N/2)-1  downto 0);
                B : in  STD_LOGIC_VECTOR ((N/2)-1  downto 0);
                Product : out  STD_LOGIC_VECTOR (N-1  downto 0));
    end component;

    component nBitAdder is
50         generic (n : integer := 32);
        port(
            A,B : in  std_logic_vector(N-1  downto 0);
55             Y : out std_logic_vector(N-1  downto 0);
            CB : out std_logic
        );
    end component;

    component nBitRegister is
60         generic (n : integer := 32);
        Port (
            nBitIn : in std_logic_vector(n-1  downto 0); -- n bits to store in the
            register
            WE : in std_logic; -- Active high write enable
65             Reset : in std_logic; -- Async reset , disabled when low
            clk : in std_logic;
            Y : out std_logic_vector(n-1  downto 0) -- 1 output , n bits wide
        );
    end component;

    component nBitRegister_32 is
70         generic (n : integer := 32);
        Port (
            nBitIn : in std_logic_vector(n-1  downto 0); -- n bits to store in the

```

```

75   register
      WE      : in std_logic; -- Active high write enable
      Reset   : in std_logic; -- Async reset, disabled when low
      clk     : in std_logic;
      Y : out std_logic_vector(n-1 downto 0) -- 1 output, n bits wide
    );
80   end component;

   component nBitRegister_16 is
      generic (n : integer := 16);
      Port (
85         nBitIn : in std_logic_vector(n-1 downto 0); -- n bits to store in the
   register
      WE      : in std_logic; -- Active high write enable
      Reset   : in std_logic; -- Async reset, disabled when low
      clk     : in std_logic;
      Y : out std_logic_vector(n-1 downto 0) -- 1 output, n bits wide
90     );
   end component;

   --SIGNAL DECLARATIONS
   signal MultA, MultB : STD_LOGIC_VECTOR((N/2)-1 downto 0);
95   signal Product : STD_LOGIC_VECTOR(N-1 downto 0);
   signal adderA, adderB, adderOut : STD_LOGIC_VECTOR(N-1 downto 0);
   signal cout : STD_LOGIC;

begin
100   RegMultInA : nBitRegister_16
      generic map( N => 16)
      port map(nBitIn => A,
105         WE => '1', clk => clk, Reset => reset,
         Y => MultA
      );

   RegMultInB : nBitRegister_16
      generic map( N => 16)
110   port map(nBitIn => B,
         WE => '1', clk => clk, Reset => reset,
         Y => MultB
      );

115   MULT1 : Multiplier
      generic map( N => 32)
      port map(A => MultA, B => MultB, Product => Product);

   RegMultOut : nBitRegister_32
120   generic map( N => 32)
      port map(nBitIn => Product, WE => '1', Reset => reset, clk => clk, Y =>
      adderB);

   BigBoyReg : nBitRegister_32
      generic map( N => 32)
125   port map(nBitIn => adderOut, WE => WE, Reset => reset, clk => clk, Y =>
      adderA);

   ADD1 : nBitAdder
      generic map ( N => 32)
      port map( A => adderA, B => adderB, Y => adderOut, CB => cout);

```

```

130      RegOut <= adderA;
end Behavioral;

```

Listing 18: MISR 32 4 VHDL

```

0  -----
--Company      : RIT
--Author       : Brandon Key
--Created      : 03/08/2018
--
5  --Project Name : Lab 5
--File         : MISR_32_4.vhd
--
--Entity       : MISR_32_4
--Architecture : behav
10 -----
--Tool Version : VHDL '93
--Description  : MISR_32_4 32 bit output, 4 tap MISR.
-----

15 library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.numeric_std.all;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

20 entity MISR_32_4 is
    generic (N : integer := 32);
    port(
        MISR_in : in std_logic_vector(N-1 downto 0);
        clk     : in std_logic;
25        rst_n  : in std_logic;
        en      : in std_logic;
        MISR_out : out std_logic_vector(N-1 downto 0)
    );
end MISR_32_4;

30 architecture behav of MISR_32_4 is

    signal internal_reg : std_logic_vector(N-1 downto 0);

35    constant SEED : std_logic_vector(N-1 downto 0) := x"12345678";

    begin

        MISR_out <= internal_reg;

40        --update the state to the next state
        the_proc : process (clk, rst_n) begin
            if rst_n = '0' then
                internal_reg <= SEED;
            elsif rising_edge(clk) then
45                if en = '1' then
                    --taps at 32,20,26,25
                    internal_reg(0) <= internal_reg(1) xor MISR_in(0);
                    internal_reg(1) <= internal_reg(2) xor MISR_in(1);
50                    internal_reg(2) <= internal_reg(3) xor MISR_in(2);
                    internal_reg(3) <= internal_reg(4) xor MISR_in(3);
                    internal_reg(4) <= internal_reg(5) xor MISR_in(4);

```

```

55         internal_reg(5) <= internal_reg(6) xor MISR_in(5);
        internal_reg(6) <= internal_reg(7) xor MISR_in(6);
        internal_reg(7) <= internal_reg(8) xor MISR_in(7);
        internal_reg(8) <= internal_reg(9) xor MISR_in(8);
        internal_reg(9) <= internal_reg(10) xor MISR_in(9);
        internal_reg(10) <= internal_reg(11) xor MISR_in(10);
        internal_reg(11) <= internal_reg(12) xor MISR_in(11);
60         internal_reg(12) <= internal_reg(13) xor MISR_in(12);
        internal_reg(13) <= internal_reg(14) xor MISR_in(13);
        internal_reg(14) <= internal_reg(15) xor MISR_in(14);
        internal_reg(15) <= internal_reg(16) xor MISR_in(15);
        internal_reg(16) <= internal_reg(17) xor MISR_in(16);
65         internal_reg(17) <= internal_reg(18) xor MISR_in(17);
        internal_reg(18) <= internal_reg(19) xor MISR_in(18);
        internal_reg(19) <= internal_reg(20) xor MISR_in(19) xor
        internal_reg(0);
        internal_reg(20) <= internal_reg(21) xor MISR_in(20);
70         internal_reg(21) <= internal_reg(22) xor MISR_in(21);
        internal_reg(22) <= internal_reg(23) xor MISR_in(22);
        internal_reg(23) <= internal_reg(24) xor MISR_in(23);
        internal_reg(24) <= internal_reg(25) xor MISR_in(24) xor
        internal_reg(0);
        internal_reg(25) <= internal_reg(26) xor MISR_in(25) xor
        internal_reg(0);
75         internal_reg(26) <= internal_reg(27) xor MISR_in(26);
        internal_reg(27) <= internal_reg(28) xor MISR_in(27);
        internal_reg(28) <= internal_reg(29) xor MISR_in(28);
        internal_reg(29) <= internal_reg(30) xor MISR_in(29);
        internal_reg(30) <= internal_reg(31) xor MISR_in(30);
        internal_reg(31) <= internal_reg(0) xor MISR_in(31);
80         end if;
        end if;
        end process the_proc;

85 end behav;

```

Listing 19: nBitRegister tb VHDL

```

0  ---
--- Company:
--- Engineer:
---
--- Create Date:    16:49:10 02/08/2018
5  --- Design Name:
--- Module Name:    /home/ise/DSDII/Lab/Lab2/Project/lab2/nBitRegister_tb.vhd
--- Project Name:   lab2
--- Target Device:
--- Tool versions:
10 --- Description:
---
--- VHDL Test Bench Created by ISE for module: nBitRegister
---
--- Dependencies:
15 ---
--- Revision:
--- Revision 0.01 -- File Created
--- Additional Comments:
---

```

```

20  -- Notes:
-- This testbench has been automatically generated using types std_logic and
-- std_logic_vector for the ports of the unit under test.  Xilinx recommends
-- that these types always be used for the top-level I/O of a design in order
-- to guarantee that the testbench will bind correctly to the post-implementation
25  -- simulation model.

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
use ieee.numeric_std.all;

30  -- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--USE ieee.numeric_std.ALL;

35  ENTITY nBitRegister_tb IS
END nBitRegister_tb;

ARCHITECTURE behavior OF nBitRegister_tb IS

40      constant N : integer := 4;

-- Component Declaration for the Unit Under Test (UUT)

COMPONENT nBitRegister
45  generic (n : integer := 32);
PORT(
    nBitIn : in std_logic_vector(n-1 downto 0); -- n bits to store in the
    register
    WE      : in std_logic; -- Active high write enable
    Reset   : in std_logic; -- Async reset, disabled when low
50    clk    : in std_logic;
    Y : out std_logic_vector(n-1 downto 0) -- 1 output, n bits wide
);
END COMPONENT;

55  --Inputs
signal nBitIn : std_logic_vector(n-1 downto 0) := (others => '0');
signal WE : std_logic := '0';
signal Reset : std_logic := '0';
60  signal clk : std_logic := '0';

--Outputs
signal Y : std_logic_vector(n-1 downto 0);

65  -- Clock period definitions
constant clk_period : time := 100 ns;

BEGIN

70  -- Instantiate the Unit Under Test (UUT)
ut: nBitRegister
generic map (N => N)
PORT MAP (
    nBitIn => nBitIn,
75    WE => WE,
    Reset => Reset,
    clk => clk,

```

```

        Y => Y
    );

80  -- Clock process definitions
    clk_process : process
    begin
        clk <= '0';
85      wait for clk_period/2;
        clk <= '1';
        wait for clk_period/2;
    end process;

90  -- Stimulus process
    stim_proc: process
    begin
        -- hold reset state for 100 ns.
95      Reset <= '0';
        wait for (1*clk_period + 15 ns);
        Reset <= '1';
        wait for clk_period*1;
        --Setup Complete, Time to load

100     --Load each register 1 by 1
        WE <= '1';
        wait for clk_period;
        nBitIn <= x"D";
105      wait for clk_period;
        WE <= '0';
        nBitIn <= x"E";
        wait for clk_period;

110      WE <= '1';
        wait for clk_period;
        for i in 0 to 15 loop
            nBitIn <= std_logic_vector(to_unsigned(i, nBitIn'length));
            wait for clk_period*1;
115      end loop;

        wait;
    end process;

120 END;

```

Listing 20: nBitAdder VHDL

```

0  --Company      : RIT
   --Author       : Brandon Key
   --Created      : 02/18/2018
   --
5  --Project Name : Lab 3
   --File         : nBitAdder.vhd
   --
   --Entity       : nBitAdder
   --Architecture : struct
10 --
   --Tool Version : VHDL '93
   --Description  : Entity and structural description of an adder subtractor

```

```

--          : SEL = 0 : A+B = Y
--          : SEL = 1 : A-B = Y
15
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.numeric_std.all;
20 use work.globals.all;

entity nBitAdder is
    generic (n : integer := 32);
    port(
25     A,B : in  std_logic_vector(n-1 downto 0);
        Y  : out std_logic_vector(n-1 downto 0);
        CB : out std_logic
    );
end nBitAdder;
30

architecture struct of nBitAdder is

    component full_adder is
        port(A,B,Cin : in  std_logic;
35         Sum,Cout : out std_logic
        );
    end component full_adder;

    --Create an array to hold all of the carries
40    type carry_array is array (n-1 downto 0) of std_logic;
    signal c_array : carry_array;

begin

45
    generate_adders : for i in 0 to n-1 generate
        i_first: if i = 0 generate
            --The first adder gets SEL as the Cin
            adder : full_adder port map(
50             A => A(i),
             B => B(i),
             Cin => '0',
             Sum => Y(i),
             Cout => c_array(i)
55         );
        end generate i_first;

        i_last : if i = (n-1) generate
            --The last adder doesn't have a carry out
60         adder : full_adder port map(
             A => A(i),
             B => B(i),
             Cin => c_array(i-1),
             Sum => Y(i),
65             Cout => c_array(i)
            );
        end generate i_last;

        --Middle adders
70        i_mid : if (i /= 0) and (i /= (n-1)) generate
            adder : full_adder port map(

```



```

75         A => A(i),
           B => B(i),
           Cin => c_array(i-1),
           Sum => Y(i),
           Cout => c_array(i)
       );
       end generate i_mid;

80   end generate generate_adders;

       CB <= c_array(n-1);

end   struct;

```

Listing 21: nBitRegister 16 VHDL

```

0  -----
   --Company       : RIT
   --Author        : Brandon Key
   --Created       : 2/8/2017
   --
5  --Project Name  : Lab 2
   --File          : nBitRegister_16.vhd
   --
   --Entity        : nBitRegister_16
   --Architecture  : struct
10  --Revision     :
   --Rev 0.01      : 2/8/2017
   --
   --Tool Version  : VHDL '93
   --Description   : Entity and behavioral description of an n-bit register
15  --Notes        :
   -----

library ieee;
20 use ieee.std_logic_1164.all;

entity nBitRegister_16 is
   generic (n : integer := 16);
25   Port (
       nBitIn : in std_logic_vector(n-1 downto 0); -- n bits to store in the
       register
       WE      : in std_logic; -- Active high write enable
       Reset   : in std_logic; -- Async reset, disabled when low
       clk     : in std_logic;
30       Y : out std_logic_vector(n-1 downto 0) -- 1 output, n bits wide
   );
end nBitRegister_16;

35 architecture behav of nBitRegister_16 is

begin

40   output_proc : process (clk, Reset) begin

```

```

    if Reset = '0' then
        Y <= (others => '0');
    elsif clk'event and clk = '1' then
        if WE = '1' then
            Y <= nBitIn;
        end if;
    end if;

end process output_proc;

end behav;

```

Listing 22: MISR 8 4 VHDL

```

0  ---Company      : RIT
   ---Author       : Brandon Key
   ---Created      : 03/08/2018
   ---
5  ---Project Name : Lab 5
   ---File         : MISR_8_4.vhd
   ---
   ---Entity       : MISR_8_4
   ---Architecture : behav
10 ---
   ---Tool Version : VHDL '93
   ---Description  : MISR_8_4 8 bit output, 4 tap MISR.
   ---

15 library IEEE;
   use IEEE.STD_LOGIC_1164.ALL;
   use IEEE.numeric_std.all;
   use IEEE.STD_LOGIC_UNSIGNED.ALL;

20 entity MISR_8_4 is
   port(
       MISR_in : in std_logic_vector(7 downto 0);
       clk      : in std_logic;
       rst_n    : in std_logic;
25      en      : in std_logic;
       MISR_out : out std_logic_vector(7 downto 0)
   );
end MISR_8_4;

30 architecture behav of MISR_8_4 is

   signal internal_reg : std_logic_vector(7 downto 0);

   constant SEED : std_logic_vector(7 downto 0) := x"6A";
35
   begin

       MISR_out <= internal_reg;

40      ---update the state to the next_state
       the_proc : process (clk, rst_n) begin
           if rst_n = '0' then

```

```

        internal_reg <= SEED;
    elsif rising_edge(clk) then
        if en = '1' then
            --taps at 7,5,4,3
            internal_reg(0) <= internal_reg(1) xor MISR_in(0);
            internal_reg(1) <= internal_reg(2) xor MISR_in(1);
            internal_reg(2) <= internal_reg(3) xor MISR_in(2);
            internal_reg(3) <= internal_reg(4) xor MISR_in(3) xor
internal_reg(0);
            internal_reg(4) <= internal_reg(5) xor MISR_in(4) xor
internal_reg(0);
            internal_reg(5) <= internal_reg(6) xor MISR_in(5) xor
internal_reg(0);
            internal_reg(6) <= internal_reg(7) xor MISR_in(6);
            internal_reg(7) <= internal_reg(0) xor MISR_in(7);
        end if;
    end if;
end process the_proc;

end behav;

```

Listing 23: nBitMux 2to1 VHDL

```

--Company      : RIT
--Author       : Brandon Key
--Created      : 3/29/2018
--
--Project Name : Lab 5
--File         : nBitMux_2to1.vhd
--
--Entity       : nBitMux_2to1
--Architecture : Dataflow
--
--Tool Version : VHDL '93
--Description  : Arbitrary width 2 to 1 mux

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity nBitMux_2to1 is
    generic (n : integer := 16);
    port (
        A,B : in  std_logic_vector(n-1 downto 0);
        sel : in  std_logic;
        Y   : out std_logic_vector(n-1 downto 0)
    );
end nBitMux_2to1;

architecture Dataflow of nBitMux_2to1 is
    begin
        --update the state to the next_state
        the_proc : process (sel, A, B) begin
            case sel is
                when '0' =>
                    Y <= A;

```

```

35         when others =>
            Y <= B;
        end case;
    end process the_proc;

40 end Dataflow;

```

Listing 24: ANDADD VHDL

```

0  -- Company:
1  -- Engineer:
2  --
3  -- Create Date:    15:25:28 03/15/2017
4  -- Design Name:
5  -- Module Name:    ANDADD - Behavioral
6  -- Project Name:
7  -- Target Devices:
8  -- Tool versions:
9  -- Description:
10 --
11 -- Dependencies:
12 --
13 -- Revision:
14 -- Revision 0.01 - File Created
15 -- Additional Comments:
16 --
17
18
19
20 library IEEE;
21 use IEEE.STD_LOGIC_1164.ALL;
22
23 -- Uncomment the following library declaration if using
24 -- arithmetic functions with Signed or Unsigned values
25 --use IEEE.NUMERIC_STD.ALL;
26
27 -- Uncomment the following library declaration if instantiating
28 -- any Xilinx primitives in this code.
29 --library UNISIM;
30 --use UNISIM.VComponents.all;
31
32 entity ANDADD is
33     Port ( A : in  STD_LOGIC;
34           B : in  STD_LOGIC;
35           D : in  STD_LOGIC;
36           Cin : in  STD_LOGIC;
37           Sum : out STD_LOGIC;
38           Cout : out STD_LOGIC);
39 end ANDADD;
40
41 architecture Behavioral of ANDADD is
42
43     --Component Declarations
44     component AND2 is
45         Port ( A : in  STD_LOGIC;
46               B : in  STD_LOGIC;
47               F : out  STD_LOGIC);
48     end component;
49
50     component FA_1bit is

```

```

50      Port ( A : in  STD_LOGIC;
           B : in  STD_LOGIC;
           Cin : in  STD_LOGIC;
           S : out  STD_LOGIC;
           Cout : out  STD_LOGIC);
55  end component;

  --Signal Assignments
  signal F : STD_LOGIC;
begin
60  AND0 : AND2
      port map(A=>A, B=>B,F=>F);

  FA : FA_1bit
65  port map(A=>F, B=>D, Cin=>Cin, S=>Sum, Cout=>Cout);

end Behavioral;

```

Listing 25: Ripple Carry FA VHDL

```

0  -- Company:
  -- Engineer:
  --
  -- Create Date:      08:27:52 03/02/2017
5  -- Design Name:
  -- Module Name:      Ripple_Carry_FA - Behavioral
  -- Project Name:
  -- Target Devices:
  -- Tool versions:
10  -- Description:
  --
  -- Dependencies:
  --
  -- Revision:
15  -- Revision 0.01 - File Created
  -- Additional Comments:
  --
20  library IEEE;
  use IEEE.STD_LOGIC_1164.ALL;

  -- Uncomment the following library declaration if using
  -- arithmetic functions with Signed or Unsigned values
  --use IEEE.NUMERIC_STD.ALL;
25  -- Uncomment the following library declaration if instantiating
  -- any Xilinx primitives in this code.
  --library UNISIM;
  --use UNISIM.VComponents.all;
30  entity Ripple_Carry_FA is
      generic(N : integer :=16);--Number of bits in A and B
      Port ( A : in  STD_LOGIC_VECTOR (N-1 downto 0);
            B : in  STD_LOGIC_VECTOR (N-1 downto 0);
35            Cin : in  STD_LOGIC;

```

```

        Sum : out  STD_LOGIC_VECTOR (N-1 downto 0);
        Cout : out  STD_LOGIC);
end Ripple_Carry_FA;

40 architecture Behavioral of Ripple_Carry_FA is
    --Interim signal used for carry ins and outs of the 1 bit full adders
    --The MSB of C is carry out
    signal C : std_logic_vector(N downto 1);

45    component FA_1bit is
        Port ( A : in  STD_LOGIC;
              B : in  STD_LOGIC;
              Cin : in  STD_LOGIC;
              S : out  STD_LOGIC;
50              Cout : out  STD_LOGIC);
    end component;

begin

55    GEN_ADD : for i in N-1 downto 0 generate
        --Generate the first full adder, which is special because it takes Cin
        FA0_GEN : if (i=0) generate
            FA0 : FA_1bit
                port map(A=>A(i), B=>B(i), Cin=>Cin, Cout=>C(1), S=>Sum(i));
60        end generate FA0_GEN;

        --Generate the other adders, the last bit of C is carry out
        FAX_GEN : if (i>0) generate
            FAN : FA_1bit
                port map(A=>A(i), B=>B(i), Cin=>C(i), Cout=>C(i+1), S=>Sum(i));
65        end generate FAX_GEN;

    end generate GEN_ADD;

70 end Behavioral;

```

Listing 26: nBitRegister 32 VHDL

```

0  -----
--Company      : RIT
--Author       : Brandon Key
--Created      : 2/8/2017
--
5  --Project Name : Lab 2
--File         : nBitRegister_32.vhd
--
--Entity       : nBitRegister_32
--Architecture : struct
10 --Revision    :
--Rev 0.01     : 2/8/2017
--
--Tool Version : VHDL '93
--Description  : Entity and behavioral description of an n-bit register
15 --Notes       :
-----

library ieee;

```

```

20 use ieee.std_logic_1164.all;

entity nBitRegister_32 is
    generic (n : integer := 32);
25   Port (
        nBitIn : in std_logic_vector(n-1 downto 0); -- n bits to store in the
        register
        WE      : in std_logic; -- Active high write enable
        Reset   : in std_logic; -- Async reset , disabled when low
        clk     : in std_logic;
30        Y : out std_logic_vector(n-1 downto 0) -- 1 output , n bits wide
    );
end nBitRegister_32;

35 architecture behav of nBitRegister_32 is

begin

40     output_proc : process (clk , Reset) begin

        if Reset = '0' then
            Y <= (others => '0');
        elsif clk'event and clk = '1' then
45             if WE = '1' then
                Y <= nBitIn;
            end if;
        end if;

50     end process output_proc;

end behav;

```

Listing 27: ALU Wrapper VHDL

```

0  ---
--- Company:
--- Engineer:
---
--- Create Date:      13:41:10 03/18/2017
5  --- Design Name:
--- Module Name:      ALU.Wrapper - Behavioral
--- Project Name:
--- Target Devices:
--- Tool versions:
10 --- Description:
---
--- Dependencies:
---
--- Revision:
15 --- Revision 0.01 - File Created
--- Additional Comments:
---
library IEEE;

```

```

20 use IEEE.STD_LOGIC_1164.ALL;
   use IEEE.MATHREAL.ALL;
   use IEEE.NUMERIC_STD.ALL;

   -- Uncomment the following library declaration if using
25 -- arithmetic functions with Signed or Unsigned values
   --use IEEE.NUMERIC_STD.ALL;

   -- Uncomment the following library declaration if instantiating
   -- any Xilinx primitives in this code.
30 --library UNISIM;
   --use UNISIM.VComponents.all;

   entity ALU_Wrapper is
       Port ( input1 : in  STD_LOGIC_VECTOR (15 downto 0);
35           input2 : in  STD_LOGIC_VECTOR (15 downto 0);
           control : in  STD_LOGIC_VECTOR (3  downto 0);
           output  : out STD_LOGIC_VECTOR (15 downto 0));
   end ALU_Wrapper;

40 architecture Behavioral of ALU_Wrapper is
   --Component Declarations
       component Multiplier is
           generic( N : integer :=16);
           Port ( A : in  STD_LOGIC_VECTOR ((N/2)-1 downto 0);
45             B : in  STD_LOGIC_VECTOR ((N/2)-1 downto 0);
             Product : out STD_LOGIC_VECTOR (N-1 downto 0));
       end component;

       component Logic_Unit is
50           generic( N : integer :=16);
           Port ( A : in  STD_LOGIC_VECTOR (N-1 downto 0);
             B : in  STD_LOGIC_VECTOR (N-1 downto 0);
             Control : in  STD_LOGIC_VECTOR (3  downto 0);
             output : out STD_LOGIC_VECTOR (N-1 downto 0));
55       end component;

       component Shifter is
           generic( N : integer:=16; Namnt : integer :=integer(ceil(log2(real(16)))));

60           Port ( A : in  STD_LOGIC_VECTOR (N-1 downto 0);
             amnt : in  STD_LOGIC_VECTOR (Namnt-1 downto 0);
             Control : in  STD_LOGIC_VECTOR (3  downto 0);
             output : out STD_LOGIC_VECTOR (N-1 downto 0));
       end component;

65       component Ripple_Carry_FA is
           generic(N : integer :=16);--Number of bits in A and B
           Port ( A : in  STD_LOGIC_VECTOR (N-1 downto 0);
             B : in  STD_LOGIC_VECTOR (N-1 downto 0);
70             Cin : in  STD_LOGIC;
             Sum : out  STD_LOGIC_VECTOR (N-1 downto 0);
             Cout : out  STD_LOGIC);
       end component;

75       component Subtractor is
           generic(N : integer :=16);
           Port ( A : in  STD_LOGIC_VECTOR (15 downto 0);
             B : in  STD_LOGIC_VECTOR (15 downto 0);

```



```

Output : out  STD_LOGIC_VECTOR (15 downto 0));
80  end component;

--Signal Declarations

signal Product, Sum, ShiftOut, LogicOut, Difference : STD_LOGIC_VECTOR(15 downto
0);
85  signal Cout : STD_LOGIC;
begin
  --map multiplier
  MULT : Multiplier
    generic map(N=>16)
90    port map(A=>input1(7 downto 0), B=>input2(7 downto 0), Product=>Product);

  --Map Logic Unit
  LOGIC : Logic_Unit
    generic map(N=>16)
95    port map( A=>input1, B=>input2, Control=>Control, output=>LogicOut);

  --Map Shifter
  SHIFT : Shifter
    generic map(N=>16, Namnt=>4)
100    port map(A=>input1, amnt=>input2(3 downto 0), Control=>Control, output=>
ShiftOut);

  --Map Adder
  ADD : Ripple_Carry_FA
    generic map(N=>16)
105    port map(A=>input1, B=>input2, Cin=>'0', Cout=>Cout, Sum=>Sum);

  --Map Subtractor
  SUB : Subtractor
    generic map(N=>16)
110    port map(A=>input1, B=>input2, Output=>Difference);

  --End mapping
  -----

115  ALU_PROC : process(input1, input2, control) begin
    C1: case control is
      when "0100"=> output<=Sum;--ADD
      when "0101"=> output<=Difference;--SUB
      when "0110"=> output<=Product;--MUL
120    when "1100"=> output<=ShiftOut;--SLL
      when "1101"=> output<=ShiftOut;--SRL
      when "1110"=> output<=ShiftOut;--SRA
      when others=> output<=LogicOut;--OR,NOT,AND,XOR
    end case C1;
125  end process;
end Behavioral;

```

Listing 28: nBitAdderSubtractor 16Bit VHDL

```

0  -----
--Company      : RIT
--Author       : Brandon Key
--Created      : 02/18/2018
--
5  --Project Name : Lab 3

```

```

--File           : nBitAdderSubtractor_16Bit.vhd
--
--Entity         : nBitAdderSubtractor_16Bit
--Architecture   : struct
10 --
--Tool Version   : VHDL '93
--Description    : Entity and structural description of an adder subtractor
--               : SEL = 0 : A+B = Y
--               : SEL = 1 : A-B = Y
15 -----

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.numeric_std.all;
20
entity nBitAdderSubtractor_16Bit is
    generic (n : integer := 16);
    port(
25         A,B : in  std_logic_vector(n-1 downto 0);
        SEL : in  std_logic;
        Y   : out std_logic_vector(n-1 downto 0);
        CB  : out std_logic
    );
end nBitAdderSubtractor_16Bit;
30
architecture struct of nBitAdderSubtractor_16Bit is

    component full_adder is
        port(A,B,Cin : in  std_logic;
35             Sum,Cout : out std_logic
        );
    end component full_adder;

    --Create an array to hold all of the carries
40    type carry_array is array (n-1 downto 0) of std_logic;
    signal c_array : carry_array;

    signal B_XOR_SEL : std_logic_vector( (n-1) downto 0);

45 begin

    --Generate the xor statements to be mapped to the full adders
    XORator : for i in 0 to n-1 generate
        B_XOR_SEL(i) <= B(i) xor SEL;
50    end generate XORator;

    generate_adders : for i in 0 to n-1 generate
        i_first : if i = 0 generate
            --The first adder gets SEL as the Cin
55            adder : full_adder port map(
                A => A(i),
                B => B_XOR_SEL(i),
                Cin => SEL,
                Sum => Y(i),
                Cout => c_array(i)
60            );
        end generate i_first;

        i_last : if i = (n-1) generate

```

```

65      --The last adder doesn't have a carry out
      adder : full_adder port map(
        A => A(i),
        B => B_XOR_SEL(i),
        Cin => c_array(i-1),
70      Sum => Y(i),
        Cout => c_array(i)
      );
      end generate i_last;

75      --Middle adders
      i_mid : if (i /= 0) and (i /= (n-1)) generate
        adder : full_adder port map(
          A => A(i),
          B => B_XOR_SEL(i),
80      Cin => c_array(i-1),
          Sum => Y(i),
          Cout => c_array(i)
        );
        end generate i_mid;

85      end generate generate_adders;

      CB <= c_array(n-1) xor SEL;

90 end struct;

```

Listing 29: ALU TESTBENCH VHDL

```

0  -- Company:
  -- Engineer:
  --
  -- Create Date:    10:35:10 03/19/2017
5  -- Design Name:
  -- Module Name:    G:/DSD2/Lab3/Xilinx/Lab3/ALU_TESTBENCH.vhd
  -- Project Name:   Lab3
  -- Target Device:
  -- Tool versions:
10 -- Description:
  --
  -- VHDL Test Bench Created by ISE for module: ALU_Wrapper
  --
  -- Dependencies:
15 --
  -- Revision:
  -- Revision 0.01 - File Created
  -- Additional Comments:
  --
20 -- Notes:
  -- This testbench has been automatically generated using types std_logic and
  -- std_logic_vector for the ports of the unit under test.  Xilinx recommends
  -- that these types always be used for the top-level I/O of a design in order
  -- to guarantee that the testbench will bind correctly to the post-implementation
25 -- simulation model.

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

```

```

30 -- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--USE ieee.numeric_std.ALL;

ENTITY ALU_TESTBENCH IS
35 END ALU_TESTBENCH;

ARCHITECTURE behavior OF ALU_TESTBENCH IS

    -- Component Declaration for the Unit Under Test (UUT)

40
    COMPONENT ALU_Wrapper
    PORT(
        input1 : IN    std_logic_vector(15 downto 0);
        input2 : IN    std_logic_vector(15 downto 0);
45        control : IN   std_logic_vector(3  downto 0);
        output  : OUT   std_logic_vector(15 downto 0)
    );
    END COMPONENT;

50
    --Inputs
    signal input1 : std_logic_vector(15 downto 0) := (others => '0');
    signal input2 : std_logic_vector(15 downto 0) := (others => '0');
    signal control : std_logic_vector(3  downto 0) := (others => '0');
55
    --Outputs
    signal output : std_logic_vector(15 downto 0);
    -- No clocks detected in port list. Replace <clock> below with
    -- appropriate port name

60

BEGIN

65
    -- Instantiate the Unit Under Test (UUT)
    uut: ALU_Wrapper PORT MAP (
        input1 => input1,
        input2 => input2,
        control => control,
70        output => output
    );

    --0100 ADD
    --0101 SUB
75    --0110 MUL
    --1000 OR
    --1001 NOT
    --1010 AND
    --1011 XOR
    --1100 SLL
    --1101 SRL
    --1110 SRA

80

    -- Stimulus process
    stim_proc: process
85    begin
        -- insert stimulus here

```

```

90      --Test ADD
      control<="0100";

      --ADD1
      input1<="1010101010101010";
      input2<="0101010101010101";
95      wait for 50 ns;
      assert output="1111111111111111"
          report "ADD1 failed , expected 1111111111111111, got: " & integer'image(
to_integer(unsigned(output)));

      --ADD2
100     input1<="1111111111111111";
      input2<="0000000000000000";
      wait for 50 ns;
      assert output="1111111111111111"
          report "ADD2 failed , expected 1111111111111111, got: " & integer'image(
to_integer(unsigned(output)));
105     --
      --ADD3
      input1<="0000000000110011";
      input2<="0000000000010010";
          --"0000000000000000"
110     wait for 50 ns;
      assert output="0000000001000101"
          report "ADD3 failed , expected 0000000001000101, got: " & integer'image(
to_integer(unsigned(output)));

      --Test SUB
115     control<="0101";

      --SUB1
      input1<="1111111111111111";
      input2<="1111111111111111";
120     --"0000000000000000"
      wait for 50 ns;
      assert output="0000000000000000"
          report "SUB1 failed , expected 0000000000000000, got: " & integer'image(
to_integer(unsigned(output)));

      --SUB2
125     input1<="0000000001000000";--64
      input2<="000000000010010";--18
          --"0000000000101110"--46
      wait for 50 ns;
      assert output="0000000000101110"
130     report "SUB2 failed , expected 0000000000101110, got: " & integer'image(
to_integer(unsigned(output)));

      --SUB3
      input1<="0000000000000111";--7
135     input2<="0000000000010000";--16
          --"111111111110111"--(-)9
      wait for 50 ns;
      assert output="111111111110111"
          report "SUB3 failed , expected 111111111110111, got: " & integer'image(
to_integer(unsigned(output)));
140     --TEST MUL

```

```

control<="0110";

--MUL1
input1<="11111111111111";
input2<="0000000000000000";
--"0000000000000000"
wait for 50 ns;
assert output="0000000000000000"
report "MUL1 failed , expected 0000000000000000, got: " & integer'image(
to_integer(unsigned(output)));

--MUL2
input1<="000000000000100";--4
input2<="000000000000101";--5
--"0000000000010100" --20
wait for 50 ns;
assert output="0000000000010100"
report "MUL2 failed , expected 0000000000010100, got: " & integer'image(
to_integer(unsigned(output)));

--Test OR
control<="1000";

--OR1
input1<="1111010101000011";
input2<="0011100100110111";
--"1111110101110111"
wait for 50 ns;
assert output="0011000100000011"
report "OR1 failed , expected 0011000100000011, got: " & integer'image(
to_integer(unsigned(output)));

--TEST NOT
control<="1001";

--NOT1
input1<="1111010101000011";
input2<="0000000000000000";
--"0000101010111100"
wait for 50 ns;
assert output="0000101010111100"
report "NOT1 failed , expected 0000101010111100, got: " & integer'image(
to_integer(unsigned(output)));

--TEST AND
control<="1010";

--AND1
input1<="1111010101000011";
input2<="0011100100110111";
--"0011000100000011"
wait for 50 ns;
assert output="0011000100000011"
report "AND1 failed , expected 0011000100000011, got: " & integer'image(
to_integer(unsigned(output)));

--TEST XOR
control<="1011";

```

```

--XOR1
input1<="1111010101000011";
input2<="0011100100110111";
--"1100110001110100"
200 wait for 50 ns;
assert output="1100110001110100"
report "XOR1 failed, expected 1100110001110100, got: " & integer'image(
to_integer(unsigned(output)));

--TEST SLL
205 control<="1100";

--SLL1
input1<="1111010101000011";
input2<="0000000000000100";
--"0101010000110000"
210 wait for 50 ns;
assert output="0101010000110000"
report "SLL1 failed, expected 0101010000110000, got: " & integer'image(
to_integer(unsigned(output)));

--TEST SRL
215 control<="1101";

--SRL1
input1<="1111010101000011";
input2<="0000000000000100";
--"0000111101010100"
220 wait for 50 ns;
assert output="0000111101010100"
report "SRL1 failed, expected 0000111101010100, got: " & integer'image(
to_integer(unsigned(output)));

225 --TEST SRA
control<="1110";

--SRA1
230 input1<="1111010101000011";
input2<="0000000000000100";
--"1111111101010100"
wait for 50 ns;
assert output="1111111101010100"
235 report "SRA1 failed, expected 1111111101010100, got: " & integer'image(
to_integer(unsigned(output)));
wait;
end process;

END;

```

Listing 30: Logic Unit VHDL

```

0 -- Company:
-- Engineer:
--
-- Create Date: 08:51:09 03/02/2017
5 -- Design Name:
-- Module Name: Logic_Unit - Behavioral
-- Project Name:

```

```

-- Target Devices:
-- Tool versions:
10 -- Description:
--
-- Dependencies:
--
-- Revision:
15 -- Revision 0.01 - File Created
-- Additional Comments:
--

```

```

library IEEE;
20 use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

25 -- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

30 entity Logic_Unit is
    generic( N : integer :=16);
    Port ( A : in  STD_LOGIC_VECTOR (N-1 downto 0);
          B : in  STD_LOGIC_VECTOR (N-1 downto 0);
35         Control : in  STD_LOGIC_VECTOR (3 downto 0);
          output : out STD_LOGIC_VECTOR (N-1 downto 0));
end Logic_Unit;
--Control:
--1000 : or
40 --1001 : not
--1010 : AND
--1011 : XOR
architecture Behavioral of Logic_Unit is

45 begin
    proc1 : process(control, A, B)
    begin
        --Depending on control, will do specific commands
        if control ="1000" then --bitwise OR
50             F0 : for i in 0 to N-1 loop
                 output(i)<=A(i) OR B(i);
             end loop;

            elsif control ="1001" then --bitwise NOT
55             F1 : for i in 0 to N-1 loop
                 output(i)<= NOT A(i);
             end loop;

            elsif control = "1010" then --bitwise AND
60             F2 : for i in 0 to N-1 loop
                 output(i)<= A(i) AND B(i);
             end loop;

            elsif control = "1011" then --bitwise XOR
65             F3 : for i in 0 to N-1 loop
                 output(i)<= A(i) XOR B(i);

```



```

        end loop;
    end if;
end process;

```

```

end Behavioral;

```

5.2 Leonardo Scripts

Listing 31: Multiplier Spectrum Script

```

0 set exclude_gates {PadInC PadOut}
load_library ~/Pyxis.SPT.HEP/ic_reflibs/external_libs/GDKgates/GDKgates_utilities/
  hdl_libs/gdk.syn
read {../SourceCode/FA_1bit.vhd ../SourceCode/AND2.vhd ../SourceCode/ANDADD.vhd ../
  SourceCode/Multiplier.vhd }
ungroup * -hierarchy
set sdf_write_flat_netlist TRUE
5 optimize
write -format verilog ./Output/Multiplier.v
write -format vhdl ./Output/Multiplier.vhdl
write -format sdf ./Output/Multiplier.sdf

```

Listing 32: LFSR 32 4 Spectrum Script

```

0 set exclude_gates {PadInC PadOut}
load_library ~/Pyxis.SPT.HEP/ic_reflibs/external_libs/GDKgates/GDKgates_utilities/
  hdl_libs/gdk.syn
read {../SourceCode/LFSR_32_4.vhd }
set sdf_write_flat_netlist TRUE
optimize
5 write -format verilog ./Output/LFSR_32_4.v
write -format vhdl ./Output/LFSR_32_4.vhdl
write -format sdf ./Output/LFSR_32_4.sdf

```

Listing 33: MISR 32 4 Spectrum Script

```

0 set exclude_gates {PadInC PadOut}
load_library ~/Pyxis.SPT.HEP/ic_reflibs/external_libs/GDKgates/GDKgates_utilities/
  hdl_libs/gdk.syn
read {../SourceCode/MISR_32_4.vhd }
set sdf_write_flat_netlist TRUE
optimize
5 write -format verilog ./Output/MISR_32_4.v
write -format vhdl ./Output/MISR_32_4.vhdl
write -format sdf ./Output/MISR_32_4.sdf

```

Listing 34: ProjectWrapper Spectrum Script

```

0 set exclude_gates {PadInC PadOut}
load_library ~/Pyxis.SPT.HEP/ic_reflibs/external_libs/GDKgates/GDKgates_utilities/
  hdl_libs/gdk.syn
read {../SourceCode/AND2.vhd ../SourceCode/ANDADD.vhd ../SourceCode/FA_1bit.vhd ../
  SourceCode/FullAdder.vhd ../SourceCode/LFSR_32_4.vhd ../SourceCode/MISR_32_4.vhd
  ../SourceCode/Multiplier.vhd ../SourceCode/nBitRegister_16.vhd ../SourceCode/
  nBitRegister_32.vhd ../SourceCode/nBitAdder.vhd ../SourceCode/Counter.vhd ../
  SourceCode/TestController.vhd ../SourceCode/nBitMux_2to1.vhd ../SourceCode/MAC.
  vhd ../SourceCode/ProjectWrapper.vhd }

```

```

ungroup * -hierarchy
set sdf_write_flat_netlist TRUE
5 optimize
write -format verilog ./Output/ProjectWrapper.v
write -format vhdl ./Output/ProjectWrapper.vhdl
write -format sdf ./Output/ProjectWrapper.sdf

```

Listing 35: nBitAdder Spectrum Script

```

0 set exclude_gates {PadInC PadOut}
load_library ~/Pyxis.SPT_HEP/ic_reflibs/external_libs/GDKgates/GDKgates_utilities/
  hdl_libs/gdk.syn
read {../SourceCode/FullAdder.vhd ../SourceCode/nBitAdder.vhd }
set sdf_write_flat_netlist TRUE
optimize
5 write -format verilog ./Output/nBitAdder.v
write -format vhdl ./Output/nBitAdder.vhdl
write -format sdf ./Output/nBitAdder.sdf

```

Listing 36: nBitAdderSubtractor Spectrum Script

```

0 set exclude_gates {PadInC PadOut}
load_library ~/Pyxis.SPT_HEP/ic_reflibs/external_libs/GDKgates/GDKgates_utilities/
  hdl_libs/gdk.syn
read {../SourceCode/FullAdder.vhd ../SourceCode/nBitAdder.vhd }
set sdf_write_flat_netlist TRUE
optimize
5 write -format verilog ./Output/nBitAdder.v
write -format vhdl ./Output/nBitAdder.vhdl
write -format sdf ./Output/nBitAdder.sdf

```

Listing 37: MAC BIST Spectrum Script

```

0 set exclude_gates {PadInC PadOut}
load_library ~/Pyxis.SPT_HEP/ic_reflibs/external_libs/GDKgates/GDKgates_utilities/
  hdl_libs/gdk.syn
read {./Output/LFSR_32_4.vhdl ./Output/MISR_32_4.vhdl ./Output/nBitAdder.vhdl ./
  Output/Multiplier.vhdl ./Output/nBitRegister_16.vhdl ./Output/nBitRegister_32.
  vhdl ./Output/nBitMux_2to1.vhdl ../SourceCode/MAC.vhd }
set sdf_write_flat_netlist TRUE
optimize
5 write -format verilog ./Output/MAC.v
write -format vhdl ./Output/MAC.vhdl
write -format sdf ./Output/MAC.sdf

```

Listing 38: nBitRegister 16 Spectrum Script

```

0 set exclude_gates {PadInC PadOut}
load_library ~/Pyxis.SPT_HEP/ic_reflibs/external_libs/GDKgates/GDKgates_utilities/
  hdl_libs/gdk.syn
read {../SourceCode/nBitRegister_16.vhd }
set sdf_write_flat_netlist TRUE
optimize
5 write -format verilog ./Output/nBitRegister_16.v
write -format vhdl ./Output/nBitRegister_16.vhdl
write -format sdf ./Output/nBitRegister_16.sdf

```

Listing 39: MAC Spectrum Script

```

0 set exclude_gates {PadInC PadOut}
load_library ~/Pyxis.SPT.HEP/ic_reflibs/external_libs/GDKgates/GDKgates_utilities/
  hdl_libs/gdk.syn
read {../SourceCode/FA_1bit.vhd ../SourceCode/AND2.vhd ../SourceCode/ANDADD.vhd ../
  SourceCode/Multiplier.vhd ../SourceCode/nBitAdder.vhd ../SourceCode/
  nBitRegister_16.vhd ../SourceCode/nBitRegister_32.vhd ../SourceCode/MAC.vhd }
ungroup * -hierarchy
set sdf_write_flat_netlist TRUE
5 optimize
write -format verilog ../SourceCode/MAC.v
write -format vhd ../SourceCode/MAC.vhd
write -format sdf ../SourceCode/MAC.sdf

```

Listing 40: nBitMux 2to1 Spectrum Script

```

0 set exclude_gates {PadInC PadOut}
load_library ~/Pyxis.SPT.HEP/ic_reflibs/external_libs/GDKgates/GDKgates_utilities/
  hdl_libs/gdk.syn
read {../SourceCode/nBitMux_2to1.vhd }
set sdf_write_flat_netlist TRUE
optimize
5 write -format verilog ./Output/nBitMux_2to1.v
write -format vhdl ./Output/nBitMux_2to1.vhdl
write -format sdf ./Output/nBitMux_2to1.sdf

```

Listing 41: nBitRegister 32 Spectrum Script

```

0 set exclude_gates {PadInC PadOut}
load_library ~/Pyxis.SPT.HEP/ic_reflibs/external_libs/GDKgates/GDKgates_utilities/
  hdl_libs/gdk.syn
read {../SourceCode/nBitRegister_32.vhd }
set sdf_write_flat_netlist TRUE
optimize
5 write -format verilog ./Output/nBitRegister_32.v
write -format vhdl ./Output/nBitRegister_32.vhdl
write -format sdf ./Output/nBitRegister_32.sdf

```

Listing 42: MAC (copy) Spectrum Script

```

0 set exclude_gates {PadInC PadOut}
load_library ~/Pyxis.SPT.HEP/ic_reflibs/external_libs/GDKgates/GDKgates_utilities/
  hdl_libs/gdk.syn
read {./Output/nBitAdder.vhdl ./Output/Multiplier.vhdl ./Output/nBitRegister_16.vhdl
  ./Output/nBitRegister_32.vhdl ../SourceCode/MAC.vhd }
set sdf_write_flat_netlist TRUE
optimize
5 write -format verilog ./Output/MAC.v
write -format vhdl ./Output/MAC.vhdl
write -format sdf ./Output/MAC.sdf

```

5.3 SPICE

Listing 43: layout test SPICE

```

0 * Example circuit file for simulating PEX

```

```

.OPTION DOTNODE
.HIER /

5 .INCLUDE "/home/bxk5113/Pyxis_SPT_HEP/ic_projects/Pyxis_SPT/digicdesign/
  ProjectWrapper/ProjectWrapper.cal/ProjectWrapper.pex.netlist"

.LIB /home/bxk5113/Pyxis_SPT_HEP/ic_reflibs/tech_libs/generic13/models/lib.eldo TT

* - Instantiate your parasitic netlist and add the load capacitor
10 ** FORMAT :
* XLAYOUT [all inputs as listed by the ".subckt" line in the included netlist, in
  the order that they appear there] [name of the subcircuit as listed in the
  included netlist]
XLAYOUT COMPLETE PASS REGOUT[31] REGOUT[30] REGOUT[29] REGOUT[28] REGOUT[27] REGOUT
[26] REGOUT[25] REGOUT[24] REGOUT[23] REGOUT[22] REGOUT[21] REGOUT[20] REGOUT[19]
REGOUT[18] REGOUT[17] REGOUT[16] REGOUT[15] REGOUT[14] REGOUT[13] REGOUT[12]
REGOUT[11] REGOUT[10] REGOUT[9] REGOUT[8] REGOUT[7] REGOUT[6] REGOUT[5] REGOUT[4]
REGOUT[3] REGOUT[2] REGOUT[1] REGOUT[0] A[15] A[14] A[13] A[12] A[11] A[10] A[9]
A[8] A[7] A[6] A[5] A[4] A[3] A[2] A[1] A[0] B[15] B[14] B[13] B[12] B[11] B[10]
B[9] B[8] B[7] B[6] B[5] B[4] B[3] B[2] B[1] B[0] CLK RESET STARTTEST WE
ProjectWrapper

* Output Capacitance
15 C.REGOUT[31] REGOUT[31] 0 120 f
C.REGOUT[30] REGOUT[30] 0 120 f
C.REGOUT[29] REGOUT[29] 0 120 f
C.REGOUT[28] REGOUT[28] 0 120 f
C.REGOUT[27] REGOUT[27] 0 120 f
20 C.REGOUT[26] REGOUT[26] 0 120 f
C.REGOUT[25] REGOUT[25] 0 120 f
C.REGOUT[24] REGOUT[24] 0 120 f
C.REGOUT[23] REGOUT[23] 0 120 f
C.REGOUT[22] REGOUT[22] 0 120 f
25 C.REGOUT[21] REGOUT[21] 0 120 f
C.REGOUT[20] REGOUT[20] 0 120 f
C.REGOUT[19] REGOUT[19] 0 120 f
C.REGOUT[18] REGOUT[18] 0 120 f
C.REGOUT[17] REGOUT[17] 0 120 f
30 C.REGOUT[16] REGOUT[16] 0 120 f
C.REGOUT[15] REGOUT[15] 0 120 f
C.REGOUT[14] REGOUT[14] 0 120 f
C.REGOUT[13] REGOUT[13] 0 120 f
C.REGOUT[12] REGOUT[12] 0 120 f
35 C.REGOUT[11] REGOUT[11] 0 120 f
C.REGOUT[10] REGOUT[10] 0 120 f
C.REGOUT[9] REGOUT[9] 0 120 f
C.REGOUT[8] REGOUT[8] 0 120 f
C.REGOUT[7] REGOUT[7] 0 120 f
40 C.REGOUT[6] REGOUT[6] 0 120 f
C.REGOUT[5] REGOUT[5] 0 120 f
C.REGOUT[4] REGOUT[4] 0 120 f
C.REGOUT[3] REGOUT[3] 0 120 f
C.REGOUT[2] REGOUT[2] 0 120 f
45 C.REGOUT[1] REGOUT[1] 0 120 f
C.REGOUT[0] REGOUT[0] 0 120 f

* - Analysis Setup - DC sweep

```

```

50 * FORMAT : .DC [name] [low] [high] [step]
*.DC VFORCE_A 0 1.2 0.01

* - Analysis Setup - Trans
* FORMAT : .TRAN [start time] [end time] [time step]
55 .TRAN 0 2000n 0.05n

* --- Forces
* FORMAT --- PULSE : [name] [port] [reference (0 means ground)] PULSE [low] [high] [
    delay] [fall time] [rise time] [pulse width] [period]
*
60 * FORMAT --- DC : [name] [port] [reference (0 means ground)] DC [voltage]
*

VFORCE_VDD VDD 0 DC 1.08
VFORCE_VSS VSS 0 DC 0

65 VFORCE_CLK CLK 0 PULSE (0 1.08 25n 0.1n 0.1n 25n 50n)

VFORCE_RESET RESET 0 pw1 (120n 1.08 120.1n 0 )
VFORCE_WE WE 0 DC 1.08

70 .SIGBUS A[15:0] VHI=1.08 VLO=0 TRISE=0.1n TFALL=0.1n TDELAY=210n THOLD=200n BASE=
    HEXA PATTERN 0002 0003 P
.SIGBUS B[15:0] VHI=1.08 VLO=0 TRISE=0.1n TFALL=0.1n TDELAY=210n THOLD=200n BASE=
    HEXA PATTERN 0003 0004 P

75 * --- Waveform Outputs
.PLOT TRAN V(COMPLETE)
.PLOT TRAN V(PASS)
.PLOT TRAN V(REGOUT[31])
.PLOT TRAN V(REGOUT[30])
80 .PLOT TRAN V(REGOUT[29])
.PLOT TRAN V(REGOUT[28])
.PLOT TRAN V(REGOUT[27])
.PLOT TRAN V(REGOUT[26])
.PLOT TRAN V(REGOUT[25])
85 .PLOT TRAN V(REGOUT[24])
.PLOT TRAN V(REGOUT[23])
.PLOT TRAN V(REGOUT[22])
.PLOT TRAN V(REGOUT[21])
.PLOT TRAN V(REGOUT[20])
90 .PLOT TRAN V(REGOUT[19])
.PLOT TRAN V(REGOUT[18])
.PLOT TRAN V(REGOUT[17])
.PLOT TRAN V(REGOUT[16])
.PLOT TRAN V(REGOUT[15])
95 .PLOT TRAN V(REGOUT[14])
.PLOT TRAN V(REGOUT[13])
.PLOT TRAN V(REGOUT[12])
.PLOT TRAN V(REGOUT[11])
.PLOT TRAN V(REGOUT[10])
100 .PLOT TRAN V(REGOUT[9])
.PLOT TRAN V(REGOUT[8])
.PLOT TRAN V(REGOUT[7])
.PLOT TRAN V(REGOUT[6])
.PLOT TRAN V(REGOUT[5])
105 .PLOT TRAN V(REGOUT[4])

```

```

110 .PLOT TRAN V(REGOUT[3])
    .PLOT TRAN V(REGOUT[2])
    .PLOT TRAN V(REGOUT[1])
    .PLOT TRAN V(REGOUT[0])
    .PLOT TRAN V(A[15])
    .PLOT TRAN V(A[14])
    .PLOT TRAN V(A[13])
    .PLOT TRAN V(A[12])
    .PLOT TRAN V(A[11])
115 .PLOT TRAN V(A[10])
    .PLOT TRAN V(A[9])
    .PLOT TRAN V(A[8])
    .PLOT TRAN V(A[7])
    .PLOT TRAN V(A[6])
120 .PLOT TRAN V(A[5])
    .PLOT TRAN V(A[4])
    .PLOT TRAN V(A[3])
    .PLOT TRAN V(A[2])
    .PLOT TRAN V(A[1])
125 .PLOT TRAN V(A[0])
    .PLOT TRAN V(B[15])
    .PLOT TRAN V(B[14])
    .PLOT TRAN V(B[13])
    .PLOT TRAN V(B[12])
130 .PLOT TRAN V(B[11])
    .PLOT TRAN V(B[10])
    .PLOT TRAN V(B[9])
    .PLOT TRAN V(B[8])
    .PLOT TRAN V(B[7])
135 .PLOT TRAN V(B[6])
    .PLOT TRAN V(B[5])
    .PLOT TRAN V(B[4])
    .PLOT TRAN V(B[3])
    .PLOT TRAN V(B[2])
140 .PLOT TRAN V(B[1])
    .PLOT TRAN V(B[0])
    .PLOT TRAN V(CLK)
    .PLOT TRAN V(RESET)
    .PLOT TRAN V(STARTTEST)
145 .PLOT TRAN V(WE)

* — Params
    .TEMP 125
150
* — Power Measurement
    .measure tran static_pwr AVG power from=90ns to=160ns
    .measure tran inst_pwr MAX power from=90ns to=160ns

```

Listing 44: power test SPICE

```

0 * Example circuit file for simulating PEX

    .OPTION DOTNODE
    .HIER /

5 .INCLUDE "/home/bxk5113/Pyxis_SPT_HEP/ic_projects/Pyxis_SPT/digicdesign/
    ProjectWrapper/ProjectWrapper.cal/ProjectWrapper.pex.netlist"

```

```

.LIB /home/bxk5113/Pyxis_SPT-HEP/ic_reflibs/tech_libs/generic13/models/lib.eldo TT

* - Instantiate your parasitic netlist and add the load capacitor
10 ** FORMAT :
* XLAYOUT [all inputs as listed by the ".subckt" line in the included netlist, in
    the order that they appear there] [name of the subcircuit as listed in the
    included netlist]
XLAYOUT COMPLETE PASS REGOUT[31] REGOUT[30] REGOUT[29] REGOUT[28] REGOUT[27] REGOUT
    [26] REGOUT[25] REGOUT[24] REGOUT[23] REGOUT[22] REGOUT[21] REGOUT[20] REGOUT[19]
    REGOUT[18] REGOUT[17] REGOUT[16] REGOUT[15] REGOUT[14] REGOUT[13] REGOUT[12]
    REGOUT[11] REGOUT[10] REGOUT[9] REGOUT[8] REGOUT[7] REGOUT[6] REGOUT[5] REGOUT[4]
    REGOUT[3] REGOUT[2] REGOUT[1] REGOUT[0] A[15] A[14] A[13] A[12] A[11] A[10] A[9]
    A[8] A[7] A[6] A[5] A[4] A[3] A[2] A[1] A[0] B[15] B[14] B[13] B[12] B[11] B[10]
    B[9] B[8] B[7] B[6] B[5] B[4] B[3] B[2] B[1] B[0] CLK RESET STARTTEST WE
    ProjectWrapper

* Output Capacitance
15 C.REGOUT[31] REGOUT[31] 0 120 f
C.REGOUT[30] REGOUT[30] 0 120 f
C.REGOUT[29] REGOUT[29] 0 120 f
C.REGOUT[28] REGOUT[28] 0 120 f
C.REGOUT[27] REGOUT[27] 0 120 f
20 C.REGOUT[26] REGOUT[26] 0 120 f
C.REGOUT[25] REGOUT[25] 0 120 f
C.REGOUT[24] REGOUT[24] 0 120 f
C.REGOUT[23] REGOUT[23] 0 120 f
C.REGOUT[22] REGOUT[22] 0 120 f
25 C.REGOUT[21] REGOUT[21] 0 120 f
C.REGOUT[20] REGOUT[20] 0 120 f
C.REGOUT[19] REGOUT[19] 0 120 f
C.REGOUT[18] REGOUT[18] 0 120 f
C.REGOUT[17] REGOUT[17] 0 120 f
30 C.REGOUT[16] REGOUT[16] 0 120 f
C.REGOUT[15] REGOUT[15] 0 120 f
C.REGOUT[14] REGOUT[14] 0 120 f
C.REGOUT[13] REGOUT[13] 0 120 f
C.REGOUT[12] REGOUT[12] 0 120 f
35 C.REGOUT[11] REGOUT[11] 0 120 f
C.REGOUT[10] REGOUT[10] 0 120 f
C.REGOUT[9] REGOUT[9] 0 120 f
C.REGOUT[8] REGOUT[8] 0 120 f
C.REGOUT[7] REGOUT[7] 0 120 f
40 C.REGOUT[6] REGOUT[6] 0 120 f
C.REGOUT[5] REGOUT[5] 0 120 f
C.REGOUT[4] REGOUT[4] 0 120 f
C.REGOUT[3] REGOUT[3] 0 120 f
C.REGOUT[2] REGOUT[2] 0 120 f
45 C.REGOUT[1] REGOUT[1] 0 120 f
C.REGOUT[0] REGOUT[0] 0 120 f

* - Analysis Setup - DC sweep
50 * FORMAT : .DC [name] [low] [high] [step]
*.DC VFORCE_A 0 1.2 0.01

* - Analysis Setup - Trans
* FORMAT : .TRAN [start time] [end time] [time step]
55 .TRAN 0 600n 0.1n

```

```

* — Forces
* FORMAT — PULSE : [name] [port] [reference (0 means ground)] PULSE [low] [high] [
    delay] [fall time] [rise time] [pulse width] [period]
*
60 * FORMAT — DC      : [name] [port] [reference (0 means ground)] DC [voltage]
*

VFORCE_C1 CONTROL[1] 0 PULSE (0 1.08 40n 0.1n 0.1n 40n 80n)
VFORCE_C0 CONTROL[0] 0 PULSE (0 1.08 20n 0.1n 0.1n 20n 40n)

65 VFORCE_VDD VDD 0 DC 1.08
VFORCE_VSS VSS 0 DC 0

VFORCE_CLK CLK 0 PULSE (0 1.08 25n 0.1n 0.1n 25n 50n)

70 VFORCE_RESET RESET 0 pw1 (120n 1.08 120.1n 0 )

.SIGBUS A[15:0] VHI=1.08 VLO=0 TRISE=0.1n TFALL=0.1n TDELAY=210n THOLD=200n BASE=
    HEXA PATTERN EFAB 3FD6 P
75 .SIGBUS B[15:0] VHI=1.08 VLO=0 TRISE=0.1n TFALL=0.1n TDELAY=210n THOLD=200n BASE=
    HEXA PATTERN 8C5F 0004 P

* — Waveform Outputs
.PLOT TRAN V(COMPLETE)
80 .PLOT TRAN V(PASS)
.PLOT TRAN V(REGOUT[31])
.PLOT TRAN V(REGOUT[30])
.PLOT TRAN V(REGOUT[29])
.PLOT TRAN V(REGOUT[28])
85 .PLOT TRAN V(REGOUT[27])
.PLOT TRAN V(REGOUT[26])
.PLOT TRAN V(REGOUT[25])
.PLOT TRAN V(REGOUT[24])
.PLOT TRAN V(REGOUT[23])
90 .PLOT TRAN V(REGOUT[22])
.PLOT TRAN V(REGOUT[21])
.PLOT TRAN V(REGOUT[20])
.PLOT TRAN V(REGOUT[19])
.PLOT TRAN V(REGOUT[18])
95 .PLOT TRAN V(REGOUT[17])
.PLOT TRAN V(REGOUT[16])
.PLOT TRAN V(REGOUT[15])
.PLOT TRAN V(REGOUT[14])
.PLOT TRAN V(REGOUT[13])
100 .PLOT TRAN V(REGOUT[12])
.PLOT TRAN V(REGOUT[11])
.PLOT TRAN V(REGOUT[10])
.PLOT TRAN V(REGOUT[9])
.PLOT TRAN V(REGOUT[8])
105 .PLOT TRAN V(REGOUT[7])
.PLOT TRAN V(REGOUT[6])
.PLOT TRAN V(REGOUT[5])
.PLOT TRAN V(REGOUT[4])
.PLOT TRAN V(REGOUT[3])
110 .PLOT TRAN V(REGOUT[2])
.PLOT TRAN V(REGOUT[1])
.PLOT TRAN V(REGOUT[0])

```

```

115 .PLOT TRAN V(A[15])
.PLOT TRAN V(A[14])
.PLOT TRAN V(A[13])
.PLOT TRAN V(A[12])
.PLOT TRAN V(A[11])
.PLOT TRAN V(A[10])
.PLOT TRAN V(A[9])
120 .PLOT TRAN V(A[8])
.PLOT TRAN V(A[7])
.PLOT TRAN V(A[6])
.PLOT TRAN V(A[5])
.PLOT TRAN V(A[4])
125 .PLOT TRAN V(A[3])
.PLOT TRAN V(A[2])
.PLOT TRAN V(A[1])
.PLOT TRAN V(A[0])
.PLOT TRAN V(B[15])
130 .PLOT TRAN V(B[14])
.PLOT TRAN V(B[13])
.PLOT TRAN V(B[12])
.PLOT TRAN V(B[11])
.PLOT TRAN V(B[10])
135 .PLOT TRAN V(B[9])
.PLOT TRAN V(B[8])
.PLOT TRAN V(B[7])
.PLOT TRAN V(B[6])
.PLOT TRAN V(B[5])
140 .PLOT TRAN V(B[4])
.PLOT TRAN V(B[3])
.PLOT TRAN V(B[2])
.PLOT TRAN V(B[1])
.PLOT TRAN V(B[0])
145 .PLOT TRAN V(CLK)
.PLOT TRAN V(RESET)
.PLOT TRAN V(STARTTEST)
.PLOT TRAN V(WE)

150 * — Params
.TEMP 125

* — Power Measurement
155 .measure tran static_pwr AVG power from=220ns to=50ns
.measure tran inst_pwr MAX power from=10ns to=600ns

```

6 References

Key, Brandon A. *CMPE 260 Laboratory Exercise 3 Arithmetic Logic Unit*. CMPE 260 Laboratory Exercise 3 Arithmetic Logic Unit.

// TODO add BIST from DSD II