

CMPE-630 Digital Integrated Circuit Design
Final Project
Multiply and Accumulate (MAC) Datapath Unit Design

Brandon Key
Chris Guarini
Performed: 9 Dec 2019
Submitted: 9 Dec 2019

Instructor: Dr. Amlan Ganguly
TAs: Abhishek Vashist
Andrew Fountain
Piers Kwan

By submitting this report, you attest that you neither have given nor have received any assistance (including writing, collecting data, plotting figures, tables or graphs, or using previous student reports as a reference), and you further acknowledge that giving or receiving such assistance will result in a failing grade for this course.

Your Signature: _____

Contents

1	Abstract	4
2	Design Methodology and Theory	4
2.1	User Operation	4
2.2	Full Adder	5
2.3	Multiplier	7
2.4	16-Bit Register	9
2.5	32-Bit Register	10
2.6	MAC	11
2.7	Mux	12
2.8	LFSR	14
2.9	MISR	14
2.10	BIST	14
2.11	Schematic	14
3	Results and Analysis	32
3.1	Full Adder	33
3.2	Multiplier	33
3.3	16-Bit Register	33
3.4	32-Bit Register	34
3.5	Mux	35
3.6	LFSR	36
3.7	MISR	36
3.8	MAC with BIST Layout	36
3.9	Timing	37
3.9.1	Setup	37

3.9.2	Hold	37
3.9.3	Maximum Frequency	37
3.10	Power	37
4	Conclusion	38
5	Appendix	38
5.1	VHDL	38
5.2	Leonardo Scripts	87
5.3	SPICE	90
6	References	96

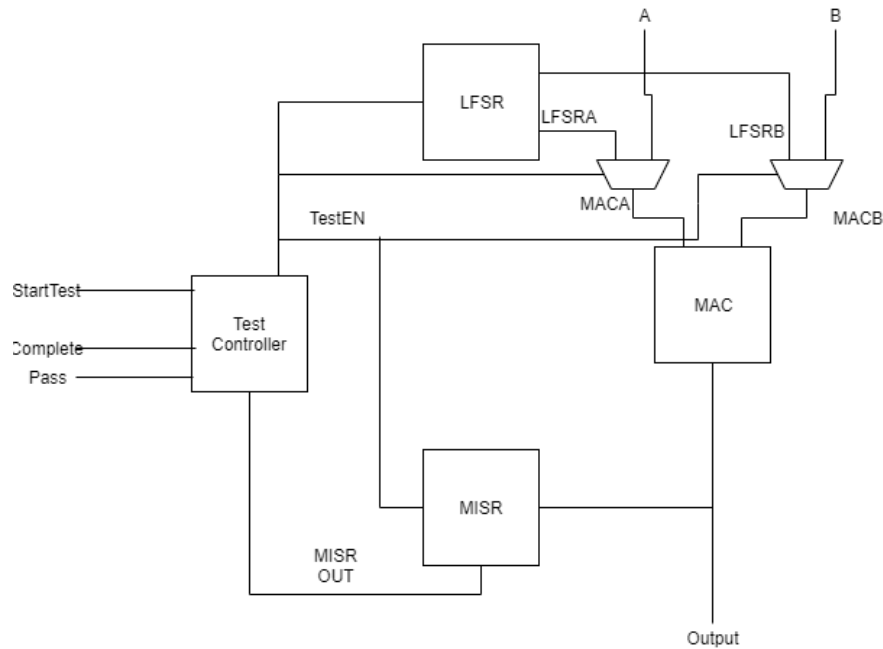


Figure 1: High Level Block Diagram of the MAC with BIST.

1 Abstract

2 Design Methodology and Theory

A cornerstone of IC design is the ability to create large, complex designs from smaller more manageable parts. The project outlined in this exercise calls for the design, testing and layout of a multiply and accumulate (MAC) unit, which takes two 16-bit inputs, multiplies them together, adds them to the value stored in a register, and then stores that output back into the register. The final component should contain a built in self test (BIST) that verifies the functionality of the MAC.

The MAC is composed of a carry-save multiplier, ripple carry full-adder, and parallel register. The BIST is implemented through the use of an LFSR for the inputs, an MISR for the output, and a test controller which controls the timing and sets the test passed and test complete outputs. A full diagram of the MAC with BIST can be seen below in Figure 1.

2.1 User Operation

//TODO Chris, talk about how to use this and go into test mode

2.2 Full Adder

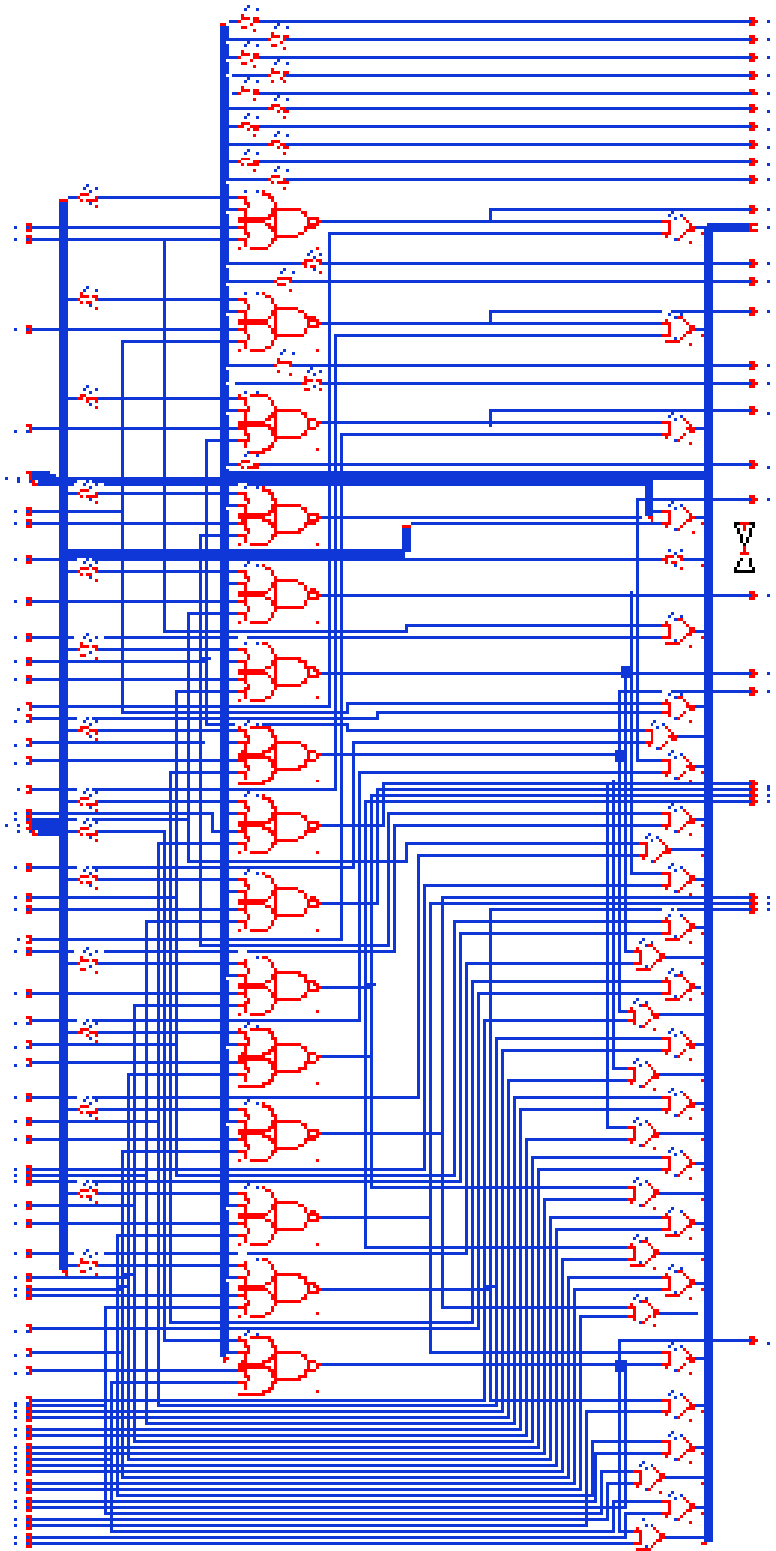


Figure 2: nBitAdder Schematic Page 1

 


Figure 3: nBitAdder Schematic Page 2

2.3 Multiplier

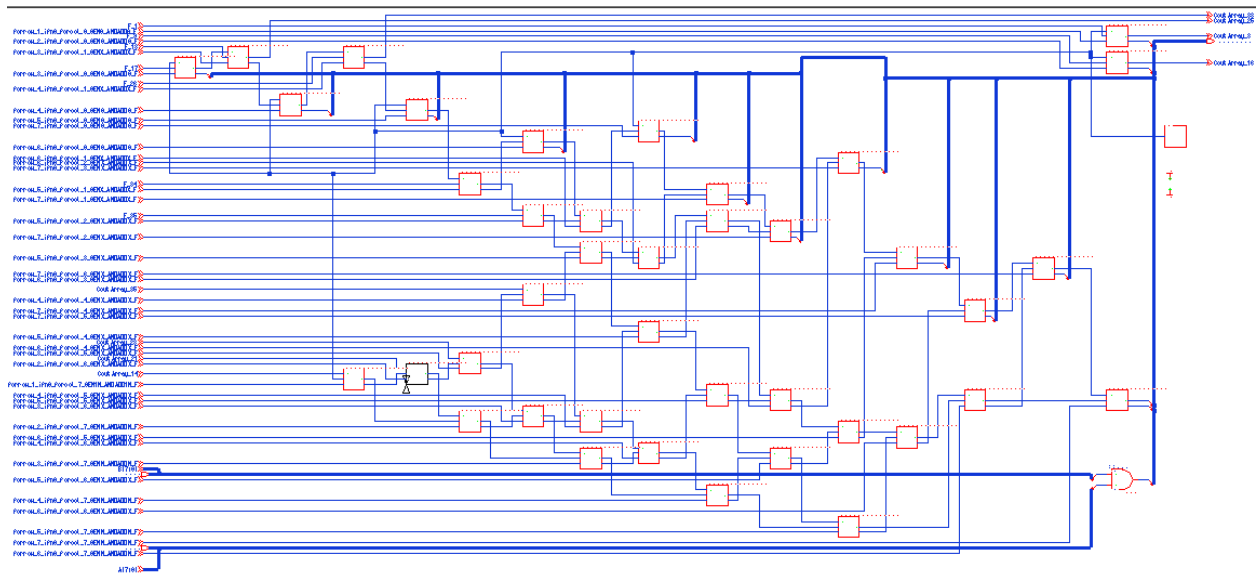


Figure 4: Multiplier Schematic Page 1

 


Figure 5: Multiplier Schematic Page 2

2.4 16-Bit Register

 


Figure 6: 16 Bit Register Schematic

2.5 32-Bit Register

 


Figure 7: 32 Bit Register Schematic

2.6 MAC

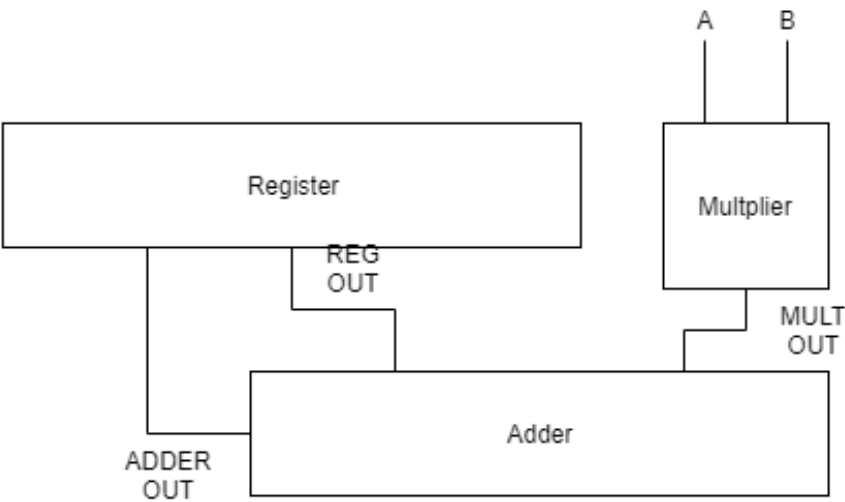


Figure 8: MAC block

 


Figure 9: MAC 16bit Test Bench

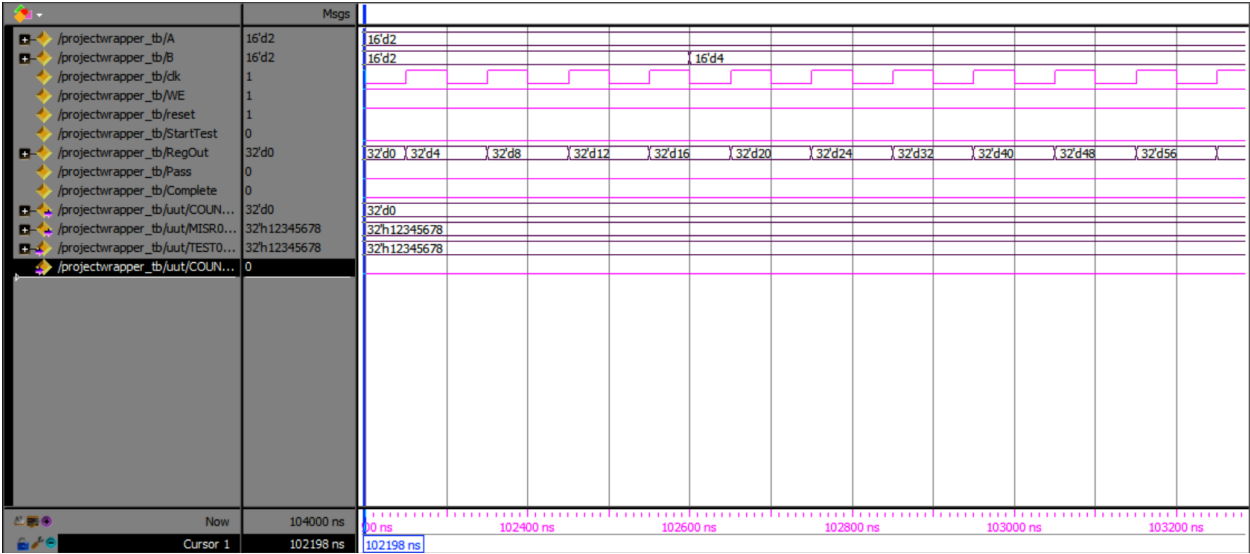


Figure 10: MAC Test Bench

2.7 Mux

The multiplexer was used to change the input from the user input to the

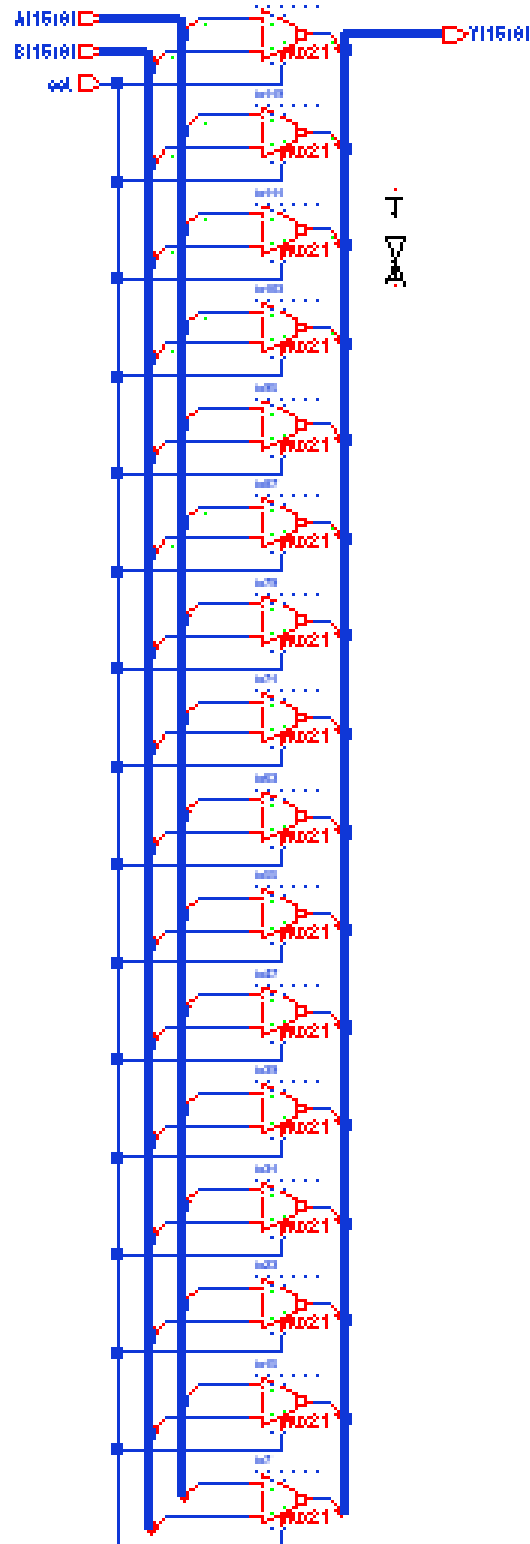


Figure 11: nBitMux 2to1 Schematic

2.8 LFSR

2.9 MISR

```
//TODO Get MISR and LFSR layoyt and schematic
```

2.10 BIST

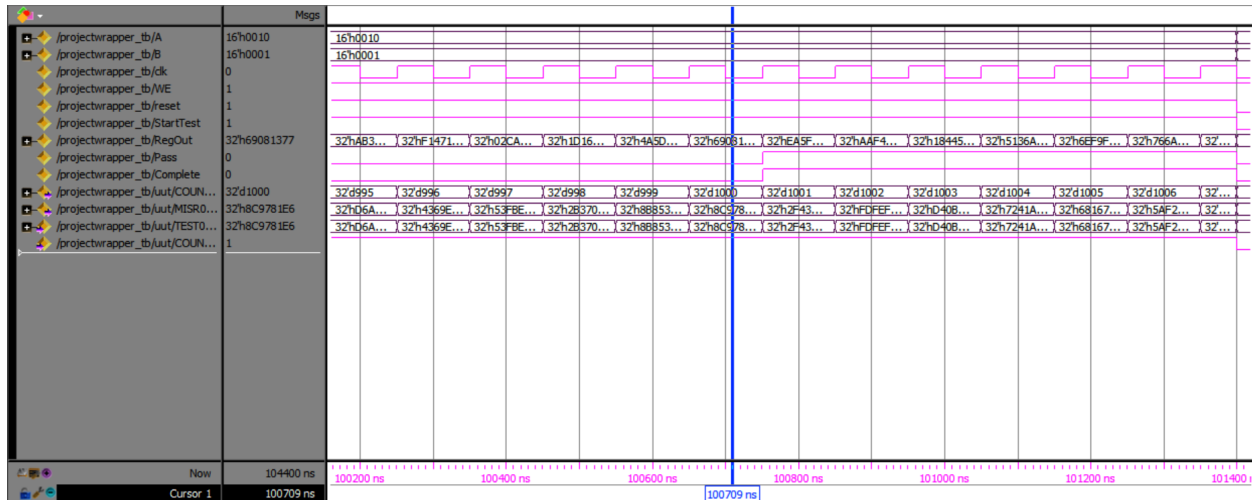


Figure 12: BIST Test Bench

2.11 Schematic

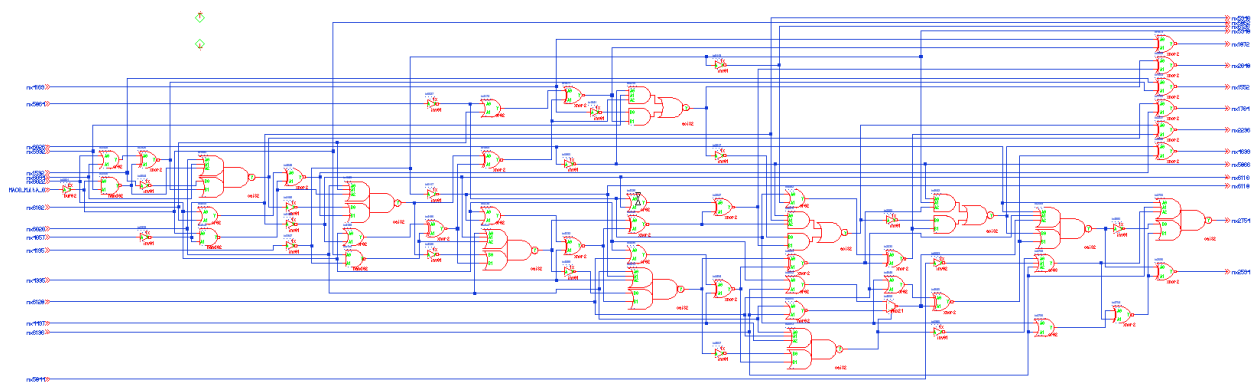


Figure 13: Full Schematic Page 1

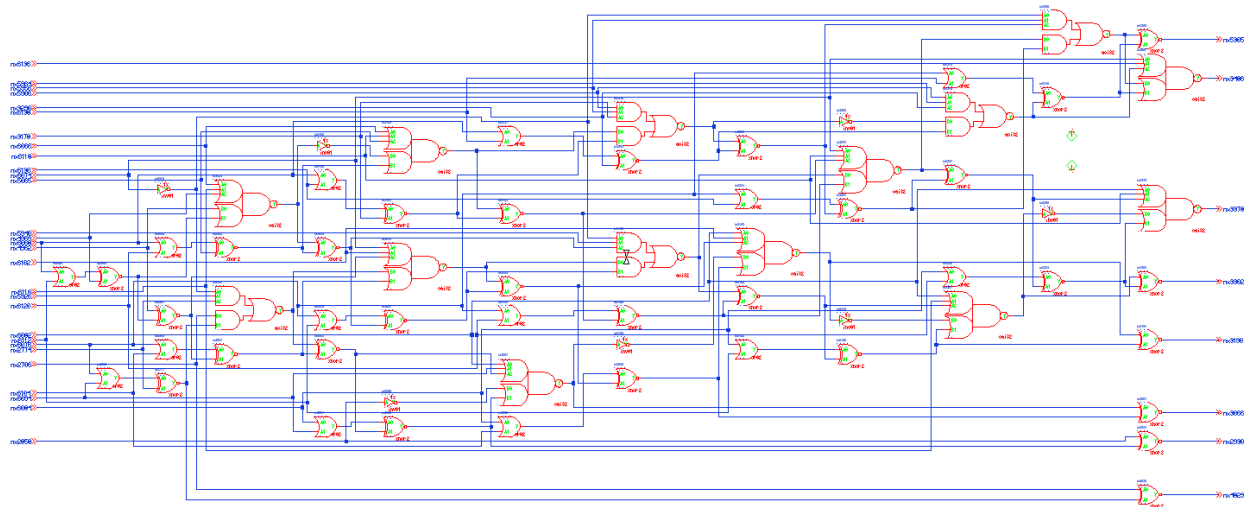


Figure 14: Full Schematic Page 2



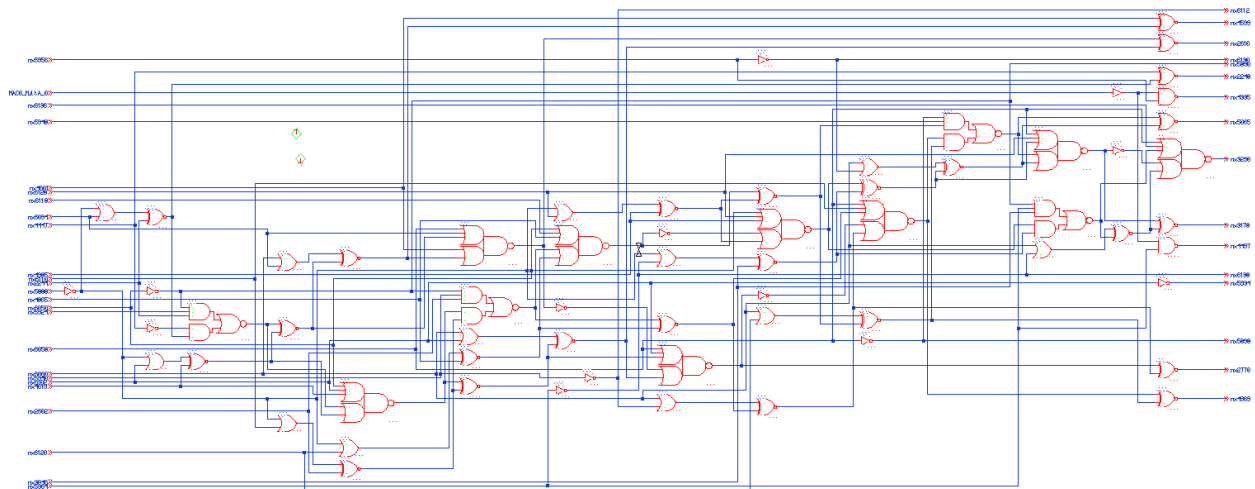


Figure 15: Full Schematic Page 3

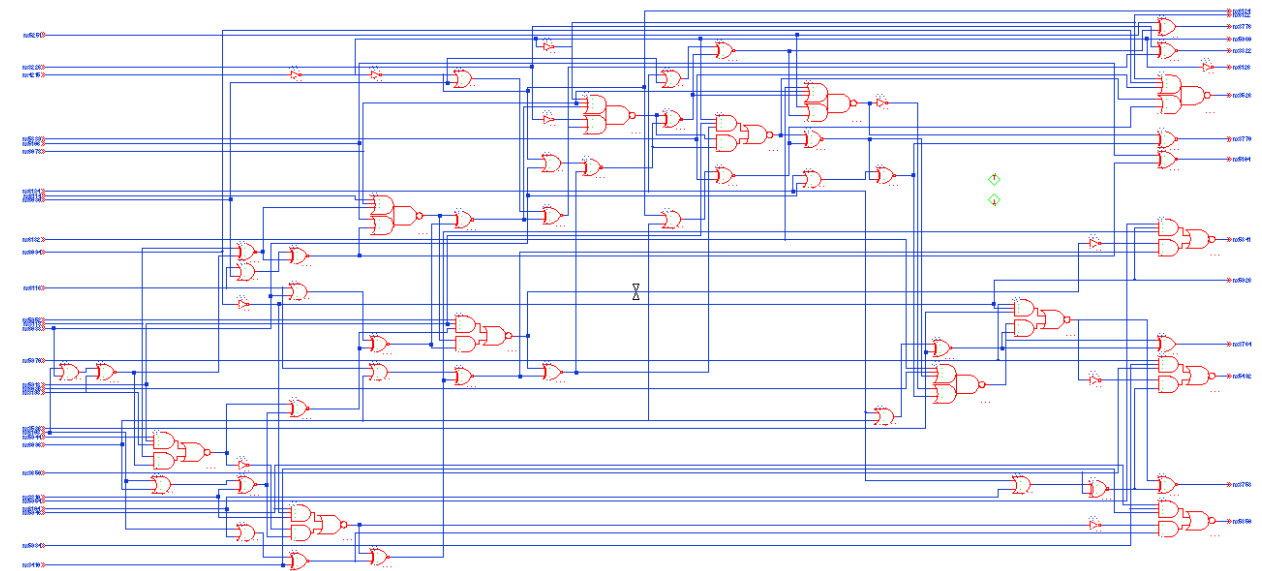

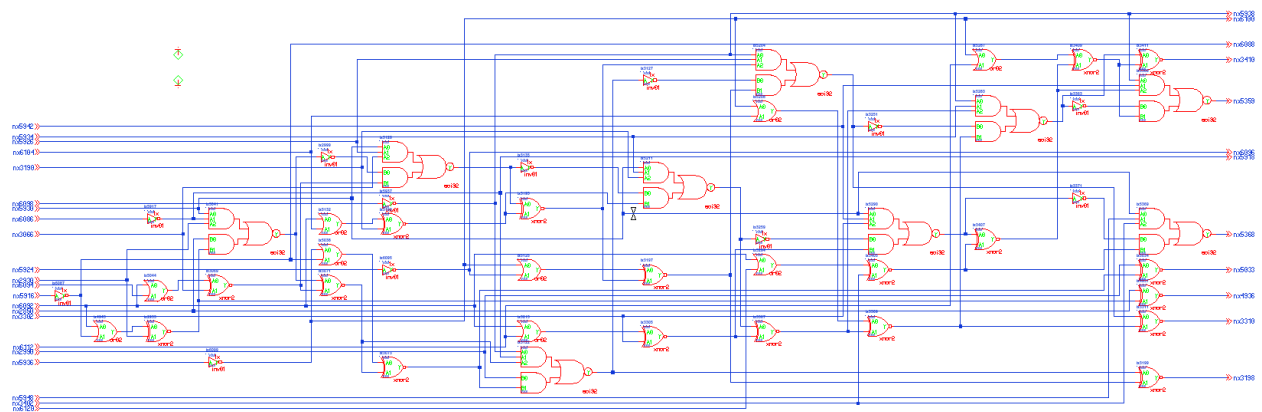

 


Figure 20: Full Schematic Page 8

 


Figure 21: Full Schematic Page 9

 


Figure 22: Full Schematic Page 10

 


Figure 23: Full Schematic Page 11

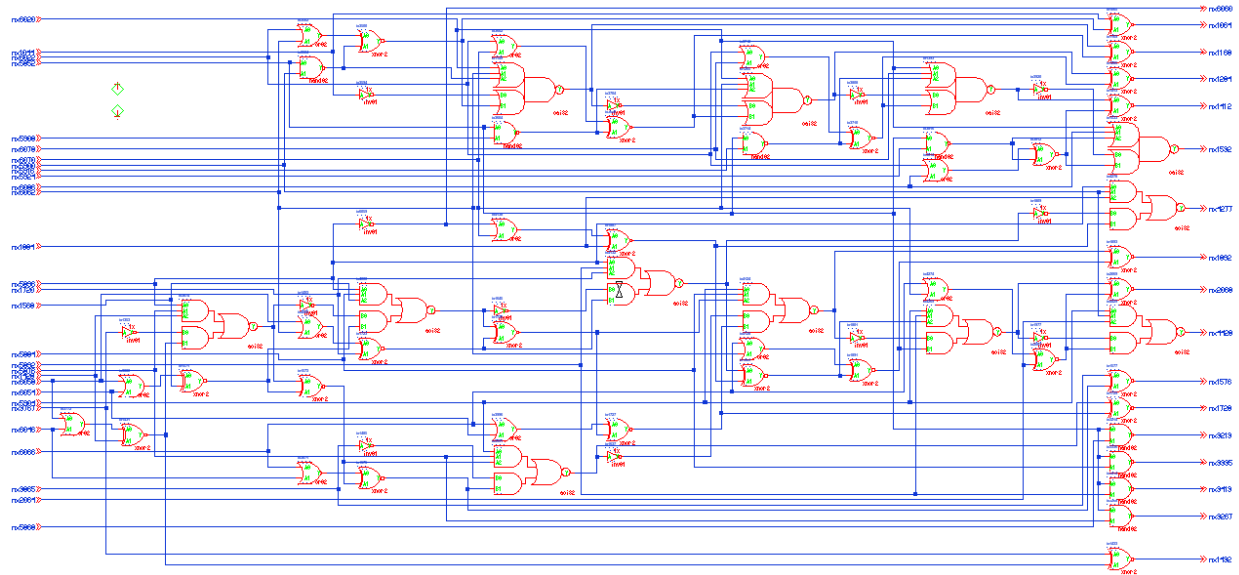


Figure 24: Full Schematic Page 12

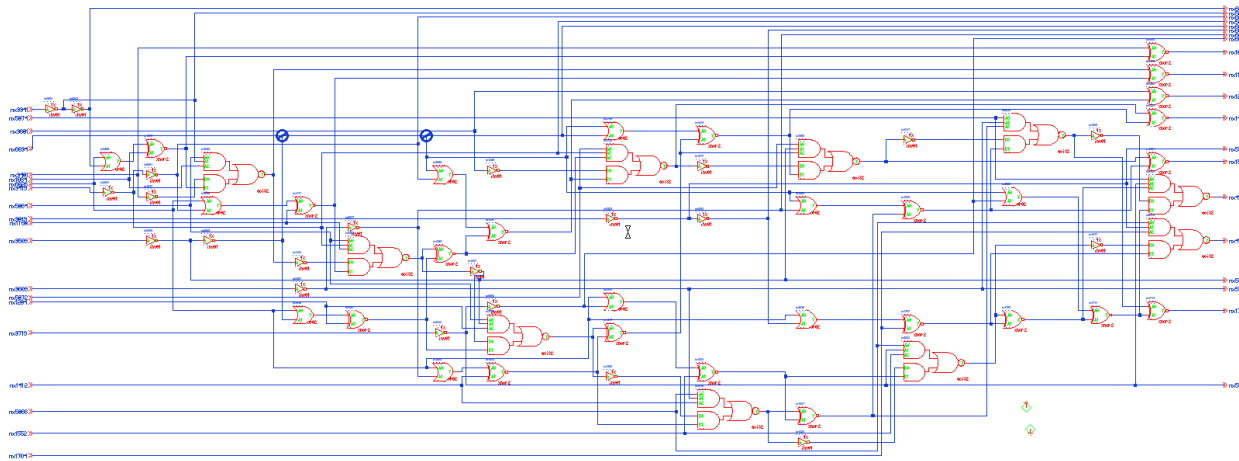


Figure 25: Full Schematic Page 13

 


Figure 26: Full Schematic Page 14

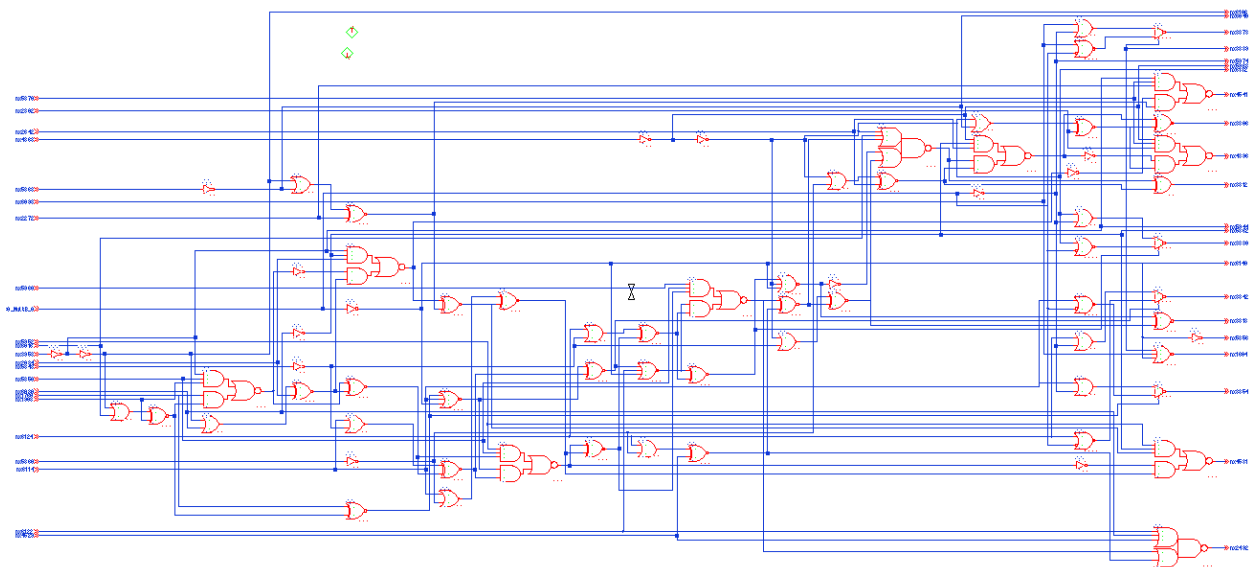


Figure 27: Full Schematic Page 15

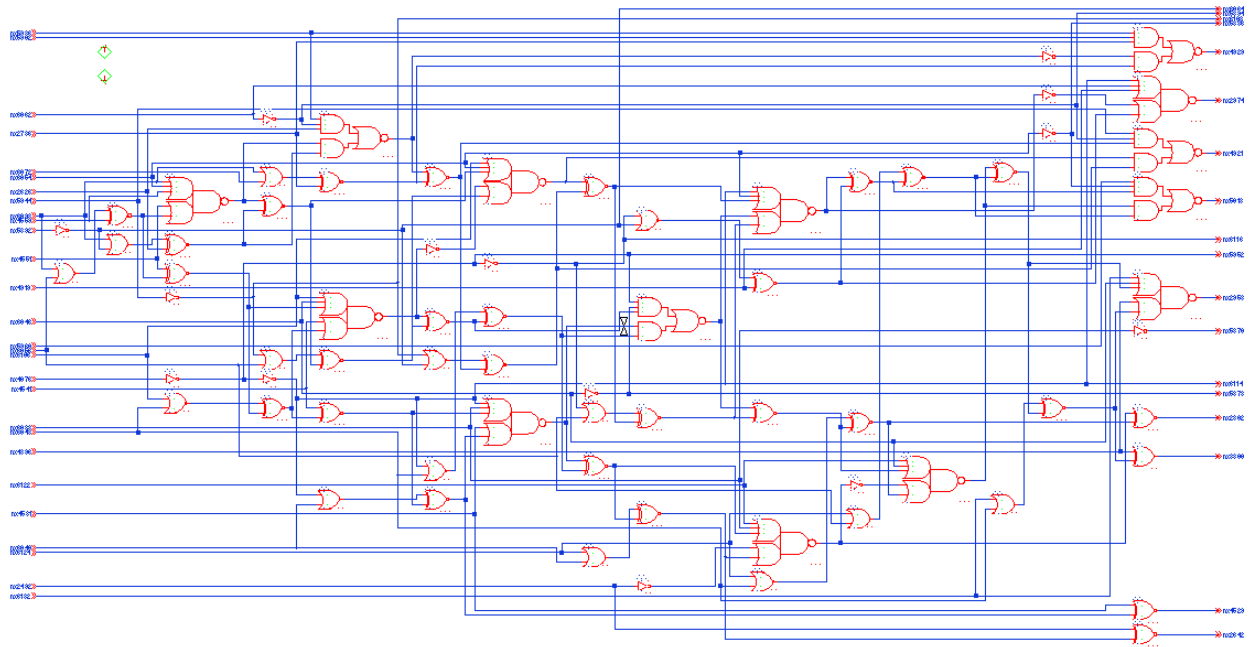


Figure 28: Full Schematic Page 16

 


Figure 29: Full Schematic Page 17

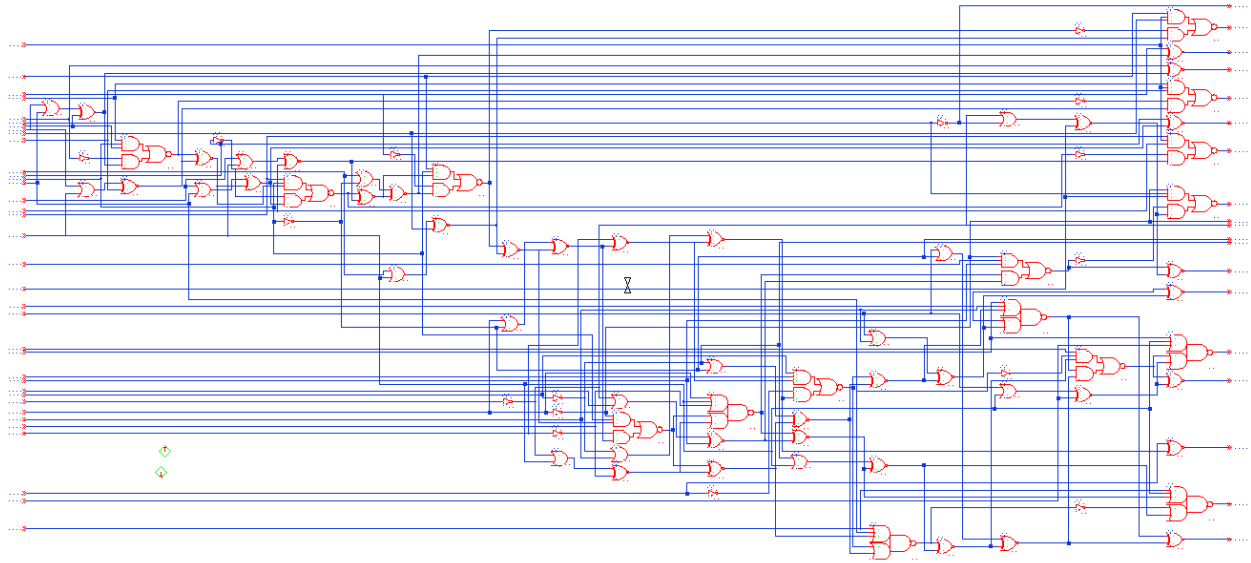


Figure 30: Full Schematic Page 18

 


Figure 31: Full Schematic Page 19

 


Figure 32: Full Schematic Page 20

 


Figure 33: Full Schematic Page 21

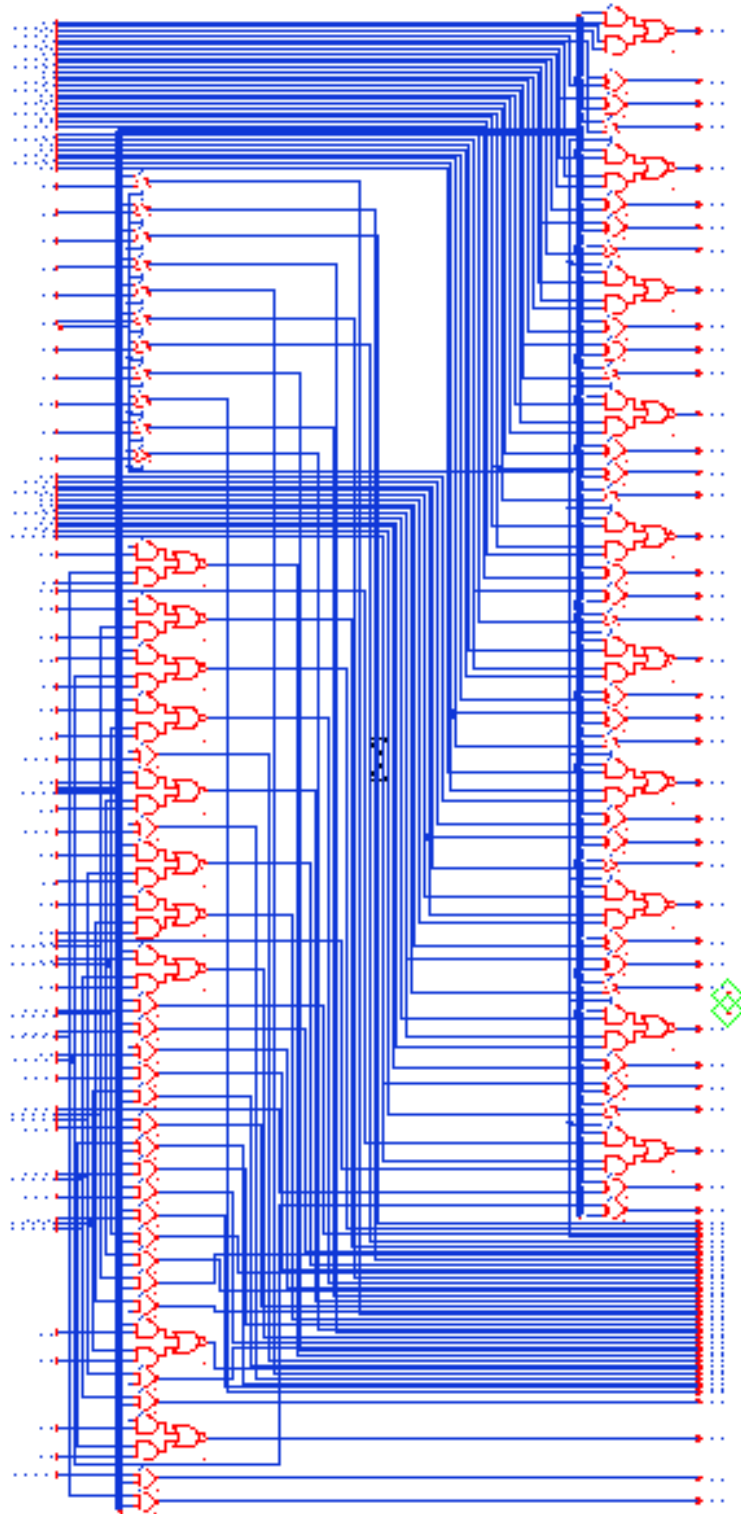


Figure 34: Full Schematic Page 22

 


Figure 35: Full Schematic Page 23

 


Figure 36: Full Schematic Page 24

 


Figure 37: Full Schematic Page 25

 


Figure 38: Full Schematic Page 26

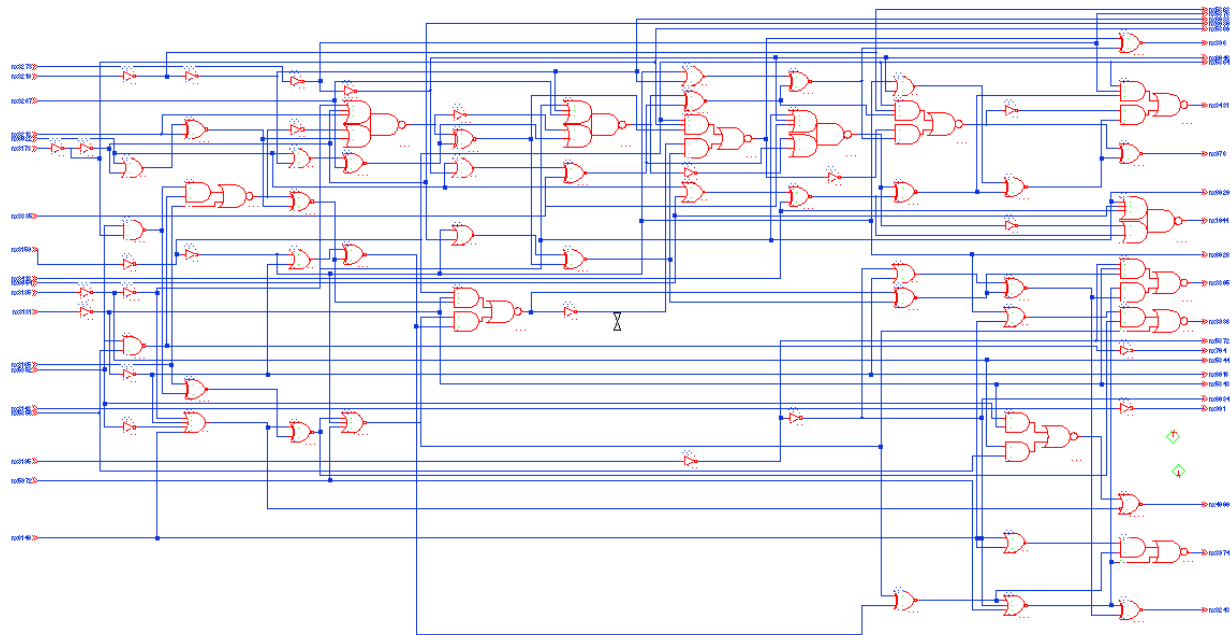


Figure 39: Full Schematic Page 27

 


Figure 40: Full Schematic Page 28

3 Results and Analysis

The MAC was initially laid out structurally; components were laid out and turned into cells that would then be connected together. This was done to limit the complexity of the final design.

3.1 Full Adder

3.2 Multiplier

3.3 16-Bit Register

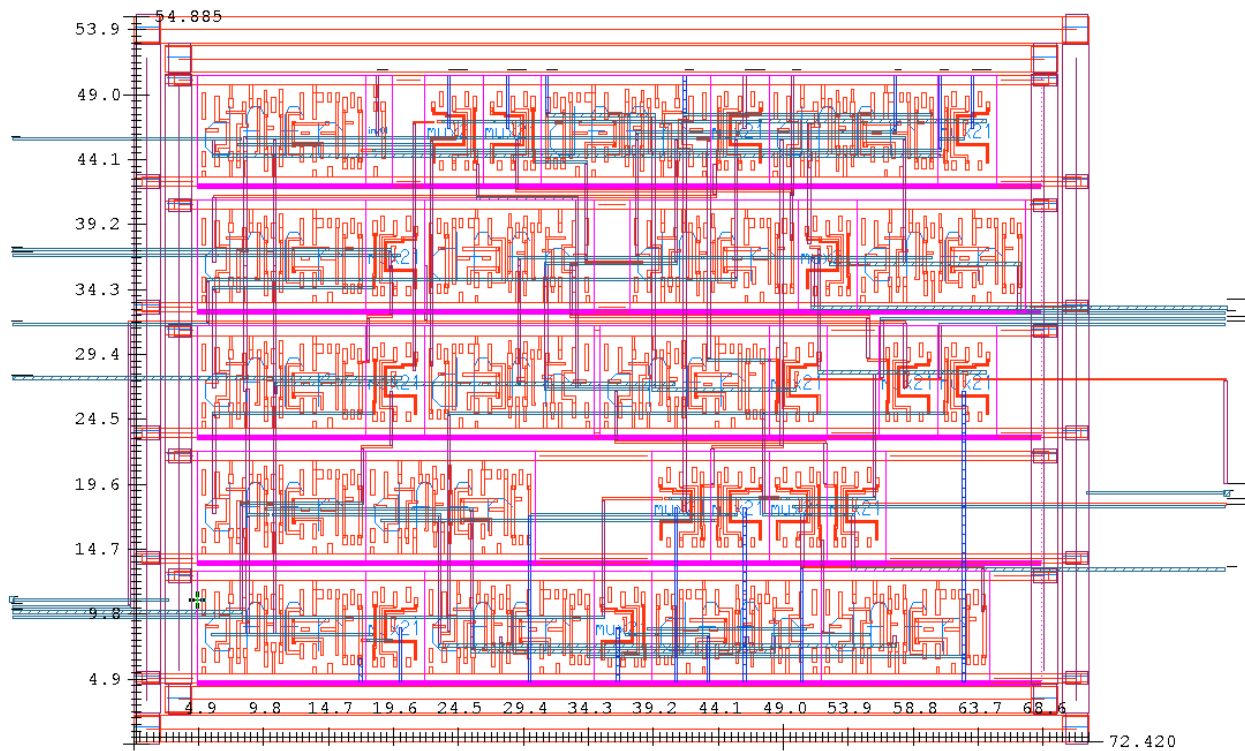


Figure 41: nBitRegister 16 Bit Layout

3.4 32-Bit Register

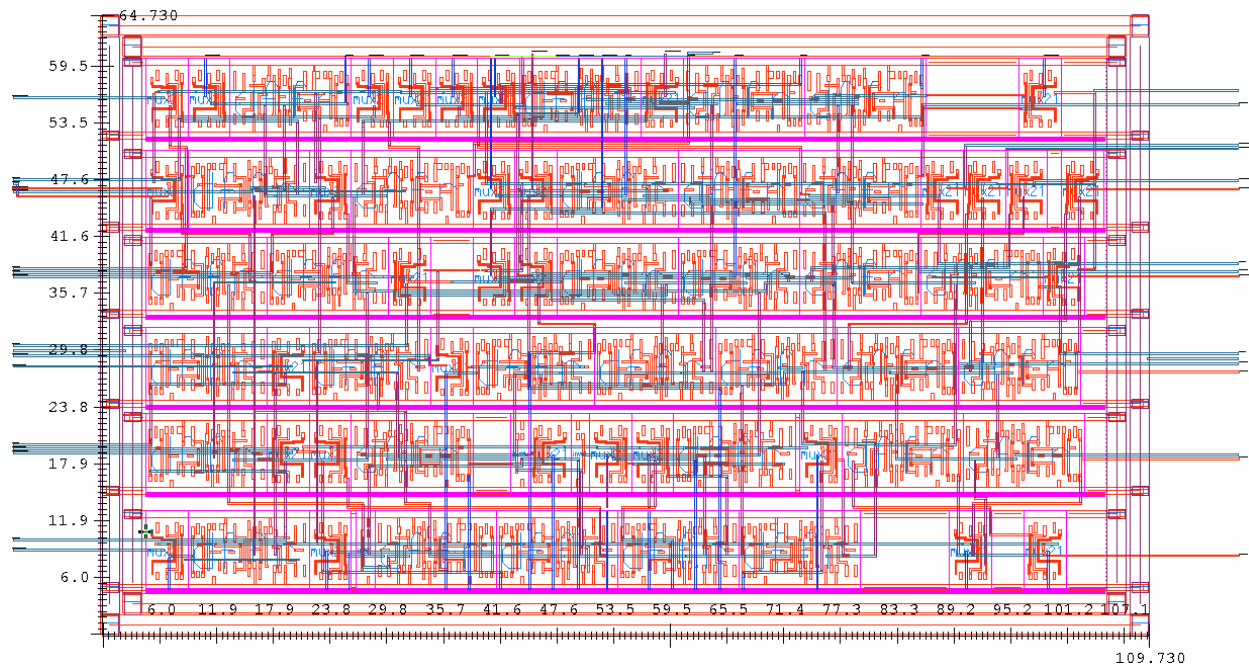


Figure 42: nBitRegister 32 Bit Layout

3.5 Mux

 


Figure 43: nBitMux 2to1 Layout

3.6 LFSR

3.7 MISR

3.8 MAC with BIST Layout

 


Figure 44: Full Layout

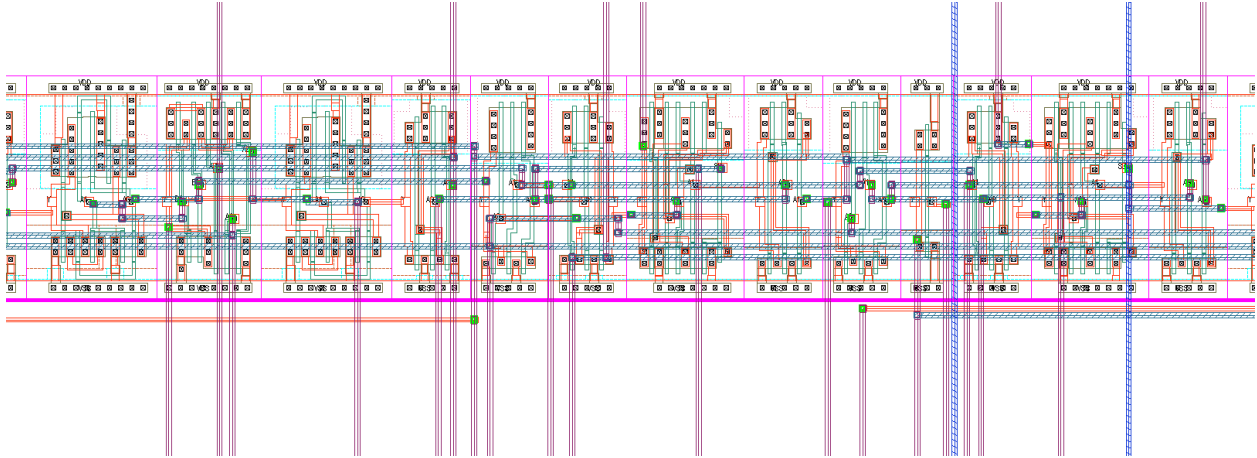


Figure 45: Full Layout Close Up View

3.9 Timing

3.9.1 Setup

3.9.2 Hold

3.9.3 Maximum Frequency

3.10 Power

Power was measured with an Eldo simulation based on the layout. To measure static power, the average power was measured while the circuit was not active but powered. The static power was measured to be 1.87nW and was recorded in Table 1.

Dynamic power was measured by recording the maximum power measured while the circuit was changing as many transistors as possible. To activate as many transistor as possible, multiple, random inputs were supplied to the circuit for a long period of time (2000us). The maximum power was found to be 16.03mW, which was recorded in Table 1.

Table 1: Simulated Power for MAC

Measured Power (W)	
Static	1.8787E-06
Dynamic	1.6029E-02

It is clear that for this circuit, dynamic power far exceeds the static power. This shows that arithmetic operations draw a lot of power. This is mostly due to their high activity factor and their high speed requirements.

4 Conclusion

5 Appendix

5.1 VHDL

Listing 1: MAC tb VHDL

```

0  -- Testbench created online at:
   -- www.doulos.com/knowhow/perl/testbench_creation/
   -- Copyright Doulos Ltd
   -- SD, 03 November 2002

5  library IEEE;
   use IEEE.Std_logic_1164.all;
   use IEEE.Numeric_Std.all;

   entity MAC_tb is
10  end;

   architecture bench of MAC_tb is

       constant N : integer := 32;

15  component MAC
       generic( N : integer := 32);
       Port ( A : in  STD_LOGIC_VECTOR ((N/2) - 1  downto 0);
             B : in  STD_LOGIC_VECTOR ((N/2) - 1  downto 0);
20             clk : in  STD_LOGIC;
             WE : in  STD_LOGIC;
             reset : in  STD_LOGIC;
             RegOut : out  STD_LOGIC_VECTOR (N-1  downto 0));
       end component;

25  signal A: STD_LOGIC_VECTOR ((N/2) - 1  downto 0);
   signal B: STD_LOGIC_VECTOR ((N/2) - 1  downto 0);
   signal clk: STD_LOGIC;
   signal WE: STD_LOGIC;
30  signal reset: STD_LOGIC;
   signal RegOut: STD_LOGIC_VECTOR (N-1  downto 0);

   begin

35  -- Insert values for generic parameters !!
   uut: MAC generic map ( N      => 32)
       port map ( A      => A,
                 B      => B,
40                 clk   => clk ,
                 WE     => WE,
                 reset  => reset ,
                 RegOut => RegOut );

       clk_proc : process
45  begin
         if clk = '0' then
             clk <= '1';

```

```

        else
            clk <= '0';
50        end if;
        wait for 50 ns;
    end process;

stimulus: process
55 begin

    -- Put initialisation code here
    WE <= '1';
    reset <= '1';
60    A <= "1111111111111111";
    B <= "1111111111111111";

    wait for 300 ns;
    WE <= '0';
65    A <= "0000000000010000";
    B <= "0000000000000001";
    wait for 300 ns;
    WE <= '1';

70    wait for 300 ns;
    B <= "0000000000000000";

    wait for 300 ns;
    reset <= '0';
75

    -- Put test bench stimulus code here

    wait;
80 end process;

end;

```

Listing 2: ProjectWrapper tb VHDL

```

0 library IEEE;
use IEEE.Std_logic_1164.all;
use IEEE.Numeric_Std.all;

entity ProjectWrapper_tb is
5 end;

architecture bench of ProjectWrapper_tb is

    constant N : integer := 32;
10

    component ProjectWrapper
        generic( N : integer := 32);
        Port ( A : in  STD_LOGIC_VECTOR ((N/2) - 1 downto 0);
              B : in  STD_LOGIC_VECTOR ((N/2) - 1 downto 0);
15        clk : in STD_LOGIC;
        WE : in STD_LOGIC;
        reset : in STD_LOGIC;
        StartTest : in STD_LOGIC;
        RegOut : out STD_LOGIC_VECTOR (N-1 downto 0);

```

```

20     Pass : out STD_LOGIC;
        Complete : out STD_LOGIC
    );
end component;

25 signal A: STD_LOGIC_VECTOR ((N/2) - 1 downto 0);
    signal B: STD_LOGIC_VECTOR ((N/2) - 1 downto 0);
    signal clk: STD_LOGIC;
    signal WE: STD_LOGIC;
    signal reset: STD_LOGIC;
30 signal StartTest: STD_LOGIC;
    signal RegOut: STD_LOGIC_VECTOR (N-1 downto 0);
    signal Pass : STD_LOGIC;
    signal Complete : STD_LOGIC;

35 begin

    -- Insert values for generic parameters !!
    uut: ProjectWrapper generic map ( N      => 32)
                        port map ( A      => A,
                                B      => B,
                                clk     => clk,
                                WE      => WE,
                                reset    => reset,
                                StartTest => StartTest,
                                RegOut   => RegOut,
                                Pass     => Pass,
                                Complete => Complete );

    clk_proc : process
50 begin
        if clk = '0' then
            clk <= '1';
        else
            clk <= '0';
55 end if;
        wait for 50 ns;
    end process;

    stimulus: process
60 begin

        -- Put initialisation code here

65        -- Put test bench stimulus code here

    -- Put initialisation code here
    WE <= '1';
    reset <= '0';
    StartTest <= '1';
    A <= "0000000000000010";
    B <= "0000000000000010";
    wait for 300 ns;
    WE <= '0';
    wait for 300 ns;
    reset <= '1';
    A <= "0000000000010000";
75

```



```

80      B <= "0000000000000001";
      WE <= '1';
      wait for 100800 ns;
      reset <= '0';
      StartTest <= '0';
85      A <= "0000000000000010";
      B <= "0000000000000010";
      wait for 600 ns;
      reset <= '1';
      wait for 600 ns;
90      B <= "0000000000000100";

      wait;
95      end process;

      end;

```

Listing 3: FullAdder VHDL

```

0  -----
  --Company      : RIT
  --Author       : Brandon Key
  --Created      : 02/18/2018
  --
5  --Project Name : Lab 3
  --File         : Full_Adder.vhd
  --
  --Entity       : Full_Adder
  --Architecture : behav
10 --
  --Tool Version : VHDL '93
  --Description  : Entity and behavioral description of a full adder
  -----
15
  library IEEE;
  use IEEE.STD_LOGIC_1164.ALL;

  entity Full_Adder is
20     port (A,B,Cin : in  std_logic;
           Sum,Cout : out std_logic
           );
  end Full_Adder;

25 architecture behav of Full_Adder is
  begin
    --uses select assignment to implement the truth table of a full adder

30     sum_proc: with std_logic_vector'(Cin&A&B) select
           Sum <= '0' when "000",
                  '1' when "001",
                  '1' when "010",
                  '0' when "011",
35                 '1' when "100",

```

```

        '0' when "101",
        '0' when "110",
        '1' when "111",
        '0' when others;

40 Cout_proc: with std_logic_vector'(Cin&A&B) select
        Cout <= '0' when "000",
        '0' when "001",
        '0' when "010",
45        '1' when "011",
        '0' when "100",
        '1' when "101",
        '1' when "110",
        '1' when "111",
50        '0' when others;

end behav;

```

Listing 4: FA 1bit VHDL

```

0  -- Company:
1  -- Engineer:
2  --
3  -- Create Date:      08:18:41 03/02/2017
4  -- Design Name:
5  -- Module Name:      FA_1bit - Behavioral
6  -- Project Name:
7  -- Target Devices:
8  -- Tool versions:
9  -- Description:
10 --
11 -- Dependencies:
12 --
13 -- Revision:
14 -- Revision 0.01 - File Created
15 -- Additional Comments:
16 --
17
18
19
20 library IEEE;
21 use IEEE.STD_LOGIC_1164.ALL;
22
23 -- Uncomment the following library declaration if using
24 -- arithmetic functions with Signed or Unsigned values
25 --use IEEE.NUMERIC_STD.ALL;
26
27 -- Uncomment the following library declaration if instantiating
28 -- any Xilinx primitives in this code.
29 --library UNISIM;
30 --use UNISIM.VComponents.all;
31
32 entity FA_1bit is
33     Port ( A : in  STD_LOGIC;
34           B : in  STD_LOGIC;
35           Cin : in  STD_LOGIC;
36           S : out STD_LOGIC;
37           Cout : out STD_LOGIC);
38 end FA_1bit;

```

```

architecture Behavioral of FA_1bit is
40
begin
    S<=((A xor B) xor Cin); --Sum
    Cout<=((A xor B) and Cin) or (A and B); --Cout
45
end Behavioral;

```

Listing 5: AND2 VHDL

```

0
-- Company:
-- Engineer:
--
-- Create Date:    15:02:42 03/15/2017
5
-- Design Name:
-- Module Name:    AND2 - Behavioral
-- Project Name:
-- Target Devices:
-- Tool versions:
10
-- Description:
--
-- Dependencies:
--
-- Revision:
15
-- Revision 0.01 - File Created
-- Additional Comments:
--

library IEEE;
20
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;
25
-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
30
entity AND2 is
    Port ( A : in  STD_LOGIC;
           B : in  STD_LOGIC;
           F : out STD_LOGIC);
35
end AND2;

architecture Behavioral of AND2 is

begin
40
    F <= A AND B;

end Behavioral;

```

Listing 6: nBitRegister VHDL

```

0
--Company      : RIT

```

```

--Author      : Brandon Key
--Created     : 2/8/2017
--
5 --Project Name : Lab 2
--File        : nBitRegister.vhd
--
--Entity      : nBitRegister
--Architecture : struct
10 --Revision    :
--Rev 0.01    : 2/8/2017
--
--Tool Version : VHDL '93
--Description  : Entity and behavioral description of an n-bit register
15 --
--Notes       :

```

```

library ieee;
20 use ieee.std_logic_1164.all;

entity nBitRegister is
    generic (n : integer := 32);
25 Port (
        nBitIn : in std_logic_vector(n-1 downto 0); -- n bits to store in the
        register
        WE      : in std_logic; -- Active high write enable
        Reset   : in std_logic; -- Async reset, disabled when low
        clk     : in std_logic;
30 Y : out std_logic_vector(n-1 downto 0) -- 1 output, n bits wide
    );
end nBitRegister;

35 architecture behav of nBitRegister is

begin

40 output_proc : process (clk, Reset) begin

        if Reset = '0' then
            Y <= (others => '0');
        elsif clk'event and clk = '1' then
45             if WE = '1' then
                Y <= nBitIn;
            end if;
        end if;

50     end process output_proc;

end behav;

```

Listing 7: Shifter VHDL

```

0 --
-- Company:

```

```

-- Engineer:
--
-- Create Date:      09:15:01 03/02/2017
5 -- Design Name:
-- Module Name:      Shifter - Behavioral
-- Project Name:
-- Target Devices:
-- Tool versions:
10 -- Description:
--
-- Dependencies:
--
-- Revision:
15 -- Revision 0.01 - File Created
-- Additional Comments:
--

```

```

library IEEE;
20 use IEEE.STD_LOGIC_1164.ALL;
use IEEE.MATHREAL.ALL;
use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if using
25 -- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
30 --library UNISIM;
--use UNISIM.VComponents.all;

entity Shifter is
    generic( N : integer:=16; Namnt : integer :=integer(ceil(log2(real(16)))));
35
    Port ( A : in  STD_LOGIC_VECTOR (N-1 downto 0);
          amnt : in  STD_LOGIC_VECTOR (Namnt-1 downto 0);
          Control : in  STD_LOGIC_VECTOR (3 downto 0);
          output : out  STD_LOGIC_VECTOR (N-1 downto 0));
40 end Shifter;

--1100 LSL
--1101 LSR
45 --1110 ASR
architecture Behavioral of Shifter is
    signal temp : integer;
begin
    proc1 : process(Control,amnt,A)
50     begin
        if control ="1101" then--LSR
            for i in integer range 0 to N-1 loop
                temp<=to_integer(unsigned(amnt));--convert amnt to unsigned integer
            for indexing
55                 if i+temp > N-1 then--bits at leftmost
                    output(i) <='0';
                else
                    output(i)<=A(i+temp);--right Shift
                end if;
            end loop;
        end loop;
    end proc1;
end Behavioral;

```

```

60      elsif control = "1100" then --LSL
        for i in integer range 0 to N-1 loop
            temp<=to_integer(unsigned(amnt));--convert amnt to unsigned integer
        for indexing
65            if i-temp < 0 then --rightmost bits
                output(i) <='0';
            else
                output(i)<=A(i-temp);--left shift
            end if;
        end loop;
70      else --ASR
        for i in integer range 0 to N-1 loop
            temp<=to_integer(unsigned(amnt));--convert amnt to unsigned integer
        for indexing
75            if A(N-1)='1' then--negative
                if i+temp > N-1 then--leftmost bits
                    output(i) <='1';--preserve the negative sign
                else
                    output(i)<=A(i+temp);-- Right Shift
                end if;
            else--Positive
80                if i+temp > N-1 then --leftmost bits
                    output(i) <='0';
                else
                    output(i)<=A(i+temp);--right shift
                end if;
85            end if;
        end loop;
    end if;
end process;
end Behavioral;

```

Listing 8: TestController VHDL

```

0  --
-- Company:
-- Engineer:
--
-- Create Date:      14:56:40 03/15/2017
5  -- Design Name:
-- Module Name:      Multiplier - Behavioral
-- Project Name:
-- Target Devices:
-- Tool versions:
10 -- Description:
--
-- Dependencies:
--
-- Revision:
15 -- Revision 0.01 - File Created
-- Additional Comments:
--
library IEEE;
20 use IEEE.STD_LOGIC_1164.ALL;
use IEEE.numeric_std.all;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

```

```

25  -- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
30  --library UNISIM;
--use UNISIM.VComponents.all;

entity TestController is
    generic( N : integer := 32);
35  Port ( clk : in STD_LOGIC;
        StartTest : in STD_LOGIC;
        reset_n : in STD_LOGIC;
        Count : in STD_LOGIC_VECTOR (N-1 downto 0);
        MISR_IN : in STD_LOGIC_VECTOR (N-1 downto 0);
40  Complete : out STD_LOGIC;
        Pass : out STD_LOGIC;
        TestEN: out STD_LOGIC
        );
end TestController;

45  architecture Datapath of TestController is

    signal complete_v, pass_v : STD_LOGIC;

50  begin

    PassProc : process (clk, reset_n) begin

        if reset_n = '0' then
85  Pass_v <= '0';
        elsif rising_edge(clk) then
            if (count = "000000000000000000000000000000001111101000" and MISR_IN = "
10001100100101111000000111100110") or Pass_v = '1' then
                Pass_v <= '1';
            else
60  Pass_v <= '0';
            end if;
        end if;
    end process;

    CompleteProc : process (clk, reset_n) begin
65  if reset_n = '0' then
        Complete_v <= '0';
        elsif rising_edge(clk) then
            if count = "000000000000000000000000000000001111101000" or Complete_v = '1' then
70  Complete_v <= '1';
            else
                Complete_v <= '0';
            end if;
        end if;
    end process;

75  TestProc : process(clk, reset_n) begin
        if reset_n = '0' then
            TestEN <= '0';
80  elsif rising_edge(clk) then
            if StartTest = '1' then

```

```

        TestEN <= '1';
    else
        TestEN <= '0';
85    end if;
    end if;
end process;

--Assign outputs
90    Complete <= Complete_v;
    Pass <= Pass_v;

95
end Datapath;

```

Listing 9: Subtractor VHDL

```

0  -- Company:
  -- Engineer:
  --
  -- Create Date:    10:15:15 03/19/2017
5  -- Design Name:
  -- Module Name:    Subtractor - Behavioral
  -- Project Name:
  -- Target Devices:
  -- Tool versions:
10 -- Description:
  --
  -- Dependencies:
  --
  -- Revision:
15 -- Revision 0.01 - File Created
  -- Additional Comments:
  --
20 library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

25 -- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

30 entity Subtractor is
    generic(N : integer :=16);
    Port ( A : in  STD_LOGIC_VECTOR (15 downto 0);
          B : in  STD_LOGIC_VECTOR (15 downto 0);
35         Output : out STD_LOGIC_VECTOR (15 downto 0));
end Subtractor;

architecture Behavioral of Subtractor is
--Component Declarations
40    --Adder, to add 1

```



```

component Ripple_Carry_FA is
  generic(N : integer :=16);--Number of bits in A and B
  Port ( A : in  STD_LOGIC_VECTOR (N-1 downto 0);
        B : in  STD_LOGIC_VECTOR (N-1 downto 0);
        Cin : in STD_LOGIC;
        Sum : out STD_LOGIC_VECTOR (N-1 downto 0);
        Cout : out STD_LOGIC);
end component;

--Logic, for bitwise not
component Logic_Unit is
  generic( N : integer :=16);
  Port ( A : in  STD_LOGIC_VECTOR (N-1 downto 0);
        B : in  STD_LOGIC_VECTOR (N-1 downto 0);
        Control : in  STD_LOGIC_VECTOR (3 downto 0);
        output : out STD_LOGIC_VECTOR (N-1 downto 0));
end component;

--Signal declarations
signal logicOut, negative : STD_LOGIC_VECTOR(N-1 downto 0);
signal logicControl : STD_LOGIC_VECTOR(3 downto 0):="1001";--Set to bitwise NOT
signal one : STD_LOGIC_VECTOR(N-1 downto 0) := "0000000000000001";
signal Cout : STD_LOGIC;--Not used

begin
--Convert Input 2 to a negative number
--Bitwise not input2
LOGIC : Logic_Unit
  generic map(N=>N)
  port map(A=>B, B=>A, Control=>logicControl, output=>logicOut);--A=>B because
  it does bitwise NOT only on A

--Add 1
ADD1 : Ripple_Carry_FA
  generic map(N=>N)
  port map(A=>logicOut, B=>one, Cin=>'0', Sum=>negative, Cout=>Cout);

--Add the positive A with the newly created negative B
ADD2 : Ripple_Carry_FA
  generic map(N=>N)
  port map(A=>A, B=>negative, Cin=>'0', Sum=>Output, Cout=>Cout);
--output now has the result of A-B

end Behavioral;

```

Listing 10: Controller VHDL

```

--Company      : RIT
--Author       : Brandon Key
--Created      : 03/29/2018
--
--Project Name : Lab 5
--File         : Controller.vhd
--
--Entity       : Controller
--Architecture : behav
--
--Tool Version : VHDL '93

```

—Description : Contoller For BIST

```

15 library IEEE;
   use IEEE.STD_LOGIC_1164.ALL;
   use IEEE.numeric_std.all;
   use IEEE.STD_LOGIC_UNSIGNED.ALL;

20 entity Controller is
    port(
        start_BIST : in std_logic;

        clk : in std_logic;
25        rst_n : in std_logic;

        is_testing : out std_logic;
        mul_input_ctrl : out std_logic;
        EN_LFSR : out std_logic;
30        rst_n_LFSR : out std_logic;
        EN_MISR : out std_logic;
        rst_n_MISR : out std_logic
    );
end Controller;

35 architecture struct of Controller is

    type state_type is (multiply, start_test, testing, test_hold);
    signal state, next_state : state_type := multiply;

40    signal counter : integer;

    begin

        —update the state to the next_state
        state_proc : process (clk, rst_n) begin
            if rst_n = '0' then
                state <= multiply;
            elsif rising_edge(clk) then
50                state <= next_state;
            end if;
        end process state_proc;

        —How to change the state
        next_state_proc : process (clk, rst_n) begin
            if rst_n = '0' then
                next_state <= multiply;
            elsif rising_edge(clk) then
                case (next_state) is
55                    when multiply =>
                        if start_BIST = '1' then
                            next_state <= start_test;
                        else
                            next_state <= multiply;
60                        end if;

                        when testing =>
                            counter <= counter + 1;
                            if counter = 255 then
65                                next_state <= test_hold;
70                                next_state <= test_hold;

```

```

        else
            next_state <= testing;
        end if;

75      when start_test =>
            next_state <= testing;
            counter <= 0;
        when test_hold =>
            if start_BIST = '1' then
80              next_state <= test_hold;
            else
                next_state <= multiply;
            end if;
        when others =>
85          next_state <= multiply;
        end case;

        end if;
    end process next_state_proc;

90    --Outputs for the states
    out_proc : process (clk) begin
        if rising_edge(clk) then
            case (state) is
95              when multiply =>
                  is_testing <= '0';
                  mul_input_ctrl <= '1';
                  EN_LFSR <= '0';
                  rst_n_LFSR <= '0';
100                 EN_MISR <= '0';
                  rst_n_MISR <= '1';

              when start_test =>
105                 is_testing <= '1';
                  mul_input_ctrl <= '0';
                  EN_LFSR <= '1';
                  rst_n_LFSR <= '1';
                  EN_MISR <= '0';
                  rst_n_MISR <= '0';

              when testing =>
110                 is_testing <= '1';
                  mul_input_ctrl <= '0';
                  EN_LFSR <= '1';
                  rst_n_LFSR <= '1';
                  EN_MISR <= '1';
                  rst_n_MISR <= '1';

              when test_hold =>
115                 is_testing <= '0';
                  mul_input_ctrl <= '0';
                  EN_LFSR <= '0';
                  rst_n_LFSR <= '1';
                  EN_MISR <= '0';
                  rst_n_MISR <= '1';

              when others =>
120                 is_testing <= '0';
                  mul_input_ctrl <= '1';
            end case;
        end if;
    end process out_proc;
end module;

```

```

130         EN_LFSR      <= '0';
            rst_n_LFSR <= '0';
            EN_MISR     <= '0';
            rst_n_MISR  <= '0';

            end case;
135     end if;
    end process out_proc;

end struct;

```

Listing 11: ProjectWrapper VHDL

```

0  library IEEE;
   use IEEE.STD_LOGIC_1164.ALL;
   use IEEE.NUMERIC_STD.ALL;

   -- Uncomment the following library declaration if using
   -- arithmetic functions with Signed or Unsigned values
5   --use IEEE.NUMERIC_STD.ALL;

   -- Uncomment the following library declaration if instantiating
   -- any Xilinx primitives in this code.
10  --library UNISIM;
   --use UNISIM.VComponents.all;

   entity ProjectWrapper is
       generic( N : integer := 32);
15   Port ( A : in  STD_LOGIC_VECTOR ((N/2) - 1 downto 0);
         B : in  STD_LOGIC_VECTOR ((N/2) - 1 downto 0);
         clk : in  STD_LOGIC;
         WE : in  STD_LOGIC;
         reset : in STD_LOGIC;
20   StartTest : in STD_LOGIC;
         RegOut : out STD_LOGIC_VECTOR (N-1 downto 0);
         Pass : out STD_LOGIC;
         Complete : out STD_LOGIC
       );
25 end ProjectWrapper;

   architecture Behavioral of ProjectWrapper is
       --COMPONENT DECLARATIONS
       component MAC is
30   generic( N : integer := 32);
       Port ( A : in  STD_LOGIC_VECTOR ((N/2) - 1 downto 0);
             B : in  STD_LOGIC_VECTOR ((N/2) - 1 downto 0);
             clk : in  STD_LOGIC;
             WE : in  STD_LOGIC;
35   reset : in  STD_LOGIC;
             RegOut : out STD_LOGIC_VECTOR (N-1 downto 0));
       end component;

       component LFSR_32_4 is
40   generic (N : integer := 32);
       port(
             clk      : in std_logic;
             rst_n    : in std_logic;
             en       : in std_logic;
45   bit_pattern : out std_logic_vector(N-1 downto 0)
       );

```

```

end component;

component MISR_32_4 is
50   generic (N : integer := 32);
   port(
       MISR_in : in std_logic_vector(N-1 downto 0);
       clk      : in std_logic;
       rst_n    : in std_logic;
55       en      : in std_logic;
       MISR_out : out std_logic_vector(N-1 downto 0)
   );
end component;

60 component nBitMux_2to1 is
   generic (n : integer := 16);
   port(
       A,B : in std_logic_vector(n-1 downto 0);
       sel : in std_logic;
65       Y  : out std_logic_vector(n-1 downto 0)
   );
end component;

component TestController is
70   generic( N : integer := 32);
   Port ( clk : in STD_LOGIC;
         StartTest : in STD_LOGIC;
         reset_n : in STD_LOGIC;
         Count : in STD_LOGIC_VECTOR (N-1 downto 0);
75         MISR_IN : in STD_LOGIC_VECTOR (N-1 downto 0);
         Complete : out STD_LOGIC;
         Pass : out STD_LOGIC;
         TestEN: out STD_LOGIC
   );
80 end component;

component Counter is
   generic( N : integer := 32);
   Port ( clk : in STD_LOGIC;
85         TestEN : in STD_LOGIC;
         reset : in STD_LOGIC;
         Count : out STD_LOGIC_VECTOR (N-1 downto 0));
end component;

90 --SIGNAL DECLARATIONS
signal MACA, MACB : STD_LOGIC_VECTOR ((N/2) - 1 downto 0);
signal MACOUT : STD_LOGIC_VECTOR (N-1 downto 0);
signal LFSROUT : std_logic_vector(N-1 downto 0);
signal MISR_out, CounterOut : std_logic_vector(N-1 downto 0);
95 signal TestEN : STD_LOGIC;

begin
    --Map those ports
    MAC0 : MAC
        generic map(N => 32)
100    port map ( A => MACA, B => MACB,
               clk => clk, WE => WE, reset => reset,
               RegOut => MACOUT);

    LFSR0 : LFSR_32_4
105    generic map (N => 32)

```

```

    port map( clk => clk , rst_n => reset , en => TestEN ,
              bit_pattern => LFSROUT);

MUXA : nBitMux_2to1
110   generic map (N => 16)
    port map (A => A, B => LFSROUT(N-1 downto N/2) ,
              sel => TestEN, Y => MACA);

MUXB : nBitMux_2to1
115   generic map (N => 16)
    port map (A => B, B => LFSROUT((N/2) - 1 downto 0) ,
              sel => TestEN, Y => MACB);

MISR0 : MISR_32_4
120   generic map(N => 32)
    port map( MISR_in => MACOUT, clk => clk ,
              rst_n => reset , en => TestEN ,
              MISR_out => MISR_out);

125   TEST0 : TestController
    generic map( N => 32)
    port map(clk => clk , StartTest => StartTest ,
              reset_n => reset , Count => CounterOut ,
              MISR_IN => MISR_out , Complete => Complete ,
130   Pass => Pass , TestEN => TestEN);

COUNT0 : Counter
    generic map( N => 32)
    port map( clk => clk , TestEN => TestEN , reset => reset ,
135   Count => CounterOut);

RegOut <= MACOUT;

end Behavioral;

```

Listing 12: Counter VHDL

```

0  ---
--- Company:
--- Engineer:
---
--- Create Date:    14:56:40 03/15/2017
5  --- Design Name:
--- Module Name:    Multiplier - Behavioral
--- Project Name:
--- Target Devices:
--- Tool versions:
10 --- Description:
---
--- Dependencies:
---
--- Revision:
15 --- Revision 0.01 - File Created
--- Additional Comments:
---
---
library IEEE;
20 use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

```

```

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
25 --use IEEE.NUMERIC.STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
30 --use UNISIM.VComponents.all;

entity Counter is
    generic( N : integer := 32);
    Port ( clk : in STD_LOGIC;
35         TestEN : in STD_LOGIC;
            reset : in STD_LOGIC;
            Count : out STD_LOGIC_VECTOR (N-1 downto 0));
end Counter;

40 architecture Behavioral of Counter is
    --COMPONENT DECLARATIONS

    component nBitAdder is
45         generic (n : integer := 32);
        port(
            A,B : in std_logic_vector(N-1 downto 0);
            Y : out std_logic_vector(N-1 downto 0);
            CB : out std_logic
50         );
    end component;

    component nBitRegister_32 is
        generic (n : integer := 32);
55         Port (
            nBitIn : in std_logic_vector(n-1 downto 0); -- n bits to store in the
            register
            WE : in std_logic; -- Active high write enable
            Reset : in std_logic; -- Async reset, disabled when low
            clk : in std_logic;
60             Y : out std_logic_vector(n-1 downto 0) -- 1 output, n bits wide
        );
    end component;

    --SIGNAL DECLARATIONS
65     signal RegOut, RegIn : STD_LOGIC_VECTOR(N-1 downto 0);
    signal cout : STD_LOGIC;

begin

70     --16 bit adder, always adds 1 to value in register
    ADDER0 : nBitAdder
        generic map(N => 32)
        port map(A => RegOut, B => "00000000000000000000000000000001", Y => RegIn,
            CB => cout);

75     --Holds the current counter value
    REG0 : nBitRegister_32
        generic map(N => 32)
        port map(nBitIn => RegIn, clk => clk, WE => TestEN, Reset => reset, Y =>

```

```

    RegOut);

80    --Map output
    Count <= RegOut;

end Behavioral;

```

Listing 13: BIST tb VHDL

```

0  -----
--Company      : RIT
--Author       : Brandon Key
--Created      : 03/29/2018
--
5  --Project Name : Lab 5
--File         : BIST_tb.vhd
--
--Entity        : BIST_tb
--Architecture  : behav
10 --
--Tool Version  : VHDL '93
--Description   : BIST
-----

LIBRARY ieee;
15 USE ieee.std_logic_1164.ALL;
   use ieee.numeric_std.all;

   -- Uncomment the following library declaration if using
   -- arithmetic functions with Signed or Unsigned values
20 --USE ieee.numeric_std.ALL;

ENTITY BIST_tb IS
END BIST_tb;

25 ARCHITECTURE behavior OF BIST_tb IS

    -- Component Declaration for the Unit Under Test (UUT)

    COMPONENT Wrapper
30     PORT(
        mul_input : IN  std_logic_vector(7 downto 0);
        start_BIST : IN  std_logic;
        disp_Sig   : IN  std_logic;
        clk        : IN  std_logic;
35        rst_n     : IN  std_logic;
        unused_anode : OUT std_logic;
        hund_anode  : OUT std_logic;
        tens_anode   : OUT std_logic;
        ones_anode   : OUT std_logic;
40        CAn : OUT std_logic;
        CBn : OUT std_logic;
        CCn : OUT std_logic;
        CDn : OUT std_logic;
        CEn : OUT std_logic;
45        CFn : OUT std_logic;
        CGn : OUT std_logic;
        is_Testing : OUT std_logic;
        mul_disp   : OUT std_logic_vector(7 downto 0);
        sig_disp   : OUT std_logic_vector(7 downto 0)
    )

```



```

50     );
    END COMPONENT;

--Inputs
55    signal mul_input : std_logic_vector(7 downto 0) := (others => '0');
    signal start_BIST : std_logic := '0';
    signal disp_Sig : std_logic := '0';
    signal clk : std_logic := '0';
    signal rst_n : std_logic := '0';

60    --Outputs
    signal unused_anode : std_logic;
    signal hund_anode : std_logic;
    signal tens_anode : std_logic;
65    signal ones_anode : std_logic;
    signal CAn : std_logic;
    signal CBn : std_logic;
    signal CCn : std_logic;
    signal CDn : std_logic;
70    signal CEn : std_logic;
    signal CFn : std_logic;
    signal CGn : std_logic;
    signal is_Testing : std_logic;
    signal mul_disp : std_logic_vector(7 downto 0);
75    signal sig_disp : std_logic_vector(7 downto 0);

-- Clock period definitions
    constant clk_period : time := 10 ns;

80 BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: Wrapper PORT MAP (
        mul_input => mul_input,
85        start_BIST => start_BIST,
        disp_Sig => disp_Sig,
        clk => clk,
        rst_n => rst_n,
        unused_anode => unused_anode,
90        hund_anode => hund_anode,
        tens_anode => tens_anode,
        ones_anode => ones_anode,
        CAn => CAn,
        CBn => CBn,
95        CCn => CCn,
        CDn => CDn,
        CEn => CEn,
        CFn => CFn,
        CGn => CGn,
100        is_Testing => is_Testing,
        mul_disp => mul_disp,
        sig_disp => sig_disp
    );

105    -- Clock process definitions
    clk_process : process
    begin
        clk <= '0';

```

```

110     wait for clk_period/2;
        clk <= '1';
        wait for clk_period/2;
    end process;

115    -- Stimulus process
    stim_proc: process
    begin
        -- hold reset state for 100 ns.
        rst_n <= '0';
120        wait for 100 ns;
        rst_n <= '1';
        wait for clk_period*3;
        -- insert stimulus here

125        start_BIST <= '1';
        wait for clk_period*10;
        start_BIST <= '0';
        wait for clk_period*30;

130        for i in 0 to 5 loop
            start_BIST <= '1';
            mul_input <= std_logic_vector(to_unsigned(i, mul_input'length));
            wait for clk_period*2;
            start_BIST <= '0';
135            wait for clk_period*2;
        end loop;

        wait for clk_period*270;

140        start_BIST <= '1';
        wait for clk_period*300;
        start_BIST <= '0';
        wait for clk_period*10;

145        wait;
    end process;

END;

```

Listing 14: Multiplier VHDL

```

0  ---
    --- Company:
    --- Engineer:
    ---
    --- Create Date:      14:56:40 03/15/2017
5  --- Design Name:
    --- Module Name:      Multiplier - Behavioral
    --- Project Name:
    --- Target Devices:
    --- Tool versions:
10 --- Description:
    ---
    --- Dependencies:
    ---
    --- Revision:
15 --- Revision 0.01 - File Created

```

```

-- Additional Comments:
--
library IEEE;
20 use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
25 --use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
30 --use UNISIM.VComponents.all;

entity Multiplier is
    generic( N : integer :=32);
    Port ( A : in  STD_LOGIC_VECTOR ((N/2)-1 downto 0);
35         B : in  STD_LOGIC_VECTOR ((N/2)-1 downto 0);
        Product : out STD_LOGIC_VECTOR (N-1 downto 0));
end Multiplier;

architecture Behavioral of Multiplier is
40 --COMPONENT DECLARATIONS
    component ANDADD is
        Port ( A : in  STD_LOGIC;
              B : in  STD_LOGIC;
              D : in  STD_LOGIC;
45              Cin : in  STD_LOGIC;
              Sum : out STD_LOGIC;
              Cout : out STD_LOGIC);
    end component;

    component AND2 is
50        Port ( A : in  STD_LOGIC;
              B : in  STD_LOGIC;
              F : out  STD_LOGIC);
    end component;
55 --SIGNAL DECLARATIONS
    signal Cin : STD_LOGIC := '0';
    signal Cout : STD_LOGIC := '0';
    signal F : STD_LOGIC_VECTOR(N*N downto 0);--interconnections within multiplier
    signal CoutArray : STD_LOGIC_VECTOR(N*N downto 0);--Signals used by the Cout
    between the 1 bit full adders
60 begin

    forrow : for i in integer range 0 to (N/2)-1 generate --Loop down the levels
        if0 : if i = 0 generate --top level, just AND gates
65            ANDOGEN : for j in integer range 0 to (N/2)-1 generate
                ANDO : AND2
                    port map(A=>A(i), B=>B(j), F=>F(j));
                end generate ANDOGEN;
                Product(0)<=F(0);--Assign first product
70            end generate if0;
            ifn0 : if i>0 generate--everything else
                forcol : for j in integer range 0 to (N/2)-1 generate

```

```

75      --Generate the first full adder / and gate combo of the row
      GEN0 : if j = 0 generate
            ANDADD0 : ANDADD
                  port map(A=>A(i), B=>B(j), D=>F((N/2)*(i-1)+(j+1)), Cin=>
Cin, Cout=>CoutArray((N/2)*i+j), Sum=>F((N/2)*i+j)); --Tons of 2D arrays as 1D
arrays
                  --D=>The sum of the full adder in the previous row and
next column (i-1) (j+1).
                  --Cout=>Corresponding coordinate in CoutArray for this
full adder [i,j].
80                  --Sum=> Corresponding coordinate in F array for this
full adder [i,j].

            --Assign the sum of the first adder of the row to its
            respective product bit
            Product(i)<=F((N/2)*i+j);
            end generate GEN0;
85

            --Last full adder of the first row, D has to be 0
            GEN1 : if i=1 AND j=((N/2)-1) generate
                  ANDADD1 : ANDADD
                        port map(A=>A(i), B=>B(j), D=>Cin, Cin=>CoutArray((N/2)*i+(
j-1)), Cout=>CoutArray((N/2)*i+j), Sum=>F((N/2)*i+j));
90                  --D=>Cin, which is equal to 0
                  --Cin=>Cout of previous full adder in same row (j-1)
                  --Cout=>Corresponding coordinate in CoutArray for
this full adder [i,j].
                  --Sum=> Corresponding coordinate in F array for this
full adder [i,j].
            end generate GEN1;
95

            --Generate the last full adder / and gate combo of the row
            GENN : if i/=1 AND j=((N/2)-1) generate
                  ANDADDN : ANDADD
                        port map(A=>A(i), B=>B(j), D=>CoutArray((N/2)*(i-1)+j), Cin
=>CoutArray((N/2)*i+(j-1)), Cout=>CoutArray((N/2)*i+j), Sum=>F((N/2)*i+j)); --Map
the last full adder in line
                        --D=>The Cout of the last full adder of the previous
row (i-1)
                        --Cin=>Cout of previous full adder in same row (j-1)
                        --Cout=>Corresponding coordinate in CoutArray for
this full adder [i,j].
                        --Sum=> Corresponding coordinate in F array for this
full adder [i,j].
100                  --Assign Sum and Cout to Product of the last row's last full
adder
            GENNI : if i=(N/2)-1 generate
                  Product(N-1)<=CoutArray((N/2)*i+j); --Product bit from
Cout
                  Product(i+j)<=F((N/2)*i+j); --Product bit from Sum
110                  end generate GENNI;
            end generate GENN;

            --Generate all the other full adders / AND gate combos
            GENX : if j/=((N/2)-1) AND j>0 generate

```

```

ANDADDDX : ANDADD
    port map(A=>A(i), B=>B(j), D=>F((N/2)*(i-1)+(j+1)), Cin
=>CoutArray((N/2)*i+(j-1)), Cout=>CoutArray((N/2)*i+j), Sum=>F((N/2)*i+j));
    --D=>The Cout of the last full adder of the previous
    row (i-1)
    --Cin=>Cout of previous full adder in same row (j-1)
    --Cout=>Corresponding coordinate in CoutArray for
120 this full adder [i,j].
    --Sum=> Corresponding coordinate in F array for this
    full adder [i,j].

    --Assign Product bits the sum bits of the last row of full
    adders
    GENXI : if i=((N/2)-1) generate
125       Product(i+j)<=F((N/2)*i+j);--Assign the sum to the
    respective product bit
        end generate GENXI;

    end generate GENX;

130
    end generate forcol;
    end generate ifn0;
    end generate forrow;

135
end Behavioral;

```

Listing 15: LFSR 32 4 VHDL

```

0  --Company      : RIT
   --Author       : Brandon Key
   --Created      : 03/08/2018
   --
5  --Project Name : Lab 5
   --File         : LFSR_32_4.vhd
   --
   --Entity       : LFSR_32_4
   --Architecture : behav
10  --
   --Tool Version : VHDL '93
   --Description  : LFSR_32_4 8 bit output, 4 tap LFSR.
   --
15  library IEEE;
   use IEEE.STD_LOGIC_1164.ALL;
   use IEEE.numeric_std.all;
   use IEEE.STD_LOGIC_UNSIGNED.ALL;

20  entity LFSR_32_4 is
    generic (N : integer := 32);
    port(
        clk      : in std_logic;
        rst_n    : in std_logic;
25        en      : in std_logic;
        bit_pattern : out std_logic_vector(N-1 downto 0)
    );
end LFSR_32_4;

```

```

30 architecture  behav of  LFSR_32_4  is

    signal internal_reg : std_logic_vector(N-1 downto 0);

    constant SEED : std_logic_vector(N-1 downto 0) := x"12345678";

35 begin

    bit_pattern <= internal_reg;

    --update the state to the next_state
    the_proc : process (clk, rst_n) begin
        if rst_n = '0' then
            internal_reg <= SEED;
        elsif rising_edge(clk) then
45             if en = '1' then
                --taps at 32,20,26,25
                internal_reg(0) <= internal_reg(1);
                internal_reg(1) <= internal_reg(2);
                internal_reg(2) <= internal_reg(3);
                internal_reg(3) <= internal_reg(4);
                internal_reg(4) <= internal_reg(5);
                internal_reg(5) <= internal_reg(6);
                internal_reg(6) <= internal_reg(7);
                internal_reg(7) <= internal_reg(8);
                internal_reg(8) <= internal_reg(9);
                internal_reg(9) <= internal_reg(10);
                internal_reg(10) <= internal_reg(11);
                internal_reg(11) <= internal_reg(12);
                internal_reg(12) <= internal_reg(13);
                internal_reg(13) <= internal_reg(14);
                internal_reg(14) <= internal_reg(15);
                internal_reg(15) <= internal_reg(16);
                internal_reg(16) <= internal_reg(17);
                internal_reg(17) <= internal_reg(18);
                internal_reg(18) <= internal_reg(19);
                internal_reg(19) <= internal_reg(20) xor internal_reg(0);
                internal_reg(20) <= internal_reg(21);
                internal_reg(21) <= internal_reg(22);
                internal_reg(22) <= internal_reg(23);
                internal_reg(23) <= internal_reg(24);
                internal_reg(24) <= internal_reg(25) xor internal_reg(0);
                internal_reg(25) <= internal_reg(26) xor internal_reg(0);
                internal_reg(26) <= internal_reg(27);
                internal_reg(27) <= internal_reg(28);
                internal_reg(28) <= internal_reg(29);
                internal_reg(29) <= internal_reg(30);
                internal_reg(30) <= internal_reg(31);
                internal_reg(31) <= internal_reg(0);

75
            end if;
        end if;
    end process the_proc;

85 end  behav;

```

Listing 16: LFSR 8 4 VHDL

```

0  ---Company      : RIT
   ---Author       : Brandon Key
   ---Created      : 03/08/2018
   ---
5  ---Project Name : Lab 5
   ---File         : LFSR_8_4.vhd
   ---
   ---Entity       : LFSR_8_4
   ---Architecture : behav
10  ---
   ---Tool Version : VHDL '93
   ---Description  : LFSR_8_4 8 bit output, 4 tap LFSR.
   ---
15  library IEEE;
   use IEEE.STD_LOGIC_1164.ALL;
   use IEEE.numeric_std.all;
   use IEEE.STD_LOGIC_UNSIGNED.ALL;
20  entity LFSR_8_4 is
      port(
          clk      : in std_logic;
          rst_n    : in std_logic;
          en       : in std_logic;
          bit_pattern : out std_logic_vector(7 downto 0)
25      );
   end LFSR_8_4;

   architecture behav of LFSR_8_4 is
30
       signal internal_reg : std_logic_vector(7 downto 0);

       constant SEED : std_logic_vector(7 downto 0) := x"6A";
35
       begin

           bit_pattern <= internal_reg;

           ---update the state to the next_state
40       the_proc : process (clk, rst_n) begin
           if rst_n = '0' then
               internal_reg <= SEED;
           elsif rising_edge(clk) then
               if en = '1' then
45                   ---taps at 7,5,4,3
                   internal_reg(0) <= internal_reg(1);
                   internal_reg(1) <= internal_reg(2);
                   internal_reg(2) <= internal_reg(3);
                   internal_reg(3) <= internal_reg(4) xor internal_reg(0);
50                   internal_reg(4) <= internal_reg(5) xor internal_reg(0);
                   internal_reg(5) <= internal_reg(6) xor internal_reg(0);
                   internal_reg(6) <= internal_reg(7);
                   internal_reg(7) <= internal_reg(0);

                   end if;
55               end if;
           end process the_proc;

```

```
end  behav ;
```

Listing 17: MAC VHDL

```

0  --- Company:
    --- Engineer:
    ---
    --- Create Date:      14:56:40 03/15/2017
    --- Design Name:
    --- Module Name:      Multiplier -- Behavioral
    --- Project Name:
    --- Target Devices:
    --- Tool versions:
    --- Description:
    ---
    --- Dependencies:
    ---
    --- Revision:
    --- Revision 0.01 -- File Created
    --- Additional Comments:
    ---
    ---
20 library IEEE;
    use IEEE.STD_LOGIC_1164.ALL;
    use IEEE.NUMERIC_STD.ALL;

    --- Uncomment the following library declaration if using
    --- arithmetic functions with Signed or Unsigned values
25 ---use IEEE.NUMERIC_STD.ALL;

    --- Uncomment the following library declaration if instantiating
    --- any Xilinx primitives in this code.
    ---library UNISIM;
30 ---use UNISIM.VComponents.all;

entity MAC is
    generic( N : integer := 32);
    Port ( A : in  STD_LOGIC_VECTOR ((N/2) - 1  downto 0);
35         B : in  STD_LOGIC_VECTOR ((N/2) - 1  downto 0);
        clk : in  STD_LOGIC;
        WE : in  STD_LOGIC;
        reset : in  STD_LOGIC;
        RegOut : out  STD_LOGIC_VECTOR (N-1  downto 0));
40 end MAC;

architecture Behavioral of MAC is
    ---COMPONENT DECLARATIONS
    component Multiplier is
45         generic( N : integer := 32);
        Port ( A : in  STD_LOGIC_VECTOR ((N/2)-1  downto 0);
            B : in  STD_LOGIC_VECTOR ((N/2)-1  downto 0);
            Product : out  STD_LOGIC_VECTOR (N-1  downto 0));
        end component;

    component nBitAdder is
50         generic (n : integer := 32);

```



```

    port(
        A,B : in  std_logic_vector(N-1 downto 0);
        Y   : out std_logic_vector(N-1 downto 0);
        CB  : out std_logic
    );
end component;

component nBitRegister is
    generic (n : integer := 32);
    Port (
        nBitIn : in std_logic_vector(n-1 downto 0); -- n bits to store in the
register
        WE      : in std_logic; -- Active high write enable
        Reset   : in std_logic; -- Async reset , disabled when low
        clk     : in std_logic;
        Y       : out std_logic_vector(n-1 downto 0) -- 1 output , n bits wide
    );
end component;

component nBitRegister_32 is
    generic (n : integer := 32);
    Port (
        nBitIn : in std_logic_vector(n-1 downto 0); -- n bits to store in the
register
        WE      : in std_logic; -- Active high write enable
        Reset   : in std_logic; -- Async reset , disabled when low
        clk     : in std_logic;
        Y       : out std_logic_vector(n-1 downto 0) -- 1 output , n bits wide
    );
end component;

component nBitRegister_16 is
    generic (n : integer := 16);
    Port (
        nBitIn : in std_logic_vector(n-1 downto 0); -- n bits to store in the
register
        WE      : in std_logic; -- Active high write enable
        Reset   : in std_logic; -- Async reset , disabled when low
        clk     : in std_logic;
        Y       : out std_logic_vector(n-1 downto 0) -- 1 output , n bits wide
    );
end component;

--SIGNAL DECLARATIONS
signal MultA,MultB : STD_LOGIC_VECTOR((N/2)-1 downto 0);
signal Product : STD_LOGIC_VECTOR(N-1 downto 0);
signal adderA, adderB, adderOut : STD_LOGIC_VECTOR(N-1 downto 0);
signal cout : STD_LOGIC;

begin

    RegMultInA : nBitRegister_16
        generic map( N => 16)
        port map(nBitIn => A,
            WE => '1', clk => clk , Reset => reset ,
            Y => MultA
        );

    RegMultInB : nBitRegister_16

```

```

110     generic map( N => 16)
port map(nBitIn => B,
        WE => '1', clk => clk, Reset => reset,
        Y=> MultB
    );

115 MULT1 : Multiplier
    generic map( N => 32)
    port map(A => MultA, B => MultB, Product => Product);

RegMultOut : nBitRegister_32
120     generic map( N => 32)
    port map(nBitIn => Product, WE => '1', Reset => reset, clk => clk, Y =>
    adderB);

BigBoyReg : nBitRegister_32
    generic map( N => 32)
125     port map(nBitIn => adderOut, WE => WE, Reset => reset, clk => clk, Y =>
    adderA);

ADD1 : nBitAdder
    generic map ( N => 32)
    port map( A => adderA, B => adderB, Y => adderOut, CB => cout);
130
    RegOut <= adderA;
end Behavioral;

```

Listing 18: MISR 32 4 VHDL

```

0  -----
--Company      : RIT
--Author       : Brandon Key
--Created      : 03/08/2018
--
5  --Project Name : Lab 5
--File         : MISR_32_4.vhd
--
--Entity       : MISR_32_4
--Architecture : behav
10 --
--Tool Version : VHDL '93
--Description  : MISR_32_4 32 bit output, 4 tap MISR.
-----

15 library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.numeric_std.all;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

20 entity MISR_32_4 is
    generic (N : integer := 32);
    port(
        MISR_in : in std_logic_vector(N-1 downto 0);
        clk      : in std_logic;
25        rst_n   : in std_logic;
        en       : in std_logic;
        MISR_out : out std_logic_vector(N-1 downto 0)
    );
end MISR_32_4;

```

```

30 architecture behav of MISR_32_4 is
35     signal internal_reg : std_logic_vector(N-1 downto 0);
36
37     constant SEED : std_logic_vector(N-1 downto 0) := x"12345678";
38
39     begin
40
41         MISR_out <= internal_reg;
42
43         --update the state to the next state
44         the_proc : process (clk, rst_n) begin
45             if rst_n = '0' then
46                 internal_reg <= SEED;
47             elsif rising_edge(clk) then
48                 if en = '1' then
49                     --taps at 32,20,26,25
50                     internal_reg(0) <= internal_reg(1) xor MISR_in(0);
51                     internal_reg(1) <= internal_reg(2) xor MISR_in(1);
52                     internal_reg(2) <= internal_reg(3) xor MISR_in(2);
53                     internal_reg(3) <= internal_reg(4) xor MISR_in(3);
54                     internal_reg(4) <= internal_reg(5) xor MISR_in(4);
55                     internal_reg(5) <= internal_reg(6) xor MISR_in(5);
56                     internal_reg(6) <= internal_reg(7) xor MISR_in(6);
57                     internal_reg(7) <= internal_reg(8) xor MISR_in(7);
58                     internal_reg(8) <= internal_reg(9) xor MISR_in(8);
59                     internal_reg(9) <= internal_reg(10) xor MISR_in(9);
60                     internal_reg(10) <= internal_reg(11) xor MISR_in(10);
61                     internal_reg(11) <= internal_reg(12) xor MISR_in(11);
62                     internal_reg(12) <= internal_reg(13) xor MISR_in(12);
63                     internal_reg(13) <= internal_reg(14) xor MISR_in(13);
64                     internal_reg(14) <= internal_reg(15) xor MISR_in(14);
65                     internal_reg(15) <= internal_reg(16) xor MISR_in(15);
66                     internal_reg(16) <= internal_reg(17) xor MISR_in(16);
67                     internal_reg(17) <= internal_reg(18) xor MISR_in(17);
68                     internal_reg(18) <= internal_reg(19) xor MISR_in(18);
69                     internal_reg(19) <= internal_reg(20) xor MISR_in(19) xor
70                     internal_reg(0);
71                     internal_reg(20) <= internal_reg(21) xor MISR_in(20);
72                     internal_reg(21) <= internal_reg(22) xor MISR_in(21);
73                     internal_reg(22) <= internal_reg(23) xor MISR_in(22);
74                     internal_reg(23) <= internal_reg(24) xor MISR_in(23);
75                     internal_reg(24) <= internal_reg(25) xor MISR_in(24) xor
76                     internal_reg(0);
77                     internal_reg(25) <= internal_reg(26) xor MISR_in(25) xor
78                     internal_reg(0);
79                     internal_reg(26) <= internal_reg(27) xor MISR_in(26);
80                     internal_reg(27) <= internal_reg(28) xor MISR_in(27);
81                     internal_reg(28) <= internal_reg(29) xor MISR_in(28);
82                     internal_reg(29) <= internal_reg(30) xor MISR_in(29);
83                     internal_reg(30) <= internal_reg(31) xor MISR_in(30);
84                     internal_reg(31) <= internal_reg(0) xor MISR_in(31);
85
86                     end if;
87                 end if;
88             end process the_proc;
89
90 end behav;

```

Listing 19: nBitRegister tb VHDL

```

0  --- Company:
1  --- Engineer:
2  ---
3  --- Create Date:    16:49:10 02/08/2018
4  --- Design Name:
5  --- Module Name:    /home/ise/DSDII/Lab/Lab2/Project/lab2/nBitRegister_tb.vhd
6  --- Project Name:   lab2
7  --- Target Device:
8  --- Tool versions:
9  --- Description:
10 ---
11 --- VHDL Test Bench Created by ISE for module: nBitRegister
12 ---
13 --- Dependencies:
14 ---
15 --- Revision:
16 --- Revision 0.01 -- File Created
17 --- Additional Comments:
18 ---
19 --- Notes:
20 --- This testbench has been automatically generated using types std_logic and
21 --- std_logic_vector for the ports of the unit under test.  Xilinx recommends
22 --- that these types always be used for the top-level I/O of a design in order
23 --- to guarantee that the testbench will bind correctly to the post-implementation
24 --- simulation model.
25 ---
26 ---
27 ---
28 ---
29 ---
30 LIBRARY ieee;
31 USE ieee.std_logic_1164.ALL;
32 use ieee.numeric_std.all;
33 ---
34 --- Uncomment the following library declaration if using
35 --- arithmetic functions with Signed or Unsigned values
36 ---USE ieee.numeric_std.ALL;
37
38 ENTITY nBitRegister_tb IS
39 END nBitRegister_tb;
40
41 ARCHITECTURE behavior OF nBitRegister_tb IS
42
43     constant N : integer := 4;
44
45     --- Component Declaration for the Unit Under Test (UUT)
46
47     COMPONENT nBitRegister
48     generic (n : integer := 32);
49     PORT(
50         nBitIn : in std_logic_vector(n-1 downto 0); -- n bits to store in the
51         register
52         WE      : in std_logic; -- Active high write enable
53         Reset   : in std_logic; -- Async reset, disabled when low
54         clk     : in std_logic;
55         Y       : out std_logic_vector(n-1 downto 0) -- 1 output, n bits wide
56     );
57     END COMPONENT;

```

```

55  --Inputs
signal nBitIn : std_logic_vector(n-1 downto 0) := (others => '0');
signal WE : std_logic := '0';
signal Reset : std_logic := '0';
60  signal clk : std_logic := '0';

    --Outputs
signal Y : std_logic_vector(n-1 downto 0);

65  -- Clock period definitions
constant clk_period : time := 100 ns;

BEGIN

    -- Instantiate the Unit Under Test (UUT)
70  uut: nBitRegister
generic map (N => N)
PORT MAP (
    nBitIn => nBitIn,
75    WE => WE,
    Reset => Reset,
    clk => clk,
    Y => Y
);

80  -- Clock process definitions
clk_process : process
begin
    clk <= '0';
85    wait for clk_period/2;
    clk <= '1';
    wait for clk_period/2;
end process;

90  -- Stimulus process
stim_proc: process
begin
    -- hold reset state for 100 ns.
95    Reset <= '0';
    wait for (1*clk_period + 15 ns);
    Reset <= '1';
    wait for clk_period*1;
    --Setup Complete, Time to load

100  --Load each register 1 by 1
    WE <= '1';
    wait for clk_period;
    nBitIn <= x"D";
105    wait for clk_period;
    WE <= '0';
    nBitIn <= x"E";
    wait for clk_period;

110    WE <= '1';
    wait for clk_period;
    for i in 0 to 15 loop

```

```

        nBitIn <= std_logic_vector(to_unsigned(i, nBitIn'length));
        wait for clk_period*1;
115    end loop;

        wait;
        end process;

120 END;
```

Listing 20: nBitAdder VHDL

```

0  -----
--Company      : RIT
--Author       : Brandon Key
--Created      : 02/18/2018
--
5  --Project Name : Lab 3
--File         : nBitAdder.vhd
--
--Entity       : nBitAdder
--Architecture : struct
10 --
--Tool Version : VHDL '93
--Description  : Entity and structural description of an adder subtractor
--              : SEL = 0 : A+B = Y
--              : SEL = 1 : A-B = Y
15 -----

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.numeric_std.all;
20 use work.globals.all;

entity nBitAdder is
    generic (n : integer := 32);
    port(
25     A,B : in  std_logic_vector(n-1 downto 0);
        Y  : out std_logic_vector(n-1 downto 0);
        CB : out std_logic
    );
end nBitAdder;
30

architecture struct of nBitAdder is

    component full_adder is
        port(A,B,Cin : in  std_logic;
35         Sum,Cout : out std_logic
        );
    end component full_adder;

    --Create an array to hold all of the carries
40    type carry_array is array (n-1 downto 0) of std_logic;
    signal c_array : carry_array;

begin

45    generate_adders : for i in 0 to n-1 generate
        i_first: if i = 0 generate
```

```

--The first adder gets SEL as the Cin
adder : full_adder port map(
50   A => A(i),
      B => B(i),
      Cin => '0',
      Sum => Y(i),
      Cout => c_array(i)
55   );
end generate i_first;

i_last : if i = (n-1) generate
--The last adder doesn't have a carry out
60   adder : full_adder port map(
      A => A(i),
      B => B(i),
      Cin => c_array(i-1),
      Sum => Y(i),
65   Cout => c_array(i)
   );
end generate i_last;

--Middle adders
70   i_mid : if (i /= 0) and (i /= (n-1)) generate
      adder : full_adder port map(
            A => A(i),
            B => B(i),
            Cin => c_array(i-1),
            Sum => Y(i),
75   Cout => c_array(i)
      );
end generate i_mid;

80   end generate generate_adders;

   CB <= c_array(n-1);

end struct;

```

Listing 21: nBitRegister 16 VHDL

```

0  --Company      : RIT
   --Author       : Brandon Key
   --Created      : 2/8/2017
   --
5  --Project Name : Lab 2
   --File         : nBitRegister_16.vhd
   --
   --Entity       : nBitRegister_16
   --Architecture : struct
10  --Revision    :
   --Rev 0.01     : 2/8/2017
   --
   --Tool Version : VHDL '93
   --Description  : Entity and behavioral description of an n-bit register
15  --Notes       :

```

```

library ieee;
20 use ieee.std_logic_1164.all;

entity nBitRegister_16 is
    generic (n : integer := 16);
25    Port (
        nBitIn : in std_logic_vector(n-1 downto 0); -- n bits to store in the
        register
        WE      : in std_logic; -- Active high write enable
        Reset   : in std_logic; -- Async reset, disabled when low
        clk     : in std_logic;
30        Y : out std_logic_vector(n-1 downto 0) -- 1 output, n bits wide
    );
end nBitRegister_16;

35 architecture behav of nBitRegister_16 is

begin

40    output_proc : process (clk, Reset) begin

        if Reset = '0' then
            Y <= (others => '0');
        elsif clk'event and clk = '1' then
45            if WE = '1' then
                Y <= nBitIn;
            end if;
        end if;

50    end process output_proc;

end behav;

```

Listing 22: MISR 8 4 VHDL

```

0  -----
--Company      : RIT
--Author       : Brandon Key
--Created      : 03/08/2018
--
5  --Project Name : Lab 5
--File         : MISR_8_4.vhd
--
--Entity       : MISR_8_4
--Architecture : behav
10 -----
--Tool Version : VHDL '93
--Description  : MISR_8_4 8 bit output, 4 tap MISR.
-----

15 library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.numeric_std.all;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

```



```

20 entity MISR_8_4 is
    port(
        MISR_in : in std_logic_vector(7 downto 0);
        clk      : in std_logic;
        rst_n    : in std_logic;
25        en      : in std_logic;
        MISR_out : out std_logic_vector(7 downto 0)
    );
end MISR_8_4;

30 architecture behav of MISR_8_4 is

    signal internal_reg : std_logic_vector(7 downto 0);

    constant SEED : std_logic_vector(7 downto 0) := x"6A";
35
    begin

        MISR_out <= internal_reg;

40        --update the state to the next_state
        the_proc : process (clk, rst_n) begin
            if rst_n = '0' then
                internal_reg <= SEED;
            elsif rising_edge(clk) then
45                if en = '1' then
                    --taps at 7,5,4,3
                    internal_reg(0) <= internal_reg(1) xor MISR_in(0);
                    internal_reg(1) <= internal_reg(2) xor MISR_in(1);
                    internal_reg(2) <= internal_reg(3) xor MISR_in(2);
                    internal_reg(3) <= internal_reg(4) xor MISR_in(3) xor
50                    internal_reg(0);
                    internal_reg(4) <= internal_reg(5) xor MISR_in(4) xor
                    internal_reg(0);
                    internal_reg(5) <= internal_reg(6) xor MISR_in(5) xor
                    internal_reg(0);
                    internal_reg(6) <= internal_reg(7) xor MISR_in(6);
                    internal_reg(7) <= internal_reg(0) xor MISR_in(7);
55                end if;
            end if;
        end process the_proc;

60 end behav;

```

Listing 23: nBitMux 2to1 VHDL

```

0  -----
--Company      : RIT
--Author       : Brandon Key
--Created      : 3/29/2018
--
5  --Project Name : Lab 5
--File         : nBitMux_2to1.vhd
--
--Entity       : nBitMux_2to1
--Architecture : Dataflow
10 -----

```

```

--Tool Version : VHDL '93
--Description  : Arbitrary width 2 to 1 mux

```

```

15 library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity nBitMux_2to1 is
    generic (n : integer := 16);
20     port (
        A,B : in  std_logic_vector(n-1 downto 0);
        sel : in  std_logic;
        Y   : out std_logic_vector(n-1 downto 0)
    );
25 end nBitMux_2to1;

architecture Dataflow of nBitMux_2to1 is
    begin
30         --update the state to the next_state
        the_proc : process (sel, A, B) begin
            case sel is
                when '0' =>
                    Y <= A;
35                 when others =>
                    Y <= B;
            end case;
        end process the_proc;
40 end Dataflow;

```

Listing 24: ANDADD VHDL

```

0  -- Company:
   -- Engineer:
   --
   -- Create Date:      15:25:28 03/15/2017
5  -- Design Name:
   -- Module Name:      ANDADD - Behavioral
   -- Project Name:
   -- Target Devices:
   -- Tool versions:
10  -- Description:
   --
   -- Dependencies:
   --
   -- Revision:
15  -- Revision 0.01 - File Created
   -- Additional Comments:
   --

```

```

20 library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;
25

```

```

-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

30 entity ANDADD is
    Port ( A : in  STD_LOGIC;
          B : in  STD_LOGIC;
          D : in  STD_LOGIC;
          Cin : in  STD_LOGIC;
          Sum : out STD_LOGIC;
          Cout : out STD_LOGIC);
35 end ANDADD;

40 architecture Behavioral of ANDADD is

    --Component Declarations
    component AND2 is
        Port ( A : in  STD_LOGIC;
              B : in  STD_LOGIC;
              F : out  STD_LOGIC);
45 end component;

    component FA_1bit is
        Port ( A : in  STD_LOGIC;
              B : in  STD_LOGIC;
              Cin : in  STD_LOGIC;
              S : out  STD_LOGIC;
              Cout : out STD_LOGIC);
50 end component;

    --Signal Assignments
    signal F : STD_LOGIC;
55 begin

    AND0 : AND2
        port map(A=>A, B=>B,F=>F);

    FA : FA_1bit
65     port map(A=>F, B=>D, Cin=>Cin, S=>Sum, Cout=>Cout);

end Behavioral;

```

Listing 25: Ripple Carry FA VHDL

```

0 --
-- Company:
-- Engineer:
--
-- Create Date:      08:27:52 03/02/2017
5 -- Design Name:
-- Module Name:      Ripple_Carry_FA - Behavioral
-- Project Name:
-- Target Devices:
-- Tool versions:
10 -- Description:
--

```

```

-- Dependencies:
--
-- Revision:
15 -- Revision 0.01 -- File Created
-- Additional Comments:
--
library IEEE;
20 use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

25 -- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

30 entity Ripple_Carry_FA is
    generic(N : integer :=16);--Number of bits in A and B
    Port ( A : in  STD_LOGIC_VECTOR (N-1 downto 0);
          B : in  STD_LOGIC_VECTOR (N-1 downto 0);
          Cin : in STD_LOGIC;
          Sum : out STD_LOGIC_VECTOR (N-1 downto 0);
          Cout : out STD_LOGIC);
35 end Ripple_Carry_FA;

40 architecture Behavioral of Ripple_Carry_FA is
    --Interim signal used for carry ins and outs of the 1 bit full adders
    --The MSB of C is carry out
    signal C : std_logic_vector(N downto 1);

    45 component FA_1bit is
        Port ( A : in  STD_LOGIC;
              B : in  STD_LOGIC;
              Cin : in  STD_LOGIC;
              S : out STD_LOGIC;
              Cout : out STD_LOGIC);
50 end component;

begin

55 GEN_ADD : for i in N-1 downto 0 generate
    --Generate the first full adder, which is special because it takes Cin
    FA0_GEN : if(i=0) generate
        FA0: FA_1bit
            port map(A=>A(i),B=>B(i), Cin=>Cin, Cout=>C(1),S=>Sum(i));
60 end generate FA0_GEN;

    --Generate the other adders, the last bit of C is carry out
    FAX_GEN : if(i>0) generate
        FAN : FA_1bit
65 port map(A=>A(i), B=>B(i), Cin=>C(i), Cout=>C(i+1), S=>Sum(i));
    end generate FAX_GEN;

    end generate GEN_ADD;
70

```

```
end Behavioral;
```

Listing 26: nBitRegister 32 VHDL

```

0  -----
   --Company      : RIT
   --Author       : Brandon Key
   --Created      : 2/8/2017
   --
   --Project Name : Lab 2
   --File         : nBitRegister_32.vhd
   --
   --Entity       : nBitRegister_32
   --Architecture : struct
10  --Revision    :
   --Rev 0.01     : 2/8/2017
   --
   --Tool Version : VHDL '93
   --Description  : Entity and behavioral description of an n-bit register
15  --
   --Notes       :
   -----

library ieee;
20 use ieee.std_logic_1164.all;

entity nBitRegister_32 is
   generic (n : integer := 32);
25   Port (
       nBitIn : in std_logic_vector(n-1 downto 0); -- n bits to store in the
       register
       WE      : in std_logic; -- Active high write enable
       Reset   : in std_logic; -- Async reset, disabled when low
       clk     : in std_logic;
30       Y : out std_logic_vector(n-1 downto 0) -- 1 output, n bits wide
   );
end nBitRegister_32;

35 architecture behav of nBitRegister_32 is

begin

40   output_proc : process (clk, Reset) begin

       if Reset = '0' then
           Y <= (others => '0');
       elsif clk'event and clk = '1' then
45           if WE = '1' then
               Y <= nBitIn;
           end if;
       end if;

50   end process output_proc;

```

```
end behav;
```

Listing 27: ALU Wrapper VHDL

```

0  --- Company:
1  --- Engineer:
2  ---
3  --- Create Date:    13:41:10 03/18/2017
4  --- Design Name:
5  --- Module Name:    ALU_Wrapper - Behavioral
6  --- Project Name:
7  --- Target Devices:
8  --- Tool versions:
9  --- Description:
10 ---
11 --- Dependencies:
12 ---
13 --- Revision:
14 --- Revision 0.01 - File Created
15 --- Additional Comments:
16 ---
17
18
19
20 library IEEE;
21 use IEEE.STD_LOGIC_1164.ALL;
22 use IEEE.MATHREAL.ALL;
23 use IEEE.NUMERIC_STD.ALL;
24
25 --- Uncomment the following library declaration if using
26 --- arithmetic functions with Signed or Unsigned values
27 ---use IEEE.NUMERIC_STD.ALL;
28
29 --- Uncomment the following library declaration if instantiating
30 --- any Xilinx primitives in this code.
31 ---library UNISIM;
32 ---use UNISIM.VComponents.all;
33
34
35 entity ALU_Wrapper is
36     Port ( input1 : in  STD_LOGIC_VECTOR (15 downto 0);
37           input2 : in  STD_LOGIC_VECTOR (15 downto 0);
38           control : in  STD_LOGIC_VECTOR (3  downto 0);
39           output  : out STD_LOGIC_VECTOR (15 downto 0));
40 end ALU_Wrapper;
41
42 architecture Behavioral of ALU_Wrapper is
43 ---Component Declarations
44     component Multiplier is
45         generic( N : integer :=16);
46         Port ( A : in  STD_LOGIC_VECTOR ((N/2)-1 downto 0);
47               B : in  STD_LOGIC_VECTOR ((N/2)-1 downto 0);
48               Product : out STD_LOGIC_VECTOR (N-1 downto 0));
49     end component;
50
51     component Logic_Unit is
52         generic( N : integer :=16);
53         Port ( A : in  STD_LOGIC_VECTOR (N-1 downto 0);
54               B : in  STD_LOGIC_VECTOR (N-1 downto 0);
55               Control : in  STD_LOGIC_VECTOR (3  downto 0);
56               output : out STD_LOGIC_VECTOR (N-1 downto 0));

```

```

55  end component;

    component Shifter is
        generic( N : integer:=16; Namnt : integer :=integer(ceil(log2(real(16)))));
60      Port ( A : in  STD_LOGIC_VECTOR (N-1 downto 0);
              amnt : in  STD_LOGIC_VECTOR (Namnt-1 downto 0);
              Control : in  STD_LOGIC_VECTOR (3 downto 0);
              output : out  STD_LOGIC_VECTOR (N-1 downto 0));
    end component;

65  component Ripple_Carry_FA is
        generic(N : integer :=16);--Number of bits in A and B
        Port ( A : in  STD_LOGIC_VECTOR (N-1 downto 0);
              B : in  STD_LOGIC_VECTOR (N-1 downto 0);
70          Cin : in STD_LOGIC;
              Sum : out  STD_LOGIC_VECTOR (N-1 downto 0);
              Cout : out  STD_LOGIC);
    end component;

75  component Subtractor is
        generic(N : integer :=16);
        Port ( A : in  STD_LOGIC_VECTOR (15 downto 0);
              B : in  STD_LOGIC_VECTOR (15 downto 0);
80          Output : out  STD_LOGIC_VECTOR (15 downto 0));
    end component;

--Signal Declarations

    signal Product, Sum, ShiftOut, LogicOut, Difference : STD_LOGIC_VECTOR(15 downto
0);
85    signal Cout : STD_LOGIC;
begin
    --map multiplier
    MULT : Multiplier
        generic map(N=>16)
90      port map(A=>input1(7 downto 0), B=>input2(7 downto 0), Product=>Product);

    --Map Logic Unit
    LOGIC : Logic_Unit
        generic map(N=>16)
95      port map( A=>input1, B=>input2, Control=>Control, output=>LogicOut);

    --Map Shifter
    SHIFT : Shifter
        generic map(N=>16, Namnt=>4)
100      port map(A=>input1, amnt=>input2(3 downto 0), Control=>Control, output=>
ShiftOut);

    --Map Adder
    ADD : Ripple_Carry_FA
        generic map(N=>16)
105      port map(A=>input1, B=>input2, Cin=>'0', Cout=>Cout, Sum=>Sum);

    --Map Subtractor
    SUB : Subtractor
        generic map(N=>16)
110      port map(A=>input1, B=>input2, Output=>Difference);

```

```

--End mapping
-----

115  ALUPROC : process(input1, input2, control) begin
        C1: case control is
            when "0100"=> output<=Sum;--ADD
            when "0101"=> output<=Difference;--SUB
            when "0110"=> output<=Product;--MUL
120      when "1100"=> output<=ShiftOut;--SLL
            when "1101"=> output<=ShiftOut;--SRL
            when "1110"=> output<=ShiftOut;--SRA
            when others=> output<=LogicOut;--OR,NOT,AND,XOR
        end case C1;
125  end process;
end Behavioral;

```

Listing 28: nBitAdderSubtractor 16Bit VHDL

```

0  -----
--Company      : RIT
--Author       : Brandon Key
--Created      : 02/18/2018
--
5  --Project Name : Lab 3
--File         : nBitAdderSubtractor_16Bit.vhd
--
--Entity       : nBitAdderSubtractor_16Bit
--Architecture : struct
10 --
--Tool Version : VHDL '93
--Description  : Entity and structural description of an adder subtractor
--              : SEL = 0 : A+B = Y
--              : SEL = 1 : A-B = Y
15 -----

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.numeric_std.all;

20  entity nBitAdderSubtractor_16Bit is
    generic (n : integer := 16);
    port(
        A,B : in  std_logic_vector(n-1 downto 0);
25      SEL : in  std_logic;
        Y  : out std_logic_vector(n-1 downto 0);
        CB : out std_logic
    );
end nBitAdderSubtractor_16Bit;

30  architecture struct of nBitAdderSubtractor_16Bit is

    component full_adder is
        port(A,B,Cin : in  std_logic;
35      Sum,Cout : out std_logic
        );
    end component full_adder;

    --Create an array to hold all of the carries
40  type carry_array is array (n-1 downto 0) of std_logic;

```



```

    signal c_array : carry_array;

    signal B_XOR_SEL : std_logic_vector( (n-1) downto 0);

45 begin

    --Generate the xor statements to be mapped to the full adders
    XORator : for i in 0 to n-1 generate
        B_XOR_SEL(i) <= B(i) xor SEL;
50 end generate XORator;

    generate_adders : for i in 0 to n-1 generate
        i_first: if i = 0 generate
            --The first adder gets SEL as the Cin
55         adder : full_adder port map(
                A => A(i),
                B => B_XOR_SEL(i),
                Cin => SEL,
                Sum => Y(i),
60             Cout => c_array(i)
            );
        end generate i_first;

        i_last : if i = (n-1) generate
65         --The last adder doesn't have a carry out
        adder : full_adder port map(
                A => A(i),
                B => B_XOR_SEL(i),
                Cin => c_array(i-1),
                Sum => Y(i),
70             Cout => c_array(i)
            );
        end generate i_last;

75         --Middle adders
        i_mid : if (i /= 0) and (i /= (n-1)) generate
            adder : full_adder port map(
                A => A(i),
                B => B_XOR_SEL(i),
80             Cin => c_array(i-1),
                Sum => Y(i),
                Cout => c_array(i)
            );
        end generate i_mid;

85     end generate generate_adders;

    CB <= c_array(n-1) xor SEL;

90 end struct;

```

Listing 29: ALU TESTBENCH VHDL

```

0  ---
--- Company:
--- Engineer:
---
--- Create Date:    10:35:10 03/19/2017
5  --- Design Name:

```

```

-- Module Name:      G:/DSD2/Lab3/Xilinx/Lab3/ALU_TESTBENCH.vhd
-- Project Name:     Lab3
-- Target Device:
-- Tool versions:
10 -- Description:
--
-- VHDL Test Bench Created by ISE for module: ALU_Wrapper
--
-- Dependencies:
15 --
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--
20 -- Notes:
-- This testbench has been automatically generated using types std_logic and
-- std_logic_vector for the ports of the unit under test.  Xilinx recommends
-- that these types always be used for the top-level I/O of a design in order
-- to guarantee that the testbench will bind correctly to the post-implementation
25 -- simulation model.

```

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

30 -- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--USE ieee.numeric_std.ALL;

ENTITY ALU_TESTBENCH IS
35 END ALU_TESTBENCH;

ARCHITECTURE behavior OF ALU_TESTBENCH IS

    -- Component Declaration for the Unit Under Test (UUT)

40
    COMPONENT ALU_Wrapper
    PORT(
        input1 : IN  std_logic_vector(15 downto 0);
        input2 : IN  std_logic_vector(15 downto 0);
45         control : IN  std_logic_vector(3 downto 0);
        output : OUT std_logic_vector(15 downto 0)
    );
    END COMPONENT;

50
    --Inputs
    signal input1 : std_logic_vector(15 downto 0) := (others => '0');
    signal input2 : std_logic_vector(15 downto 0) := (others => '0');
    signal control : std_logic_vector(3 downto 0) := (others => '0');
55
    --Outputs
    signal output : std_logic_vector(15 downto 0);
    -- No clocks detected in port list. Replace <clock> below with
    -- appropriate port name

60
BEGIN

```

```

65  -- Instantiate the Unit Under Test (UUT)
    uut: ALU_Wrapper PORT MAP (
        input1 => input1,
        input2 => input2,
        control => control,
70      output => output
    );

--0100 ADD
--0101 SUB
75 --0110 MUL
--1000 OR
--1001 NOT
--1010 AND
--1011 XOR
80 --1100 SLL
--1101 SRL
--1110 SRA

-- Stimulus process
85 stim_proc: process
begin
    -- insert stimulus here

    --Test ADD
90     control<="0100";

    --ADD1
    input1<="1010101010101010";
    input2<="0101010101010101";
95     wait for 50 ns;
    assert output="1111111111111111"
        report "ADD1 failed, expected 1111111111111111, got: " & integer'image(
            to_integer(unsigned(output)));

    --ADD2
100    input1<="1111111111111111";
    input2<="0000000000000000";
    wait for 50 ns;
    assert output="1111111111111111"
        report "ADD2 failed, expected 1111111111111111, got: " & integer'image(
            to_integer(unsigned(output)));
105    --
    --ADD3
    input1<="0000000000110011";
    input2<="000000000010010";
    --"0000000000000000"
110    wait for 50 ns;
    assert output="0000000001000101"
        report "ADD3 failed, expected 0000000001000101, got: " & integer'image(
            to_integer(unsigned(output)));

    --Test SUB
115    control<="0101";

    --SUB1
    input1<="1111111111111111";
    input2<="1111111111111111";
120    --"0000000000000000"

```

```

    wait for 50 ns;
    assert output=="0000000000000000"
        report "SUB1 failed, expected 0000000000000000, got: " & integer'image(
to_integer(unsigned(output)));

125    --SUB2
    input1<="0000000001000000";--64
    input2<="000000000010010";--18
        --"0000000000101110"--46
    wait for 50 ns;
130    assert output=="0000000000101110"
        report "SUB2 failed, expected 0000000000101110, got: " & integer'image(
to_integer(unsigned(output)));

    --SUB3
    input1<="0000000000000111";--7
135    input2<="0000000000010000";--16
        --"111111111110111"--(-)9
    wait for 50 ns;
    assert output=="111111111110111"
        report "SUB3 failed, expected 111111111110111, got: " & integer'image(
to_integer(unsigned(output)));
140

    --TEST MUL
    control<="0110";

    --MUL1
145    input1<="1111111111111111";
    input2<="0000000000000000";
        --"0000000000000000"
    wait for 50 ns;
    assert output=="0000000000000000"
150    report "MUL1 failed, expected 0000000000000000, got: " & integer'image(
to_integer(unsigned(output)));

    --MUL2
    input1<="0000000000000100";--4
155    input2<="0000000000000101";--5
        --"0000000000010100"--20
    wait for 50 ns;
    assert output=="0000000000010100"
        report "MUL2 failed, expected 0000000000010100, got: " & integer'image(
to_integer(unsigned(output)));

160    --Test OR
    control<="1000";

    --OR1
165    input1<="1111010101000011";
    input2<="0011100100110111";
        --"1111110101110111"
    wait for 50 ns;
    assert output=="0011000100000011"
        report "OR1 failed, expected 0011000100000011, got: " & integer'image(
to_integer(unsigned(output)));
170

    --TEST NOT
    control<="1001";

```

```

175      --NOT1
      input1<="1111010101000011";
      input2<="0000000000000000";
            --"0000101010111100"
      wait for 50 ns;
      assert output="0000101010111100"
180      report "NOT1 failed , expected 0000101010111100, got: " & integer'image(
to_integer(unsigned(output)));

      --TEST AND
      control<="1010";

185      --AND1
      input1<="1111010101000011";
      input2<="0011100100110111";
            --"0011000100000011"
      wait for 50 ns;
      assert output="0011000100000011"
190      report "AND1 failed , expected 0011000100000011, got: " & integer'image(
to_integer(unsigned(output)));

      --TEST XOR
      control<="1011";

195      --XOR1
      input1<="1111010101000011";
      input2<="0011100100110111";
            --"1100110001110100"
      wait for 50 ns;
      assert output="1100110001110100"
200      report "XOR1 failed , expected 1100110001110100, got: " & integer'image(
to_integer(unsigned(output)));

      --TEST SLL
      control<="1100";

205      --SLL1
      input1<="1111010101000011";
      input2<="0000000000000100";
            --"0101010000110000"
      wait for 50 ns;
      assert output="0101010000110000"
210      report "SLL1 failed , expected 0101010000110000, got: " & integer'image(
to_integer(unsigned(output)));

      --TEST SRL
      control<="1101";

215      --SRL1
      input1<="1111010101000011";
      input2<="0000000000000100";
            --"0000111101010100"
      wait for 50 ns;
      assert output="0000111101010100"
220      report "SRL1 failed , expected 0000111101010100, got: " & integer'image(
to_integer(unsigned(output)));

225      --TEST SRA
      control<="1110";

```

```

--SRA1
230  input1<="1111010101000011";
    input2<="000000000000100";
        --"1111111101010100"

    wait for 50 ns;
    assert output="1111111101010100"
235  report "SRA1 failed , expected 1111111101010100, got: " & integer'image(
    to_integer(unsigned(output)));
    wait;
end process;

END;

```

Listing 30: Logic Unit VHDL

```

0  -- Company:
    -- Engineer:
    --
    -- Create Date:      08:51:09 03/02/2017
5  -- Design Name:
    -- Module Name:      Logic_Unit - Behavioral
    -- Project Name:
    -- Target Devices:
    -- Tool versions:
10 -- Description:
    --
    -- Dependencies:
    --
    -- Revision:
15 -- Revision 0.01 - File Created
    -- Additional Comments:
    --
20 library IEEE;
    use IEEE.STD_LOGIC_1164.ALL;

    -- Uncomment the following library declaration if using
    -- arithmetic functions with Signed or Unsigned values
    --use IEEE.NUMERIC_STD.ALL;
25
    -- Uncomment the following library declaration if instantiating
    -- any Xilinx primitives in this code.
    --library UNISIM;
    --use UNISIM.VComponents.all;
30
entity Logic_Unit is
    generic( N : integer :=16);
    Port ( A : in  STD_LOGIC_VECTOR (N-1 downto 0);
          B : in  STD_LOGIC_VECTOR (N-1 downto 0);
35          Control : in  STD_LOGIC_VECTOR (3 downto 0);
          output : out STD_LOGIC_VECTOR (N-1 downto 0));
end Logic_Unit;
--Control:
--1000 : or
40 --1001 : not
    --1010 : AND
    --1011 : XOR

```

```

architecture Behavioral of Logic_Unit is
45 begin
    proc1 : process(control, A, B)
        begin
            --Depending on control, will do specific commands
            if control = "1000" then --bitwise OR
50         F0 : for i in 0 to N-1 loop
                output(i) <= A(i) OR B(i);
            end loop;

            elsif control = "1001" then --bitwise NOT
55         F1 : for i in 0 to N-1 loop
                output(i) <= NOT A(i);
            end loop;

            elsif control = "1010" then --bitwise AND
60         F2 : for i in 0 to N-1 loop
                output(i) <= A(i) AND B(i);
            end loop;

            elsif control = "1011" then --bitwise XOR
65         F3 : for i in 0 to N-1 loop
                output(i) <= A(i) XOR B(i);
            end loop;
        end if;
    end process;
70

end Behavioral;

```

5.2 Leonardo Scripts

Listing 31: Multiplier Spectrum Script

```

0 set exclude_gates {PadInC PadOut}
load_library ~/Pyxis.SPT.HEP/ic_reflibs/external_libs/GDKgates/GDKgates_utilities/
  hdl_libs/gdk.syn
read {../SourceCode/FA_1bit.vhd ../SourceCode/AND2.vhd ../SourceCode/ANDADD.vhd ../
  SourceCode/Multiplier.vhd }
ungroup * -hierarchy
set sdf_write_flat_netlist TRUE
5 optimize
write -format verilog ./Output/Multiplier.v
write -format vhdl ./Output/Multiplier.vhdl
write -format sdf ./Output/Multiplier.sdf

```

Listing 32: LFSR 32 4 Spectrum Script

```

0 set exclude_gates {PadInC PadOut}
load_library ~/Pyxis.SPT.HEP/ic_reflibs/external_libs/GDKgates/GDKgates_utilities/
  hdl_libs/gdk.syn
read {../SourceCode/LFSR_32_4.vhd }
set sdf_write_flat_netlist TRUE
optimize
5 write -format verilog ./Output/LFSR_32_4.v

```

```
write -format vhdl ./Output/LFSR_32_4.vhdl
write -format sdf ./Output/LFSR_32_4.sdf
```

Listing 33: MISR 32 4 Spectrum Script

```
0 set exclude_gates {PadInC PadOut}
load_library ~/Pyxis.SPT.HEP/ic_reflibs/external_libs/GDKgates/GDKgates_utilities/
  hdl_libs/gdk.syn
read {../SourceCode/MISR_32_4.vhd }
set sdf_write_flat_netlist TRUE
optimize
5 write -format verilog ./Output/MISR_32_4.v
write -format vhdl ./Output/MISR_32_4.vhdl
write -format sdf ./Output/MISR_32_4.sdf
```

Listing 34: ProjectWrapper Spectrum Script

```
0 set exclude_gates {PadInC PadOut}
load_library ~/Pyxis.SPT.HEP/ic_reflibs/external_libs/GDKgates/GDKgates_utilities/
  hdl_libs/gdk.syn
read {../SourceCode/AND2.vhd ../SourceCode/ANDADD.vhd ../SourceCode/FA_1bit.vhd ../
  SourceCode/FullAdder.vhd ../SourceCode/LFSR_32_4.vhd ../SourceCode/MISR_32_4.vhd
  ../SourceCode/Multiplier.vhd ../SourceCode/nBitRegister_16.vhd ../SourceCode/
  nBitRegister_32.vhd ../SourceCode/nBitAdder.vhd ../SourceCode/Counter.vhd ../
  SourceCode/TestController.vhd ../SourceCode/nBitMux_2to1.vhd ../SourceCode/MAC.
  vhd ../SourceCode/ProjectWrapper.vhd }
ungroup * -hierarchy
set sdf_write_flat_netlist TRUE
5 optimize
write -format verilog ./Output/ProjectWrapper.v
write -format vhdl ./Output/ProjectWrapper.vhdl
write -format sdf ./Output/ProjectWrapper.sdf
```

Listing 35: nBitAdder Spectrum Script

```
0 set exclude_gates {PadInC PadOut}
load_library ~/Pyxis.SPT.HEP/ic_reflibs/external_libs/GDKgates/GDKgates_utilities/
  hdl_libs/gdk.syn
read {../SourceCode/FullAdder.vhd ../SourceCode/nBitAdder.vhd }
set sdf_write_flat_netlist TRUE
optimize
5 write -format verilog ./Output/nBitAdder.v
write -format vhdl ./Output/nBitAdder.vhdl
write -format sdf ./Output/nBitAdder.sdf
```

Listing 36: nBitAdderSubtractor Spectrum Script

```
0 set exclude_gates {PadInC PadOut}
load_library ~/Pyxis.SPT.HEP/ic_reflibs/external_libs/GDKgates/GDKgates_utilities/
  hdl_libs/gdk.syn
read {../SourceCode/FullAdder.vhd ../SourceCode/nBitAdder.vhd }
set sdf_write_flat_netlist TRUE
optimize
5 write -format verilog ./Output/nBitAdder.v
write -format vhdl ./Output/nBitAdder.vhdl
write -format sdf ./Output/nBitAdder.sdf
```


Listing 37: MAC BIST Spectrum Script

```

0 set exclude_gates {PadInC PadOut}
load_library ~/Pyxis.SPT_HEP/ic_reflibs/external_libs/GDKgates/GDKgates_utilities/
  hdl_libs/gdk.syn
read {./Output/LFSR_32_4.vhdl ./Output/MISR_32_4.vhdl ./Output/nBitAdder.vhdl ./
  Output/Multiplier.vhdl ./Output/nBitRegister_16.vhdl ./Output/nBitRegister_32.
  vhdl ./Output/nBitMux_2to1.vhdl ../SourceCode/MAC.vhd }
set sdf_write_flat_netlist TRUE
optimize
5 write -format verilog ./Output/MAC.v
write -format vhdl ./Output/MAC.vhdl
write -format sdf ./Output/MAC.sdf

```

Listing 38: nBitRegister 16 Spectrum Script

```

0 set exclude_gates {PadInC PadOut}
load_library ~/Pyxis.SPT_HEP/ic_reflibs/external_libs/GDKgates/GDKgates_utilities/
  hdl_libs/gdk.syn
read {../SourceCode/nBitRegister_16.vhd }
set sdf_write_flat_netlist TRUE
optimize
5 write -format verilog ./Output/nBitRegister_16.v
write -format vhdl ./Output/nBitRegister_16.vhdl
write -format sdf ./Output/nBitRegister_16.sdf

```

Listing 39: MAC Spectrum Script

```

0 set exclude_gates {PadInC PadOut}
load_library ~/Pyxis.SPT_HEP/ic_reflibs/external_libs/GDKgates/GDKgates_utilities/
  hdl_libs/gdk.syn
read {../SourceCode/FA_1bit.vhd ../SourceCode/AND2.vhd ../SourceCode/ANDADD.vhd ../
  SourceCode/Multiplier.vhd ../SourceCode/nBitAdder.vhd ../SourceCode/
  nBitRegister_16.vhd ../SourceCode/nBitRegister_32.vhd ../SourceCode/MAC.vhd }
ungroup * -hierarchy
set sdf_write_flat_netlist TRUE
5 optimize
write -format verilog ../SourceCode/MAC.v
write -format vhd ../SourceCode/MAC.vhd
write -format sdf ../SourceCode/MAC.sdf

```

Listing 40: nBitMux 2to1 Spectrum Script

```

0 set exclude_gates {PadInC PadOut}
load_library ~/Pyxis.SPT_HEP/ic_reflibs/external_libs/GDKgates/GDKgates_utilities/
  hdl_libs/gdk.syn
read {../SourceCode/nBitMux_2to1.vhd }
set sdf_write_flat_netlist TRUE
optimize
5 write -format verilog ./Output/nBitMux_2to1.v
write -format vhdl ./Output/nBitMux_2to1.vhdl
write -format sdf ./Output/nBitMux_2to1.sdf

```

Listing 41: nBitRegister 32 Spectrum Script

```

0 set exclude_gates {PadInC PadOut}
load_library ~/Pyxis.SPT_HEP/ic_reflibs/external_libs/GDKgates/GDKgates_utilities/
  hdl_libs/gdk.syn
read {../SourceCode/nBitRegister_32.vhd }

```

```

set sdf_write_flat_netlist TRUE
optimize
5 write -format verilog ./Output/nBitRegister_32.v
write -format vhdl ./Output/nBitRegister_32.vhdl
write -format sdf ./Output/nBitRegister_32.sdf

```

Listing 42: MAC (copy) Spectrum Script

```

0 set exclude_gates {PadInC PadOut}
load_library ~/Pyxis_SPT_HEP/ic_reflibs/external_libs/GDKgates/GDKgates_utilities/
    hdl_libs/gdk.syn
read {./Output/nBitAdder.vhdl ./Output/Multiplier.vhdl ./Output/nBitRegister_16.vhdl
    ./Output/nBitRegister_32.vhdl ../SourceCode/MAC.vhd }
set sdf_write_flat_netlist TRUE
optimize
5 write -format verilog ./Output/MAC.v
write -format vhdl ./Output/MAC.vhdl
write -format sdf ./Output/MAC.sdf

```

5.3 SPICE

Listing 43: layout test SPICE

```

0 * Example circuit file for simulating PEX

.OPTION DOINODE
.HIER /

5 .INCLUDE "/home/bxk5113/Pyxis_SPT_HEP/ic_projects/Pyxis_SPT/digicdesign/
    ProjectWrapper/ProjectWrapper.cal/ProjectWrapper.pex.netlist"

.LIB /home/bxk5113/Pyxis_SPT_HEP/ic_reflibs/tech_libs/generic13/models/lib.eldo TT

* - Instantiate your parasitic netlist and add the load capacitor
10 ** FORMAT :
* XLAYOUT [all inputs as listed by the ".subckt" line in the included netlist, in
    the order that they appear there] [name of the subcircuit as listed in the
    included netlist]
XLAYOUT COMPLETE PASS REGOUT[31] REGOUT[30] REGOUT[29] REGOUT[28] REGOUT[27] REGOUT
    [26] REGOUT[25] REGOUT[24] REGOUT[23] REGOUT[22] REGOUT[21] REGOUT[20] REGOUT[19]
    REGOUT[18] REGOUT[17] REGOUT[16] REGOUT[15] REGOUT[14] REGOUT[13] REGOUT[12]
    REGOUT[11] REGOUT[10] REGOUT[9] REGOUT[8] REGOUT[7] REGOUT[6] REGOUT[5] REGOUT[4]
    REGOUT[3] REGOUT[2] REGOUT[1] REGOUT[0] A[15] A[14] A[13] A[12] A[11] A[10] A[9]
    A[8] A[7] A[6] A[5] A[4] A[3] A[2] A[1] A[0] B[15] B[14] B[13] B[12] B[11] B[10]
    B[9] B[8] B[7] B[6] B[5] B[4] B[3] B[2] B[1] B[0] CLK RESET STARTTEST WE
    ProjectWrapper

* Output Capacitance
15 C.REGOUT[31] REGOUT[31] 0 120f
C.REGOUT[30] REGOUT[30] 0 120f
C.REGOUT[29] REGOUT[29] 0 120f
C.REGOUT[28] REGOUT[28] 0 120f
C.REGOUT[27] REGOUT[27] 0 120f
20 C.REGOUT[26] REGOUT[26] 0 120f
C.REGOUT[25] REGOUT[25] 0 120f
C.REGOUT[24] REGOUT[24] 0 120f

```

```

C.REGOUT[23] REGOUT[23] 0 120 f
C.REGOUT[22] REGOUT[22] 0 120 f
25 C.REGOUT[21] REGOUT[21] 0 120 f
C.REGOUT[20] REGOUT[20] 0 120 f
C.REGOUT[19] REGOUT[19] 0 120 f
C.REGOUT[18] REGOUT[18] 0 120 f
C.REGOUT[17] REGOUT[17] 0 120 f
30 C.REGOUT[16] REGOUT[16] 0 120 f
C.REGOUT[15] REGOUT[15] 0 120 f
C.REGOUT[14] REGOUT[14] 0 120 f
C.REGOUT[13] REGOUT[13] 0 120 f
C.REGOUT[12] REGOUT[12] 0 120 f
35 C.REGOUT[11] REGOUT[11] 0 120 f
C.REGOUT[10] REGOUT[10] 0 120 f
C.REGOUT[9] REGOUT[9] 0 120 f
C.REGOUT[8] REGOUT[8] 0 120 f
C.REGOUT[7] REGOUT[7] 0 120 f
40 C.REGOUT[6] REGOUT[6] 0 120 f
C.REGOUT[5] REGOUT[5] 0 120 f
C.REGOUT[4] REGOUT[4] 0 120 f
C.REGOUT[3] REGOUT[3] 0 120 f
C.REGOUT[2] REGOUT[2] 0 120 f
45 C.REGOUT[1] REGOUT[1] 0 120 f
C.REGOUT[0] REGOUT[0] 0 120 f

* - Analysis Setup - DC sweep
50 * FORMAT : .DC [name] [low] [high] [step]
*.DC VFORCE_A 0 1.2 0.01

* - Analysis Setup - Trans
* FORMAT : .TRAN [start time] [end time] [time step]
55 .TRAN 0 2000n 0.05n

* --- Forces
* FORMAT --- PULSE : [name] [port] [reference (0 means ground)] PULSE [low] [high] [
    delay] [fall time] [rise time] [pulse width] [period]
*
60 * FORMAT --- DC : [name] [port] [reference (0 means ground)] DC [voltage]
*

VFORCE_VDD VDD 0 DC 1.08
VFORCE_VSS VSS 0 DC 0

65 VFORCE_CLK CLK 0 PULSE (0 1.08 25n 0.1n 0.1n 25n 50n)

VFORCE_RESET RESET 0 pw1 (120n 1.08 120.1n 0 )
VFORCE_WE WE 0 DC 1.08

70 .SIGBUS A[15:0] VHI=1.08 VLO=0 TRISE=0.1n TFALL=0.1n TDELAY=210n THOLD=200n BASE=
    HEXA PATTERN 0002 0003 P
.SIGBUS B[15:0] VHI=1.08 VLO=0 TRISE=0.1n TFALL=0.1n TDELAY=210n THOLD=200n BASE=
    HEXA PATTERN 0003 0004 P

75 * --- Waveform Outputs
.PLOT TRAN V(COMPLETE)
.PLOT TRAN V(PASS)
.PLOT TRAN V(REGOUT[31])

```

```

80 .PLOT TRAN V(REGOUT[30])
.PLOT TRAN V(REGOUT[29])
.PLOT TRAN V(REGOUT[28])
.PLOT TRAN V(REGOUT[27])
.PLOT TRAN V(REGOUT[26])
.PLOT TRAN V(REGOUT[25])
85 .PLOT TRAN V(REGOUT[24])
.PLOT TRAN V(REGOUT[23])
.PLOT TRAN V(REGOUT[22])
.PLOT TRAN V(REGOUT[21])
.PLOT TRAN V(REGOUT[20])
90 .PLOT TRAN V(REGOUT[19])
.PLOT TRAN V(REGOUT[18])
.PLOT TRAN V(REGOUT[17])
.PLOT TRAN V(REGOUT[16])
.PLOT TRAN V(REGOUT[15])
95 .PLOT TRAN V(REGOUT[14])
.PLOT TRAN V(REGOUT[13])
.PLOT TRAN V(REGOUT[12])
.PLOT TRAN V(REGOUT[11])
.PLOT TRAN V(REGOUT[10])
100 .PLOT TRAN V(REGOUT[9])
.PLOT TRAN V(REGOUT[8])
.PLOT TRAN V(REGOUT[7])
.PLOT TRAN V(REGOUT[6])
.PLOT TRAN V(REGOUT[5])
105 .PLOT TRAN V(REGOUT[4])
.PLOT TRAN V(REGOUT[3])
.PLOT TRAN V(REGOUT[2])
.PLOT TRAN V(REGOUT[1])
.PLOT TRAN V(REGOUT[0])
110 .PLOT TRAN V(A[15])
.PLOT TRAN V(A[14])
.PLOT TRAN V(A[13])
.PLOT TRAN V(A[12])
.PLOT TRAN V(A[11])
115 .PLOT TRAN V(A[10])
.PLOT TRAN V(A[9])
.PLOT TRAN V(A[8])
.PLOT TRAN V(A[7])
.PLOT TRAN V(A[6])
120 .PLOT TRAN V(A[5])
.PLOT TRAN V(A[4])
.PLOT TRAN V(A[3])
.PLOT TRAN V(A[2])
.PLOT TRAN V(A[1])
125 .PLOT TRAN V(A[0])
.PLOT TRAN V(B[15])
.PLOT TRAN V(B[14])
.PLOT TRAN V(B[13])
.PLOT TRAN V(B[12])
130 .PLOT TRAN V(B[11])
.PLOT TRAN V(B[10])
.PLOT TRAN V(B[9])
.PLOT TRAN V(B[8])
.PLOT TRAN V(B[7])
135 .PLOT TRAN V(B[6])
.PLOT TRAN V(B[5])
.PLOT TRAN V(B[4])

```

```

140 .PLOT TRAN V(B[3])
.PLOT TRAN V(B[2])
.PLOT TRAN V(B[1])
.PLOT TRAN V(B[0])
.PLOT TRAN V(CLK)
.PLOT TRAN V(RESET)
.PLOT TRAN V(STARTTEST)
145 .PLOT TRAN V(WE)

* — Params
.TEMP 125

150 * — Power Measurement
.measure tran static_pwr AVG power from=90ns to=160ns
.measure tran inst_pwr MAX power from=90ns to=160ns

```

Listing 44: power test SPICE

```

0 * Example circuit file for simulating PEX

.OPTION DOINODE
.HIER /

5 .INCLUDE "/home/bxk5113/Pyxis_SPT_HEP/ic_projects/Pyxis_SPT/digicdesign/
ProjectWrapper/ProjectWrapper.cal/ProjectWrapper.pex.netlist"

.LIB /home/bxk5113/Pyxis_SPT_HEP/ic_reflibs/tech_libs/generic13/models/lib.eldo TT

* - Instantiate your parasitic netlist and add the load capacitor
10 ** FORMAT :
* XLAYOUT [all inputs as listed by the ".subckt" line in the included netlist, in
the order that they appear there] [name of the subcircuit as listed in the
included netlist]
XLAYOUT COMPLETE PASS REGOUT[31] REGOUT[30] REGOUT[29] REGOUT[28] REGOUT[27] REGOUT
[26] REGOUT[25] REGOUT[24] REGOUT[23] REGOUT[22] REGOUT[21] REGOUT[20] REGOUT[19]
REGOUT[18] REGOUT[17] REGOUT[16] REGOUT[15] REGOUT[14] REGOUT[13] REGOUT[12]
REGOUT[11] REGOUT[10] REGOUT[9] REGOUT[8] REGOUT[7] REGOUT[6] REGOUT[5] REGOUT[4]
REGOUT[3] REGOUT[2] REGOUT[1] REGOUT[0] A[15] A[14] A[13] A[12] A[11] A[10] A[9]
A[8] A[7] A[6] A[5] A[4] A[3] A[2] A[1] A[0] B[15] B[14] B[13] B[12] B[11] B[10]
B[9] B[8] B[7] B[6] B[5] B[4] B[3] B[2] B[1] B[0] CLK RESET STARTTEST WE
ProjectWrapper

* Output Capacitance
15 C.REGOUT[31] REGOUT[31] 0 120 f
C.REGOUT[30] REGOUT[30] 0 120 f
C.REGOUT[29] REGOUT[29] 0 120 f
C.REGOUT[28] REGOUT[28] 0 120 f
C.REGOUT[27] REGOUT[27] 0 120 f
20 C.REGOUT[26] REGOUT[26] 0 120 f
C.REGOUT[25] REGOUT[25] 0 120 f
C.REGOUT[24] REGOUT[24] 0 120 f
C.REGOUT[23] REGOUT[23] 0 120 f
C.REGOUT[22] REGOUT[22] 0 120 f
25 C.REGOUT[21] REGOUT[21] 0 120 f
C.REGOUT[20] REGOUT[20] 0 120 f
C.REGOUT[19] REGOUT[19] 0 120 f
C.REGOUT[18] REGOUT[18] 0 120 f
C.REGOUT[17] REGOUT[17] 0 120 f

```

```

30 C.REGOUT[16] REGOUT[16] 0 120 f
   C.REGOUT[15] REGOUT[15] 0 120 f
   C.REGOUT[14] REGOUT[14] 0 120 f
   C.REGOUT[13] REGOUT[13] 0 120 f
   C.REGOUT[12] REGOUT[12] 0 120 f
35 C.REGOUT[11] REGOUT[11] 0 120 f
   C.REGOUT[10] REGOUT[10] 0 120 f
   C.REGOUT[9] REGOUT[9] 0 120 f
   C.REGOUT[8] REGOUT[8] 0 120 f
   C.REGOUT[7] REGOUT[7] 0 120 f
40 C.REGOUT[6] REGOUT[6] 0 120 f
   C.REGOUT[5] REGOUT[5] 0 120 f
   C.REGOUT[4] REGOUT[4] 0 120 f
   C.REGOUT[3] REGOUT[3] 0 120 f
   C.REGOUT[2] REGOUT[2] 0 120 f
45 C.REGOUT[1] REGOUT[1] 0 120 f
   C.REGOUT[0] REGOUT[0] 0 120 f

* - Analysis Setup - DC sweep
50 * FORMAT : .DC [name] [low] [high] [step]
   *.DC VFORCE_A 0 1.2 0.01

* - Analysis Setup - Trans
* FORMAT : .TRAN [start time] [end time] [time step]
55 .TRAN 0 600n 0.1n

* --- Forces
* FORMAT --- PULSE : [name] [port] [reference (0 means ground)] PULSE [low] [high] [
   delay] [fall time] [rise time] [pulse width] [period]
*
60 * FORMAT --- DC : [name] [port] [reference (0 means ground)] DC [voltage]
*

VFORCE_C1 CONTROL[1] 0 PULSE (0 1.08 40n 0.1n 0.1n 40n 80n)
VFORCE_C0 CONTROL[0] 0 PULSE (0 1.08 20n 0.1n 0.1n 20n 40n)
65 VFORCE_VDD VDD 0 DC 1.08
   VFORCE_VSS VSS 0 DC 0

VFORCE_CLK CLK 0 PULSE (0 1.08 25n 0.1n 0.1n 25n 50n)
70 VFORCE_RESET RESET 0 pw1 (120n 1.08 120.1n 0 )

.SIGBUS A[15:0] VHI=1.08 VLO=0 TRISE=0.1n TFALL=0.1n TDELAY=210n THOLD=200n BASE=
   HEXA PATTERN EFAB 3FD6 P
75 .SIGBUS B[15:0] VHI=1.08 VLO=0 TRISE=0.1n TFALL=0.1n TDELAY=210n THOLD=200n BASE=
   HEXA PATTERN 8C5F 0004 P

* --- Waveform Outputs
.PLOT TRAN V(COMPLETE)
80 .PLOT TRAN V(PASS)
   .PLOT TRAN V(REGOUT[31])
   .PLOT TRAN V(REGOUT[30])
   .PLOT TRAN V(REGOUT[29])
   .PLOT TRAN V(REGOUT[28])
85 .PLOT TRAN V(REGOUT[27])

```

```

.PLOT TRAN V(REGOUT[26])
.PLOT TRAN V(REGOUT[25])
.PLOT TRAN V(REGOUT[24])
.PLOT TRAN V(REGOUT[23])
90 .PLOT TRAN V(REGOUT[22])
.PLOT TRAN V(REGOUT[21])
.PLOT TRAN V(REGOUT[20])
.PLOT TRAN V(REGOUT[19])
.PLOT TRAN V(REGOUT[18])
95 .PLOT TRAN V(REGOUT[17])
.PLOT TRAN V(REGOUT[16])
.PLOT TRAN V(REGOUT[15])
.PLOT TRAN V(REGOUT[14])
.PLOT TRAN V(REGOUT[13])
100 .PLOT TRAN V(REGOUT[12])
.PLOT TRAN V(REGOUT[11])
.PLOT TRAN V(REGOUT[10])
.PLOT TRAN V(REGOUT[9])
.PLOT TRAN V(REGOUT[8])
105 .PLOT TRAN V(REGOUT[7])
.PLOT TRAN V(REGOUT[6])
.PLOT TRAN V(REGOUT[5])
.PLOT TRAN V(REGOUT[4])
.PLOT TRAN V(REGOUT[3])
110 .PLOT TRAN V(REGOUT[2])
.PLOT TRAN V(REGOUT[1])
.PLOT TRAN V(REGOUT[0])
.PLOT TRAN V(A[15])
.PLOT TRAN V(A[14])
115 .PLOT TRAN V(A[13])
.PLOT TRAN V(A[12])
.PLOT TRAN V(A[11])
.PLOT TRAN V(A[10])
.PLOT TRAN V(A[9])
120 .PLOT TRAN V(A[8])
.PLOT TRAN V(A[7])
.PLOT TRAN V(A[6])
.PLOT TRAN V(A[5])
.PLOT TRAN V(A[4])
125 .PLOT TRAN V(A[3])
.PLOT TRAN V(A[2])
.PLOT TRAN V(A[1])
.PLOT TRAN V(A[0])
.PLOT TRAN V(B[15])
130 .PLOT TRAN V(B[14])
.PLOT TRAN V(B[13])
.PLOT TRAN V(B[12])
.PLOT TRAN V(B[11])
.PLOT TRAN V(B[10])
135 .PLOT TRAN V(B[9])
.PLOT TRAN V(B[8])
.PLOT TRAN V(B[7])
.PLOT TRAN V(B[6])
.PLOT TRAN V(B[5])
140 .PLOT TRAN V(B[4])
.PLOT TRAN V(B[3])
.PLOT TRAN V(B[2])
.PLOT TRAN V(B[1])
.PLOT TRAN V(B[0])

```

```
145 .PLOT TRAN V(CLK)
    .PLOT TRAN V(RESET)
    .PLOT TRAN V(STARTTEST)
    .PLOT TRAN V(WE)

150
* — Params
.TEMP 125

* — Power Measurement
155 .measure tran static_pwr AVG power from=220ns to=50ns
    .measure tran inst_pwr MAX power from=10ns to=600ns
```

6 References

Key, Brandon A. *CMPE 260 Laboratory Exercise 3 Arithmetic Logic Unit*. CMPE 260 Laboratory Exercise 3 Arithmetic Logic Unit.

//TODO add BIST from DSD II //TODO Added Chris's DSD II lab